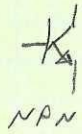


Electronics Review

Transistors

BJT's



NPN




PNP


FET's



NMOS

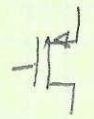

PMOS


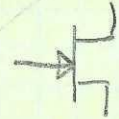


JFET's / MESFET's

We will concentrate on BJTs
but theory developed is general


BJTs


Recall ~~BJT~~ Structure & Operation

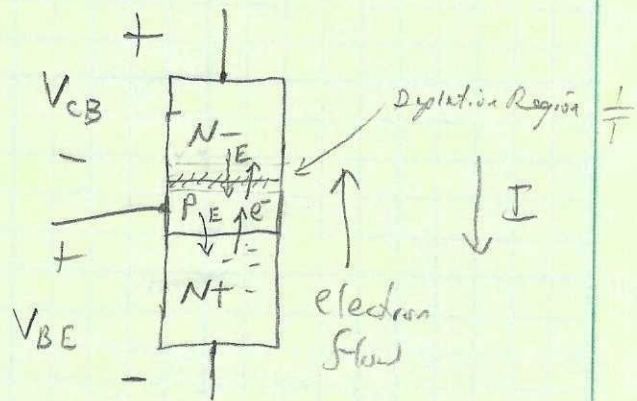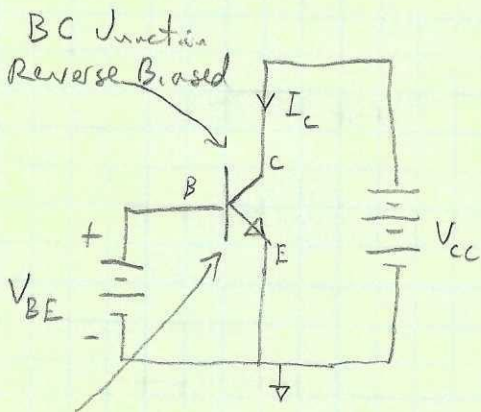

BE Junction Forward Biased

I-V Curve

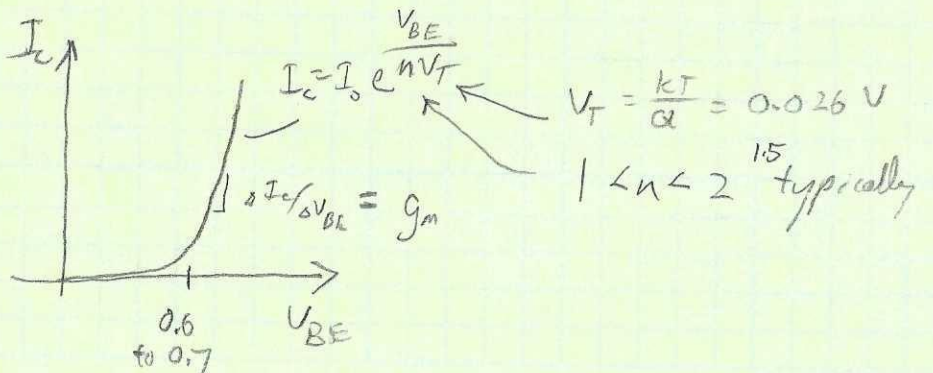

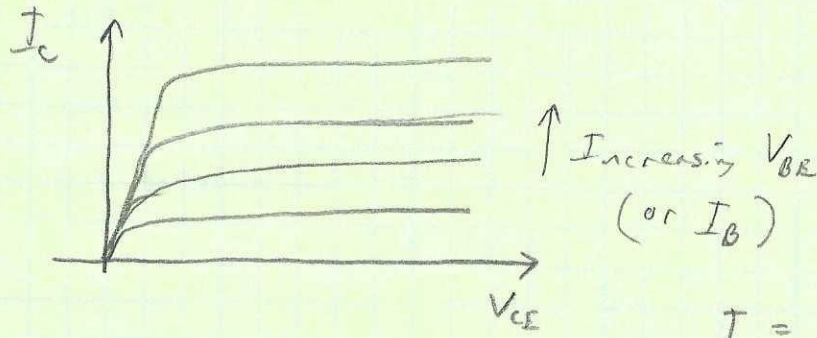



$$I_B = \frac{1}{h_{FE}} I_C \quad \text{why?}$$

← 30 to 300
(a.k.a "β")

Basic Amplifier Concept

- Add resistor between V_{CC} and Collector
- Vary V_{BE} with input signal
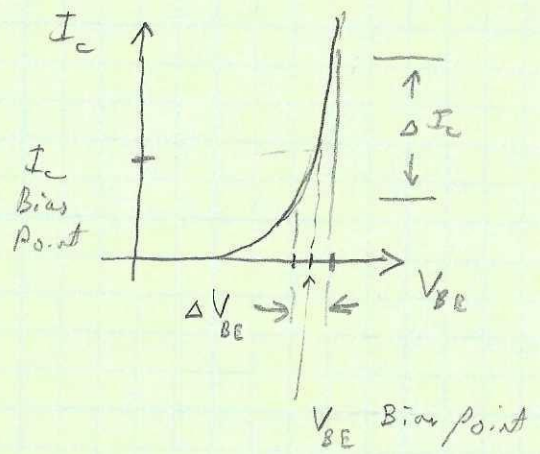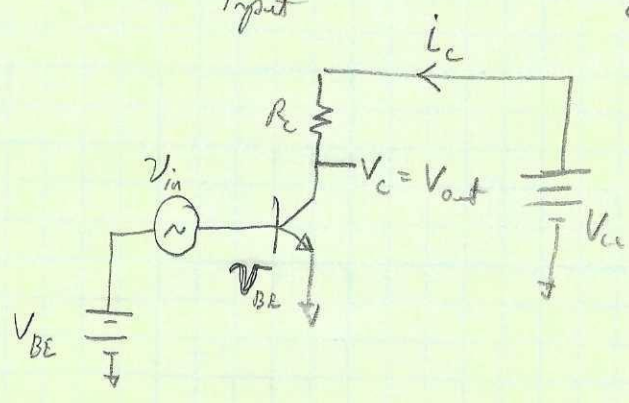
$$\Delta V_{BE} \xrightarrow{\text{input}} \Delta I_C \xrightarrow{\text{output}} \Delta V_C \quad \Delta V_C = (\Delta I_C)(R_C)$$



Amplifier Voltage Gain:


$$\begin{aligned} \Delta V_C &= - \Delta I_C R_C \quad \leftarrow \text{why?} \\ &= - \Delta V_{BE} \left(\frac{dI_C}{dV_{BE}} \right) R_C \\ &= - \Delta V_{BE} g_m R_C \end{aligned}$$

$$\frac{dI_C}{dV_{BE}} = g_m = \frac{I_C}{nV_T}$$

$$\Rightarrow A_V = \frac{\Delta V_C}{\Delta V_{BE}} = -g_m R_C$$

Practical Designs (BJT used here)

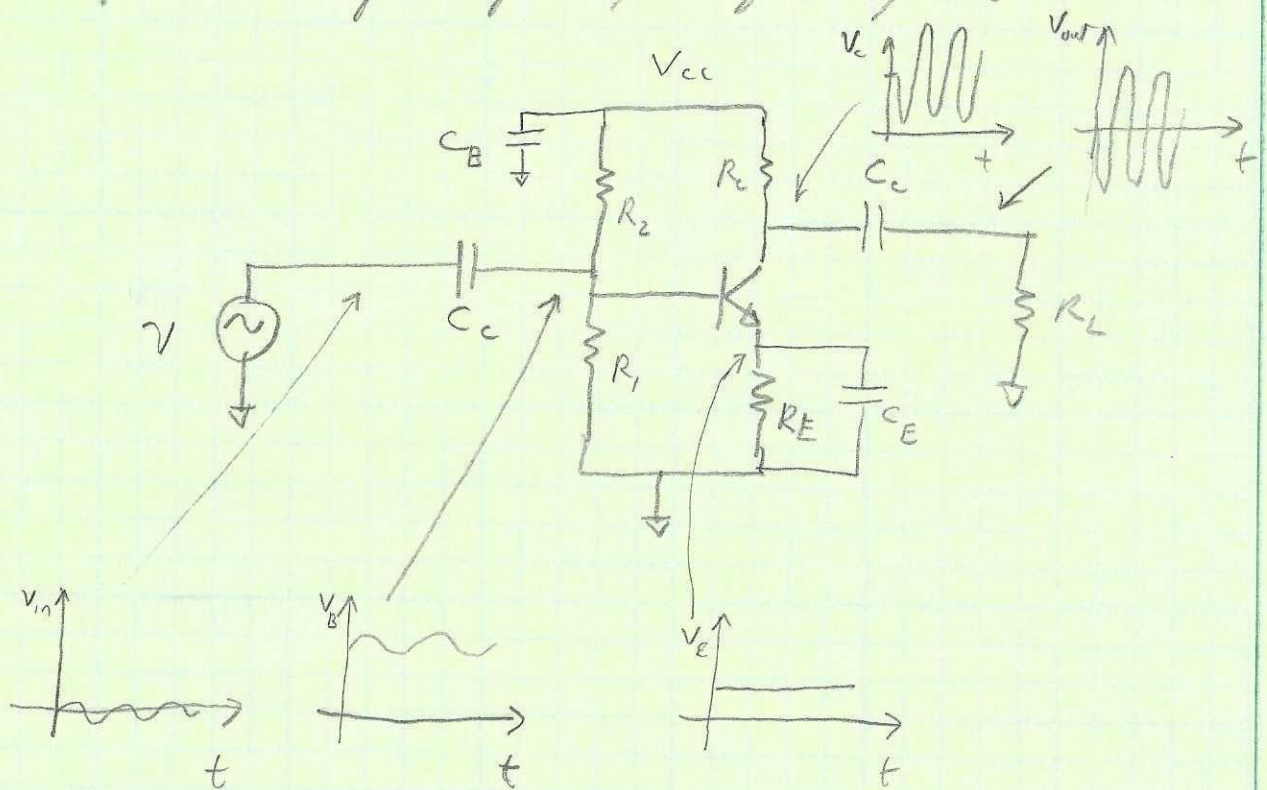- Bias transistor in "active region"
 - BE forward biased
 - CB reverse biased " (or at least not forward) "
- AC Couple input & output signals




3-0235 — 50 SHEETS — 5 SQUARES
 3-0236 — 100 SHEETS — 5 SQUARES
 3-0237 — 200 SHEETS — 5 SQUARES
 3-0137 — 200 SHEETS — FILLER


COMET

Triodes

Vacuum Tubes

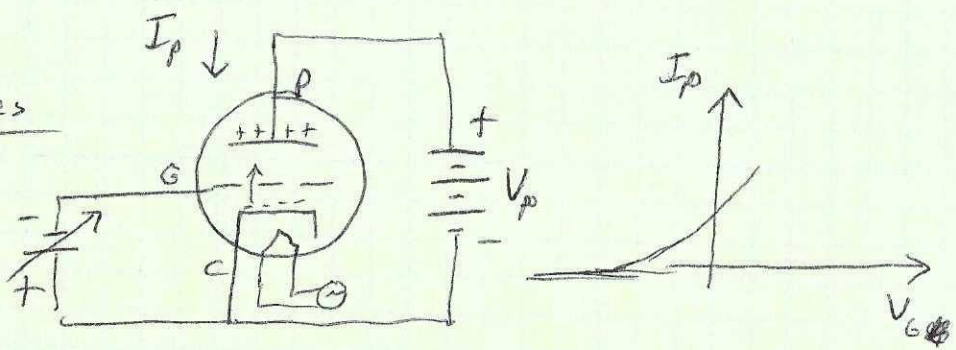

JFETs

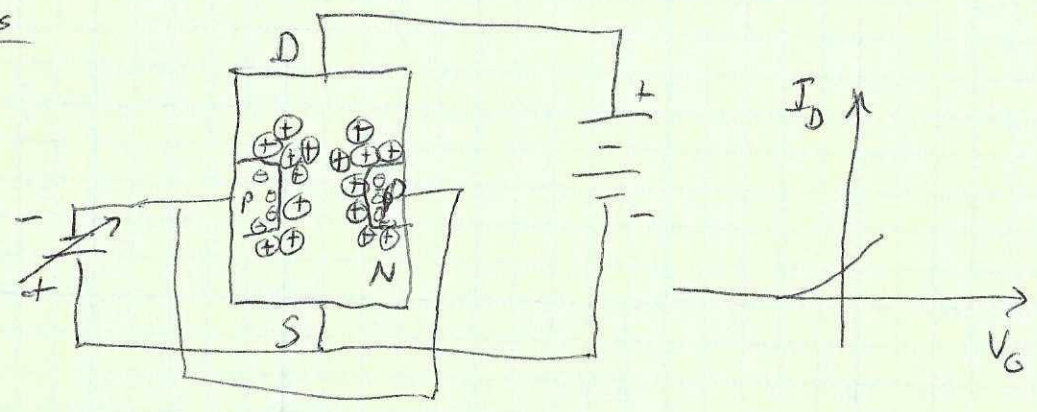



Control terminal (volts) varies current through device ☺

Review


Recall basic ^{CE} amplifier concept:

Forward bias BE junction, Reverse bias CB junction
wiggle V_{BE} w/ v_s

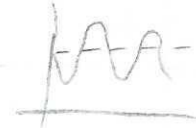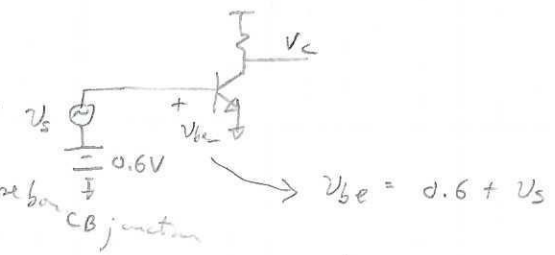$\Rightarrow \Delta I_c \Rightarrow \Delta V_c$



Practical circuit

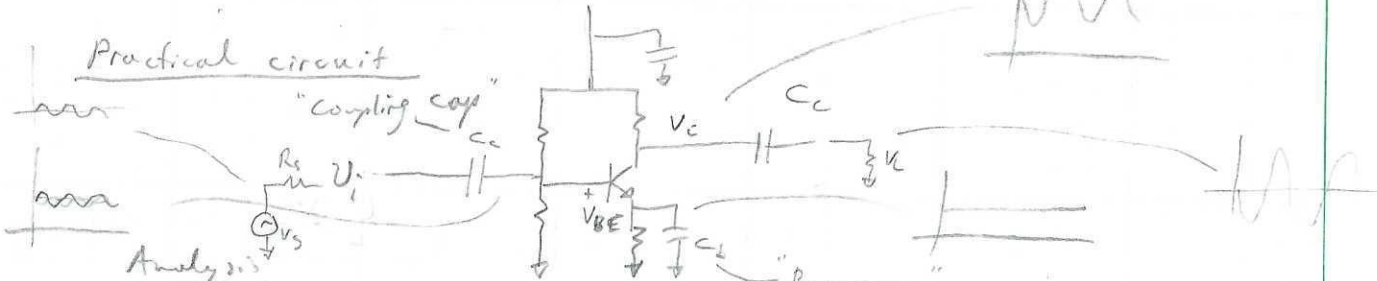


Analysis


Solve DC Bias w/ AC signal set to zero, capacitors open.
Solve AC chrt w/ DC sources at zero
Add solutions.] Superposition

DC Solution - See handout

AC Solution

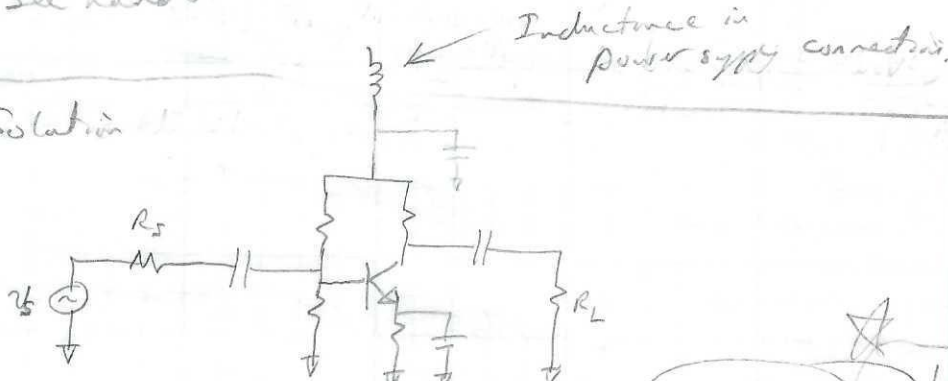

AC circuit:

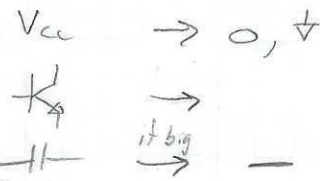

OR $h_{ie} = r_{\pi} = \frac{1}{g_m}$
 $g_m = \frac{I_c}{V_T}$



1.5 for 5179 davis

$$V_L = (-g_m V_{be}) (R_c \parallel R_L)$$

$$= \underbrace{V_s \frac{R_{in}}{R_{in} + R_s}}_{V_{in}} (-g_m (R_c \parallel R_L))$$

$R_{in} = R_{b1} \parallel R_{b2} \parallel R_{\pi}$

$A_v = \frac{V_o}{V_s} = fcn \text{ of } R_s, R_L !$

Go over example


13-782 500 SHEETS, FILLER, 5 SQUARE
42-381 50 SHEETS, VE-EASER, 5 SQUARE
42-382 100 SHEETS, VE-EASER, 5 SQUARE
42-392 100 RECYCLED, WHITE, 5 SQUARE
42-393 200 RECYCLED, WHITE, 5 SQUARE
42-399 200 RECYCLED, WHITE, 5 SQUARE
MADE IN U.S.A.



AC Ckt. Solution Continued

Input / Output \geq , Unloaded & Loaded A_v

Separate amp from source / Load ckt

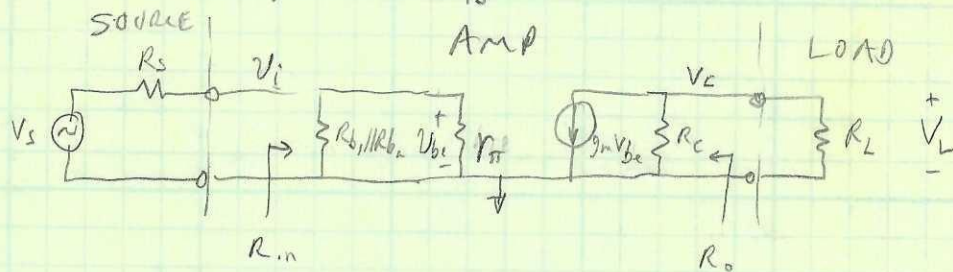


Consider Amp in isolation and characterize by

$$R_{in} = R_{b1} \parallel R_{b2} \parallel r_{\pi}$$

$$R_o = R_c \quad \text{"(set independent sources to zero)"}$$

$$A_{v_{no\ load}} = \left. \frac{V_o}{V_i} \right|_{R_L \rightarrow \infty} = \frac{-g_m V_{be} R_c}{V_{be}} = -g_m R_c$$

Now consider Loading Effects:

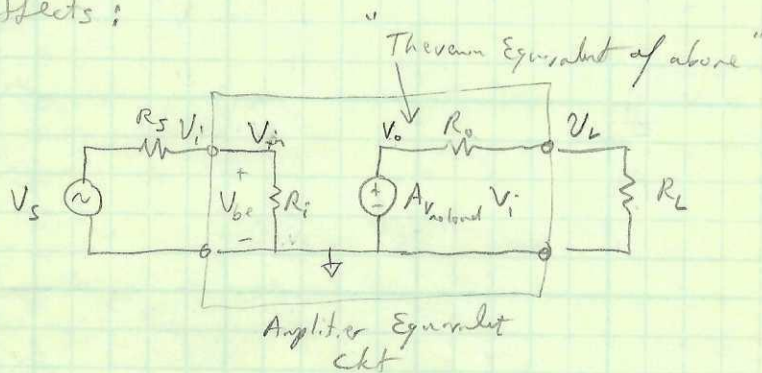

$$A_v \triangleq \frac{V_L}{V_s} = \frac{V_{i_a}}{V_s} \frac{V_o}{V_{i_n}} \frac{V_L}{V_o}$$

$$= \left(\frac{R_i}{R_i + R_s} \right) A_{v_{no\ load}} \left(\frac{R_L}{R_o + R_L} \right)$$

$$= \left(\frac{R_i}{R_i + R_s} \right) (-g_m R_c) \left(\frac{R_L}{R_o + R_L} \right)$$

$$= - \left(\frac{R_i}{R_i + R_s} \right) g_m \left(\frac{R_c R_L}{R_o + R_L} \right)$$

$$= - \left(\frac{R_i}{R_i + R_s} \right) g_m (R_c \parallel R_L)$$

Same as before!