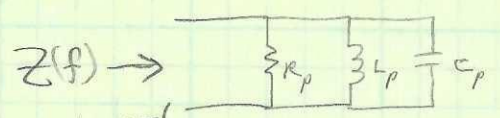



General Parallel Resonant ^{RLC} Circuits



$$Z(f) = \left(\frac{1}{R_p} + \frac{1}{j\omega L_p} + \frac{1}{j\omega C_p} \right)^{-1} = \left(\frac{1}{R_p} + \frac{1}{jX_{L_p}} + \frac{1}{-jX_{C_p}} \right)^{-1}$$

- Behavior
- $Z = R_p$ when $X_{L_p} = X_{C_p}$ at $f_0 = \frac{1}{2\pi\sqrt{L_p C_p}}$ ↖ why?
 - Low Z off resonance

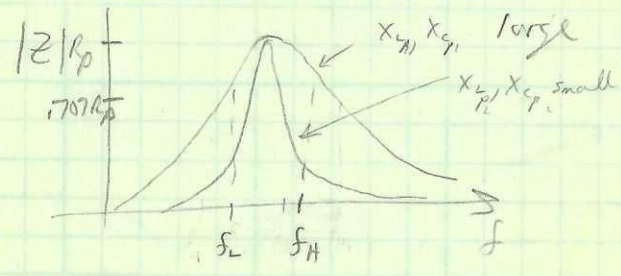" Z varies faster if X_L & X_C are small at resonance" (related to R_p)



Define Quality Factor

$$Q_p = \frac{R_p}{X_L|_{f_0}} = \frac{R_p}{X_C|_{f_0}}$$

Can be shown that $|Z|$ falls to $\frac{1}{\sqrt{2}} R_p$ at freqs f_L, f_H given by


$$f_H, f_L = f_0 \left[\sqrt{1 + \left(\frac{1}{2Q_p}\right)^2} \pm \frac{1}{2Q_p} \right]$$

So 3dB BW is $f_H - f_L = \frac{f_0}{Q_p} \triangleq B_{3dB}$
 $f_H \approx f_0 + \frac{B_{3dB}}{2}$
 $f_L \approx f_0 - \frac{B_{3dB}}{2}$

- Called "Half power or 3dB bandwidth"
- This is range of freqs over which A_v is within 0.7071 A_{vmax}


Example Application:

Use as image filter in RF Amp

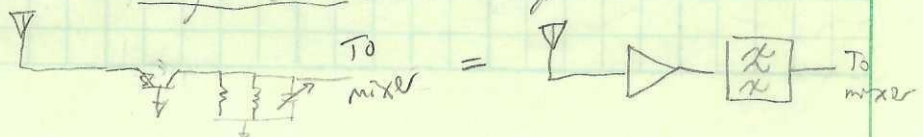


Series Resonance


Consider series RLC circuit

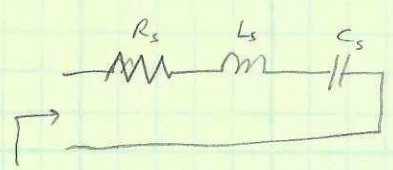
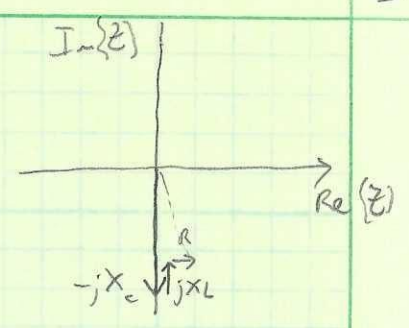
$$Z(f) = R_s + j\omega L_s + \frac{1}{j\omega C_s} = R_s + jX_{L_s} - jX_{C_s}$$



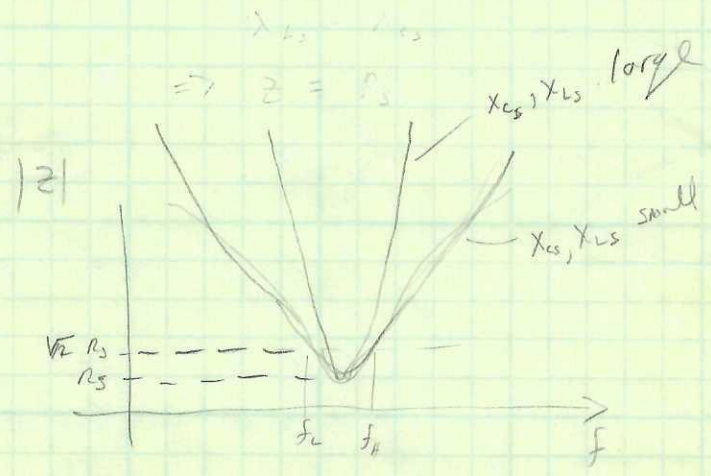Ask them:
 At low freq, $Z \approx -jX_{C_s}$ why?? "Lard guy wms!"
 At high freq $Z \approx jX_{L_s}$
 At resonance freq $f_0 = \frac{1}{2\pi\sqrt{L_s C_s}}$, $X_{L_s} = X_{C_s} \Rightarrow Z = R_s$




Varies faster if X_{L_s}, X_{C_s} large compared w/ R_s at resonance

Can slow $f_H - f_L = \frac{f_0}{Q_s} = B_{3dB}$

where $Q_s = \frac{X_{L_s}}{R_s} = \frac{X_{C_s}}{R_s}$

← Inverse of parallel case

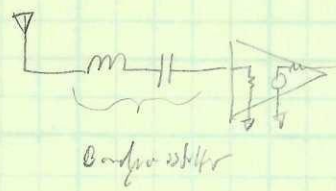Example Application: Use as preselect filter



Bandpass filter

Large impedance to unwanted signals (e.g. CB or cell phone) in car

Show Example schematic!