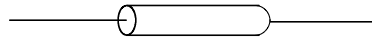


Component Parasitics at RF


Resistors





Ideal Model



Model at RF

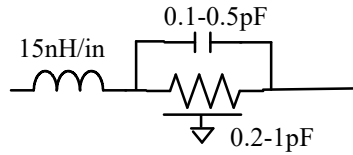


Impedance vs Frequency

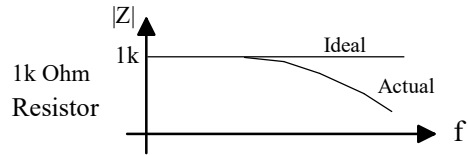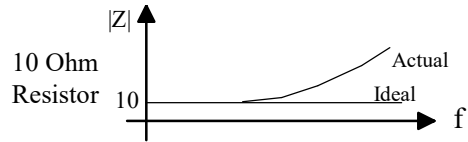


Capacitors




Ideal model

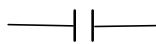


Model at RF

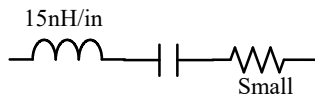

Impedance vs. Frequency

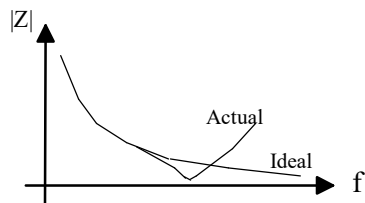


Inductors

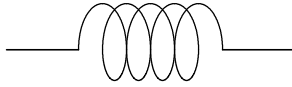


Ideal Model


Model at RF

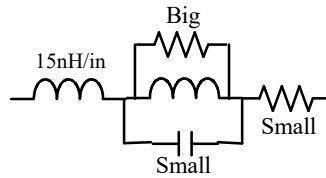

Impedance vs Frequency

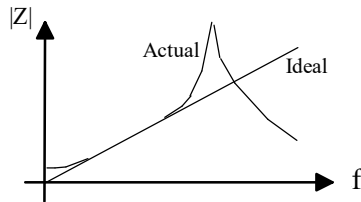


PC Board Trace

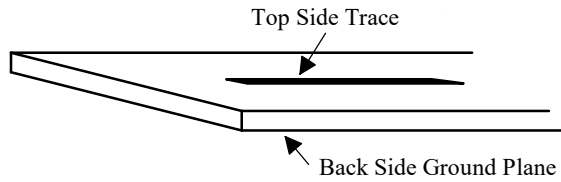

Ideal Model



Model at RF

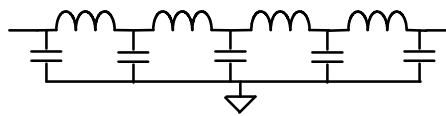

Impedance vs. Frequency (*Terminated at one end with a resistor to ground.*)

