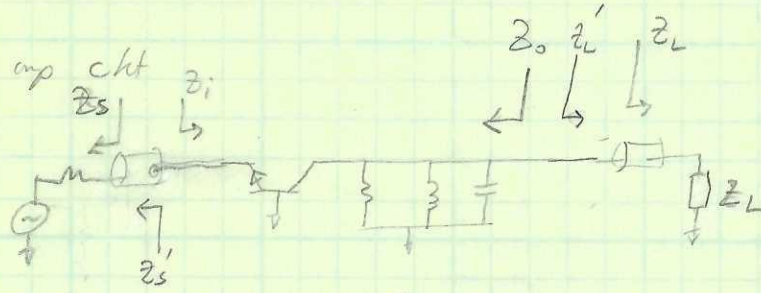


# Show Power Gain Handout

9/19 Impedance matching ~~etc~~

Consider RF amp ckt



$$A_v = g_m Z_L$$

$$G_p = Z_L' Z_L$$

Problems: 1) Coax modities  $Z_L$  (Varies w/ length of coax)


Problem: 2) Need  $Z_i = Z_s^*$  &  $Z_L = Z_o^*$  for good power gain

Solns. 1) Use TX lines with proper termination

Next Problem: 2) Ant dependent match, reliability (MNC)

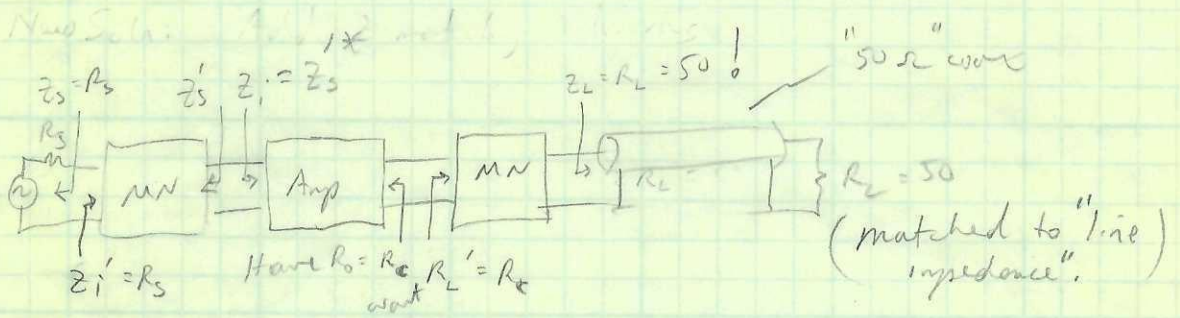
- 2) Impedance mismatch ( $Z_L = 50 \Omega$ )
- 3) Lower power gain

gains  
 $V_L^2/R_L$   
 $V_i^2/R_i$   
 $N^2 \frac{R_i}{R_L}$   
 $(N^2)^2 \frac{R_i}{R_L}$   
 $g_m R_L$



Low Freq  $\approx$  lumped network ( $f \ll 100\text{MHz}$  at PCB level)

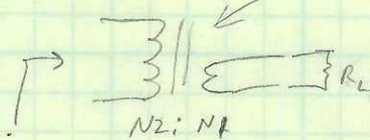hard to get good cores above  $\sim 100\text{MHz}$



$$R_L' \approx \left(\frac{N_2}{N_1}\right)^2 R_L$$

why?

Because  $V_2 = \frac{N_2}{N_1} V_1$


And for power conservation

$$V_2 I_2 = V_1 I_1 \Rightarrow I_2 = \frac{V_1}{V_2} I_1 = \frac{N_1}{N_2} I_1$$

$$\text{So } Z_2 = \frac{V_2}{I_2} = \frac{N_2/N_1 V_1}{N_1/N_2 I_1} = \left(\frac{N_2}{N_1}\right)^2 Z_1$$


High Freq matching networks

Lumped  
 $f \ll 26\text{GHz}$

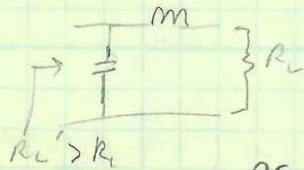

ECE 662 ☺

Distributed  
 $f \gg 26\text{GHz}$

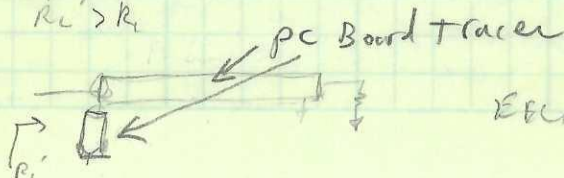

ECE 764


matching  
L Network Design

why? Because BP systems { 10.7 MHz ± 0.1  
 100 MHz ± 10


Background: Series/Parallel equivalent Circuits  
 At a single freq, Consider an arbitrary Z

$$Z = R + jX$$

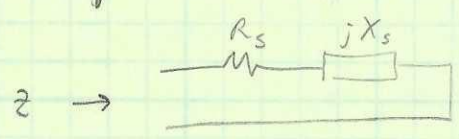Theorem: At a given freq Z can be "realized" either in series form



or in parallel form

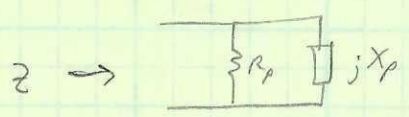

Proof: "Constructive"

Series Form: (Easy) Set  $R_s = R$   
 $X_s = X \Rightarrow L = \frac{X}{2\pi f}$  or  $C = \frac{1}{2\pi f X}$

Parallel Form: (Harder)

Work with Admittance value

$$Y = \frac{1}{Z} = \frac{1}{R + jX}$$

$$= \frac{R - jX}{R^2 + X^2}$$

$$= \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$$

Compare with parallel circuit:  $Y_{in} = \frac{1}{R_p} + \frac{1}{jX_p}$

To be same, we need:

$$R_p = \frac{R^2 + X^2}{R} \quad X_p = \frac{R^2 + X^2}{X}$$



Series/Parallel Equivalents

Compare of series/parallel

$$R_p \equiv \frac{R_s^2 + X_s^2}{R_s} \quad X_p \equiv \frac{R_s^2 + X_s^2}{X_s}$$

$R + jX$   
 $Y = \frac{1}{R + jX}$

# Summary



Alternative Formulation

Define  $g = \frac{X_s}{R_s}$

Then  $R_p = (1 + g^2) R_s$        $X_p = \frac{1 + g^2}{g^2} X_s$


Can also show:  $\frac{R_p}{X_p} = g$

Compare w/ previous formulas for  $Q_p, Q_s!$

Example:

Consider  $Z = 50 + j100 \Omega$  at 100 MHz

Series combination.

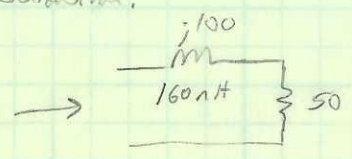

Parallel equivalent (at 100 MHz)

$$g = \frac{X_s}{R_s} = \frac{100}{50} = 2$$

$$R_p = (1 + g^2) R_s = (5)(50) = 250 \Omega$$

$$X_p = \frac{1 + g^2}{g^2} X_s = \frac{5}{4} 100 = 125 \Omega$$




Z matching with L networks


Example

Convert  $50 \Omega$  to  $250 \Omega$  at 100 MHz


Step 1  
Add series reactance

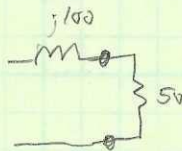

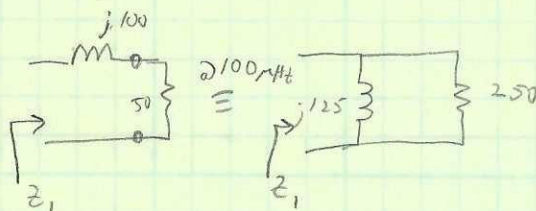
Step 2  
View as parallel form (see prev. example)



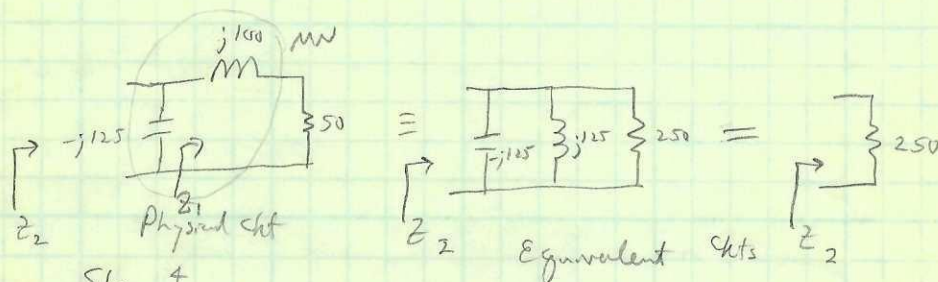Step 3  
Resonate out parallel squared reactance



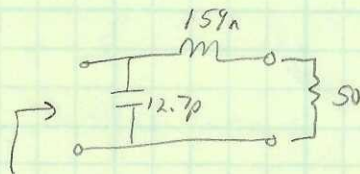Step 4  
Convert reactances to L, C values



$Z = 250 \Omega + j0$

@ f<sub>0</sub> only

$$X_L = 2\pi f L \Rightarrow L = \frac{X_L}{2\pi f}$$

$$= \frac{100}{2\pi \cdot 100} = 159 \text{ nH}$$

$$X_C = \frac{1}{2\pi f C} \Rightarrow C = \frac{1}{2\pi f X_C}$$

$$= \frac{1}{2\pi (100)(125)} = 12.7 \text{ pF}$$


Step 5 check for practicality (PCB level)

- $C \geq 1 \text{ pF}$  ✓
- $L \geq 10 \text{ nH}$  ✓

# Additional MN Topics

Why does this work?

Recall transformer Z transformation

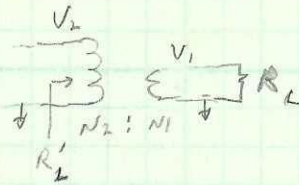

By power conservation, must have

$$\frac{V_2^2}{R_L'} = \frac{V_1^2}{R_L}$$



$$\Rightarrow \frac{R_L'}{R_L} = \left(\frac{V_2}{V_1}\right)^2 = N^2$$

$$\equiv R_p \parallel -jX_c \parallel jX_L'$$

Now look at resonant circuits

①

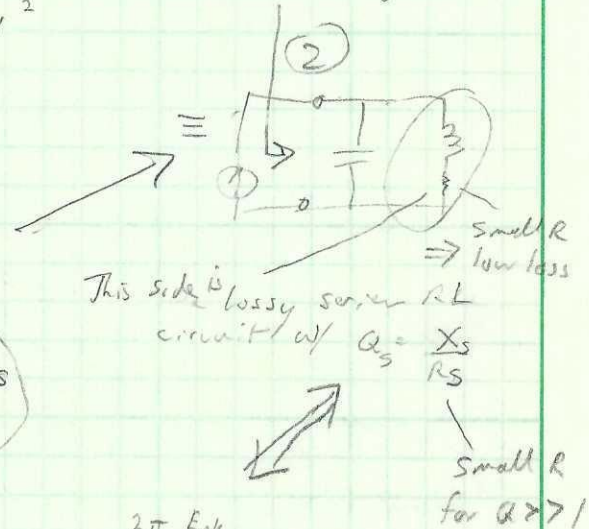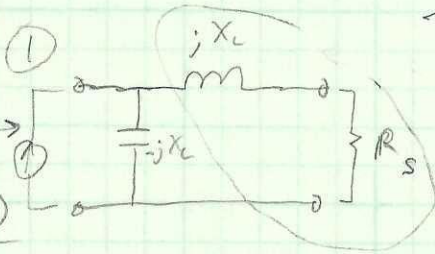If \$R\_S\$ small (\$\ll X\_L\$), looks like (lossy) parallel tuned ckt w/ \$Q = Q\_p = \frac{R\_p}{X\_p}\$



Recall from physics,  $Q = \frac{2\pi E_{pk}}{E_{loss/cycle}}$

By power conservation  $Q_s = Q_p = Q$

But  $Q = \frac{R_p}{X_p}$  ← Large for  $Q \gg 1$   
 since  $X_L' \approx X_L$  if  $Q \gg 1$


Hence  $Q \approx \frac{R_p}{Q R_s} \leftarrow X_L$

$$\Rightarrow \frac{R_p}{R_s} \approx Q^2$$

NOTE: Z match network behaves like T from

with  $Q \approx \frac{N_2}{N_1}$

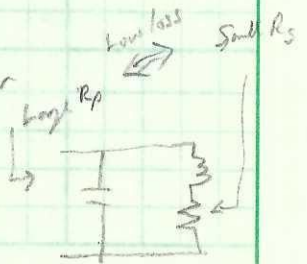$\Rightarrow V$  higher on parallel side!




## Additional MN Topics

### • Matching to Complex Loads


### • Bandwidth & "Loaded Q"

MN driven w/ I source

#### Matching to Complex Loads:

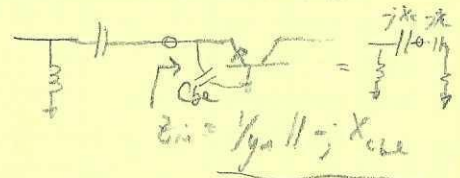

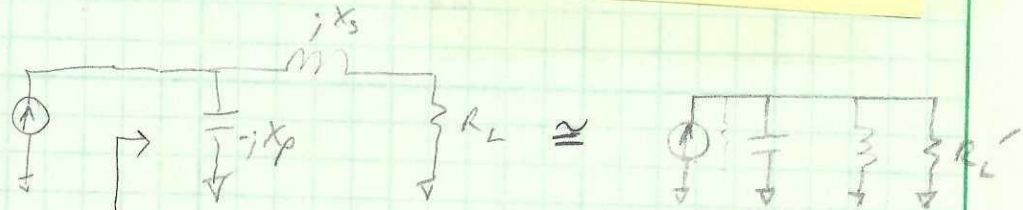convert to series form and absorb C into MN




$$R_L' = R_L (1 + g^2)$$

$$BW = \frac{f_0}{Q} \quad w/ \quad Q = \frac{R_L'}{X} \equiv g$$

So  $BW = f_0/g$  in this case

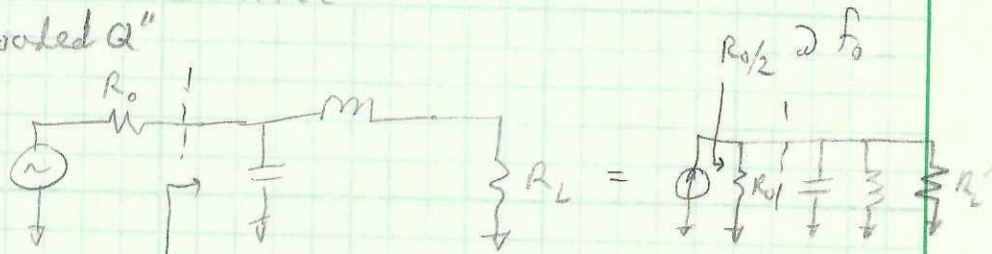MN driven from matched source and definition of "Loaded Q"



$$R_L' = (1 + g^2) R_L = R_0 \quad (\text{for max } G_p)$$

$$BW = \frac{f_0}{Q_{\text{loaded}}} \quad w/ \quad Q_{\text{loaded}} = \frac{R_0 \parallel R_0}{X_p} = \frac{1}{2} Q_{\text{unloaded}} = \frac{1}{2} g$$

⇒ 2x bandwidth of unloaded case


NOTE: Inductor has losses and will degrade Q & BW more

See handout on "Component Parasitics"

# Additional MN Topics

## Other MN types:

### Pi Network

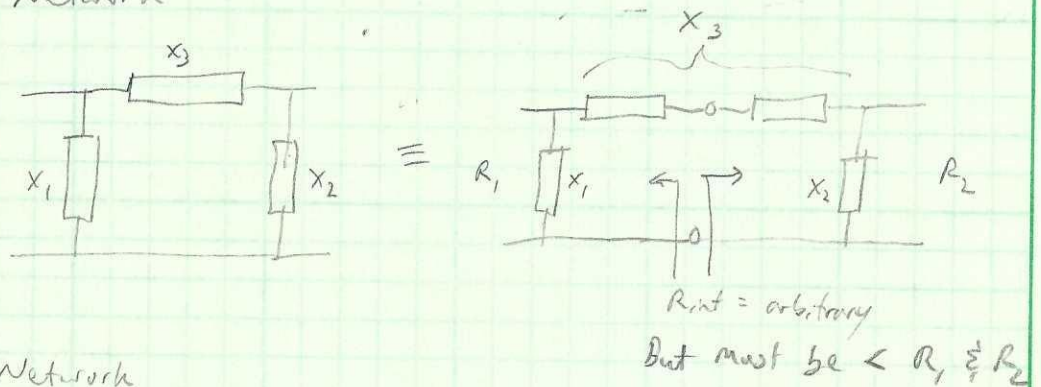


### T Network



- often used for "tunes"
- Advantages - • may allow better L, C values
- narrower bandwidth realizable

### LL Network


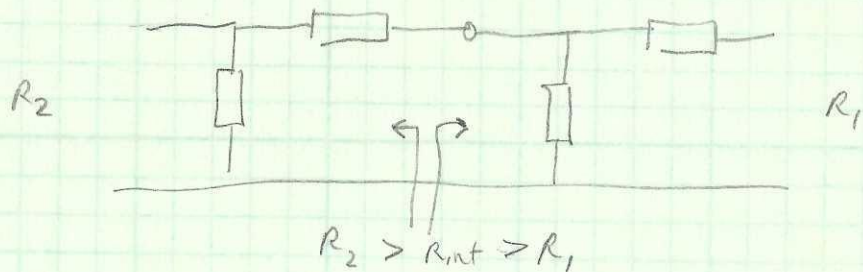


### Advantages

- Broader bandwidth
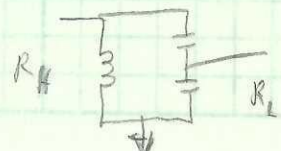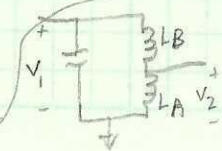
### Others Tapped L or C

- View as Pi Network, or
- Think of as V divider



$Z_{ratio} = X_{ratio} \text{ squared}$   
 $R_L = \left( \frac{X_A}{X_A + X_B} \right)^2 R_H$   
 iff  $Q \gg 1$