
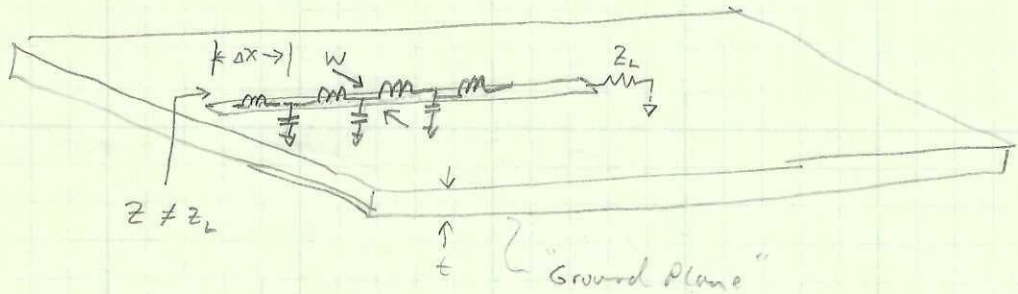


Intro to Transmission Lines

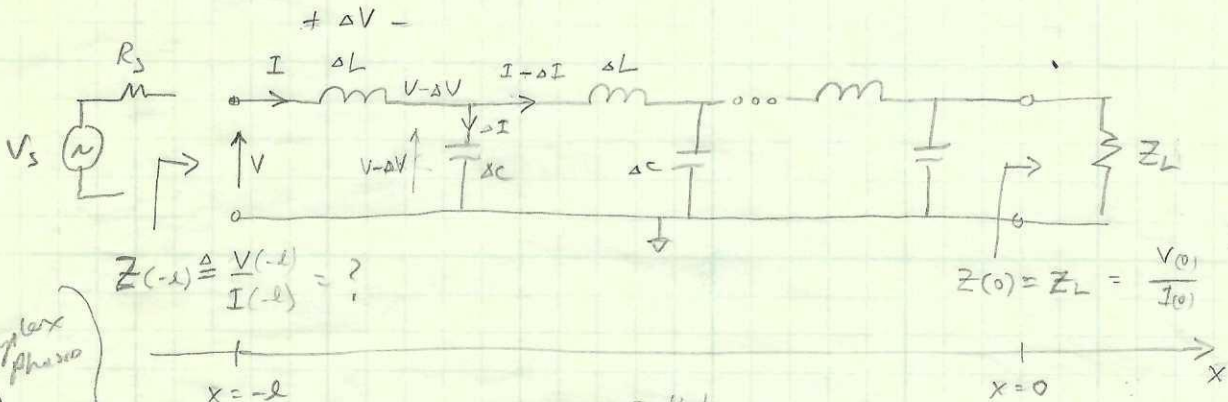PC Board parasitics (one example of TX line effects)



Lumped Element Model of PC board trace (A transmission line!)



Complex Phasors
 We need $V(x)$
 and $I(x)$
 to get $Z(x) = \frac{V(x)}{I(x)}$

$\Delta L = L \Delta x$ $\Delta C = C \Delta x$ See EM Textbook
 $C = \frac{\epsilon A}{d \Delta x}$ $\epsilon_r \frac{W \Delta x}{t \Delta x} = f \frac{W}{t}$

$$\Delta V = -j\omega(L \Delta x) I$$

$$\Delta I = -j\omega(C \Delta x) V$$

$$\frac{\partial V}{\partial x} = -j\omega L I(x)$$

$$\frac{\partial I}{\partial x} = -j\omega C V(x)$$

$$\frac{\partial^2 V(x)}{\partial x^2} = -\omega^2 LC V(x)$$

2nd order P.D.E.,

13-782 500 SHEETS FILLER 5 SQUARE
 42-381 50 SHEETS EYEGLASS 5 SQUARE
 42-382 100 SHEETS EYEGLASS 5 SQUARE
 42-383 200 SHEETS EYEGLASS 5 SQUARE
 42-384 100 SHEETS WEAR 5 SQUARE
 42-385 100 RECYCLED WHITE 5 SQUARE
 42-386 200 RECYCLED WHITE 5 SQUARE
 Made in U.S.A.



(complex) constants to fit boundary conditions amp/phase of voltage
 phase variation of distance

Solve to find

V at location x
 is sum of 2 phasors
 & varies w/ x
 (since $e^{j\theta} \neq e^{j\theta x}$)

$$V(x) = V^+ e^{-j\beta x} + V^- e^{+j\beta x}$$

same $\Delta \theta$ but Δx for $\Delta x = \lambda$

where $\beta = \omega \sqrt{LC} = \frac{2\pi}{\lambda}$
 $\lambda = v_p / f$ or $v_p = \frac{1}{\beta C} = v_r C$

velocity, speed of light

and solution also given:

$$I(x) = I^+ e^{-j\beta x} - I^- e^{+j\beta x}$$

with $I^+ = \frac{V^+}{Z_0}$ $I^- = \frac{V^-}{Z_0}$

where $Z_0 = \sqrt{\frac{L}{C}}$ "characteristic impedance"

Interpretation:

V & I are sums of forward and backward traveling waves (FTW, BTW)
 V^+, I^+ V^-, I^-

OPT


Why?

$$V(x,t) = |V^+| e^{j\theta^+} e^{-j\beta x} e^{j\omega t} + |V^-| e^{j\theta^-} e^{+j\beta x} e^{j\omega t}$$

$$= |V^+| e^{j[\omega t - \beta x + \theta^+]} + |V^-| e^{j[\omega t + \beta x + \theta^-]}$$

Time Delayed $e^{j\omega t}$ Time advanced $e^{j\omega t}$
 \Rightarrow moving in +x direction \Rightarrow moving in -x direction
 Phase of sinusoid at $x=0$

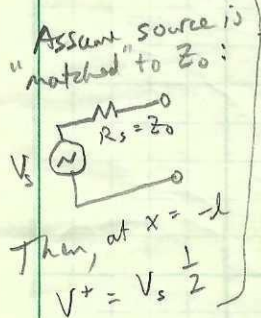Finding V^+, V^- (Fitting Boundary Conditions)



At $x=0$, $Z = Z_L$

But $Z_L = Z|_{x=0} = \frac{V(0)}{I(0)} = \frac{V^+ e^{-j\beta \cdot 0} + V^- e^{+j\beta \cdot 0}}{I^+ e^{-j\beta \cdot 0} - I^- e^{+j\beta \cdot 0}}$

$\Rightarrow Z(0) \equiv Z_L = \frac{V^+ + V^-}{\frac{V^+}{Z_0} - \frac{V^-}{Z_0}}$

NOTE at load
 V, I in phase if $Z_L = R_L$
 But not in phase at other locations $\Rightarrow Z \neq R_L$

Solve to find:


$$V^- = V^+ \frac{Z_L - Z_0}{Z_L + Z_0}$$

"Reflection coefficient" Γ

13,782 42,382 42,382 42,382 42,382 42,382 42,382 42,382 42,382 42,382
 500 SHEETS FULLER 5 SQUARE
 50 SHEETS FULLER 5 SQUARE
 100 SHEETS FULLER 5 SQUARE
 200 SHEETS FULLER 5 SQUARE
 400 SHEETS FULLER 5 SQUARE
 800 SHEETS FULLER 5 SQUARE
 1600 SHEETS FULLER 5 SQUARE
 3200 SHEETS FULLER 5 SQUARE
 Made in U.S.A.



Interpretation:

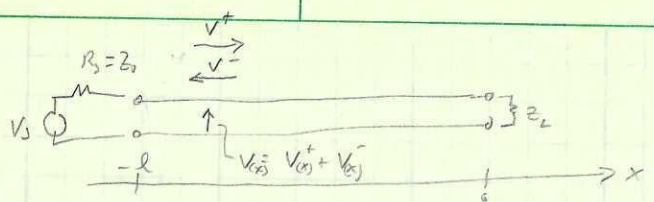

$$V^- = \Gamma V^+ \quad \text{where } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Backward Traveling wave (Dependent Variable) / "Reflection Coefficient" / Forward Traveling wave (Independent Variable)

"Because we can place a source at left side to launch V^+ "

NOTE: If $Z_L = Z_0$, $V^- \equiv 0$! (no reflection)

So, ...

$$V(-l) = V^+ e^{-j\beta(-l)} \quad I(-l) = I^+ e^{-j\beta(-l)}$$

$$\Rightarrow Z(-l) = \frac{V(-l)}{I(-l)} = \frac{V^+}{I^+} \frac{V^+}{V^+} = Z_0 = Z_L !$$

Smith Charts

Recall

$$V^- = V^+ \Gamma$$

or $\Gamma = \frac{V^-}{V^+}$

we found:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Can also get Z_L if Γ known (Γ easier to measure)

$$Z_L = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$$




Smith chart is

a graphical tool for mapping between Γ & Z
 a method for displaying impedances
 a method for finding Z_L given Γ

① On Polar Chart

Find $0, 50, \infty, 10, 500, +j50, -j50, \pm j10$

Ⓐ $\Gamma = -1 = 1 \angle 180^\circ$

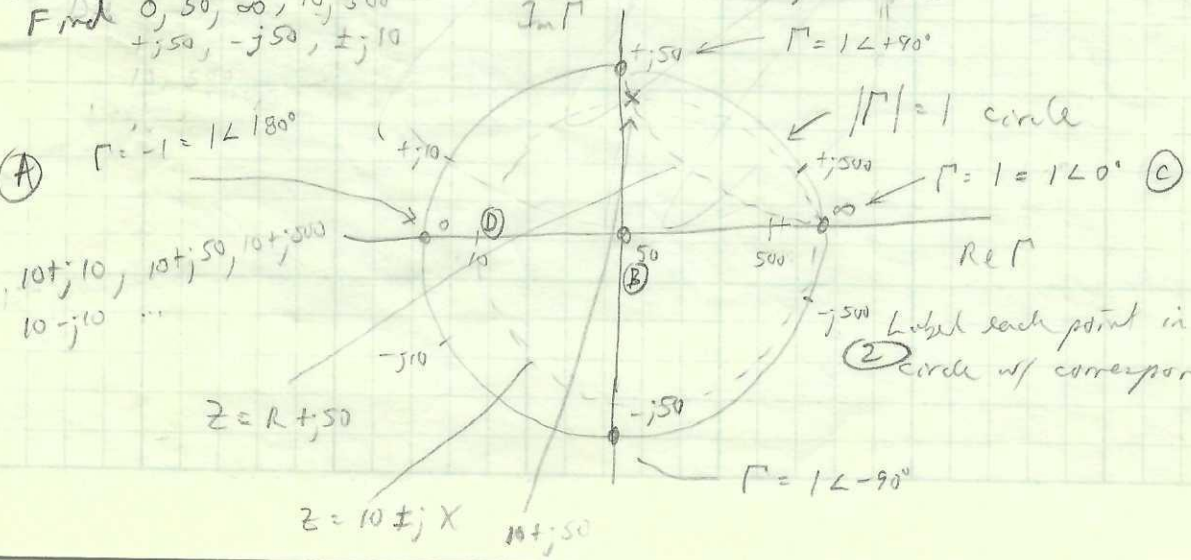


Label each point in circle w/ corresponding Z_L

13762 500 SHEETS FILLER 5 SQUARE
 42381 50 SHEETS FILLER 5 SQUARE
 42382 100 SHEETS FILLER 5 SQUARE
 42383 200 SHEETS FILLER 5 SQUARE
 42384 100 RECYCLED WHITE 5 SQUARE
 42385 200 RECYCLED WHITE 5 SQUARE
 Made in U.S.A.



Review of TX line Equations:

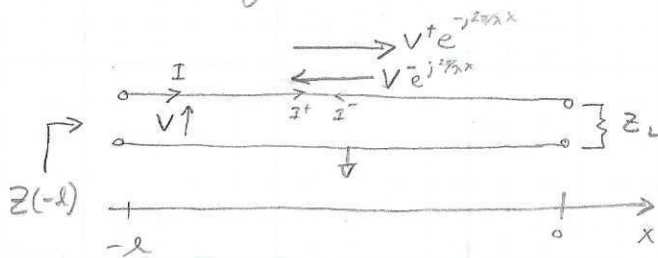

$$V(x) = V^+ e^{-j\frac{2\pi}{\lambda}x} + V^- e^{j\frac{2\pi}{\lambda}x}$$

$$I(x) = I^+ e^{-j\frac{2\pi}{\lambda}x} - I^- e^{j\frac{2\pi}{\lambda}x} \text{ where } I^+ = \frac{V^+}{Z_0} \quad I^- = \frac{V^-}{Z_0}$$

$$Z_0 = \sqrt{\frac{L}{C}} \quad \text{typically } 50 \Omega$$

$$\lambda = \frac{v_p}{f} \quad 0.5 \leq v_p < 1 \quad v_p = \frac{1}{\sqrt{\epsilon_r}}$$

V^- found from V^+ at load by

$$\Gamma_L \triangleq \frac{V^-(l)}{V^+(l)} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

or, if Γ_L is known

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

* NOTE: Equation also applies at other points on line.
 (Normalized) Smith Charts


Want to do Smith Chart for any Z_0

First normalize Z : $\bar{Z} \triangleq \frac{Z}{Z_0}$

Then $\Gamma = \frac{V^-}{V^+} = \frac{Z/Z_0 - Z_0/Z_0}{Z/Z_0 + Z_0/Z_0} = \frac{\bar{Z} - 1}{\bar{Z} + 1} = \Gamma$

and
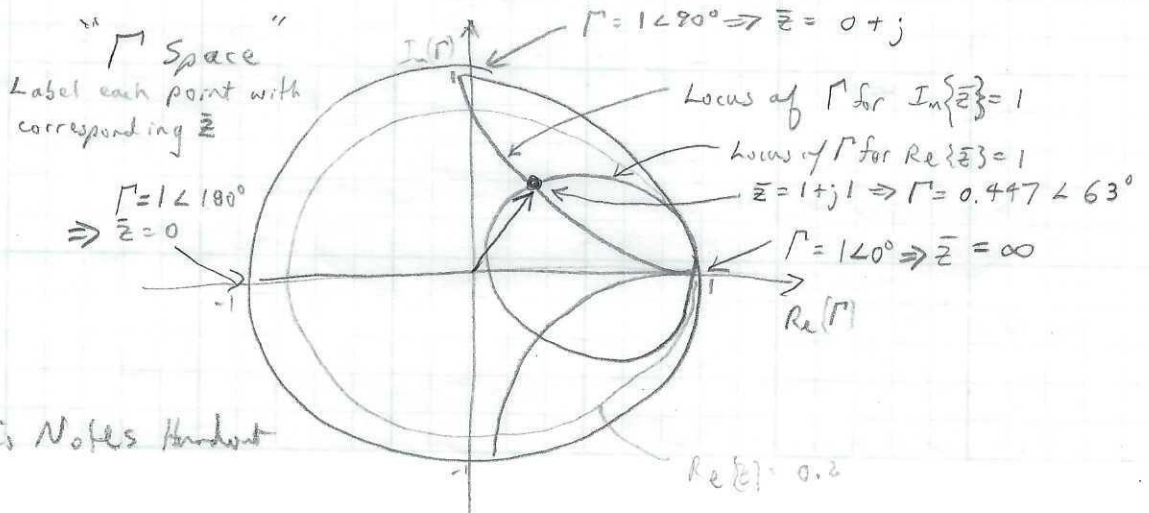
$$\bar{Z} = \frac{1 + \Gamma}{1 - \Gamma}$$



Show Davis Notes Handout

500 SHEETS, FILLER, 5 SQUARE
 50 SHEETS, EYE-EASE, 5 SQUARE
 100 SHEETS, EYE-EASE, 5 SQUARE
 42-382 100 SHEETS, EYE-EASE, 5 SQUARE
 42-389 100 SHEETS, EYE-EASE, 5 SQUARE
 42-396 200 RECYCLED WHITE, 5 SQUARE
 Made in U.S.A.



- What's a Smith Chart?
- 1) A graphical mapping between $\Gamma \leftrightarrow Z$
 - 2) A format for displaying Z
 - 3) A tool for finding $Z(l)$ given Z_L
 - 4) The coolest thing in the world
 - 5) All of the above

Finding Z at $-l$ (distance of l "toward generator")

Recall $V^+(x) = V_L^+ e^{-j\beta x}$, $V^-(x) = V_L^- e^{+j\beta x}$, $\omega/\beta = \frac{2\pi}{\lambda}$


Hence, $\Gamma(x) = \frac{V^-(x)}{V^+(x)} = \frac{V_L^-}{V_L^+} e^{+j2(2\pi \frac{x}{\lambda})}$

and $\Gamma(-l) = \Gamma_L e^{-j2(2\pi \frac{l}{\lambda})}$ Phase change \rightarrow $\begin{cases} 360^\circ \text{ for } l = \lambda/2 \\ -180^\circ \text{ for } l = \lambda/4 \\ -90^\circ \text{ for } l = \lambda/8 \end{cases}$

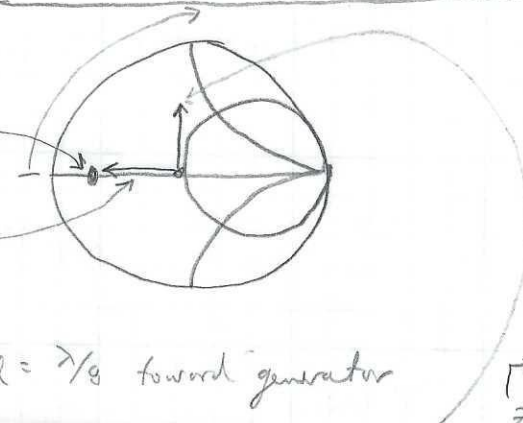Example $\lambda/8 = \frac{1}{8}$

On Smith Chart:

$Z_L = 10 \Omega$ w/ $Z_0 = 50 \Omega$
 $\Rightarrow \bar{Z}_L = 0.2$
 $\Rightarrow \Gamma_L = 0.667 \angle 180^\circ$



$\lambda = \frac{c v_r}{f}$
 $= \frac{(3 \times 10^8)(0.66)}{16 \times 10^6} = 1.22 \text{ m}$
 $\lambda/8 = 15 \text{ cm}$


At distance $l = \lambda/8$ toward generator

$\Gamma_{-l} = 0.667 \angle (180^\circ - 90^\circ)$
 $= 0.667 \angle 90^\circ$

$\Rightarrow \bar{Z} = 0.385 + j 0.923$ (From eqn or chart)

$\Rightarrow Z = 19.2 + j 46.2$

change in R also \uparrow series L

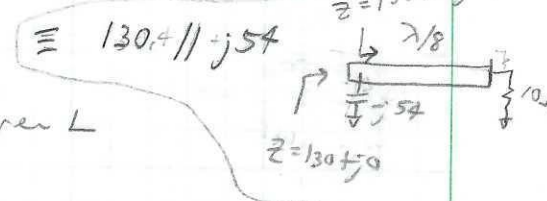

★ Show Amplifier

Am ^{BIG} Impedance transformation!

Important special cases

Z_L	l	$Z(-l)$	Comments
∞	$\lambda/4$	zero!	Open becomes a short!
0	$\lambda/4$	∞	Short becomes open
∞	$l < \lambda/4$	$0 - jX$	Open becomes capacitor
∞	$\lambda/4 < l < \lambda/2$	$0 + jX$	
0	$l < \lambda/4$	$0 + jX$	Short becomes inductor
0	$\lambda/4 < l < \lambda/2$	$0 - jX$	
Z_0	Anything	Z_0	Unchanged since load is "matched" to line impedance

16-782 500 SHEETS FILLER 5 SQUARE
 42-381 50 SHEETS EYE EASY 5 SQUARE
 42-380 100 SHEETS EYE EASY 5 SQUARE
 42-382 100 SHEETS EYE EASY 5 SQUARE
 42-389 100 SHEETS EYE EASY 5 SQUARE
 42-388 100 SHEETS EYE EASY 5 SQUARE
 42-389 200 RECYCLED WHITE 5 SQUARE
 42-389 200 RECYCLED WHITE 5 SQUARE
 Made in U.S.A.
 National Brand



Measures of "Goodness of match" to Z_0

Incident Power = $\frac{|V^+|^2}{Z_0}$

Reflected Power = $\frac{|V^-|^2}{Z_0}$

$V_{tot} = \Gamma V_{inc}$ $V_{tot} = V_{inc}^+ + V_{inc}^-$

SWR (or VSWR) (Voltage) Standing Wave Ratio

RL Return Loss

SWR
(or VSWR)

$SWR \triangleq$

$\frac{\text{max voltage on line}}{\text{min voltage on line}} = \frac{|V^+| + |V^-|}{|V^+| - |V^-|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$

Good = small e.g. $SWR < 2:1$
(i.e. $\Gamma < 0.333$)


Ideal = 1:1 why?

RL

Return Loss $\triangleq 10 \log \left[\frac{\text{Incident power}}{\text{Reflected power}} \right]$ (in dB)

Good = Big e.g. $RL \geq 12 \text{ dB}$
 $\Rightarrow \Gamma \leq 10^{-\frac{RL}{20}} \Rightarrow \Gamma \leq 0.25$

$RL = -20 \log |\Gamma|$

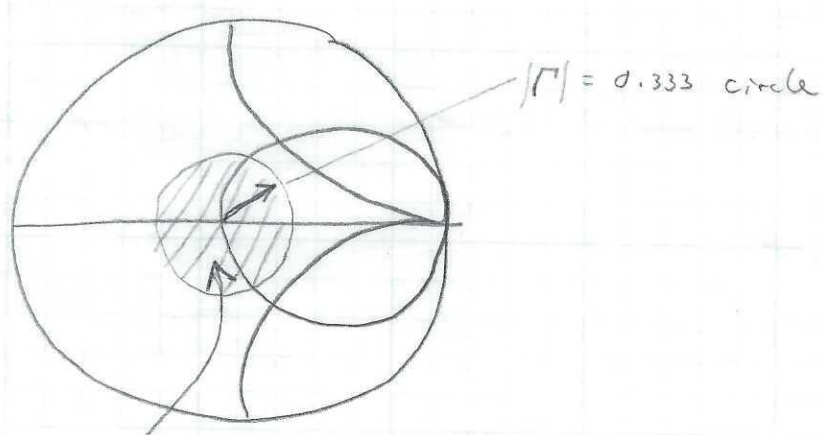


$RL \geq 10 \text{ dB}$, $SWR \leq 2$
inside this region

(i.e. Z "close to" Z_0)

$|S_{11}|$

Like Return loss - but opposite sign in dB

$|S_{11}| = +20 \log |\Gamma|$

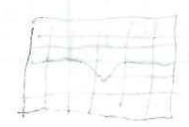

13 780 500 SHEETS, FULLER 5 SQUARE
42 381 50 SHEETS, EYE-EASE 5 SQUARE
42 382 100 SHEETS, EYE-EASE 5 SQUARE
42 383 50 SHEETS, EYE-EASE 5 SQUARE
42 384 100 SHEETS, EYE-EASE 5 SQUARE
42 385 200 SHEETS, EYE-EASE 5 SQUARE
42 386 200 RECYCLED, WHITE 5 SQUARE
42 389 200 RECYCLED, WHITE 5 SQUARE
Made in U.S.A.

National Brand