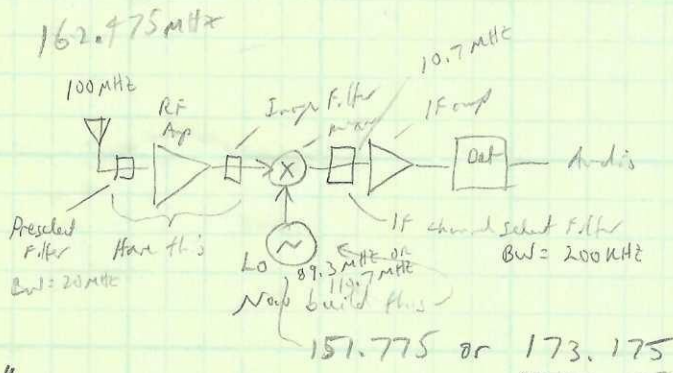



(Intentional) 10/8
Oscillator Design

Recall $\omega = 2\pi f$ & Bandwidth

Semester Product




"Midterm" FM TX Block Diagram

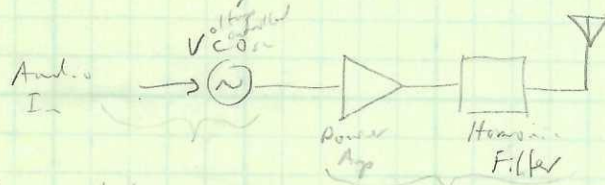

Add freq control to osc
Connect to amp & get complete TX (Midterm "Exam")


(INTENTIONAL) OSCILLATOR DESIGN

Draw CB amp 1st

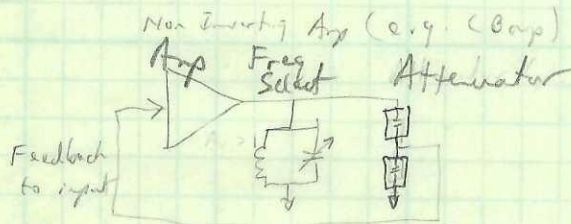

"Colpitts"

OR
Inverting Amp (e.g. CE amp)

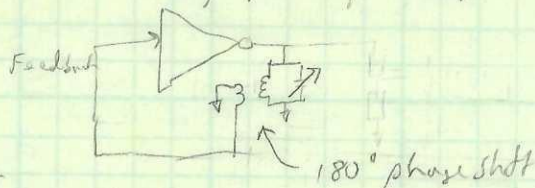

"Hartley"



Condition for osc:

- 1 "Loop gain" (either $|A_v|$ or G_p) ≥ 1
- 2 Phase shift around loop = 0° or $\pm n(360^\circ)$

1. Determine osc "start time" (together with chf α)
2. Determine frequency of osc

C B Oscillator

Ac chit

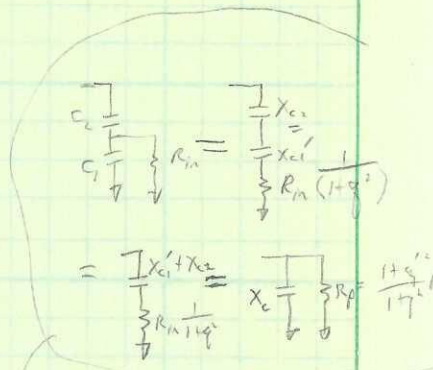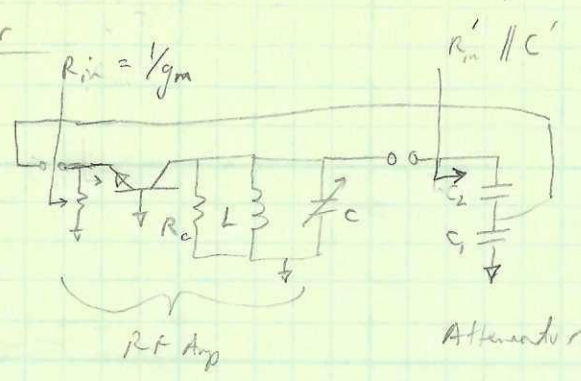

NOTES:

- Use C_1, C_2 for "voltage divider" (attenuator) instead of R_s because a) R_s is not R_s at HF, b) R_s load fault chit

- Effect of (C_1 series C_2) must be considered in determining f_o
- C_1, C_2 acts as a simple V divider iff $X_{C1} \ll R_m$
- ~~R_m~~ R_m is transformed to $R_m' \parallel C'$ and is in \parallel w/ R_c
 \Rightarrow loop gain is decreased, tank freq changed
- Effect of C' must be considered in calculation of f_o

Simplified analysis:

Let $X_{C1} \ll R_m$

Then $A_{th} \approx \frac{-jX_{C1}}{jX_{C1} + jX_{C2}} \approx \frac{C_2}{C_1 + C_2}$
 $C' \approx C_1 - C_2 = \frac{C_1 C_2}{C_1 + C_2}$

$R_m' \approx \left(\frac{X_{C1} + X_{C2}}{X_{C1}} \right)^2 R_m$

Loop Gain = $g_m \left(R_c \parallel R_m' \right) \frac{X_{C1}}{X_{C1} + X_{C2}}$
 Remove physical

Loop Gain $\approx g_m R_m' \frac{X_{C1}}{X_{C1} + X_{C2}}$
 $\approx g_m R_m \left(\frac{X_{C1} + X_{C2}}{X_{C1}} \right)^2 \left(\frac{X_{C1}}{X_{C1} + X_{C2}} \right)$
 $= g_m R_m \frac{X_{C2} + X_{C1}}{X_{C1}}$
 $\approx g_m \frac{1}{g_m} \frac{X_{C2} + X_{C1}}{X_{C1}}$

$= 1 + \frac{X_{C2}}{X_{C1}}$ (flipped)
 $= 1 + \frac{C_1}{C_2}$


Set loop gain = 2 to 4 for robustness

$\Rightarrow C_1 = 1 \text{ to } 3 \text{ times } C_2$

Pure Conservation
 $\frac{V_2^2}{R_m'} = \frac{V_1^2}{R_m}$
 $\Rightarrow \frac{R_m'}{R_m} = \left(\frac{V_1}{V_2} \right)^2$

(.04) (200)
 $\frac{1}{X_{C1}}$
 $\frac{1}{X_{C2}}$
 $\frac{1}{X_{C1} + X_{C2}}$
 $g_m R_m$
 $g_m \frac{1}{g_m}$
 $\frac{C_1}{C_1 + C_2}$
 $\frac{C_2}{C_1 + C_2}$
 $\frac{C_1 C_2}{C_1 + C_2}$
 $\frac{X_{C1} + X_{C2}}{X_{C1}}$
 $\frac{X_{C2} + X_{C1}}{X_{C1}}$

Colpitts Osc

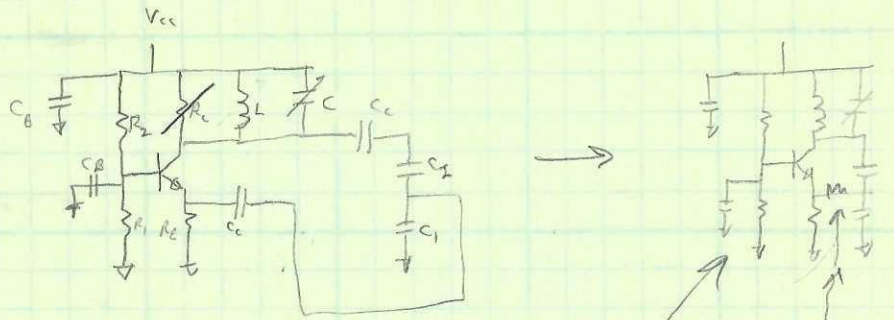

Which components are needed? (R_C & C_C)


Show Example

Design Procedure

- 1) Start with tuned load RF amp config (w/o R_C)
- 2) Choose $C_1 \Rightarrow X_{C1} \approx \frac{1}{2} r_e = \frac{1}{2g_m}$
- 3) Pick C_2 on 1 to 3 times C_1
- 4) Pick C & L to give desired freq / tuning range (Influence of choice & step)
- 5) Consider using emitter input resistor to raise R_{in}

Osc Output

Can take output from E or C nodes

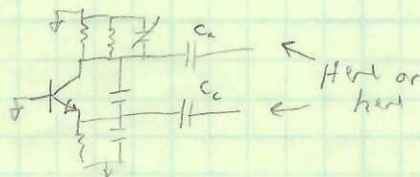

Constraints

Pick C_C to

- Introduce minimal loading (gain change)
- Cause minimal freq shift
- Get desired signal V, P to load.


Amplitude

At emitter $v_e \approx 50$ to $200mV_{RMS}$


Why?

CC Colpitts Osc


Recall CB Osc

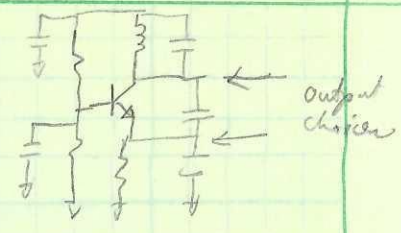


AC ckt for CB Colpitts osc is

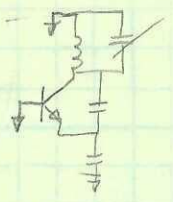

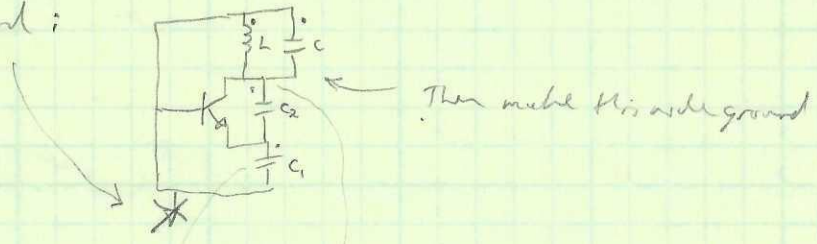
What is ckt good? Just a reference point for other voltages
 Connected, then
 Remove ground:



Redraw:

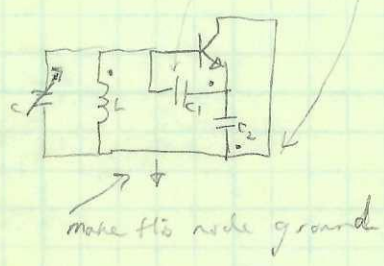

Ckt with Bias included:

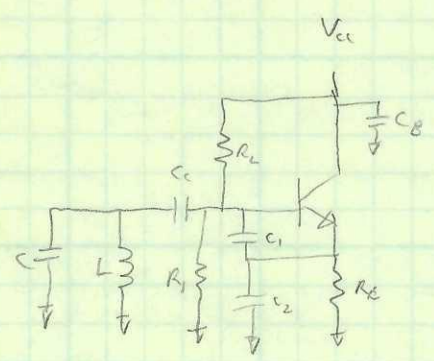

★ Can also view as CC
 ckt with C_2, C_1 forming
 V steps feeding back
 to base
 $V_b = \frac{R_2 + R_c}{R_2} V_i$


★ Show Example (from μW journal)

★ Discuss CC buffering

Voltage Controlled Oscillators (VCO)

Recall

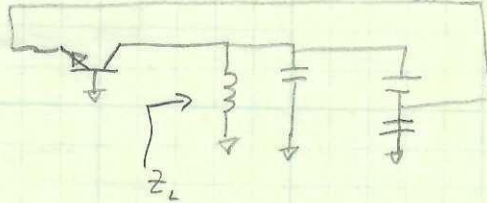Osc Freq determined by phase shift around loop



$$\omega f_0 = \frac{1}{2\pi\sqrt{LC_{tot}}}, \quad \angle Z_L = 0 \implies \text{oscillation}$$

To vary f_0 , use pot or var


$$A_{V_{loop}} = g_m Z_L \frac{X_{c1}}{X_{c1} + X_{c2}}$$

$f = f_{osc}$

$Z_L = \text{circle}$

$f = f_{high}$

Voltage controlled capacitors

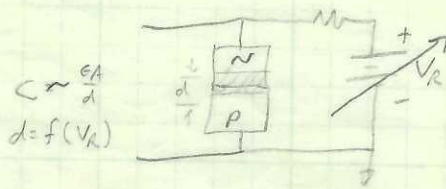


Varactor Diode:



Provides high cap change per volt


★ Show Data Sheet MMBV609L

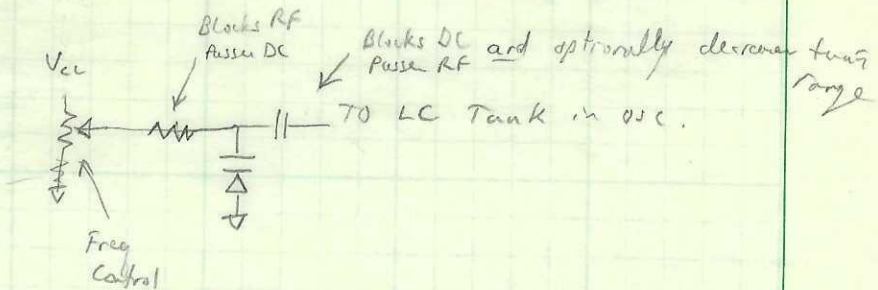Practical ckt for voltage controlled tuning



- ★ Slow pot & mounting
- ★ Show mic

FM modulation:

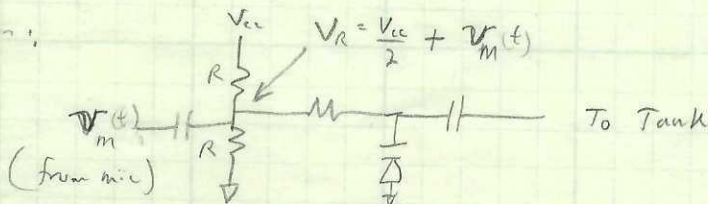


Skip

★ Show Examples: RS cell phone

10/10
Additional Osc Types

Freq Stability

CB colpitts
Consider OSC

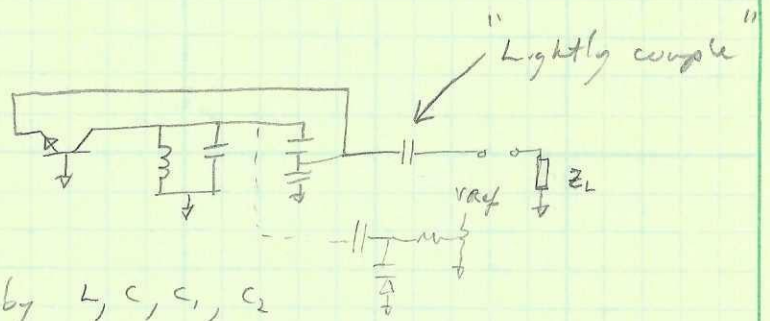

f_0 primarily determined by L, C, C_1, C_2


Also affected by:

- Changes in C_{cb}, C_{be} with ~~osc~~ supply voltage, temperature
- changes in L, C values w/ temperature ($\approx 50 \text{ ppm}/^\circ\text{C}$)
- changes in load resistance/reactance!
- Changes in varactor reference voltage

Solns:

★ Show data sheet.

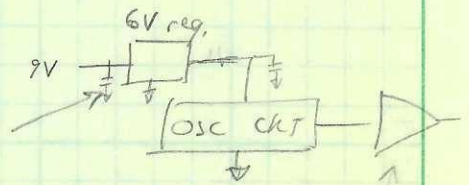
- Use regulated pure supply (filtered)
- Add buffer caps at output (to isolate oscillator from load)
- Use temperature stable components (NPO capacitors)
- And/or Use crystal controlled PLLs! (discussed later)





Short Term Stability & Phase Noise

Ideal Osc Spectrum

a way to vary f_0 under V (or I) control

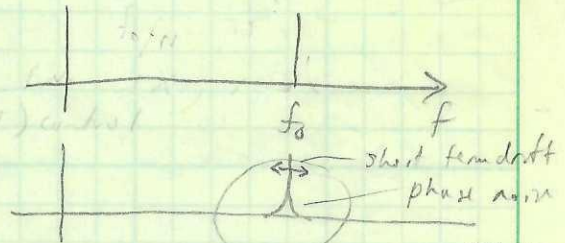

Actual Spectrum

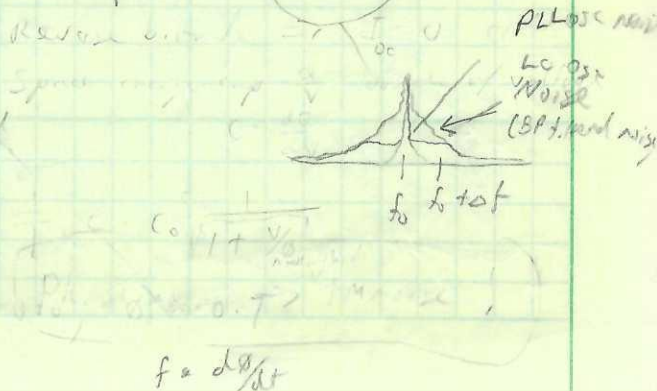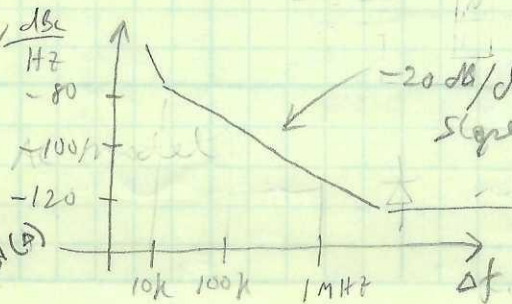

Brim Example

(0650 + Spectra)

$V_{osc} = A_e \cdot i_{osc}$
 $\approx A_e \cdot i_{osc}$
 $A_e = \frac{V_{osc}}{i_{osc}}$
 $A_e = \frac{V_{osc}}{i_{osc}} \cdot \frac{1}{\sqrt{2}}$
 $A_e = \frac{V_{osc}}{i_{osc}} \cdot \frac{1}{\sqrt{2}}$

$f_0 \frac{df_0}{dt}$

Modeling Phase Noise and measuring in "dBc/Hz"

Ideal Oscillator

$$V_{osc}(t) = A \cos(\omega_0 t)$$

or


$$V_{osc} = \text{Re} \{ A e^{j\omega_0 t} \}$$

Oscillator w/ phase noise (Re{ } implied)

$$V_{osc}(t) = A e^{j(\omega_0 t + n(t))}$$

$$= A e^{j\omega_0 t} e^{jn(t)}$$

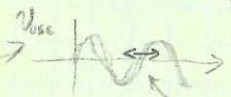random phase variations
due to thermal noise etc




By Taylor Series Expansion (for $n(t) \ll 1$) greatly exaggerated

$$V_{osc}(t) \approx A e^{j\omega_0 t} (1 + jn(t))$$

Taking Fourier Transform
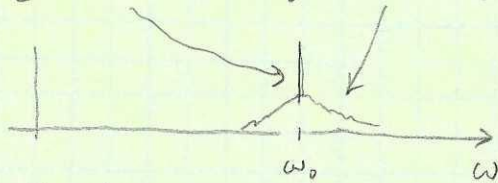
$$V(\omega) = A [2\pi \delta(\omega - \omega_0) + jN(\omega - \omega_0)]$$



PN is measured using spectrum analyzer as ratio of power in noise side bands to the total osc power

difference
is dB units

$$PN \Big|_{\text{dBc/Hz}} \triangleq P_{osc} \Big|_{\text{dBm}} - P_n(\Delta\omega) \Big|_{\text{dBm in 1Hz bandwidth}}$$

★ Show/draw a spectrum w/ spec an measur

Phase Noise measurement


Measure total P_{osc} in dBm

Measure $P_n(\Delta f)$ in dBm

Normalize by RBW $P_n(\Delta f) \Big|_{dBm} = P_n(\Delta f) \Big|_{dBm} - 10 \log(RBW)$


Compute/Plot $PN(\Delta f) \Big|_{dBc/Hz} = P_{osc} \Big|_{dBm} - P_n(\Delta f) \Big|_{dBm}$

Δf	$P_n(\Delta f)$	$P_{noise}(\Delta f)$	$PN_{dBc/Hz}$
1K			
3K			
10K			
30K			
100K			
300K			

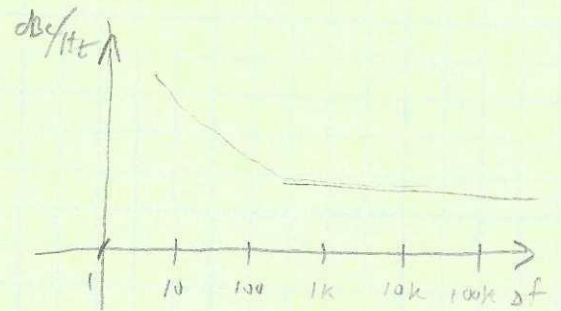

PN Effects on Systems

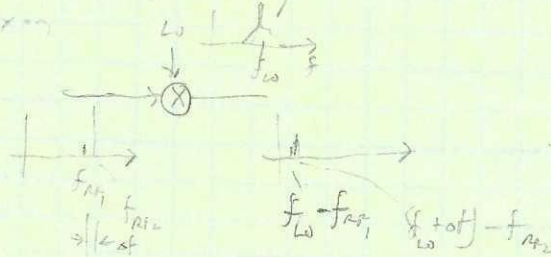- FM noise in analog modulation - limits audio SNR
- Phase variations in PSK signal constellations
- Residual mixer



PN Reduction

- Use higher Q oscillators
- Use PLL with high quality reference oscillator
- Other - BJT better than CMOS, etc.