


Crystal Osc <sup>(XO)</sup> & Voltage Controlled Crystal Osc (VCXO)

Frequency ~~of XO~~ must normally be tightly controlled  
 Typical accuracy requirements

FM  $\ll \pm 200 \text{ kHz}$  @ 100 MHz      2000 ppm (0.2%)  
 NBFM (Cellular)  $\ll \pm 30 \text{ kHz}$  at 900 MHz!      33 ppm (0.0033%)

Can't achieve with standard components  
 Even if aligned, will drift  $\approx \pm 25 \text{ ppm}/^\circ\text{C}$  (or 0.1% for 50° change)  
 = 1 MHz out of 1 GHz

SOLN: Use Electro-acoustic Resonators!

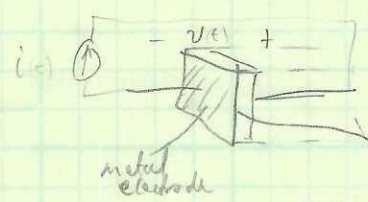


AC current  $\Rightarrow$  Voltage  $\Rightarrow$  E field  $\Rightarrow$  Stress  $\Rightarrow$  Strain (delayed)  $\Rightarrow$  Voltage


Resonant when thickness =  $\frac{1}{2}$  acoustic wavelength, or  $\frac{3}{2}$ , or  $\frac{5}{2}$ , etc

PASS OUT crystals

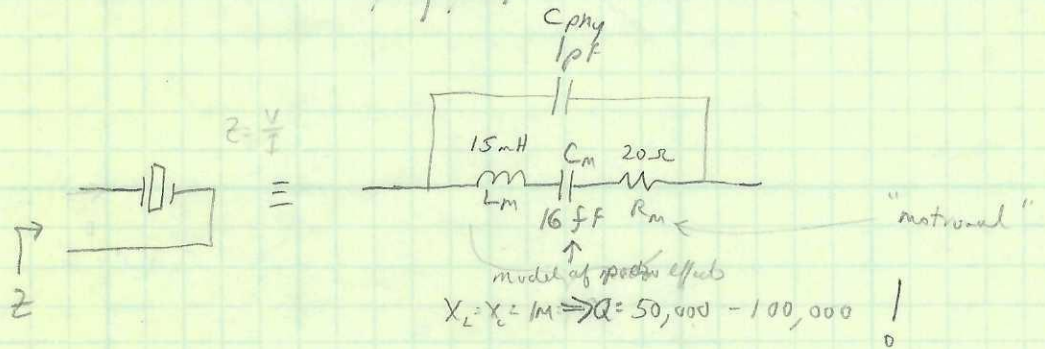
Electrical model of I/V characteristic (fundamental resonance)



Reactance vs freq

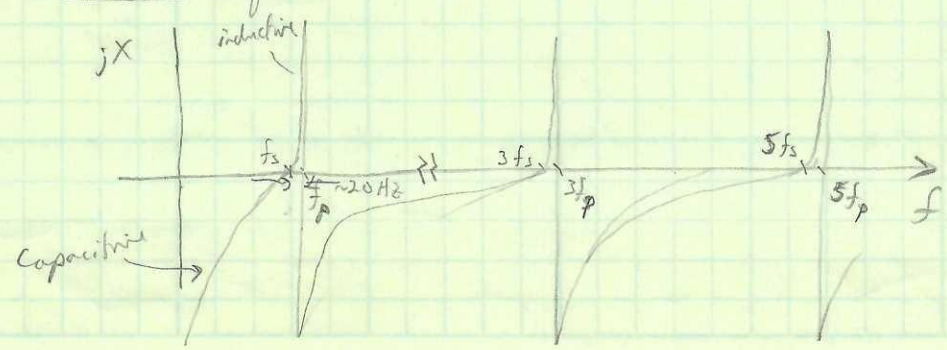


Stable Oscillators  
Varactor Oscillator

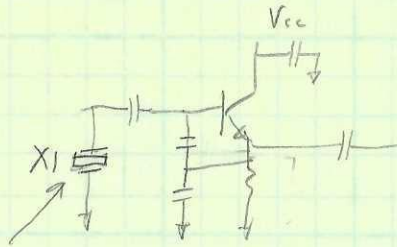

ckt oscillator between  $f_s$  &  $f_p$  where  $X1$  is inductive and reactance  $X_L = X_{C1} - C_2$

Voltage Controlled Crystal Osc Vcxo

Add varactor across crystal

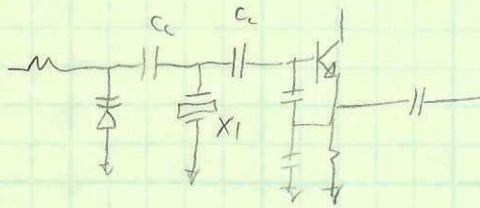

Temperature Compensated XO (TCXO)

Add temp sensor and freq drift compensation ckt




Result:  $f_0$  accurate to  $< 1 \text{ ppm}$  over temperature!  
 ( $\pm 162 \text{ Hz}$  at  $162 \text{ MHz}$ )

Problems

fundamental  $f_0$  limited to  $< 50 \text{ MHz}$  for crystal based oscillators  
 Cant "pull"  $f_0$  very far e.g.  $\pm 1 \text{ kHz}$

Solns Frequency Synthesis

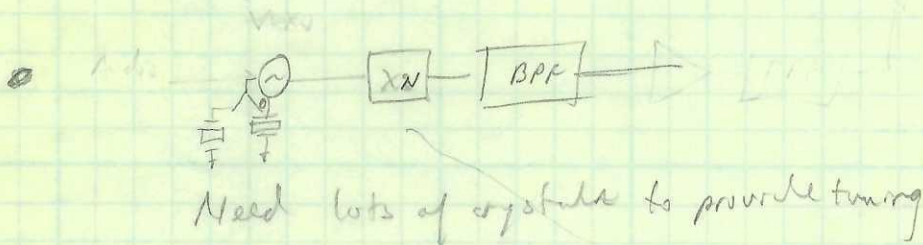

Use as reference for PLL frequency synthesizer

