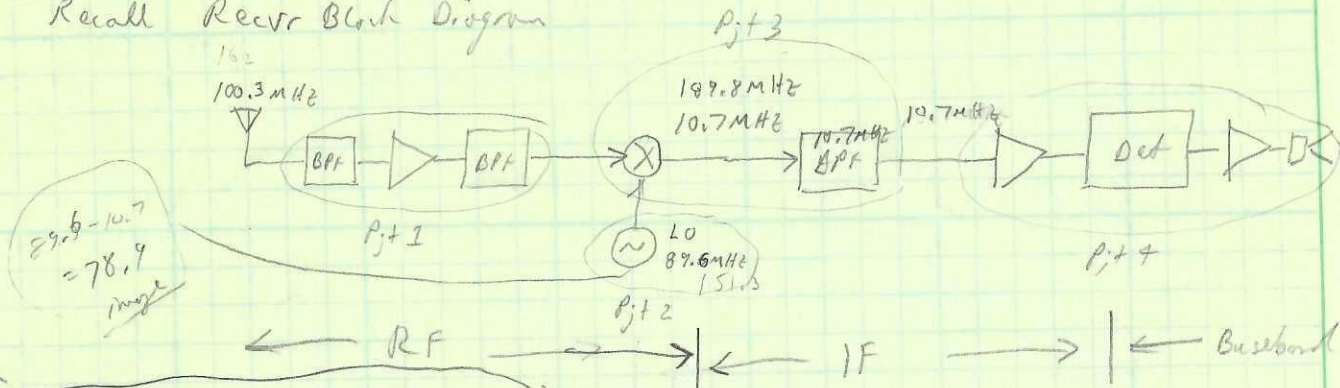


10/26
Mixer Designs

Recall Recvr Block Diagram




Slow Cell phone Schematic (mixer + filter)

Next step is Mixer Downconvert

"Down conversion"

Consider "Ideal" mixer

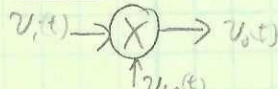

$$V_o(t) = A_v V_{RF}(t) V_{LO}(t)$$

Simplified Analysis

Let $V_{RF}(t) = V_1 \cos(\omega_{RF} t)$
Input amplitude


$V_{LO}(t) = V_2 \cos(\omega_{LO} t)$
LO amplitude

Result $\cos(\alpha) \cos(\beta) = \frac{1}{2} \cos(\alpha + \beta) + \frac{1}{2} \cos(\alpha - \beta)$

Then $V_o(t) = \underbrace{\frac{A_v}{2} V_1 V_2 \cos((\omega_{RF} + \omega_{LO}) t)}_{\text{Undesired output Filter to remove}} + \underbrace{\frac{1}{2} V_1 V_2 \cos((\omega_{RF} - \omega_{LO}) t)}_{\text{Desired "product" at 10.7 MHz}}$

In Frequency Domain:
FM Station
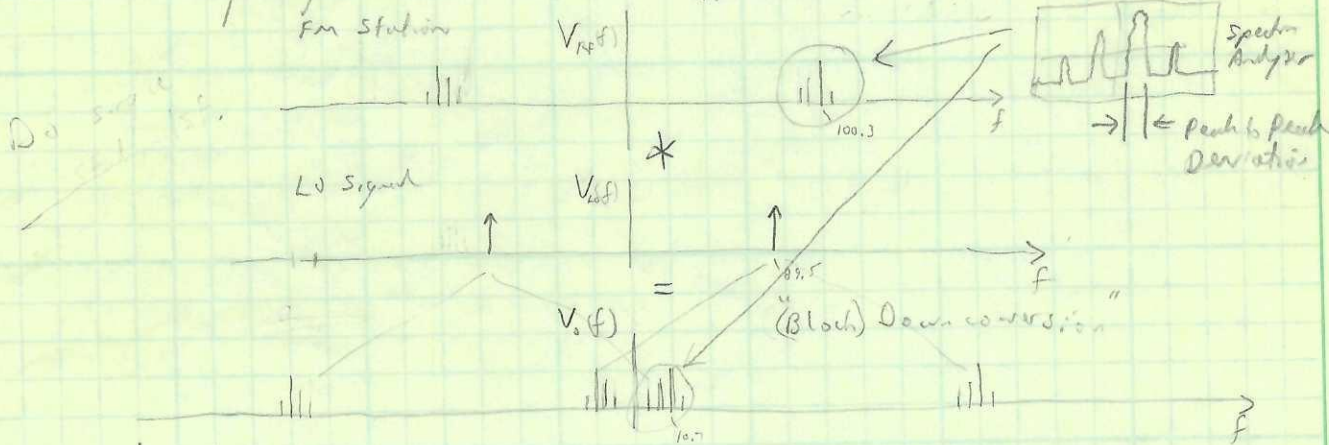
$$V_o(f) = V_{RF}(f) V_{LO}(f) \leftrightarrow V_o(f) = V_{RF}(f) * V_{LO}(f)$$



After IF BPF:




Practical Implementation

- Diode & Transistor mixers
- Switching mixers
- Diode Ring
- Gilbert Cell
- Image


Practical Implementations

- { Diode & Transistor mixers
- { Diode Ring mixers
- { IC mixers - Gilbert Cell

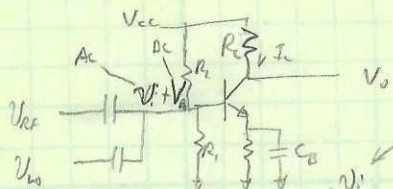older BJT mixer (simple, cheap, and high frequency)



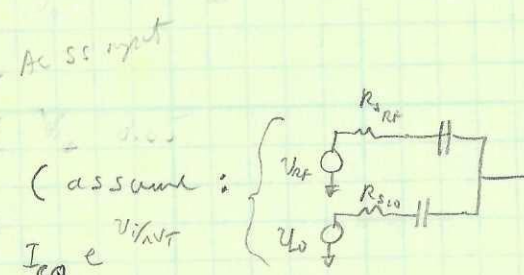$V_B \approx \frac{R_1 V_{CC} + R_2 V_{CC}}{R_1 + R_2}$
 $V_i = k_1 V_{RF} + k_2 V_{LO}$
 $I_c \approx I_e = I_0 e^{\frac{V_{BE} + V_i}{nV_T}} = I_{CQ} e^{V_i/nV_T}$
 $V_o = V_{CC} - R_C I_c$ ("a scaled - offset version of I_c ")



Look at I_c :

$$I_c = I_{CQ} e^{\frac{k_1 V_{RF} + k_2 V_{LO}}{nV_T}}$$

$$= I_{CQ} \left(e^{\frac{k_1 V_{RF}}{nV_T}} \right) \left(e^{\frac{k_2 V_{LO}}{nV_T}} \right)$$

Recall $e^x = 1 + x + \frac{x^2}{2} + \dots$


$$\stackrel{\substack{k_1 V_{RF} \ll nV_T \\ V_{LO} = \cos(\omega_{LO} t)}}{=} I_{CQ} \left(1 + \frac{k_1 V_{RF}}{nV_T} + \dots \right) \left(e^{\frac{k_2 \cos(\omega_{LO} t)}{nV_T}} \right)$$

McLaurin Expansion ← periodic

$$\approx I_{CQ} \left(1 + \frac{k_1 V_{RF}}{nV_T} \right) \left(\sum_{n=0}^{\infty} c_n \cos(n\omega_{LO} t + \theta_n) \right)$$


$$= \left(\frac{I_{CQ} k_1}{nV_T} V_{RF} \right) \left(c_1 \cos(\omega_{LO} t + \theta_1) \right) + \text{extra terms}$$

Spectrum

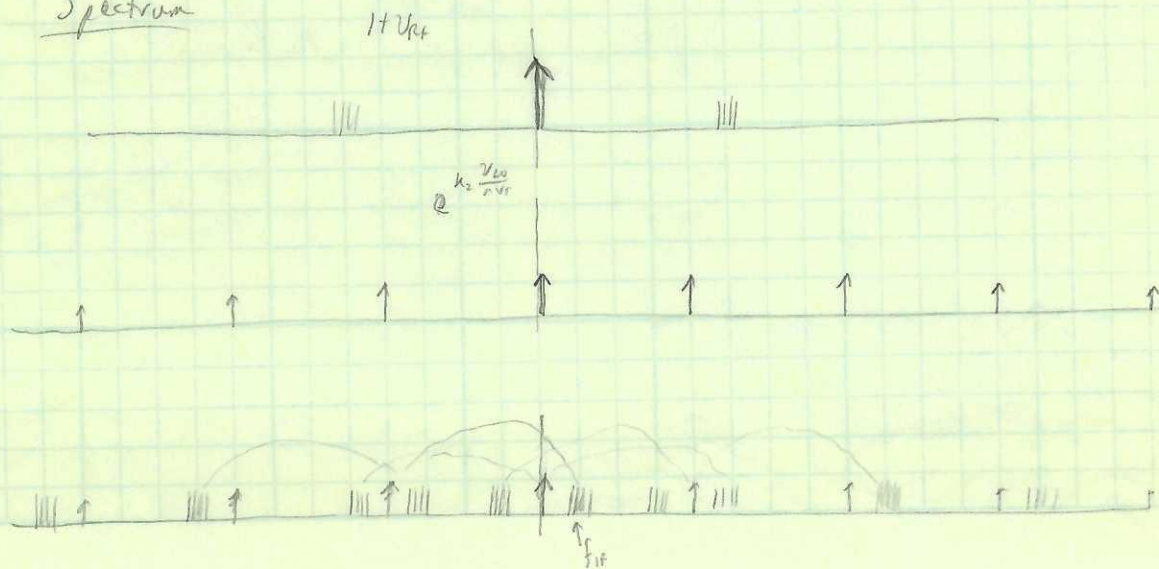

Switching mixers


Concept

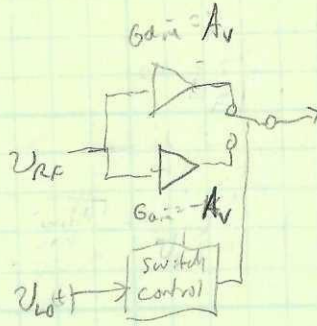

$$V_{IF} = V_{RF}(t) \cdot \text{sgn}[V_{LO}(t)] \cdot A_v$$

Spectrum:

Diode Ring Mixer

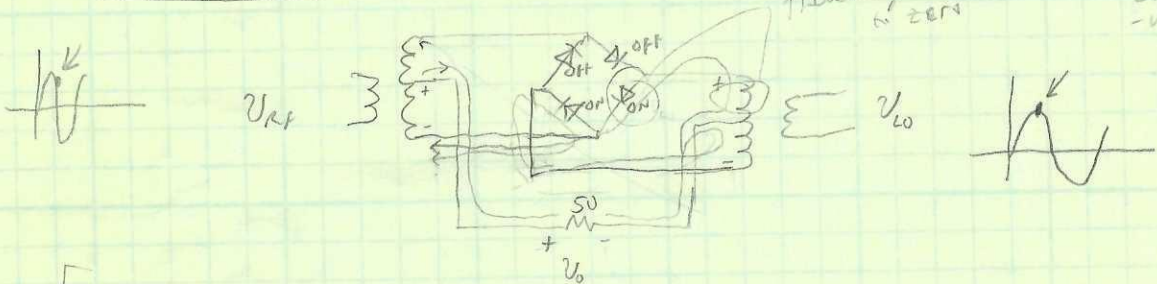

Diode Behavior

Diode off \rightarrow $1pF$ "open circuit" ("large" reactance)

Diode on \rightarrow "small" resistance

$r_d = \frac{nV_T}{I_D}$ ← From $I_D = I_0 e^{\frac{V}{nV_T}}$

$\frac{dI_D}{dV} = \frac{1}{nV_T} I_0 e^{\frac{V}{nV_T}} = \frac{I_D}{nV_T}$

$\Rightarrow \frac{dV}{dI_D} = R = \frac{nV_T}{I_D}$

Called Double Balanced because...

RF isolated from LO - "No" LO signal goes out RF port

IF isolated from LO & RF - "No" LO or RF signal goes to IF ideally

★ Show Example from MCL

Typical Impedance

Diode off:

$1pF @ 160MHz \approx -j1K\Omega$

Diode on:


$r_d @ 1mA = 26\Omega$

1E12
6(5016)
21K
3
3
0.025
1

① Result Ideal mixer
 Demodulator mixer
 factor
 fr-tu


② Switching mixer
 $A_v = k$
 $A_v = k$
 $V_{IF} = U_{RF} \times A_v$
 $U_{LO} = \dots = A_v \times U_{RF} \times \left[\frac{4}{\pi} \sin(\omega_{LO} t) - \frac{1}{3} \frac{\sin(3\omega_{LO} t)}{3} + \dots \right]$

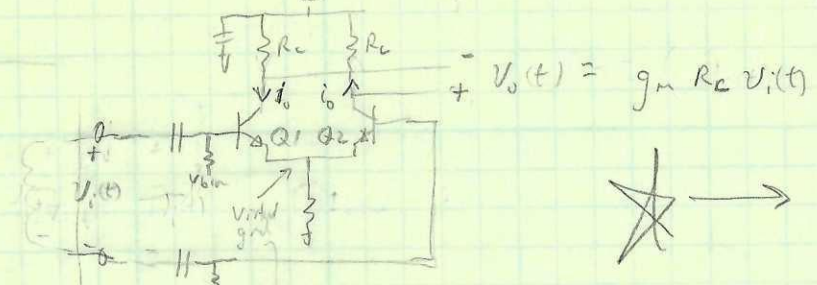IC Switching mixers 2x2
 Begin with a Differential Amplifier



★ → Slow cascade version:

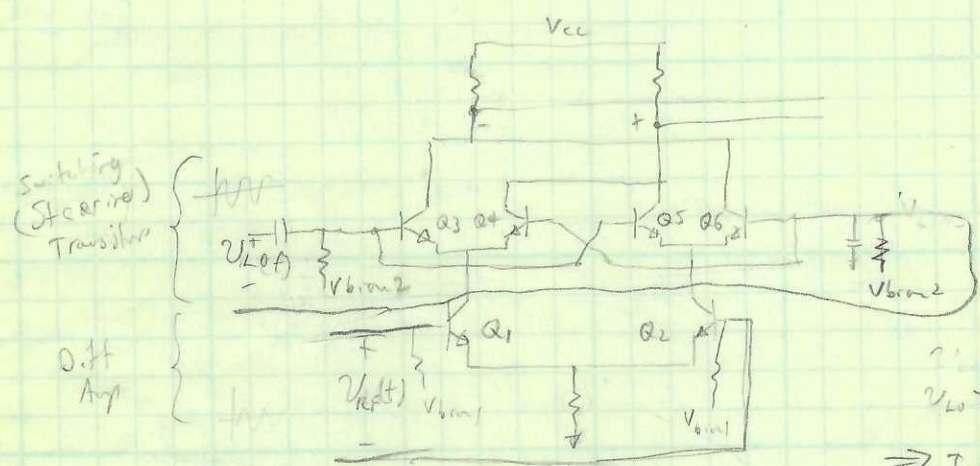Mixer: Don't need C_E ! because voltage stays constant due to balance
 cascode
 A del. switching transistors



$v_{LO} > 0V \Rightarrow Q_3, Q_5$ on
 \Rightarrow Inverting amp (cascode) Q_4, Q_6 off
 $v_{LO} < -0V \Rightarrow Q_3, Q_5$ off
 Q_4, Q_6 on
 \Rightarrow Non-inverting amp

Result: Switching mixer with gain

Called "Gilbert Cell mixer"
 Abstract V.ew.
 after Berry Gilbert

