

Double-balanced mixer and oscillator

SA602A

BLOCK DIAGRAM

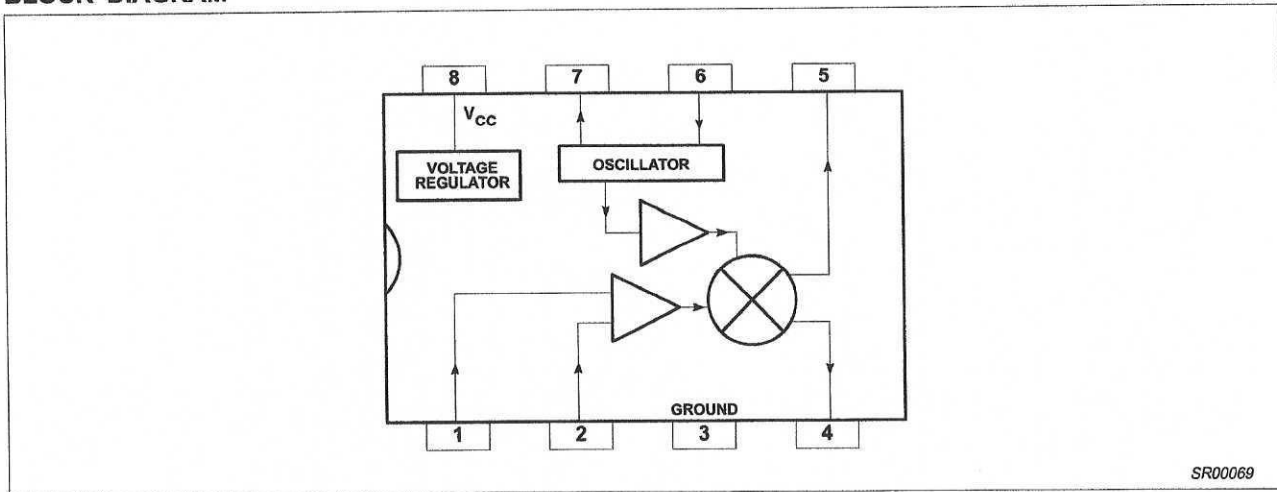


Figure 2. Block Diagram

AC/DC ELECTRICAL CHARACTERISTICS

$V_{CC} = +6V$, $T_A = 25^\circ C$; unless otherwise stated.

SYMBOL	PARAMETER	TEST CONDITIONS	LIMITS			UNITS
			SA602A			
			MIN	TYP	MAX	
V_{CC}	Power supply voltage range		4.5		8.0	V
	DC current drain			2.4	2.8	mA
f_{IN}	Input signal frequency			500		MHz
f_{OSC}	Oscillator frequency			200		MHz
	Noise figure at 45MHz			5.0	5.5	dB
	Third-order intercept point	$RF_{IN} = -45dBm$; $f_1 = 45.0MHz$ $f_2 = 45.06MHz$		-13	-15	dBm
	Conversion gain at 45MHz		14	17		dB
R_{IN}	RF input resistance		1.5			$k\Omega$
C_{IN}	RF input capacitance			3	3.5	pF
	Mixer output resistance	(Pin 4 or 5)		1.5		$k\Omega$

DESCRIPTION OF OPERATION

The SA602A is a Gilbert cell, an oscillator/buffer, and a temperature compensated bias network as shown in the equivalent circuit. The Gilbert cell is a differential amplifier (Pins 1 and 2) which drives a balanced switching cell. The differential input stage provides gain and determines the noise figure and signal handling performance of the system.

The SA602A is designed for optimum low power performance. When used with the SA604 as a 45MHz cellular radio second IF and demodulator, the SA602A is capable of receiving -119dBm signals with a 12dB S/N ratio. Third-order intercept is typically -13dBm (that is approximately +5dBm output intercept because of the RF gain). The system designer must be cognizant of this large signal limitation. When designing LANs or other closed systems where transmission levels are high, and small-signal or signal-to-noise issues are not critical, the input to the SA602A should be appropriately scaled.


Besides excellent low power performance well into VHF, the SA602A is designed to be flexible. The input, RF mixer output and oscillator ports can support a variety of configurations provided the designer understands certain constraints, which will be explained here.

The RF inputs (Pins 1 and 2) are biased internally. They are symmetrical. The equivalent AC input impedance is approximately $1.5k \parallel 3pF$ through 50MHz. Pins 1 and 2 can be used interchangeably, but they should not be DC biased externally. Figure 5 shows three typical input configurations.

The mixer outputs (Pins 4 and 5) are also internally biased. Each output is connected to the internal positive supply by a $1.5k\Omega$ resistor. This permits direct output termination yet allows for balanced output as well. Figure 6 shows three single ended output configurations and a balanced output.

10/24
 Synetics NE/SA 602 / 612

Classic Example:
 Overview of NE 602:

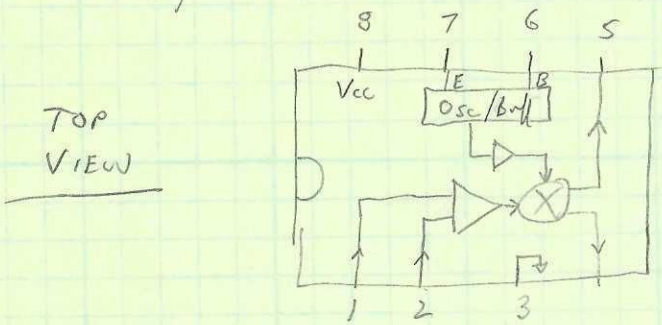

Pass Out Data Sheet

Pg 1

Read Description
Features
 ...

Walk thru data sheet pg 2 then specs

Comment on Test chrt \neq Application chrt

* max Voltage = 8V (To use 9V battery, do




Describe purpose of each part of test chrt

Pg 3


Equivalent chrt \neq actual e.g. Bias on Osc BUT
 Shows enough to understand I/O constraints only
 E.g. Pins 1 & 2 at same V, but not be AC coupled

Discuss Input correction

3a = test chrt 3c vs (w.r.k 50 Hz)

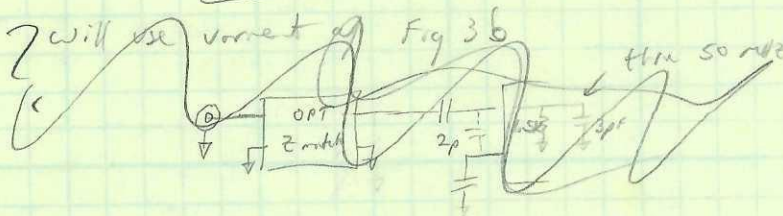

Suggest initially

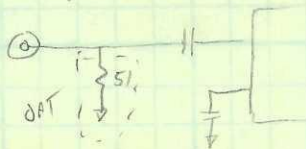

\Rightarrow Gain decreased by 14dB = $20 \log \sqrt{\frac{1.5k}{50}}$

i.e. Z_{match} would step up voltage by $\sqrt{\frac{1.5k}{50}}$
 (think about transformer match to EN Ho)

pg 4

Output Connection

Fig 4a ^{carin} 155 kHz filter has $Z_{in} = 1.5 k\Omega$
 \Rightarrow no match needed


Fig 4b Shows MNs (L networks of alignment)

4d shows balanced (3 dB better gain)

20.5
- 3
17.5
15
2.5

USE SINGLE ended δ MN to match to 300 Ω (will see next wk)

let them choose

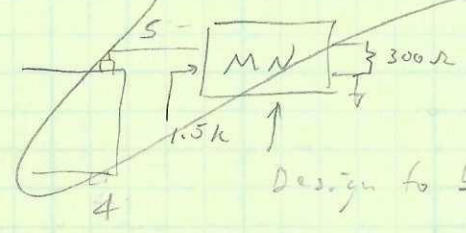


Design to be LBPASS

Osc ~~Fig~~

See discussion on pg 3 - can use external osc input on 6 must be 200 mV peak-peak

\Rightarrow 70 mV rms
 \Rightarrow -10 dBm

If you use p.t.s out this, can do

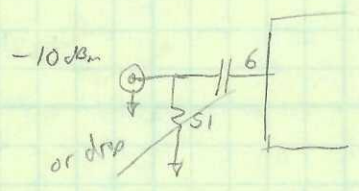

Pg 5 Ignore

Pg 6 Discuss