

low frequency
Introduction To RF Transformers
Toroidal Inductors &

Consider toroid L



Toroid made of powdered iron or ferrite

- Concentrate & confine magnetic flux
- Increase inductance (by factor equal to relative permeability)

$$L = k N^2 \Rightarrow k = \frac{L}{N^2}$$

Example 1 T37-2 core (.37 00) #2 material ^{powder iron} $\mu_r = 30$

From table $k = 40 \mu H$ for 100 turns

$$\Rightarrow k = 4 \text{ nH/turn}^2 \leftarrow !$$

$$10 \text{ turns} = 400 \text{ nH}$$

Example 2 FT37-67 core (.37 00, #67 material)

$L = 17.7 \text{ mH} / 1000 \text{ turns}$ \leftarrow Bad terminology


$$k = \frac{17.7 \text{ m}}{1000^2} = 17.7 \text{ nH/t}^2$$

$$10 \text{ turns} = 1.8 \mu H$$

13782 500 SHEETS, FILLER, 5 SQUARE
42381 50 SHEETS, EYE-BASE, 5 SQUARE
42382 100 SHEETS, EYE-BASE, 5 SQUARE
42383 200 SHEETS, EYE-BASE, 5 SQUARE
42384 100 RECYCLED WHITE, 5 SQUARE
42385 200 RECYCLED WHITE, 5 SQUARE
Made in U.S.A.

Why?
 $V = N \frac{d\phi}{dt}$
But $\phi \propto NI$
So $V \propto N^2 \frac{dI}{dt}$
or $V = k N^2 \frac{dI}{dt}$
Compare $V = L \frac{dI}{dt}$
 $\Rightarrow L = k N^2$

Transformers

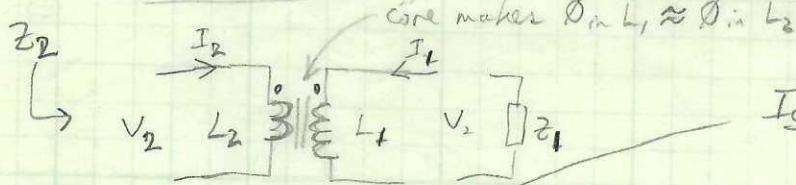

Ideal:

$$L_1 \rightarrow \infty$$

$$L_2 \rightarrow \infty$$

$$V_2 = \frac{N_2}{N_1} V_1$$

$$Z_2 = \left(\frac{N_2}{N_1}\right)^2 Z_1$$

IV Characteristics


Practical: $V_1 = j\omega L_1 I_1 + j\omega M I_2$

$$V_2 = j\omega L_2 I_2 + j\omega M I_1$$

where $M = k \sqrt{L_1 L_2}$

\uparrow coupling coeff (frac of flux from L_1 that links L_2)

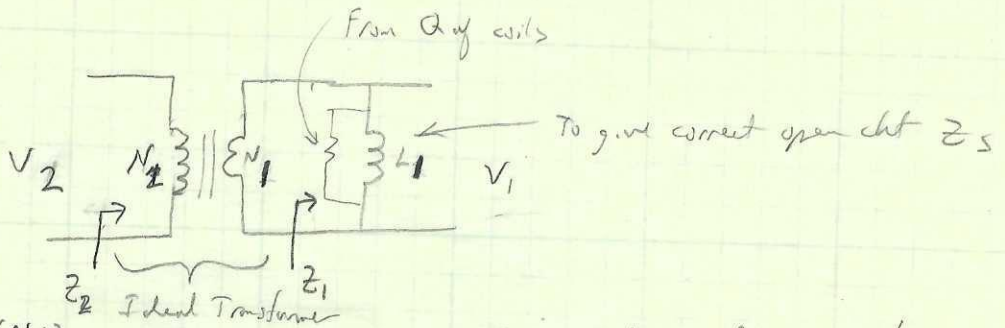If $k \approx 1$, then model simplifies to:



$Z_2 = \left(\frac{N_2}{N_1}\right)^2 Z_1$ This reduces to L_2 if unloaded

SKIP


Ideal Transformer Behavior

$$\left. \begin{aligned} V_2 &= \frac{N_2}{N_1} V_1 \\ I_2 &= \left(\frac{N_1}{N_2}\right) I_1 \end{aligned} \right\} \text{why?}$$


$V_2 I_2 = \frac{N_2}{N_1} V_1 \left(\frac{N_1}{N_2}\right) I_1 = V_1 I_1$
Power conservation!

$Z_2 = \frac{V_2}{I_2} = \left(\frac{N_2}{N_1}\right)^2 \frac{V_1}{I_1} = \left(\frac{N_2}{N_1}\right)^2 Z_1$

Applications
Matching

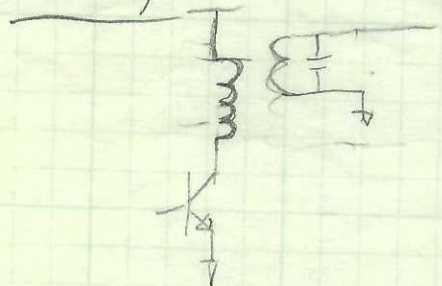


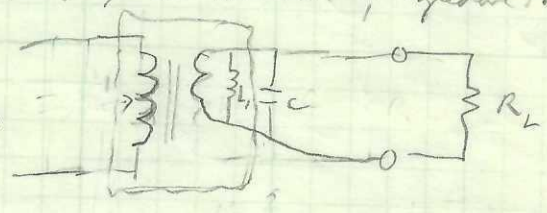Tuned Ckt's (BPF) w/ DC isolation & Ideal Transformer




$Z_L' = \left(\frac{N_2}{N_1}\right)^2 \left((j\omega L \parallel \frac{1}{j\omega C}) \parallel R_L \right) \approx \left(\frac{N_2}{N_1}\right)^2 R_L$
Show RX Diagram open @ ω_0

Mixer

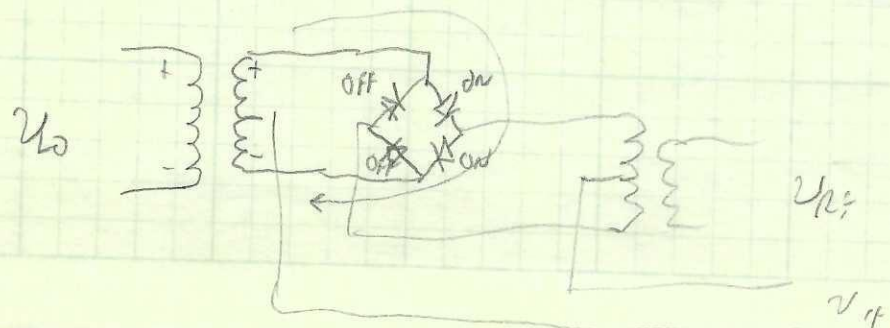


Transformer Realization

BAD

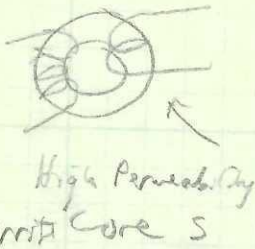


Good

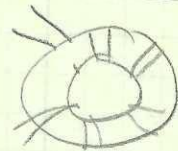


OR

TX-Line Construction
(Broader Bandwidth)
Better flux linkage

Model:

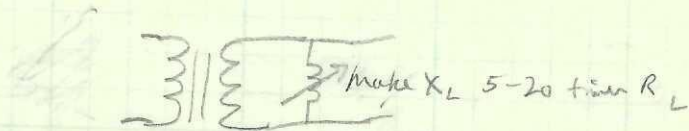

2:1 Center Tapped TX Line construction

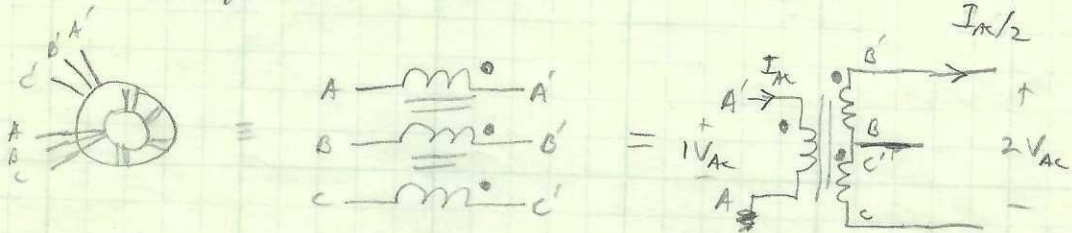


2:1 voltage, 4:1 Z transformation

Application:


mixer!

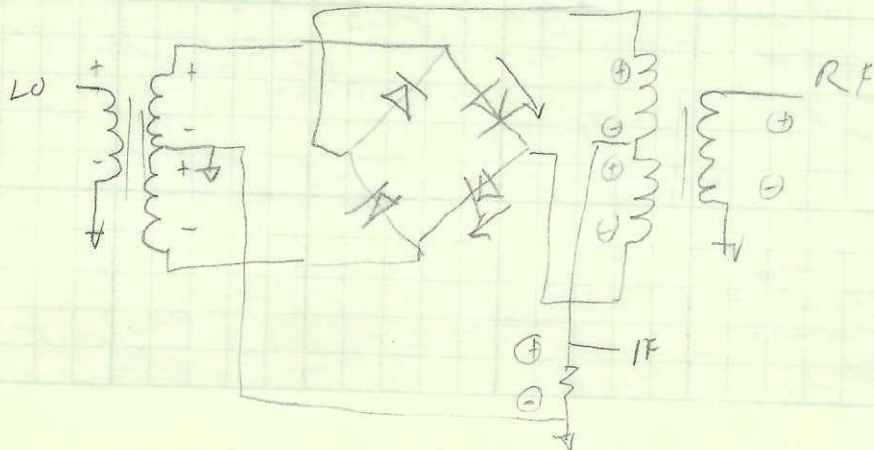Goal: Pass RF to IF with polarity reversal every half cycle of L_0




Additional applications

Baluns

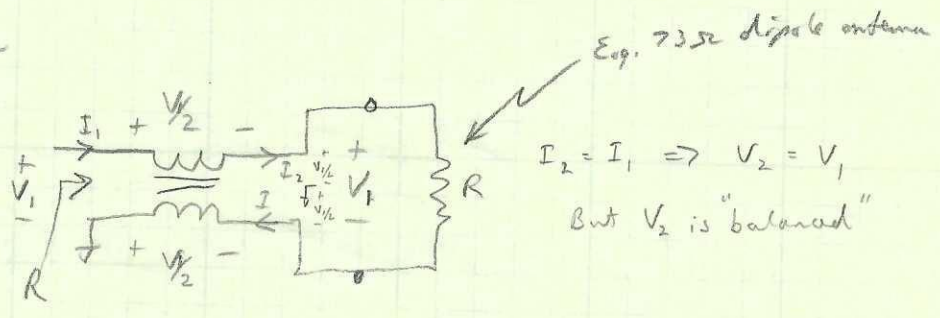

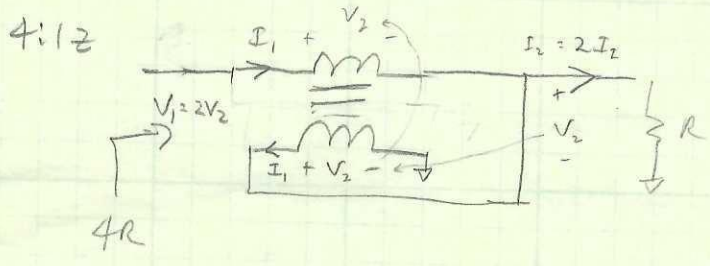$I_2 = I_1 \Rightarrow V_2 = V_1$
 But V_2 is "balanced"



13-782 500 SHEETS FILLED 5 SQUARE
 42-381 50 SHEETS FOLDED 5 SQUARE
 42-382 100 SHEETS FOLDED 5 SQUARE
 42-383 200 SHEETS FOLDED 5 SQUARE
 42-384 200 SHEETS FOLDED 5 SQUARE
 42-385 200 SHEETS FOLDED 5 SQUARE
 42-386 200 SHEETS FOLDED 5 SQUARE
 42-387 200 SHEETS FOLDED 5 SQUARE
 42-388 200 SHEETS FOLDED 5 SQUARE
 42-389 200 SHEETS FOLDED 5 SQUARE
 42-390 200 SHEETS FOLDED 5 SQUARE
 42-391 200 SHEETS FOLDED 5 SQUARE
 42-392 200 SHEETS FOLDED 5 SQUARE
 42-393 200 SHEETS FOLDED 5 SQUARE
 42-394 200 SHEETS FOLDED 5 SQUARE
 42-395 200 SHEETS FOLDED 5 SQUARE
 42-396 200 SHEETS FOLDED 5 SQUARE
 42-397 200 SHEETS FOLDED 5 SQUARE
 42-398 200 SHEETS FOLDED 5 SQUARE
 42-399 200 SHEETS FOLDED 5 SQUARE
 42-400 200 SHEETS FOLDED 5 SQUARE
 Made in U.S.A.

