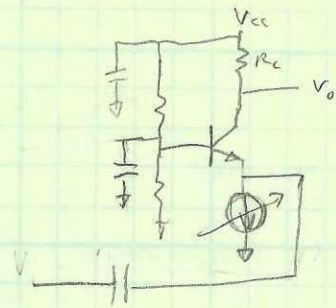




Typical AGC Amplifier (Simplified)




$A_v = g_m R_C$   
 $g_m = \frac{I_c}{V_T}$


$I_c$	$A_v$	$A_v$ dB
1mA	100	40
100µA	10	20
10µA	1	0
1µA	0.1	-20

IC Implementation (MC 1350)

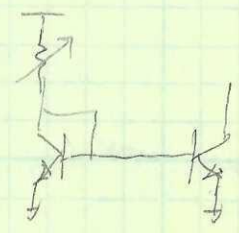- Show Ckt
- Discuss Current Control
- Show Gain Curve



Typical Limiter Ckt Simplified

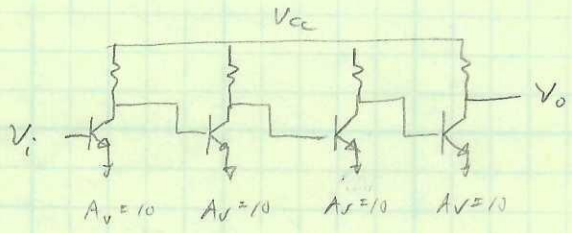

IC Implementation

- max 3 App
- Show • LM 3089 (Our Chip)
- LM 3089
- Show - LM 3089 Pg 2 w/ 3dB sens of 12µV




11/7  
Demodulator cmts

Recall

Basic  
Classical modulation Types

7.1)  
2)

AM  
ASK (OOK)  
BPSK

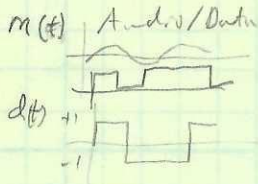

RF out



Math model

$$V_{RF}(t) = [1+m(t)] \cos(\omega_c t)$$

$$= d(t) \cos(\omega_c t)$$

$$V(t) = d(t) \cos(\omega_c t)$$

$d(t) \in \{-1, 1\}$  modulation = a x c!


QPSK = 2 BPSK data streams on quadrature carriers

$$V(t) = d_1(t) \cos(\omega_c t) + d_2(t) \sin(\omega_c t)$$

Other QAM, GMSK, ... DSSS


see ECE661

5) FM

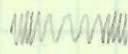

$$V(t) \doteq \cos[(\omega_c + k m(t))t]$$

6) FSK

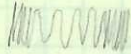

$$V(t) \doteq \cos[(\omega_c + k d(t))t]$$


AM Detectors (Demodulators)

Some subtle problems.

Actually need to use:


$$\cos[\omega_c t + \pi/2] = \sin(\omega_c t)$$

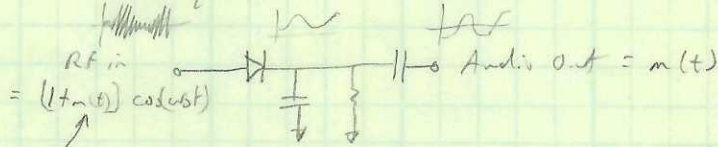Simple Diode ("Square-law") Detector for AM (OOK/ASK)



Audio waveform  
"Can see why need ~ 1V @ demand"  
 $|m(t)| < 1$  to prevent "overmodulation"

Modern Synchronous Detection

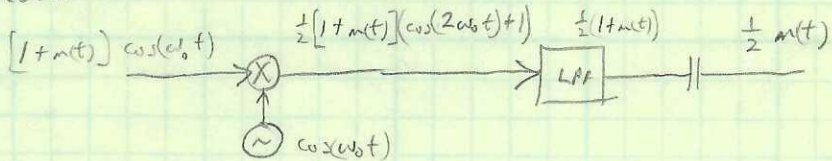


Better sensitivity & noise performance

★ What would happen if mixed w/  $\sin(\omega_0 t)$ ? ? ★ Zero output!  
 Where do we get  $\cos(\omega_0 t)$  from?

1) Phase Locked Loop (Later in class)

Skip the math!

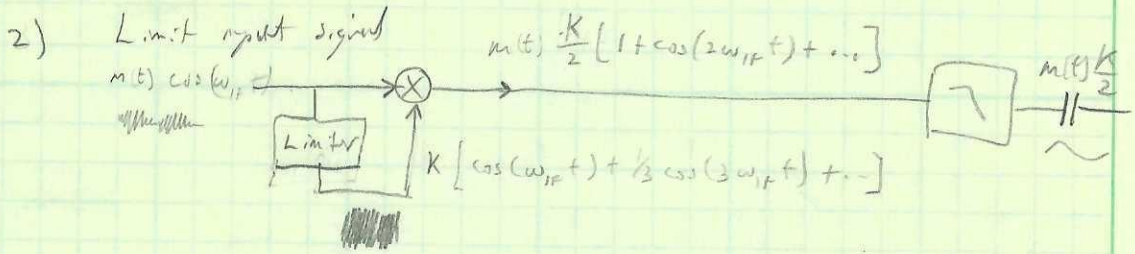


BPSK (~~QPSK~~) Demodulators

(Similar, but trickier to get sinusoid to mix with...)


Can use Sync Detector to demodulate BPSK/QPSK also
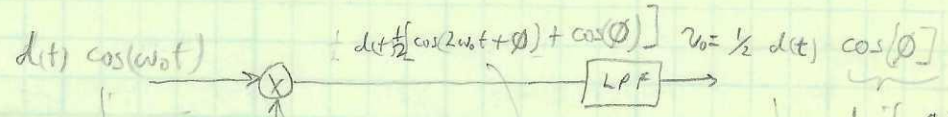
$$\frac{1}{2} [\cos(\alpha + \theta) + \cos(\alpha - \theta)]$$



1 if osc in phase  
 0 if osc  $\pm 90^\circ$  out of phase  
 -1 if osc  $180^\circ$

Do Venn graph of this

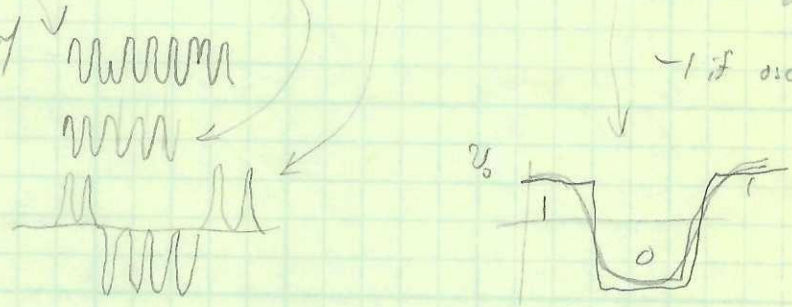


Consider QPSK:

$$V(t) = d_I(t) \cos(\omega_c t) + d_Q(t) \sin(\omega_c t)$$

what is output of above detector?

$$\begin{aligned} V(t) \cos(\omega_c t) / LP &= \\ &= d_I(t) \cos^2(\omega_c t) + d_Q(t) \cos(\omega_c t) \sin(\omega_c t) / LP \\ &= \frac{1}{2} d_I(t) + 0 \end{aligned}$$

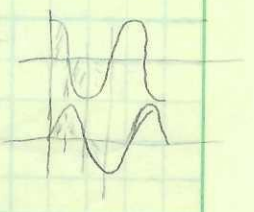$d_Q(t)$  portion is in Quadrature with  $d_I(t)$  portion



SKIP




What is output to detector using  $\sin(\omega_0 t)$ ?

$$V_o(t) \sin(\omega_0 t) \Big|_{LP}$$

$$= d_i(t) \cos(\omega_0 t) \sin(\omega_0 t) + d_a(t) \sin^2(\omega_0 t) \Big|_{LP}$$

$$= 0 + \frac{1}{2} d_a(t)$$

Complete Detector

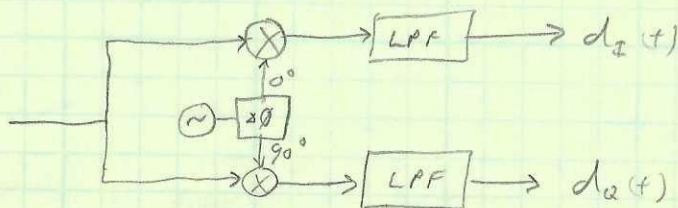


Quadrature FM Detector




Ideal Detector

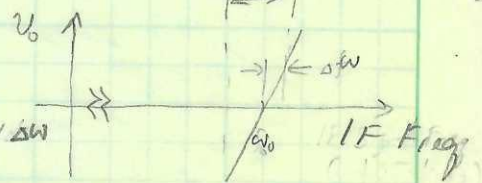Output = 0 at center freq  $\omega_{IF} = \omega_0$   
 Output =  $k\Delta\omega$  for deviation from  $\omega_0$  of  $\Delta\omega$





Typical Implementation

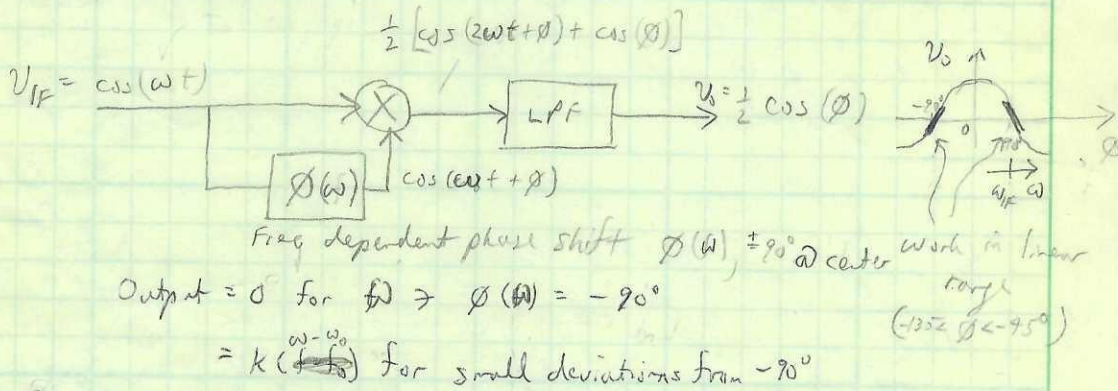

Design  $\phi(\omega)$  circuit to produce  $90^\circ$  shift at  $\omega = \omega_{IF}$  and linear change in phase,  $\omega \neq \omega_{IF}$


SKIP to next pg

Typical circuit

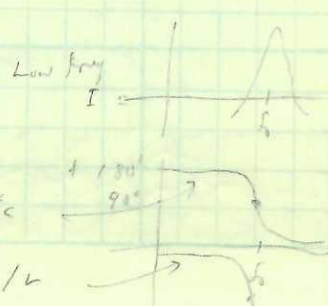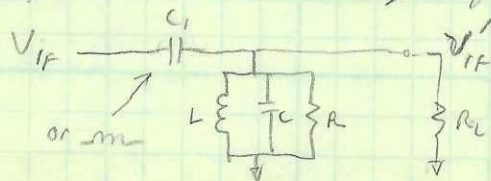


★ (Show Data sheet)

$\phi(f)$  analysis on:

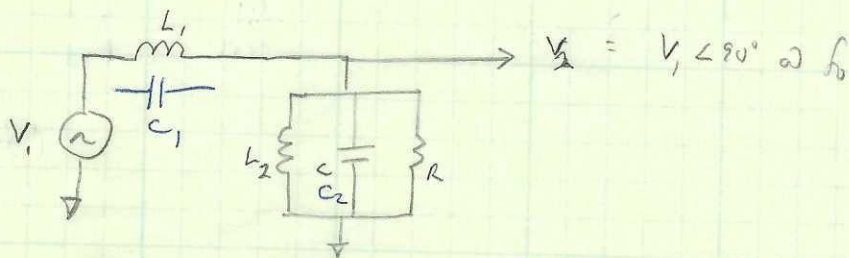

Analysis

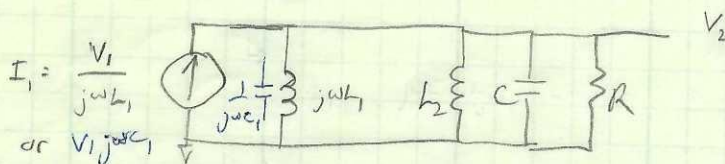1) Convert source,  $L_1$  to Norton equivalent:



2) Combine  $L_1, L_2$  into  $L = L_1 || L_2$   
 or  $C_1, C_2$  into  $C = C_1 + C_2$

3) Solve for  $V_2 / V_1$

$$V_2 = I_1 Z \quad Z = L || C || R$$


$$= \frac{V_1}{j\omega L_1} Z \text{ or } j\omega C_1 Z V_1$$

$$\Rightarrow V_2 / V_1 = \frac{1}{j\omega L_1} Z \text{ or } j\omega C_1 Z$$

At resonance  $\frac{V_2}{V_1} = \frac{1}{j} \frac{R}{\omega L_1} = |L - 90^\circ$  if  $X_{L_1} = R$

$j\omega C_1 R = j \frac{R}{\omega C_1} = |L + 90^\circ$  if  $X_{C_1} = R$



At other freqs:

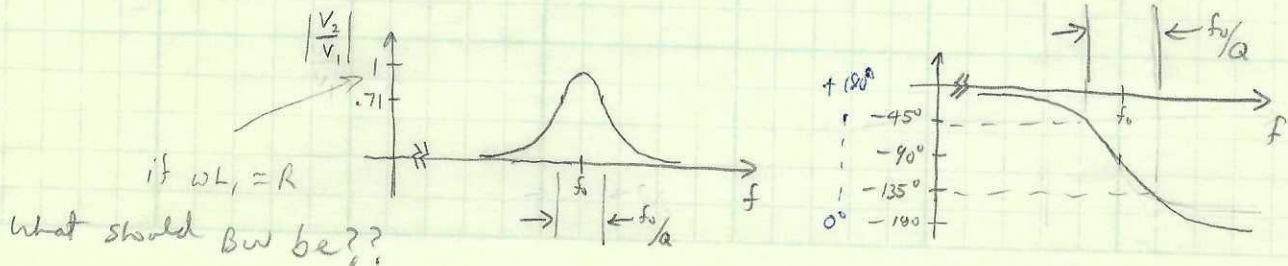

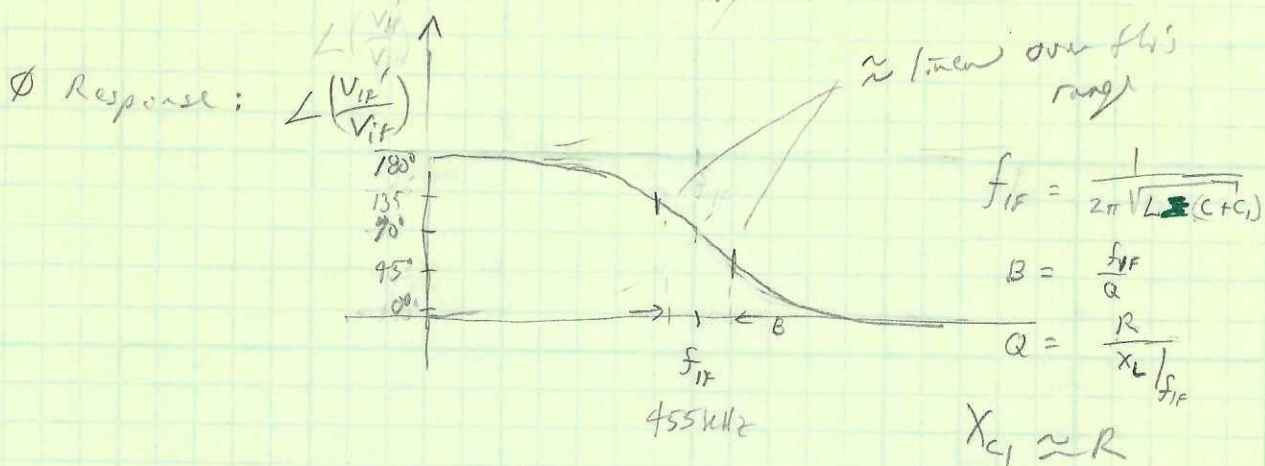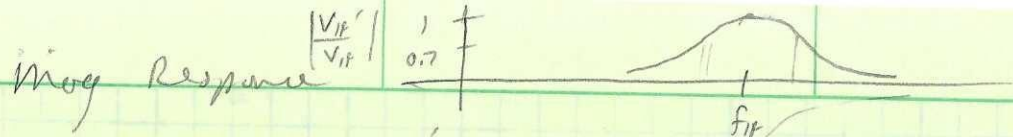
15-782 500 SHEETS, FILLER, 5 SQUARE  
 42-381 50 SHEETS, CYEASER, 5 SQUARE  
 42-382 100 SHEETS, CYEASER, 5 SQUARE  
 42-383 200 SHEETS, CYEASER, 5 SQUARE  
 42-384 100 SHEETS, CYEASER, 5 SQUARE  
 42-385 100 RECYCLED WHITE, 5 SQUARE  
 42-386 200 RECYCLED WHITE, 5 SQUARE  
 Made in U.S.A.










Proof

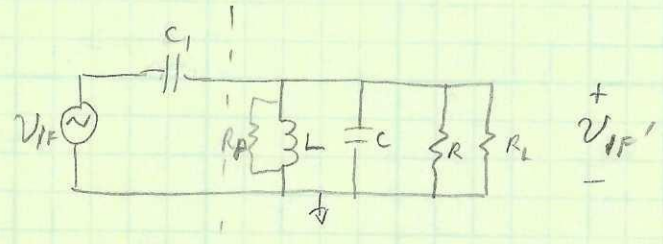

Norton Equiv Src:

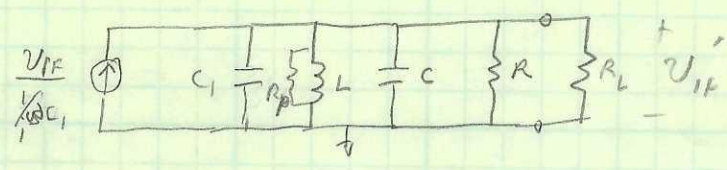

$R' = R_p || R || R_L$

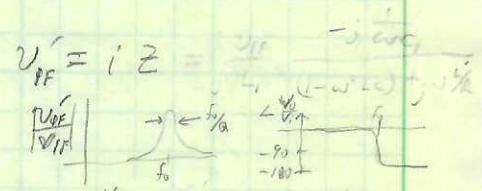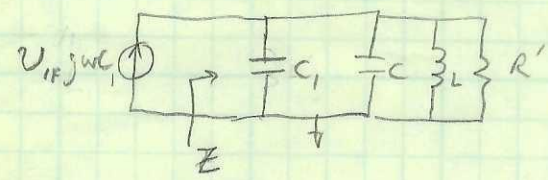

- At  $f = f_0$ ,  $V_{IF}' = i R' = V_i j\omega C_1 R' \Rightarrow \angle \frac{V_o}{V_i} = 90^\circ$
- At  $f \ll f_0$ ,  $X_L \ll X_C \text{ or } R' \Rightarrow Z \approx j\omega L' \Rightarrow V_o \approx i j\omega L' = V_i (j\omega C_1 j\omega L) \Rightarrow \frac{V_o}{V_i} = -\frac{X_L}{X_{C_1}} \Rightarrow \angle \approx -90^\circ$
- At  $f \gg f_0$ ,  $X_C \ll X_L \text{ or } R' \Rightarrow Z \approx \frac{1}{j\omega C} \Rightarrow V_o \approx i \frac{1}{j\omega C} = V_i j\omega C_1 \frac{1}{j\omega C} \Rightarrow \frac{V_o}{V_i} = \frac{X_C}{X_{C_1}} \Rightarrow \angle = 0^\circ$

Recall circuit Q is  $\frac{R'}{X_{C_1}} = \frac{R'}{X_C}$

Large Q  $\Rightarrow X_L = X_C \ll R'$

$\Rightarrow$  Transitions to looking like just L or C very quickly

NOTE:  $\left| \frac{V_{IF}'}{V_{IF}} \right|$  should be  $\approx 1$  at  $f_{IF}$

$$\left| \frac{V_{IF}'}{V_{IF}} \right|_{f_{IF}} = \left| j\omega C_1 R' \right|_{f_{IF}} = \frac{R'}{X_{C_1}} \Big|_{f_{IF}} \Rightarrow \text{make } X_{C_1} \approx R' \text{ at } f_{IF}$$
