

Radio Design 101 Epilogue 2 – Debugging and Troubleshooting


Slides downloaded from: <https://ecefiles.org/rf-design/>

Companion video at: <https://www.youtube.com/watch?v=31MhI3RSQEI>

This material is [provided by ecefiles.org](https://ecefiles.org) for educational use only.

This second follow-up (epilogue) to the Radio Design 101 series offers tips on how to troubleshoot electronic circuits. The problems found in Epilogue 1 are addressed and the radio performance is improved - but the main focus is on general troubleshooting techniques. A preview look at emerging Q-enhanced filter technology is also provided, as is an example of applying the troubleshooting techniques to car repair to illustrate that the techniques are useful in general problem-solving.


Troubleshooting (collected clues)

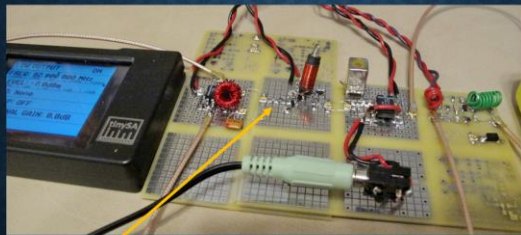

WARNING: Obviously – don't touch high voltage or high-power circuits.

- Touching here, or on inductor stopped oscillation and receiver came alive
- Oscillation stayed gone after finger removed (hmm...)
- Removing probe (or touching antenna) could start it again...

Application to a '92 Corvette ☺

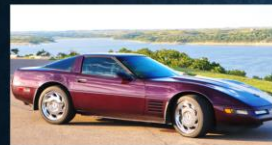

Radio Design 101

Epilogue 2

Debugging / Troubleshooting

“Radio Design 101” and “NanoVNA” Series

20+ videos based on and supporting a university senior-design class in RF/wireless circuits



Receiver Performance -
Radio Design 101 Epilogue 1

368 views • 1 month ago



Radio Design 101 - Finishing
the Receiver (Episode 6)

685 views • 3 months ago




Radio Design 101 - RF
Mixers, Part 2 of Episode 5

724 views • 3 months ago



Radio Design 101 - RF Mixers
and Frequency Conversions...

1.2K views • 4 months ago

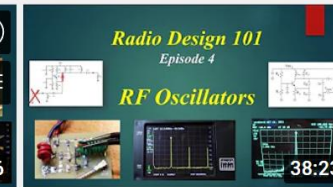

Radio Design 101 - RF
Oscillators (Episode 4)

1.9K views • 4 months ago



Radio Design 101 - Episode 3
- RF Amplifiers

1.4K views • 5 months ago



Radio Design 101 - Episode 2
- Impedance Matching - Par...

1.1K views • 6 months ago




Radio Design 101 - Episode 2
- Impedance Matching - Par...

1.5K views • 6 months ago



Radio Design 101 - Episode 1
- Transceivers and Filters - ...

1.9K views • 7 months ago

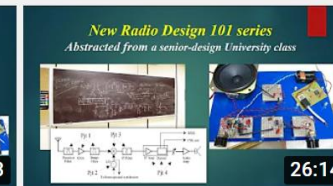


Radio Design 101 - Episode 1
- Transceivers and Filters - ...

2.6K views • 7 months ago




NanoVNA - Antennas and
Tuners

2.4K views • 9 months ago

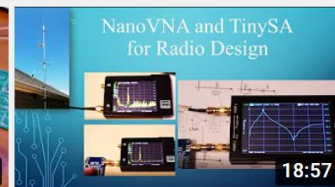


NanoVNA and TinySA for
Radio Design

6.2K views • 1 year ago

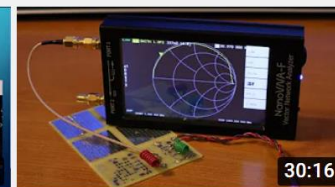

NanoVNA - Measuring RLC
Components

12K views • 1 year ago

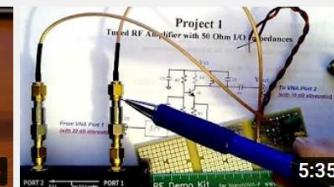

NanoVNA - Measuring S21
and S11 of a small-signal...



3.5K views • 1 year ago





NanoVNA - Measuring
Impedances

7.3K views • 1 year ago

FM Receiver built in Radio Design 101

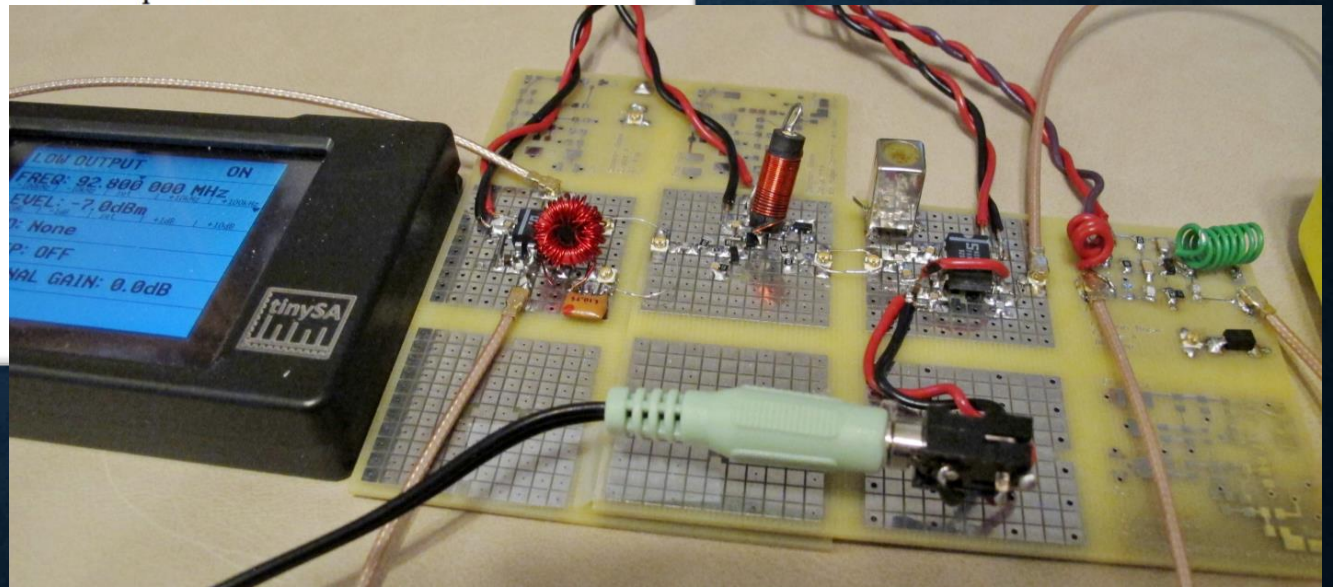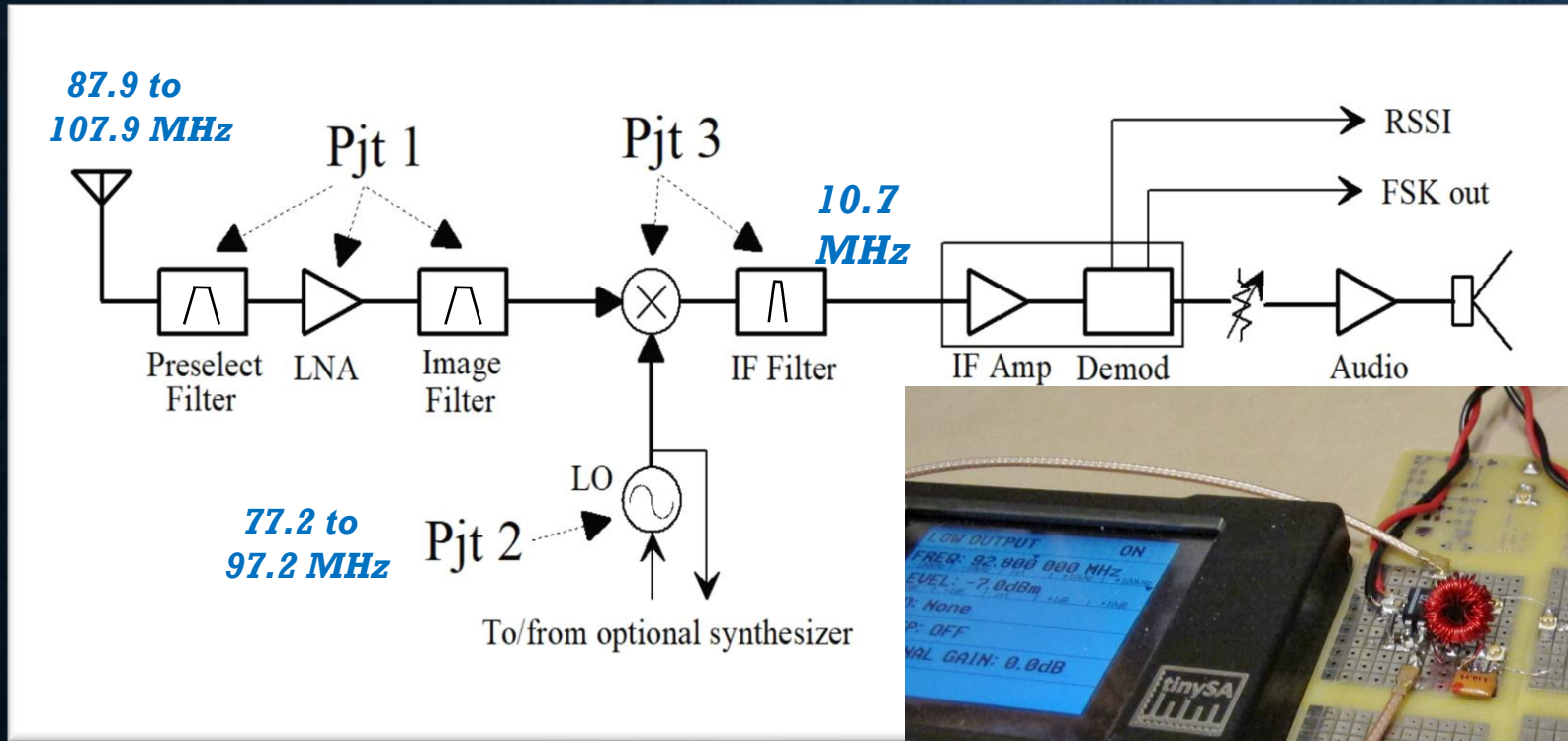

Test Results from Epilogue 1

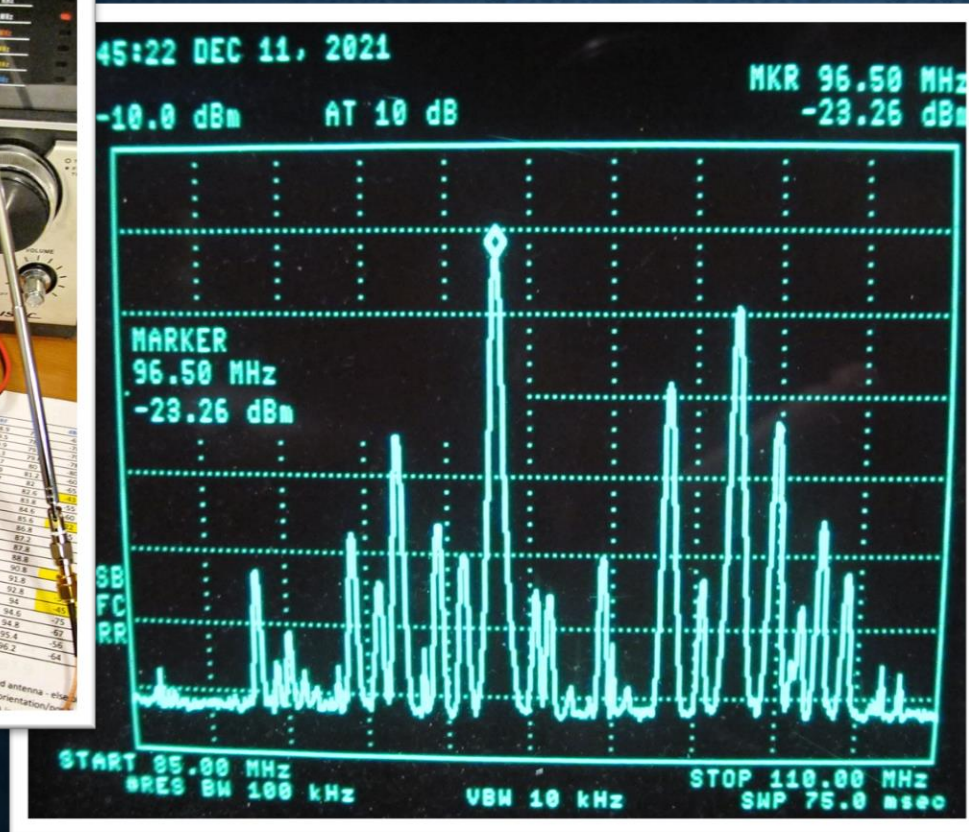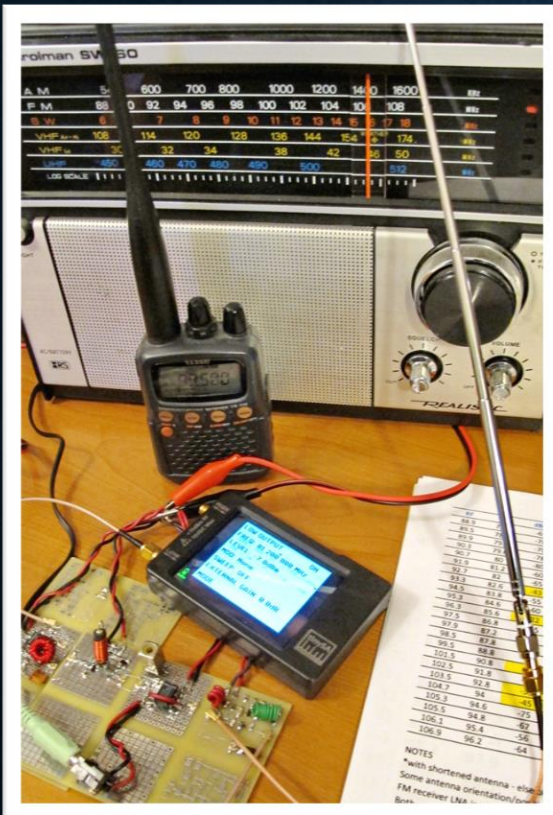


RF	LO	dBm	FMrx	VR120	VR120atten	Old Radio
88.9	78.2	-65			yes	yes
89.5	78.8	-78		yes		yes
89.9	79.2	-70	quiet	yes	yes	yes
90.3	79.6	-78			yes	yes
90.7	80	-80				yes
91.9	81.2	-60	quiet	yes	yes	yes
92.7	82	-65			yes	yes
93.3	82.6	-43	excellent	yes	yes	yes
94.5	83.8	-55	quiet	yes	yes	yes
95.3	84.6	-60	quiet	yes	yes	yes
96.3	85.6	-22	excellent	yes	yes	yes
97.5	86.8	-65			yes	yes
97.9	87.2	-67	quiet	yes	yes	yes
98.5	87.8	-80				?
99.5	88.8	-61	?		yes	yes
101.5	90.8	-40	excellent	yes	yes	yes
102.5	91.8	-62				yes
103.5	92.8	-30	excellent	yes	yes	yes
104.7	94	-45	good	yes	yes	yes
105.3	94.6	-75				yes
105.5	94.8	-67		yes	yes	yes
106.1	95.4	-56		yes	yes	yes
106.9	96.2	-64		yes	yes	yes

Outline of Today's Episode

- *Review of problems found in Epilogue 1*
- *Troubleshooting and fixing it*
- *General troubleshooting techniques*
- *Future topics*

Recall Epilogue 1 Conclusions

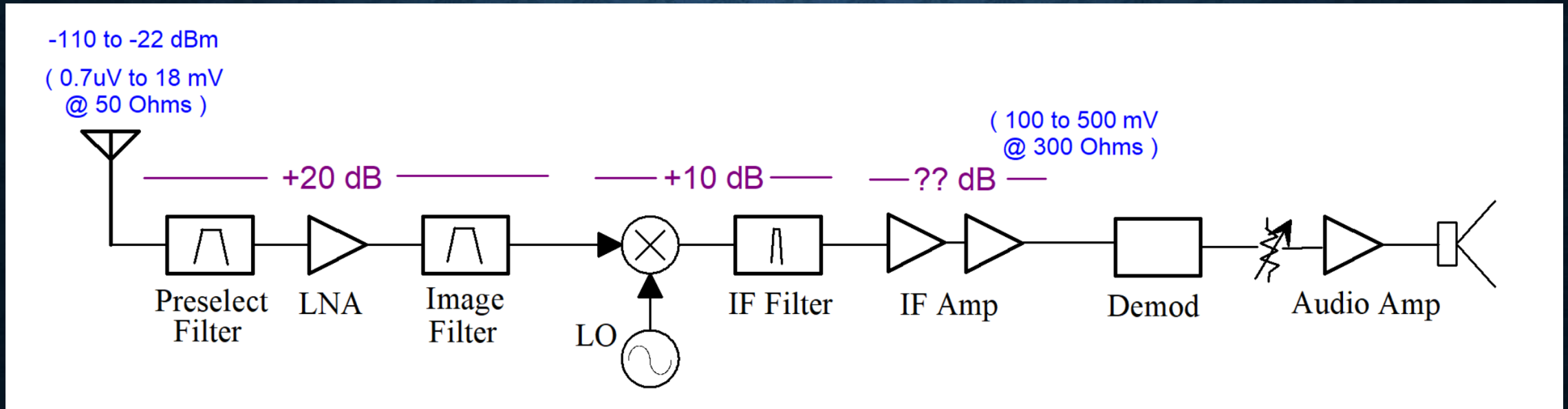



Front-end bandwidth is too narrow, desensitizing top and bottom of FM band

Mixer is overdriven in local area due to 96.3 MHz station, reducing overall gain

IF filter has limited off-channel rejection causing some “signal blocking”

IF amp gain is low and not centered at 10.7 MHz **(We need more gain at IF!)**

Simple IF Amp Modifications

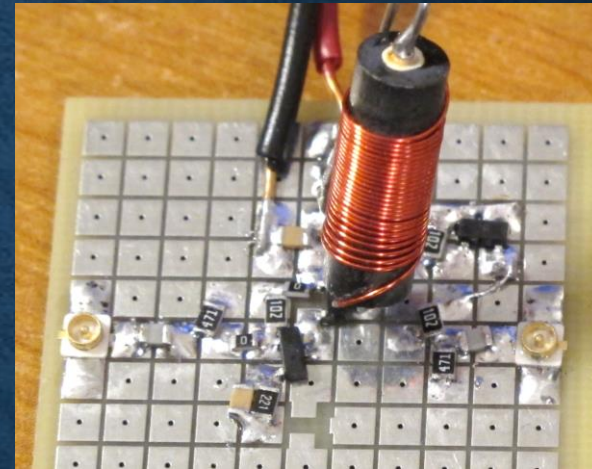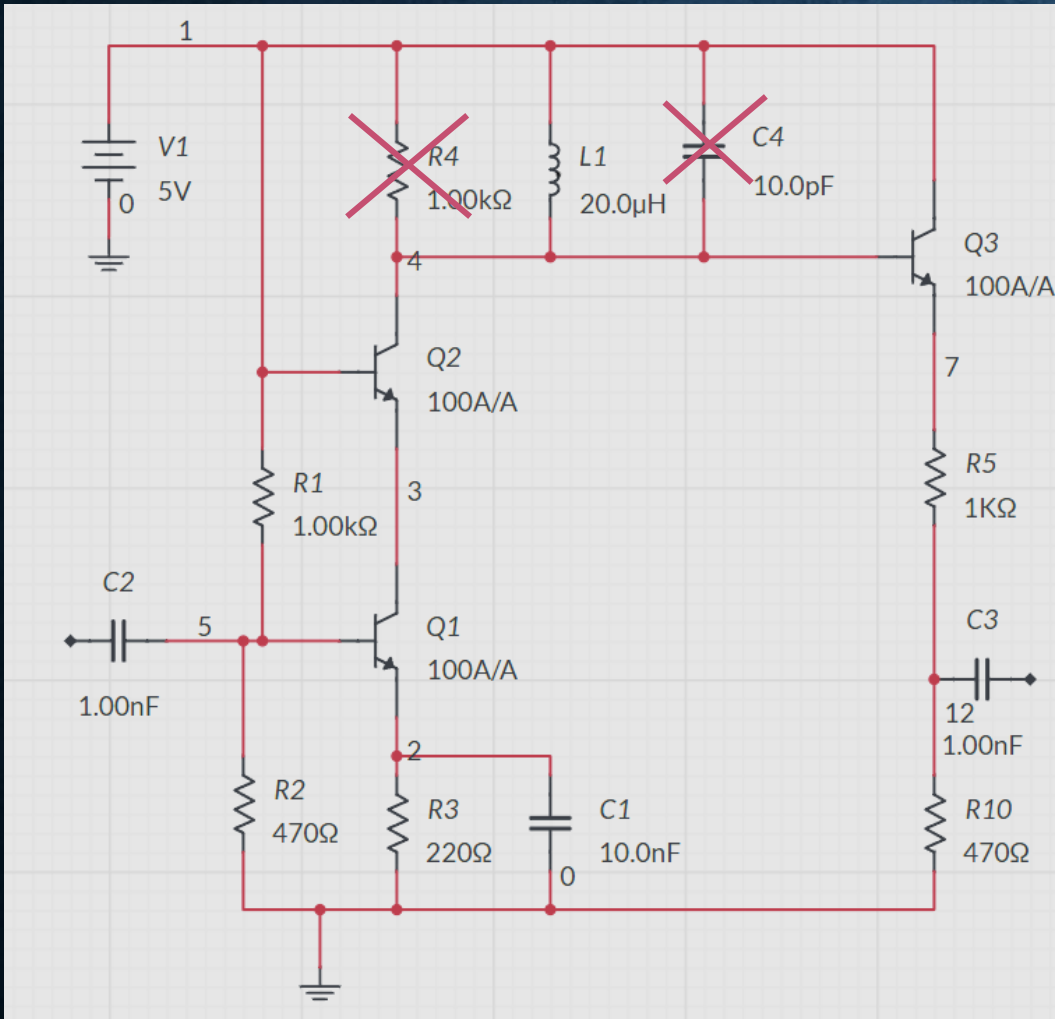


- Removed R4 and C4 to increase gain and raise resonant frequency.

$$A_v = -g_m R \quad f_o = \frac{1}{2\pi\sqrt{LC}}$$

- Receiver lost virtually all sensitivity ! ☹



The Problem

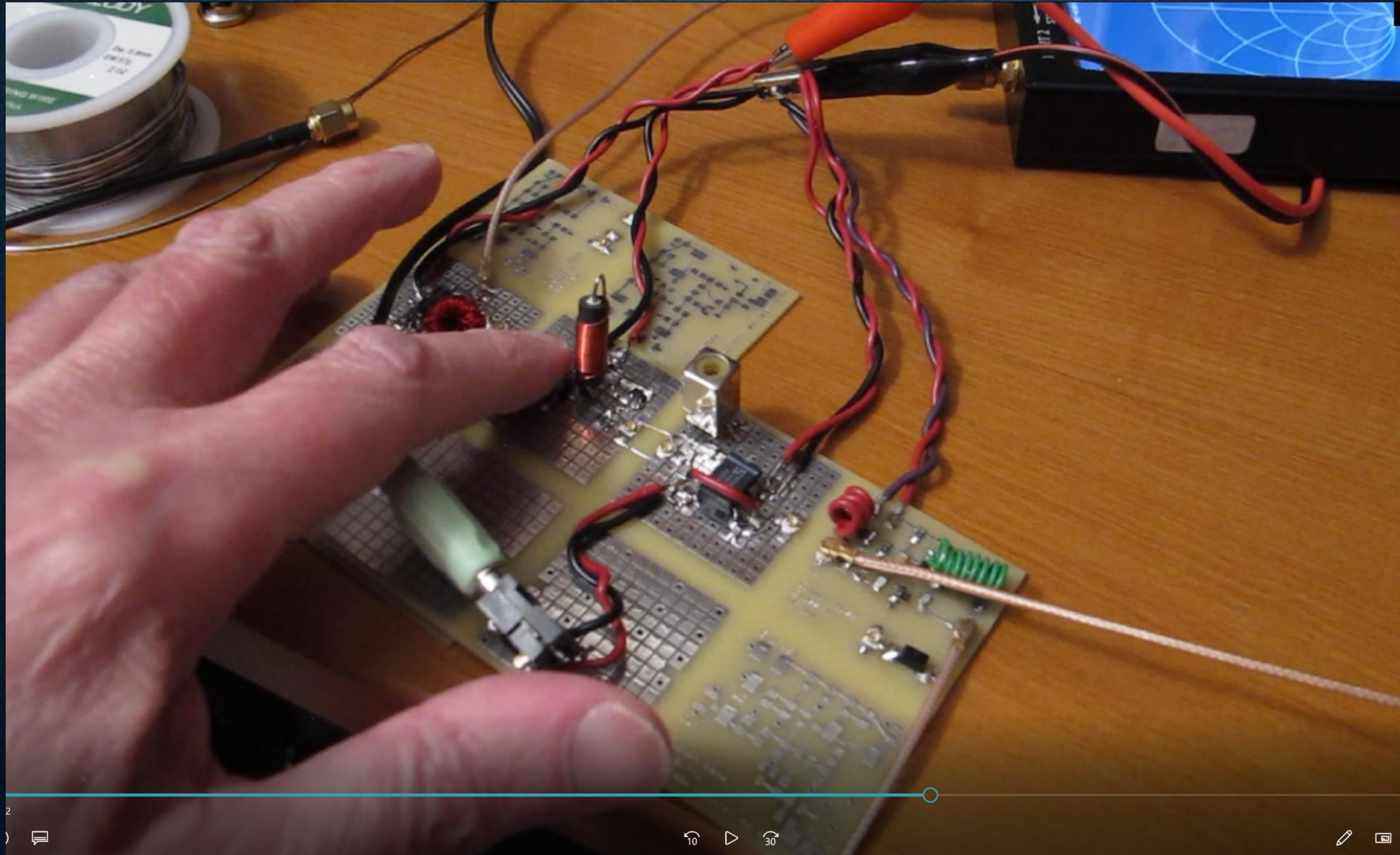

Outline of Today's Episode

- *Review of problems found in Epilogue 1*
- *Troubleshooting and fixing it*
- *General troubleshooting techniques*
- *Future topics*

Troubleshooting (basic checks)

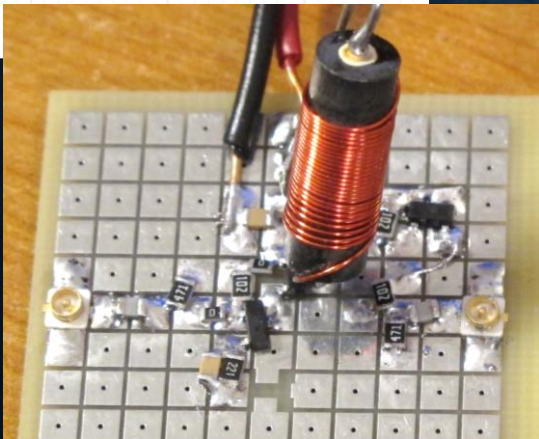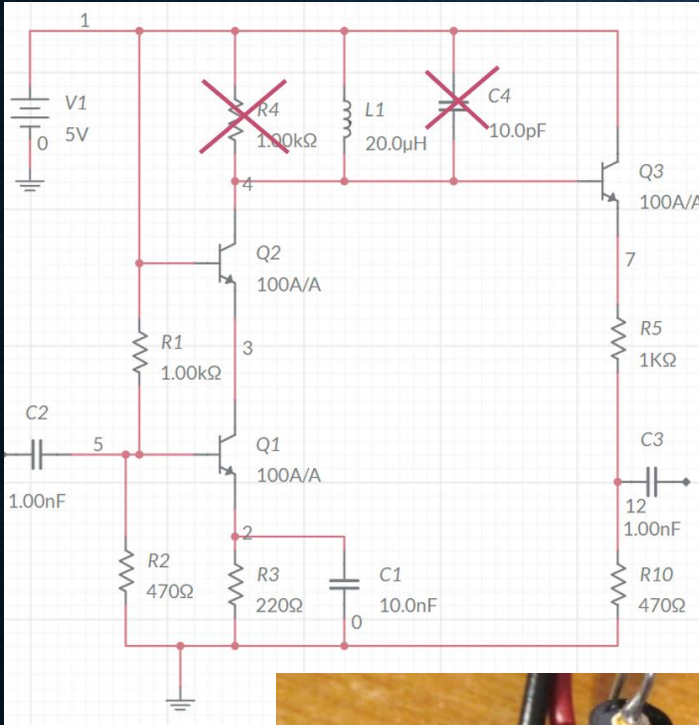


- What changes were made since last time it worked? (de-soldering in IF amp output stage)
- Verified visually and with Ohm meter that connections were OK
- Verified DC bias voltages at V_{cc} , and at Q2 and Q3 base and emitter
- Probed signal at IF amp output with receiver tuned to a strong station
- Noticed it's oscillating around 6 MHz !

Troubleshooting (RF probing)

WARNING: Only for low voltage, low-power circuits and with a DC block (and suitable attenuation)!





Troubleshooting (collected clues)

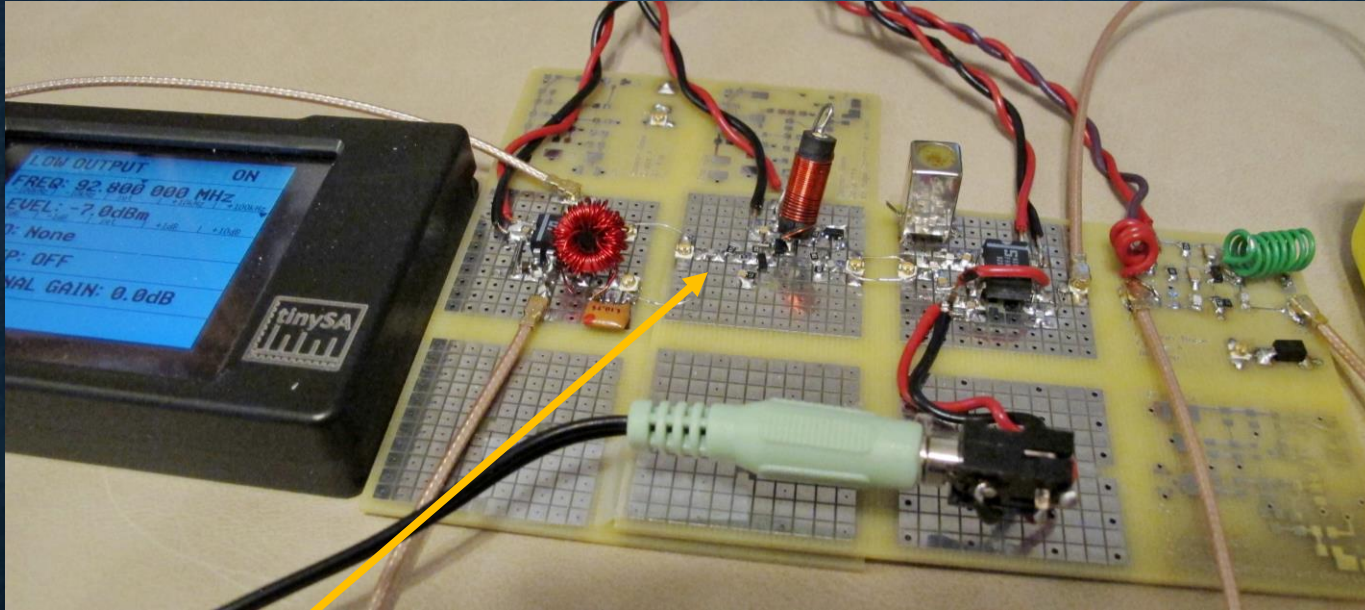

WARNING: Obviously – don't touch high voltage or high-power circuits.

- Touching here, or on inductor stopped oscillation and receiver came alive
- Oscillation stayed gone after finger removed (hmm...)
- Removing probe (or touching antenna) could start it again...



Developing Theories

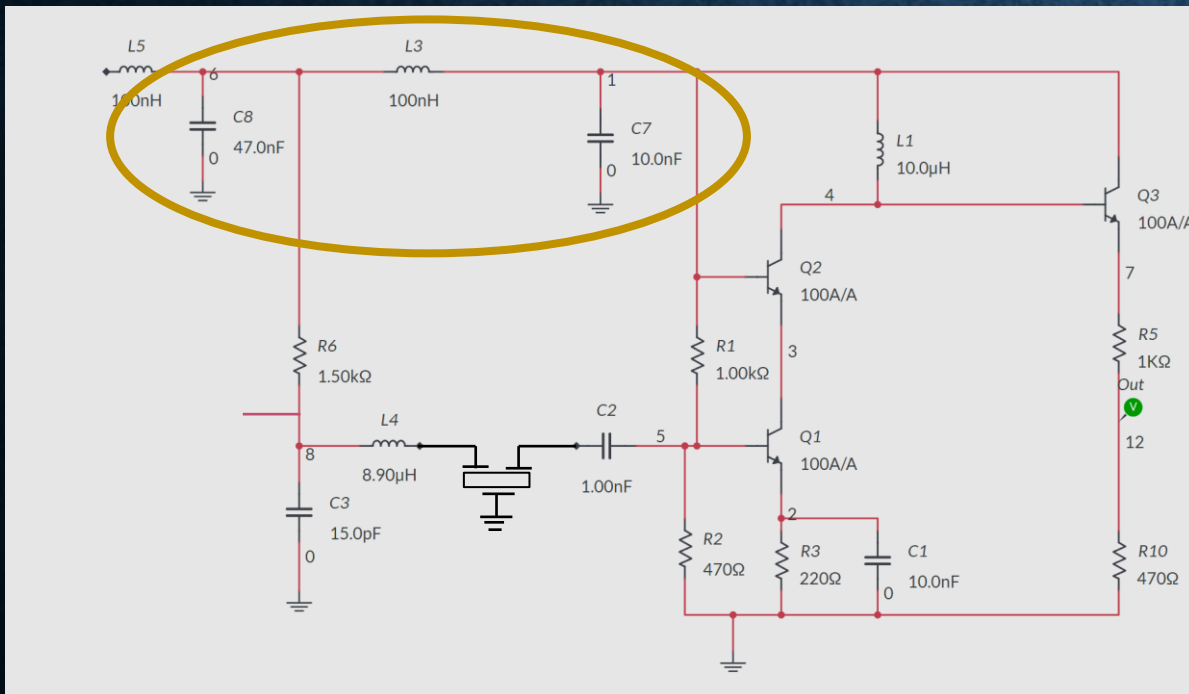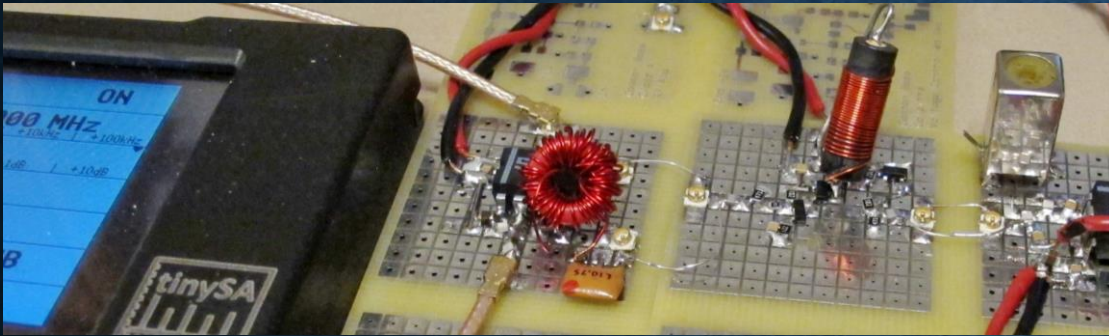

- Clues include frequency (6 MHz), and 'stickiness' of oscillation
- Ruled out common cause of RF oscillation: (CC amplifier with capacitive load at emitter and inductive base impedance)
- Remaining theories included parasitic 100 nH L in Vcc lead resonating with 10 nF C7 bypass, or possible loop back through mixer stage (unlikely due to filter in-line)
- Also, high C from forward biasing of Q3 base - collector junction during limiting could shift resonance from 11 MHz to 6 MHz, making it sticky. Hmm...


Testing Theories

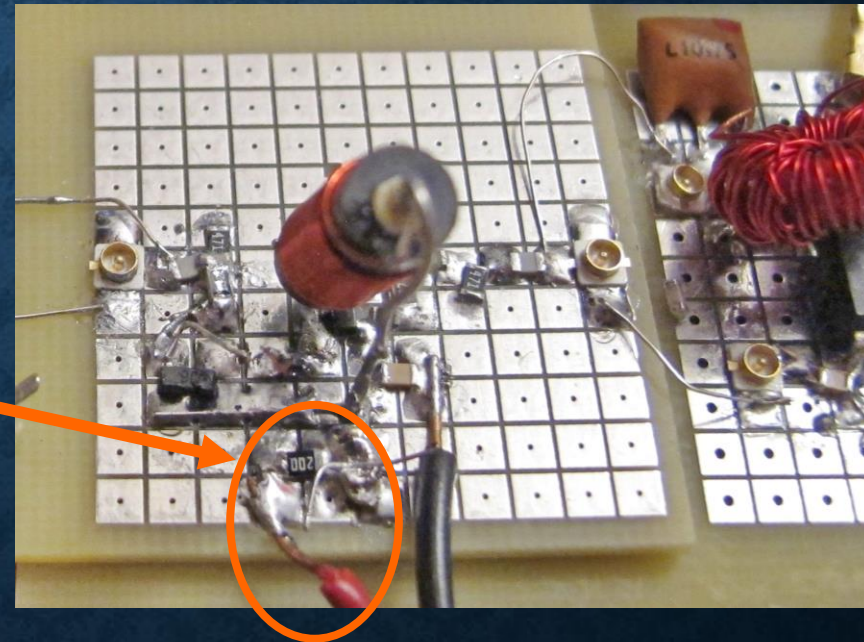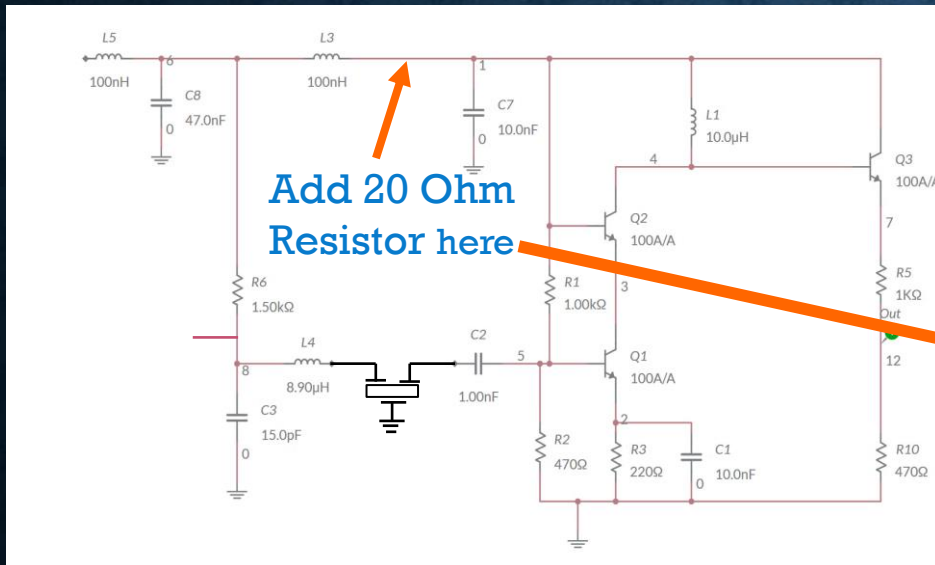- Proposed solutions included adding series R in supply lead to “de-Q” resonance between C7, L3.
- Added 20 Ohm series R with supply feed and got excellent, stable reception 😊





NOTE: This was standard practice in older designs. Modern books / papers / PCB layout guidelines surrounding bypass cap issues fall under the term “Power Integrity”

Fixed 😊


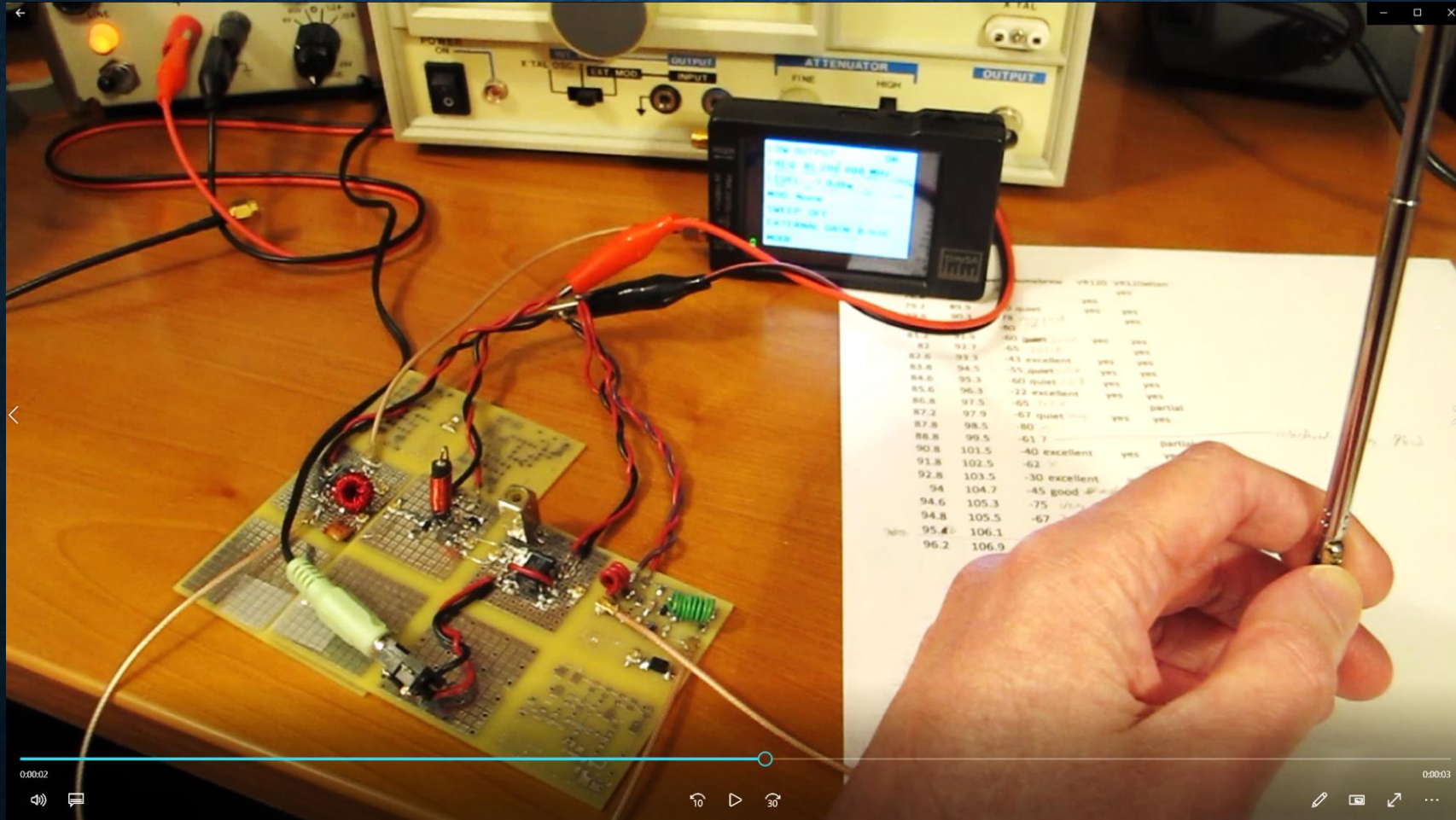


Performance Now

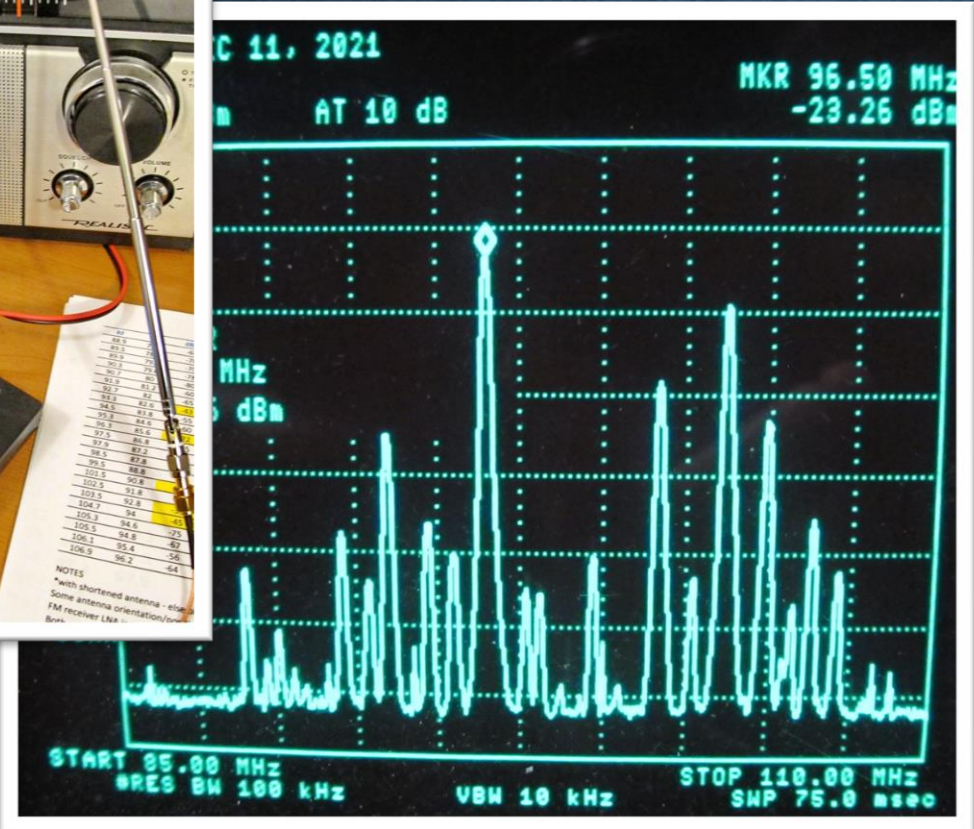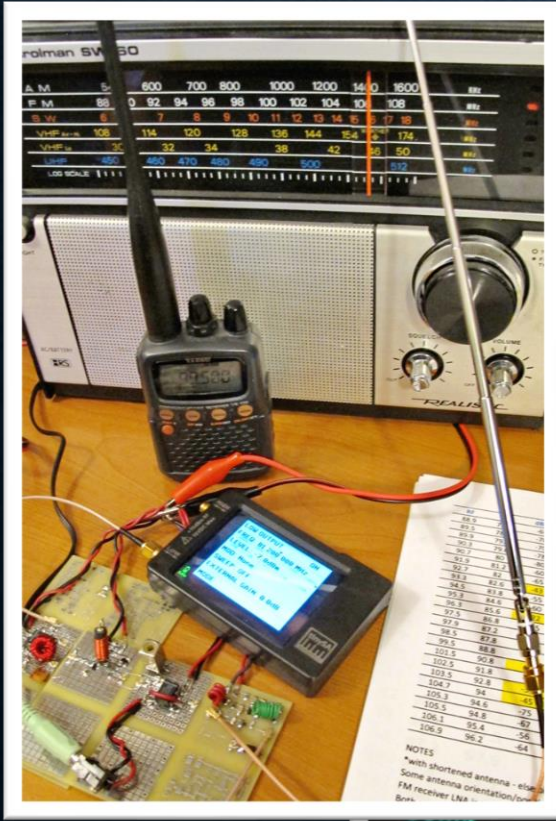

RF	LO	dBm	FMrx	FMrxFixed	VR120	VR120atten	Old Radio
88.9	78.2	-65				yes	yes
89.5	78.8	-78			yes		yes
89.9	79.2	-70	quiet	quiet	yes	yes	yes
90.3	79.6	-78		quiet		yes	yes
90.7	80	-80					yes
91.9	81.2	-60	quiet	good	yes	yes	yes
92.7	82	-65		good		yes	yes
93.3	82.6	-43	excellent	excellent	yes	yes	yes
94.5	83.8	-55	quiet	good	yes	yes	yes
95.3	84.6	-60	quiet	good	yes	yes	yes
96.3	85.6	-22	excellent	excellent	yes	yes	yes
97.5	86.8	-65		good		yes	yes
97.9	87.2	-67	quiet	quiet	yes	yes	yes
98.5	87.8	-80					?
99.5	88.8	-61	?	excellent*		yes	yes
101.5	90.8	-40	excellent	excellent	yes	yes	yes
102.5	91.8	-62					yes
103.5	92.8	-30	excellent	excellent	yes	yes	yes
104.7	94	-45	good	excellent	yes	yes	yes
105.3	94.6	-75					yes
105.5	94.8	-67			yes	yes	yes
106.1	95.4	-56		very quiet	yes	yes	yes
106.9	96.2	-64			yes	yes	yes

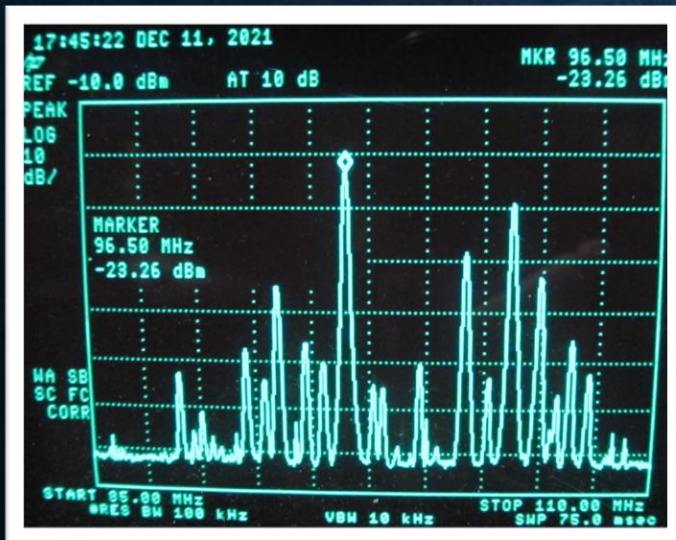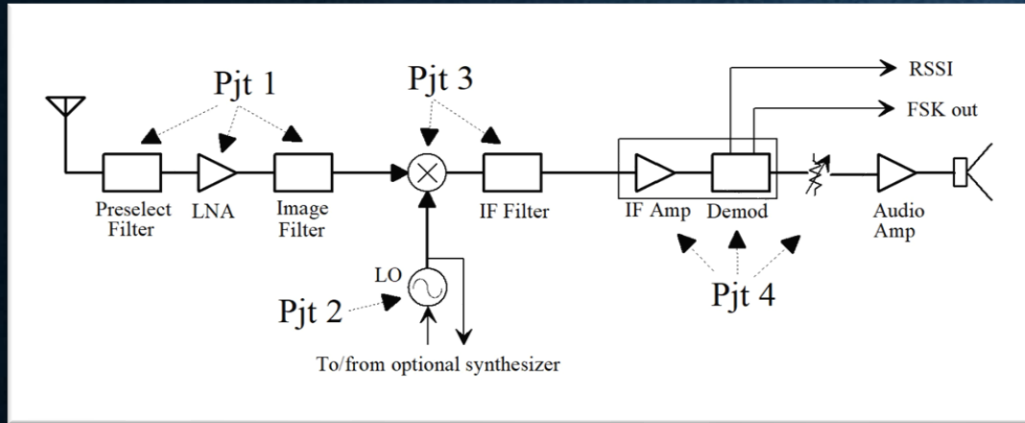Performance Now (and future improvements)



- Approaching performance of commercial VR120 receiver
- Both require moving antenna to get clear reception sometimes
- Low and high frequency sensitivity issues remain due to narrow LNA bandwidth and low IF gain
- Maybe add additional IF amp stage and second IF filter, and reduce Q in LNA to lower its gain and increase its bandwidth.
- Could also change mixer to diode-ring type (higher compression point) at cost of higher power
- OR... Use techniques like tracking preselection or a “Q-enhanced” LNA ! (modern use of regen :-)

Outline of Today's Episode




- *Review of problems found in Epilogue 1*
- *Troubleshooting and fixing it*
- *General troubleshooting techniques*
- *Future topics*

Generalizing ...

- Review / understand the system being debugged (and safety issues)
- Ask what changed since last time it worked
- Assess the known symptoms and try to localize the problem
- Do the simple / quick things first (visual checks, DC bias checks, etc.)
- Consider, but don't overemphasize common causes

- Collect additional clues (e.g., inject known signals and do signal tracing)
- Test theories (but consider KISS principle and time and monetary costs)
- Recognize that faults will change circuit, so it may be different than we think
- Sleep on it if needed and restart fresh 😊

Application to a '92 Corvette ☺

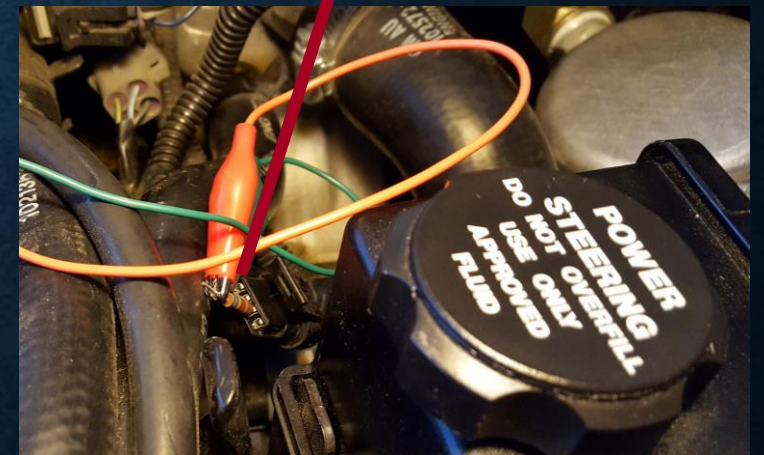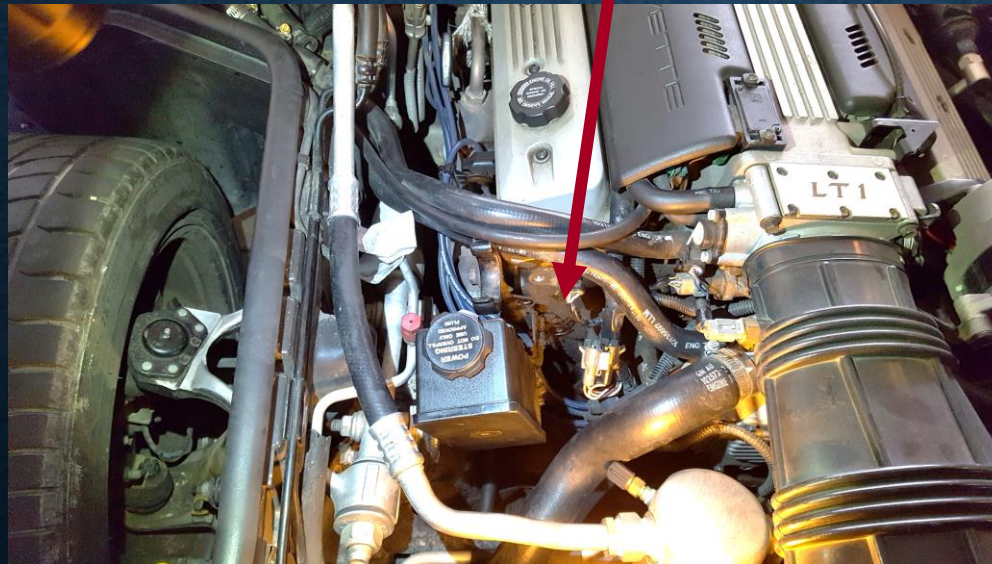
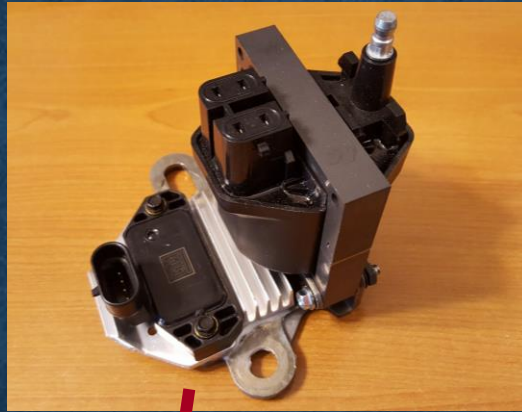


Outline of Today's Episode

- *Review of problems found in Epilogue 1*
- *Troubleshooting and fixing it*
- *General troubleshooting techniques*
- *Future topics*

Future Topics

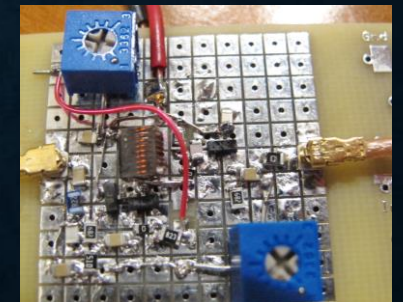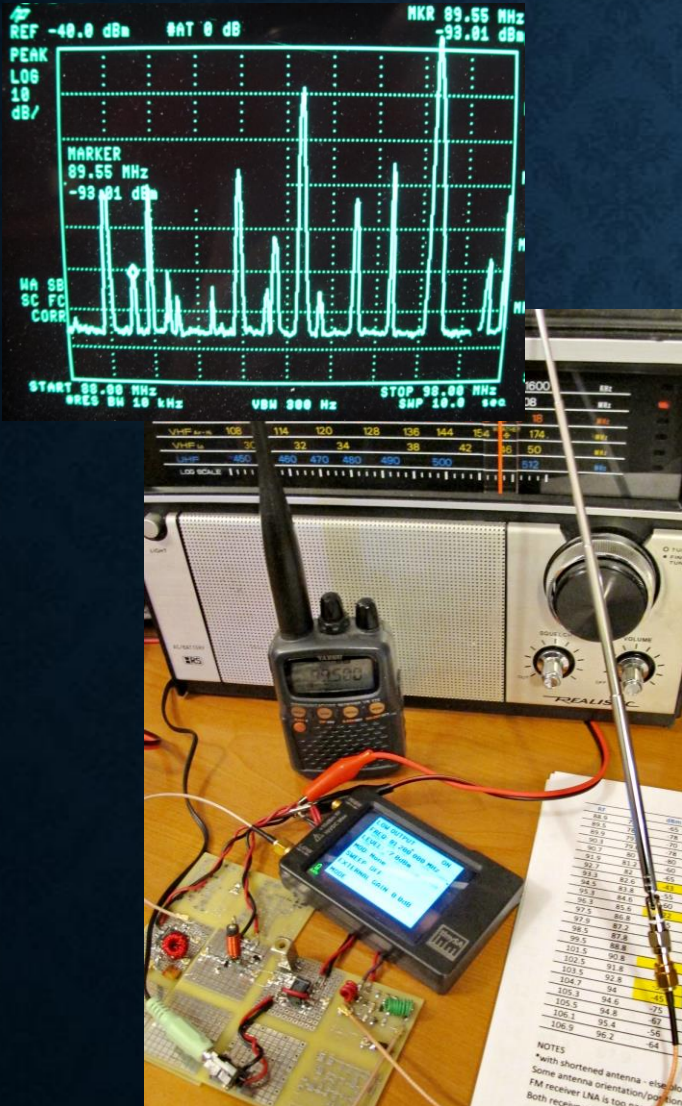- Study commercial radio designs and schematics
- Performance considerations (compression points, intermodulation, power consumption)
- Spurious products from mixers
- Receiver ideal sensitivity (MDS, Noise Figure, etc.)
- Elevated Noise Floors (RFI caused by modern switch-mode power supplies and lighting)
- Project 😊
 - Q-enhanced Low Noise Amplifier




Preview of Q-enhanced LNA

Signals from Antenna

Bottom end of Band
(88 to 98 MHz)


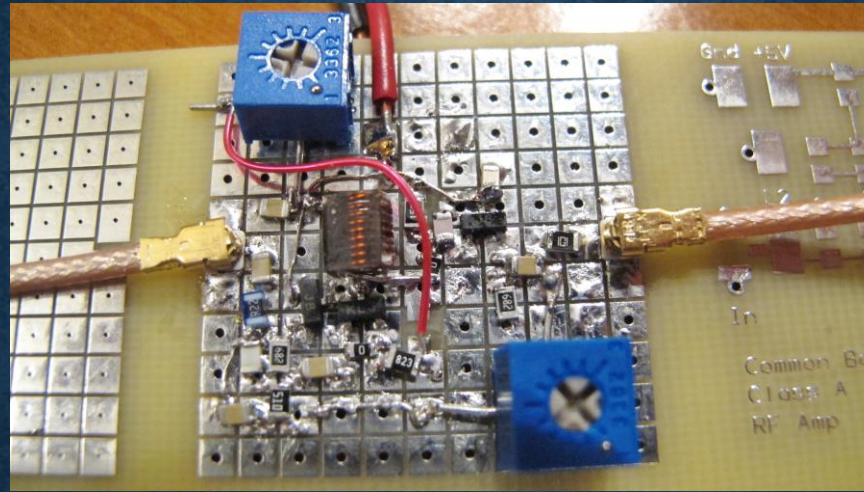
Spectrum analyzer noise
floor of -104 dBm (30 dB NF)






Output from Q-enhanced LNA

RF filtering tuned to 89.5 MHz

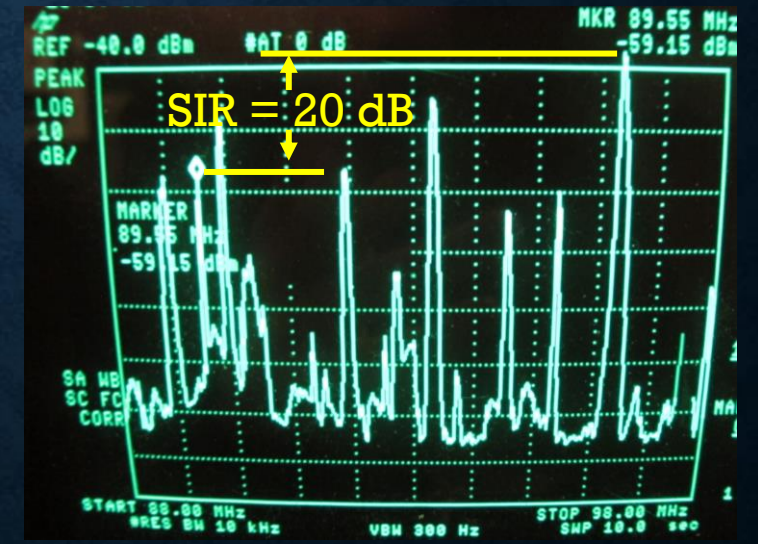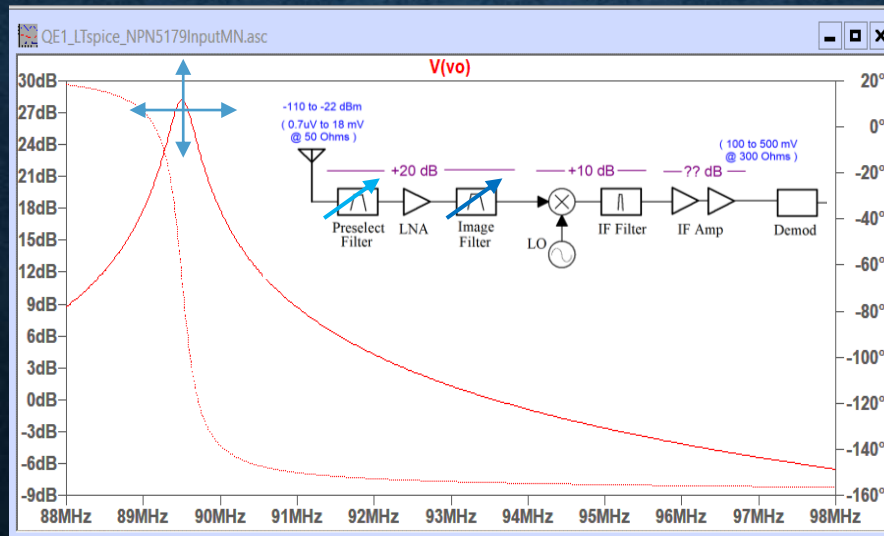Q enhanced to 500 => 200 kHz
bandwidth (at RF, before mixer !)



Troubleshooting a '92 Corvette ☺

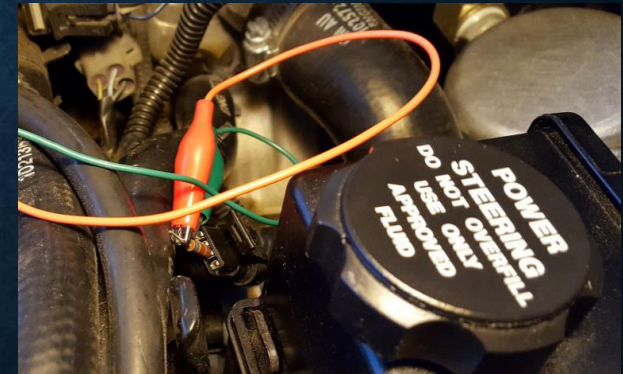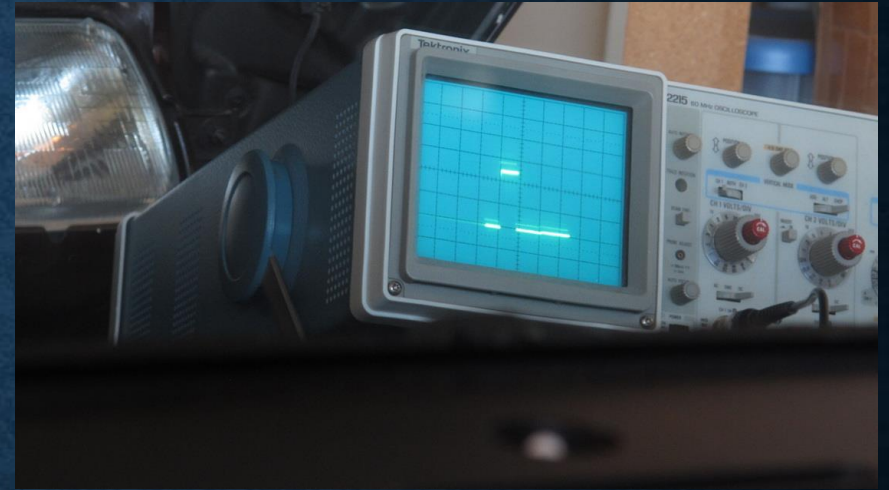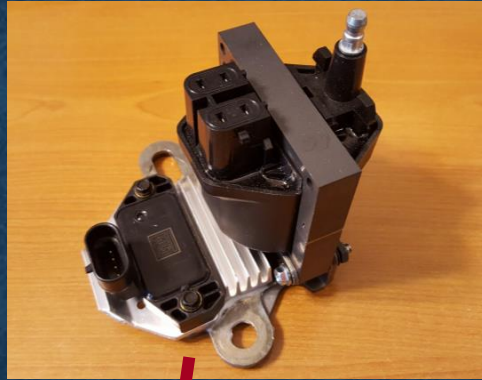

Troubleshooting Techniques

- Review / understand the system being debugged (and safety issues)
- Ask what changed since last time it worked
- Consider, but don't overemphasize common causes
- Assess the known symptoms and try to localize the problem
- Do the simple / quick things first (visual checks, etc.)

- Collect additional clues (e.g., do signal tracing)
- Test theories (but consider KISS principle and time and monetary costs)
- Recognize that faults will change system, so it may be different than we think
- Sleep on it if needed and restart fresh 😊

*Thanks For
Watching !*