

Radio Design 101

Episode 2 – Impedance Matching

Slides downloaded from: <https://ecefiles.org/rf-design/>

Companion videos at: <https://www.youtube.com/watch?v=WXdGKErCjZw> (part 1)

and: <https://www.youtube.com/watch?v=ZWBem8GTzNs> (part 2)

This material is **provided by ecefiles.org for educational use only.**

This episode starts with the "big picture" on why impedance matching is needed in RF circuits and then focuses on a design example using a low noise amplifier (LNA). The example uses L-type matching circuit architectures, but the material is general. The second part of this episode discusses alternative Pi, T, and LL networks as well as RF transformers and tapped LC designs. Part 2 also shows how these are used in actual radio / wireless products including a unique TR switch, LNA, and power amp combination in a UHF integrated circuit transceiver.


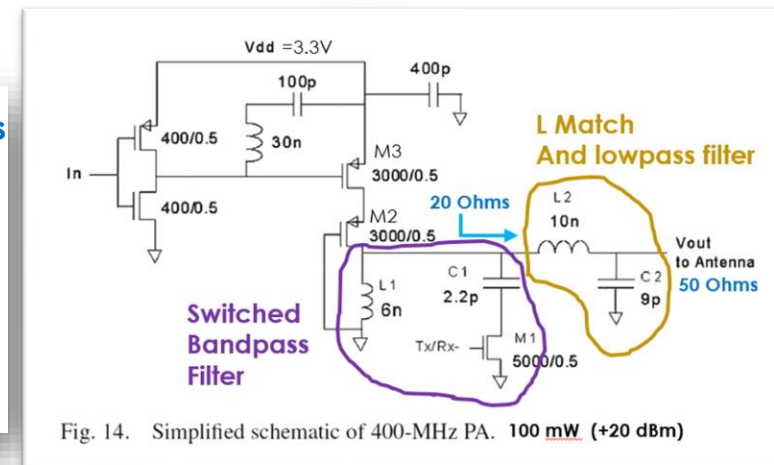
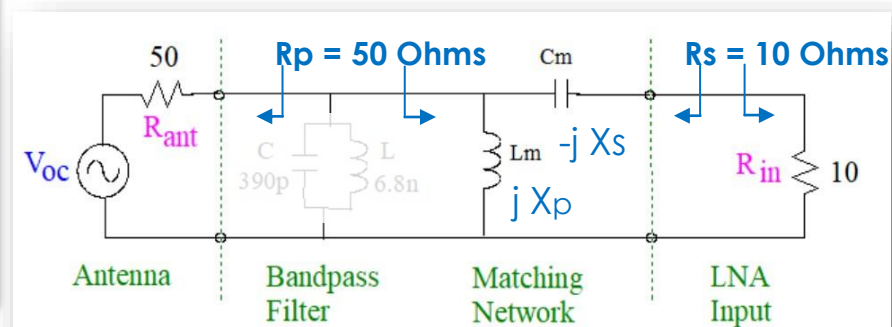
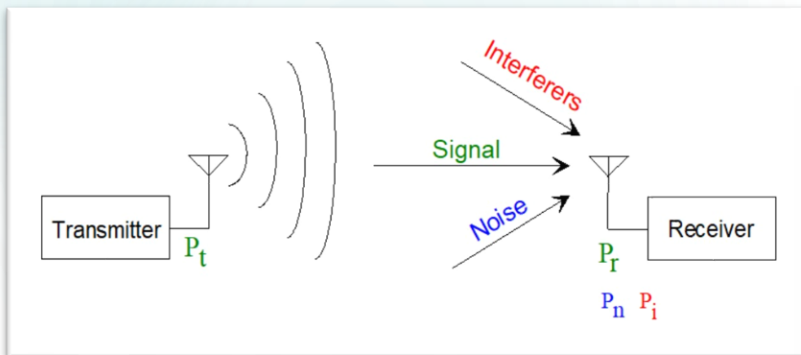
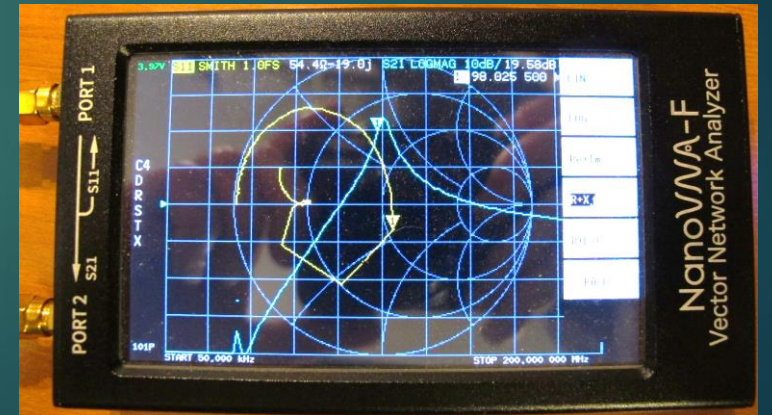
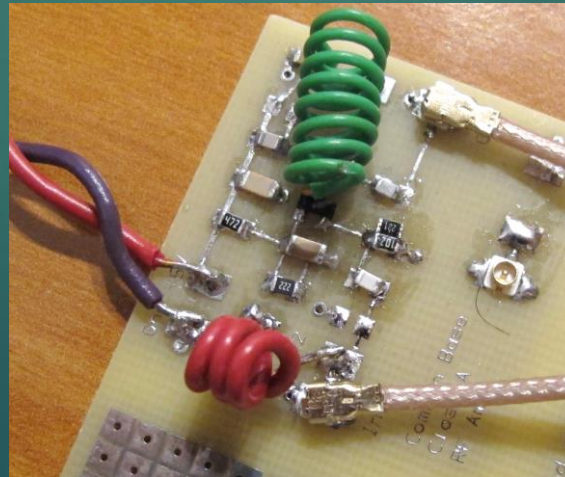


Fig. 14. Simplified schematic of 400-MHz PA. 100 mW (+20 dBm)

Radio Design 101

Episode 2


Impedance Matching

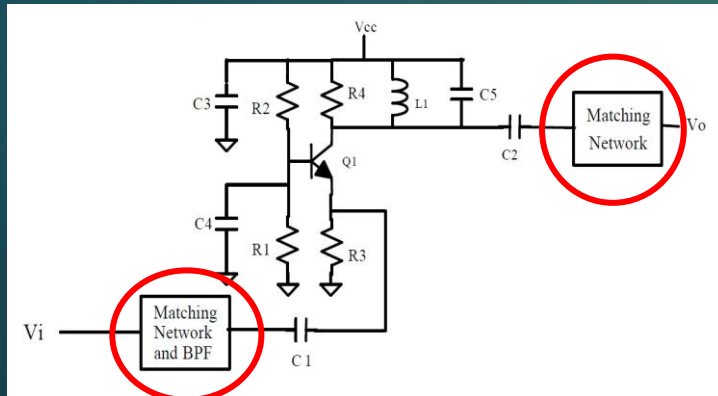

Topic Outline

- *Why use matching networks ?*
- *L Matching Network for Receiver Input*
- *Using NanoVNA to validate design*
- *Other MN circuit topologies*
- *Examples in real-world applications*

Topic Outline

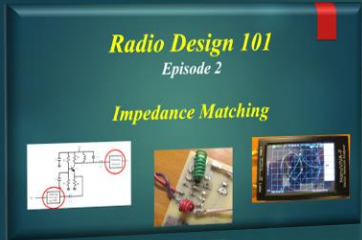

Part 1

- *Why use matching networks ?*
- *L Matching Network for Receiver Input*
- *Using NanoVNA to validate design*


Part 2

- *Other MN circuit topologies*
- *Examples in real-world applications*



Why Use Matching Networks ?

The Big Picture ...

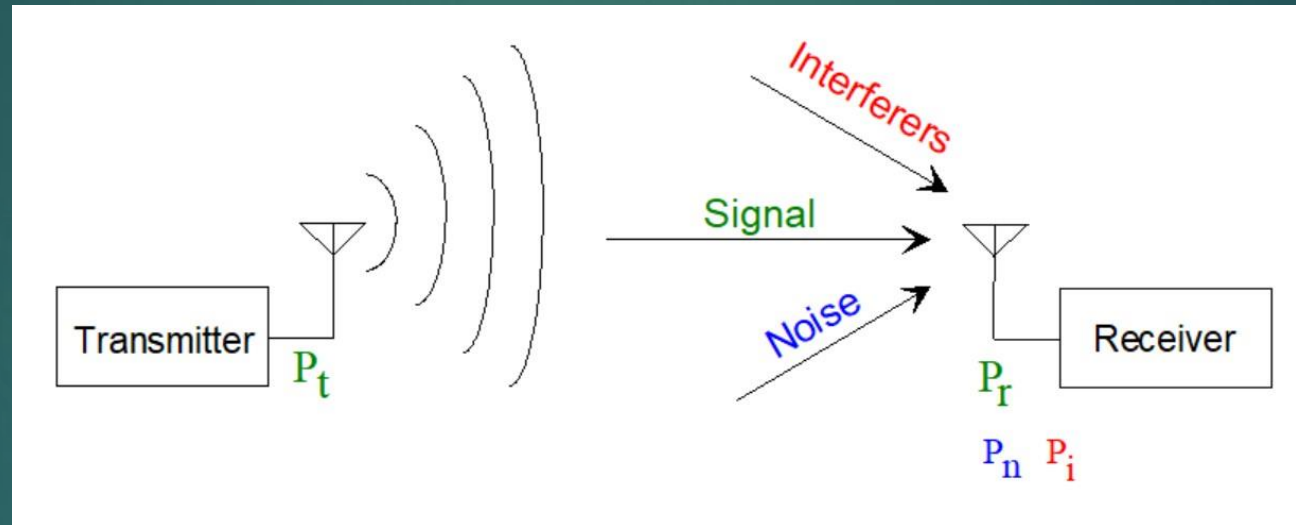

$$P_r = \left[\frac{P_t}{4\pi R^2} G_t \right] A_e$$



$$P_n = kTB$$

We usually need received power P_r greater than noise power P_n

For example, $P_r = 10 P_n$ to $100 P_n$ (i.e. 10 to 20 dB SNR) or more

NOTE: "Path loss exponent is 2 for free-space only. Terrestrial propagation may use 3 to 5.
See "Propagation comparisons at VHF and UHF frequencies," 2009 IEEE Radio and Wireless Symposium

Circuit Level View

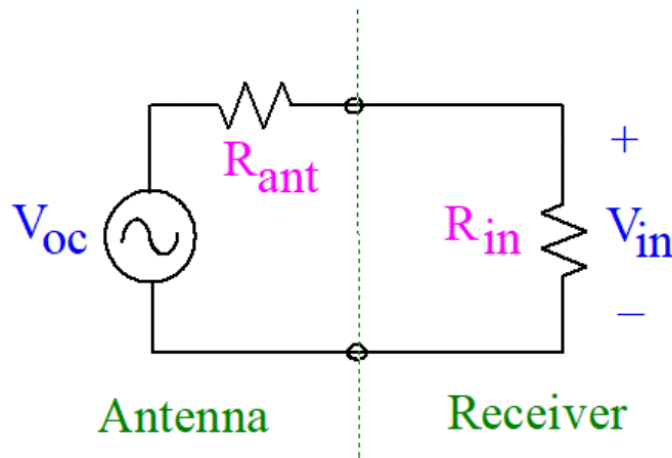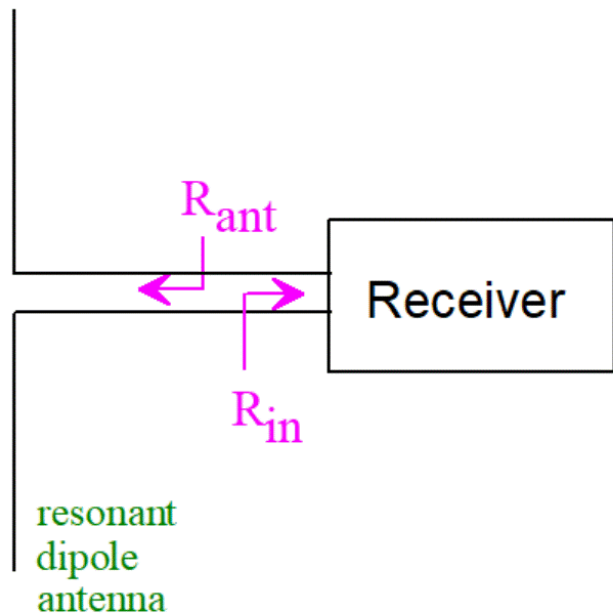

$$V_{in} = V_{oc} \frac{R_{in}}{R_{in} + R_{ant}}$$


$$P_r = \frac{(V_{in})^2}{R_{in}}$$

$$P_r \text{ (dBm)} = 10 \log \left(\frac{P_r}{1 \text{ mW}} \right)$$

Max Power Transfer

Let $V_{oc} = 1 \mu\text{V RMS}$ and $R_{ant} = 50 \text{ Ohms}$

Then ...

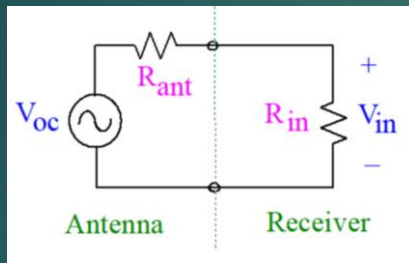

R _{in}	V _{in}	P _r	P _r (dBm)
10	0.17 μV	2.8 fW	-116
50	0.50 μV	5.0 fW	-113
1K	0.95 μV	0.91 fW	-120

P_r is maximized when $R_{in} = R_{ant}$




Or in general, when $Z_{in} = Z_{ant}^*$

V_{in} is maximized here, but P_r is low since R_{in} is big

Topic Outline

- *Why use matching networks ?*
- *L Matching Networks in Low-Noise Amp*
- *Using NanoVNA to validate design*
- *Other MN circuit topologies*
- *Examples in real-world applications*

Project 1 – FM Receiver Front End

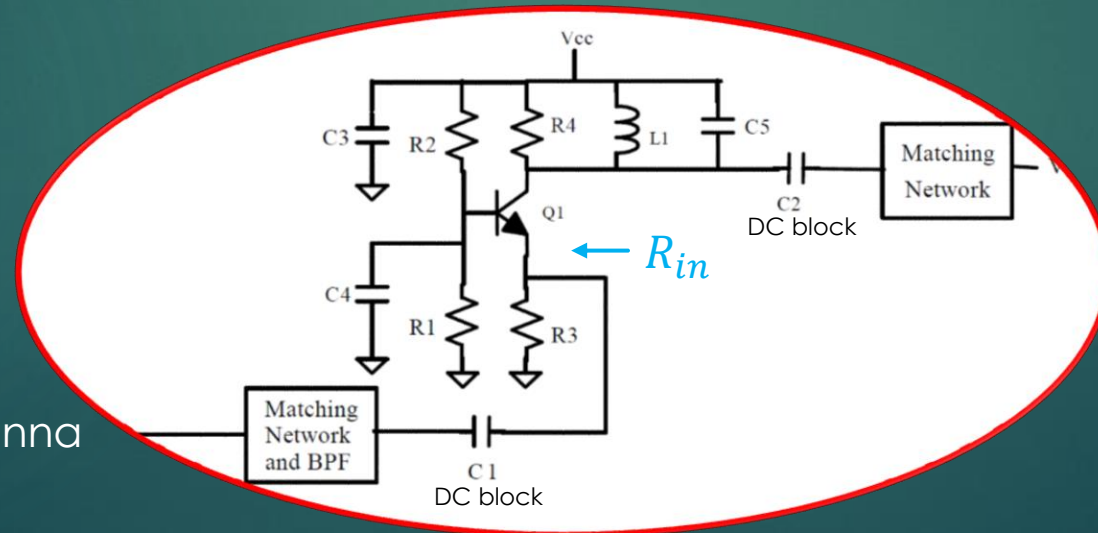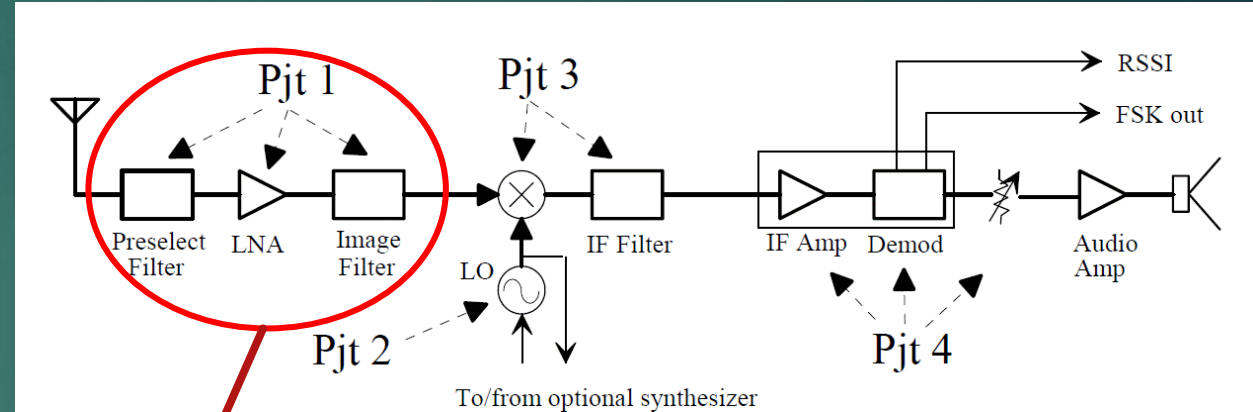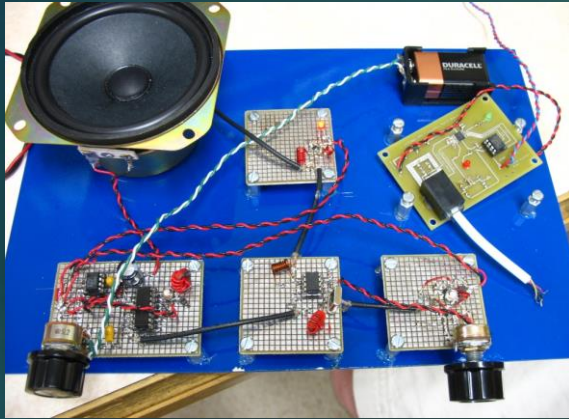


From 50 Ohm antenna

To 50 Ohm load (project 3 input)

Review (from Episode 1)

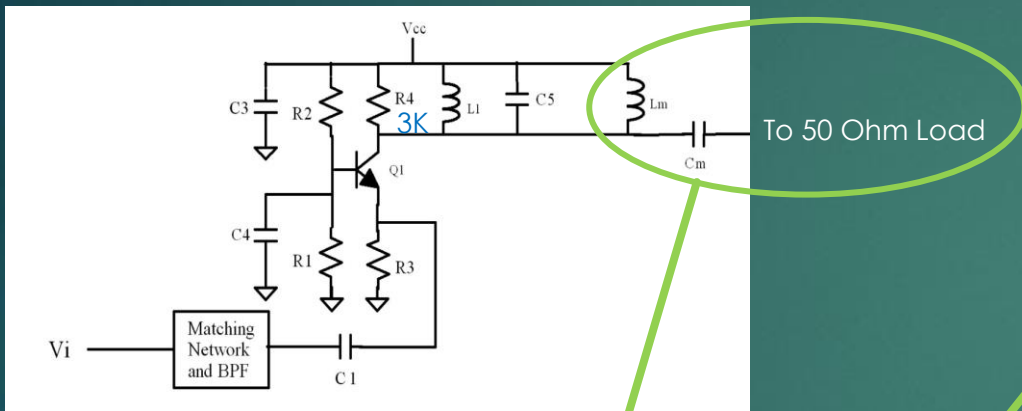Output “L-type” matching network uses LC resonator to convert 50 Ohm load to 3.2K Ohms (with minimal power loss)



Viewed from load (series resonant circuit view):

$$Q = \frac{X_o}{R_s} = \frac{400}{50} = 8$$


Viewed from amplifier (parallel resonant circuit view):

$$Q = 8 \quad \text{and} \quad Q = \frac{R_p}{X_o}$$


$$\Rightarrow R_p = Q X_o = Q^2 R_s = 3.2 \text{ K Ohms}$$

NOTE: Above is approximately true at for high Q case.


In general: $R_p = (1+Q^2) R_s$

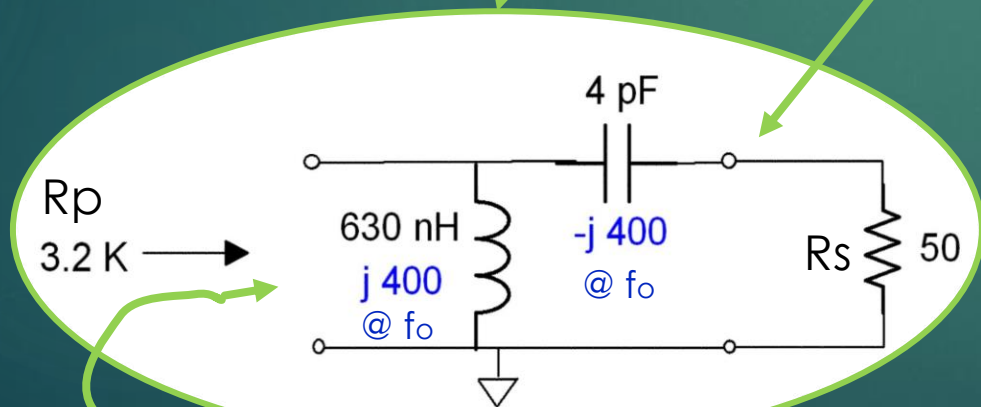

Solution for Input MN and Filter

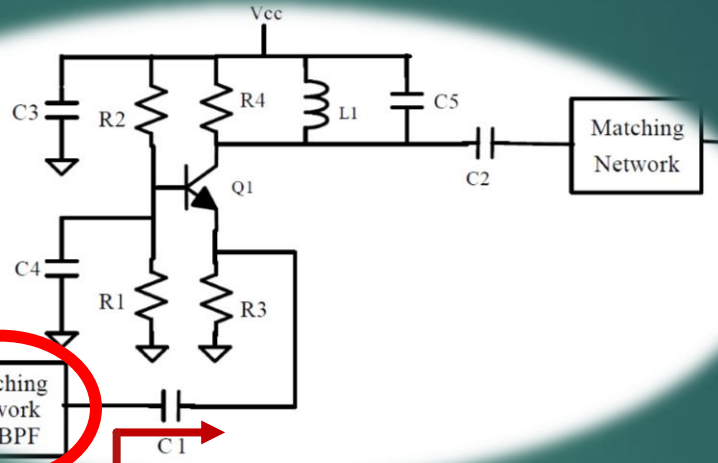

From 50 Ohm antenna

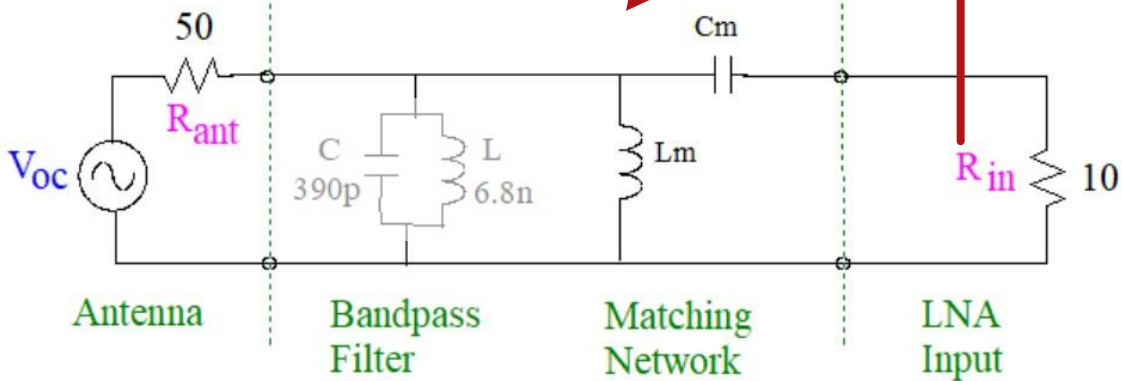


Bandpass Filter designed in Episode 1

Parallel LC filter becomes open circuit at f_0

For matching network, need to convert 10 Ohms to 50 Ohms

Solution for MN Components

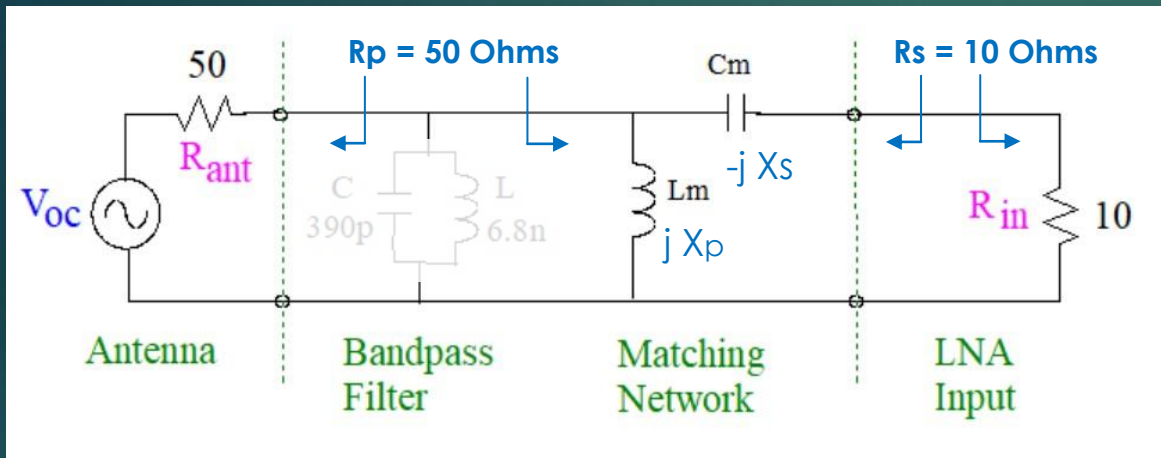

With $R_p = 50$ and $R_s = 10$:

$$Q = \sqrt{\frac{50}{10} - 1} = 2$$

$$X_p = \frac{50}{2} = 25 \text{ Ohms}$$

$$X_s = (10)(2) = 20 \text{ Ohms}$$

$$L_m = \frac{25}{2\pi 100 \text{ MHz}} = 39.8 \text{ nH}$$

$$C_m = \frac{1}{2\pi (100 \text{ MHz})(20)} = 79.6 \text{ pF}$$

Analysis Formulas:

$$R_p = (1 + Q^2) R_s$$

$$Q = \frac{R_p}{X_p} \quad Q = \frac{X_s}{R_s}$$

$$X_p = 2\pi f L_m \quad X_s = \frac{1}{2\pi f C_m}$$

Design Formulas:

$$Q = \sqrt{\frac{R_p}{R_s} - 1}$$

$$X_p = \frac{R_p}{Q} \quad X_s = R_s Q$$


$$L_m = \frac{X_p}{2\pi f} \quad C_m = \frac{1}{2\pi f X_s}$$

Topic Outline

- *Why use matching networks ?*
- *L Matching Networks in Low-Noise Amp*
- *Using NanoVNA to validate design*
- *Other MN circuit topologies*
- *Examples in real-world applications*

Testing amplifiers with NanoVNA

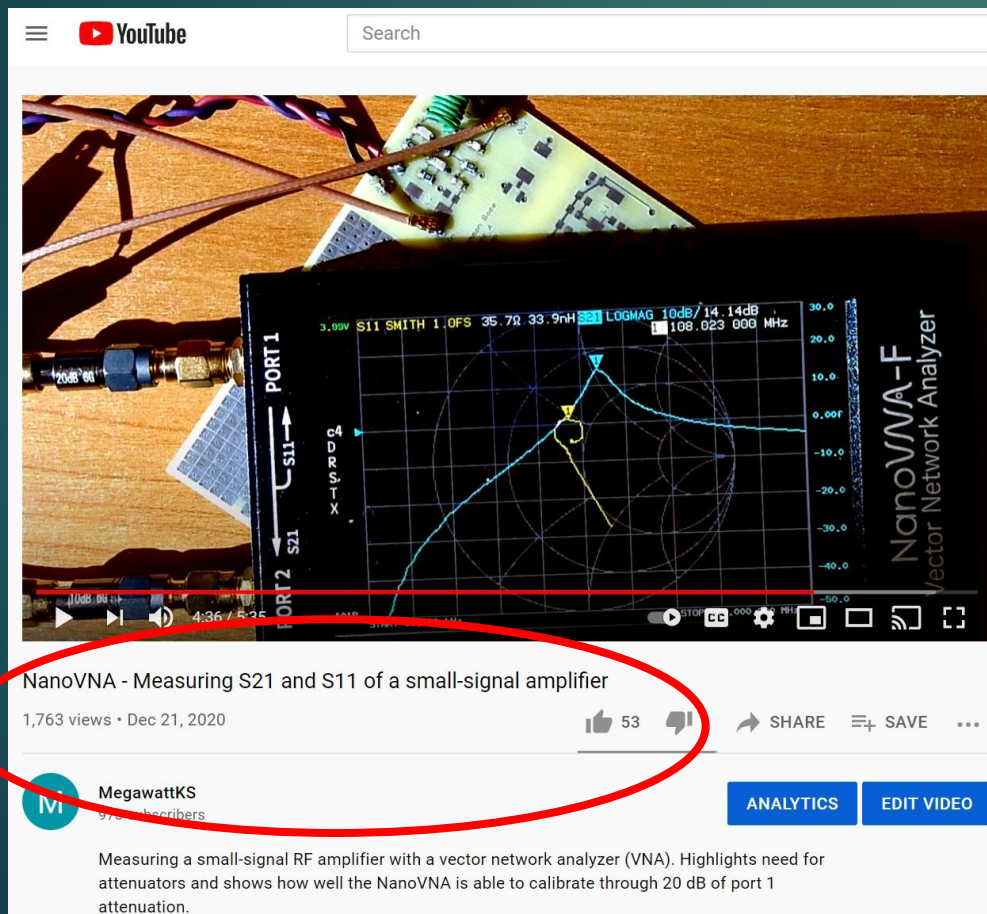In previous video from the NanoVNA series...



NanoVNA - Measuring S21 and S11 of a small-signal amplifier



1,763 views · Dec 21, 2020

MegawattKS
973 subscribers

Measuring a small-signal RF amplifier with a vector network analyzer (VNA). Highlights need for attenuators and shows how well the NanoVNA is able to calibrate through 20 dB of port 1 attenuation.




- Transistor was originally biased at 0.9 mA to give 50 Ohm R_{in} , so no input matching was used.
- Measured power gain S_{21} was 14 dB.

Testing Upgraded Amp

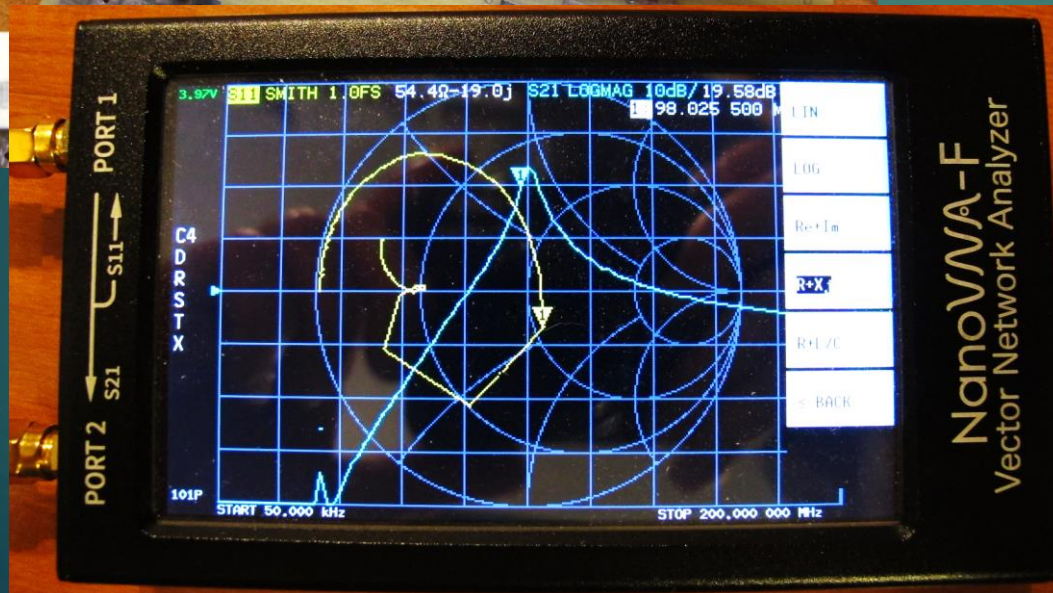
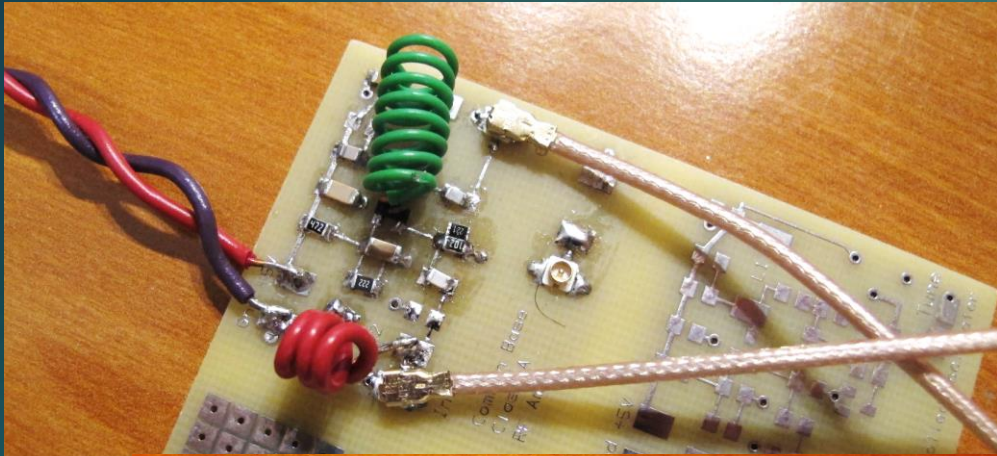


- Here, amplifier is re-biased at 4.5 mA to increase power gain by 5X.
- Input MN added.
- Measured power gain S21 increased from 14 dB to 22 dB.
- Measured input Z is $54 - j19$, so MN is working 😊
- Still needs a little tweaking maybe...

Inductor Measurements

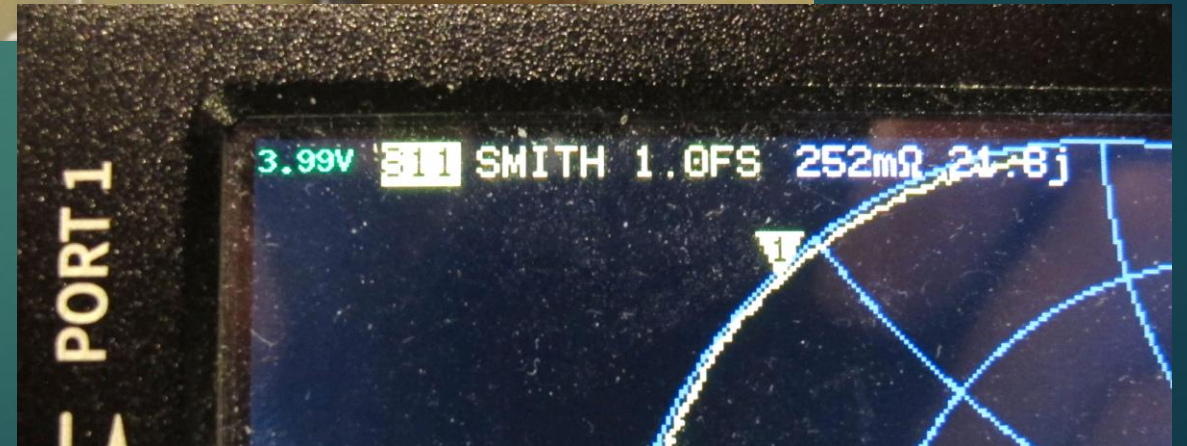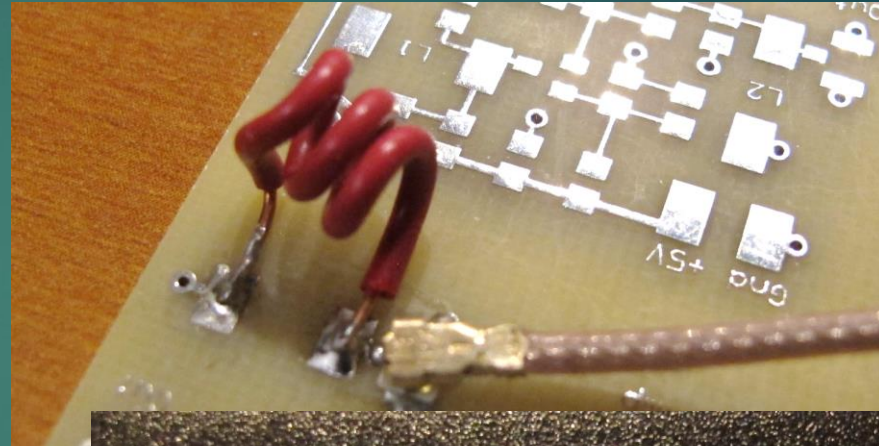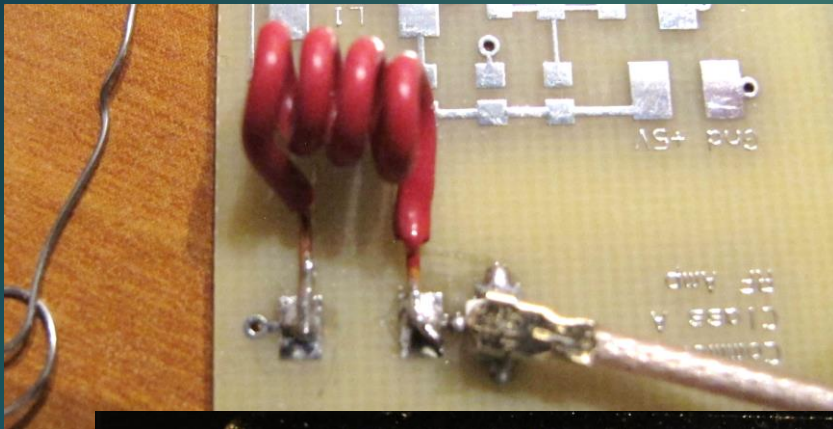

Initial Tuning / Stability Issues

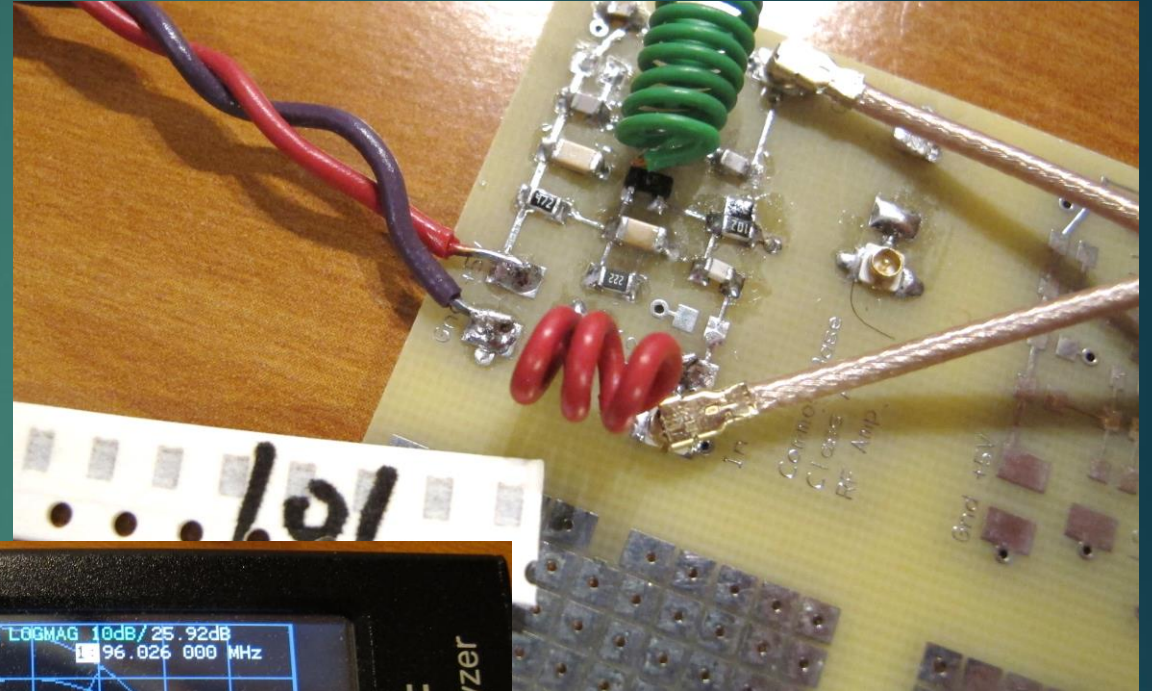
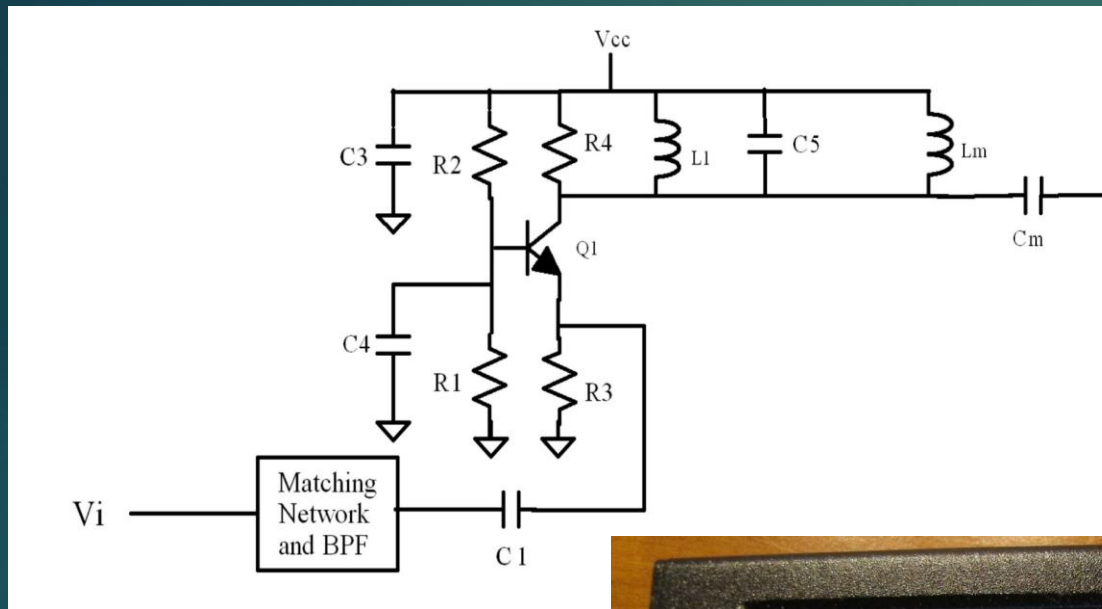


Radio Design 101


Episode 2

Impedance Matching

Part 2

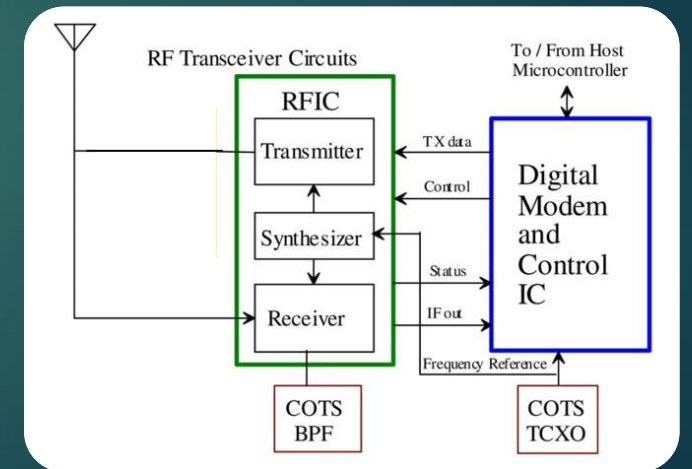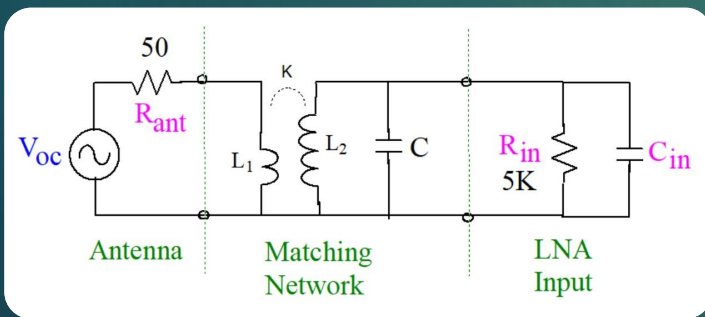

Topic Outline

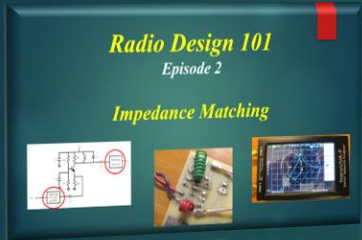

Part 1

- *Why use matching networks ?*
- *L Matching Network for Receiver Input*
- *Using NanoVNA to validate design*



Part 2

- *Other MN circuit topologies*
- *Examples in real-world applications*




Converting from Low Z to High Z

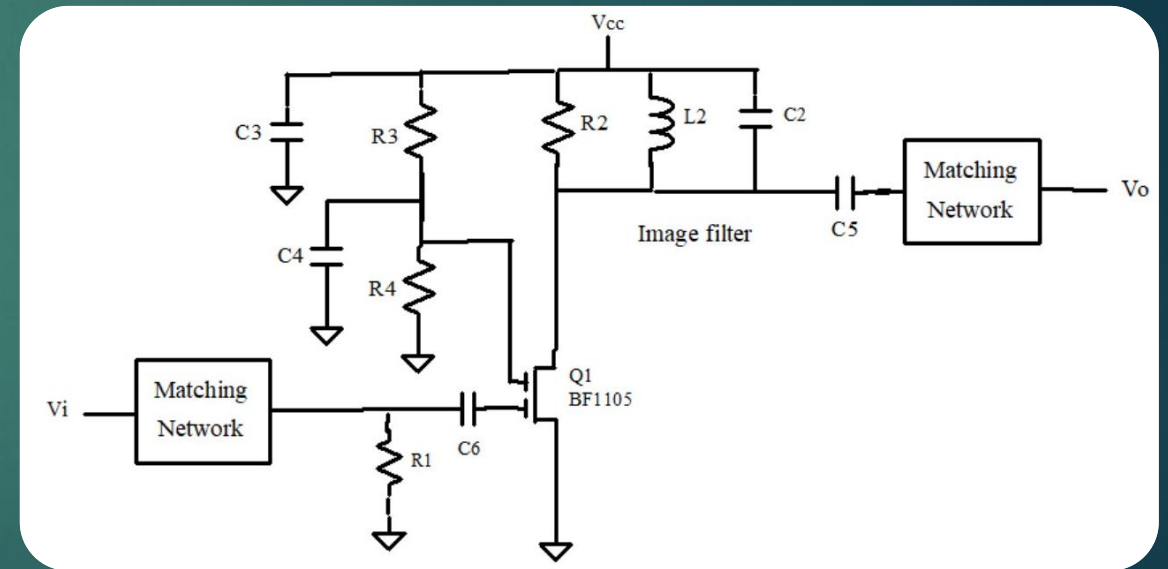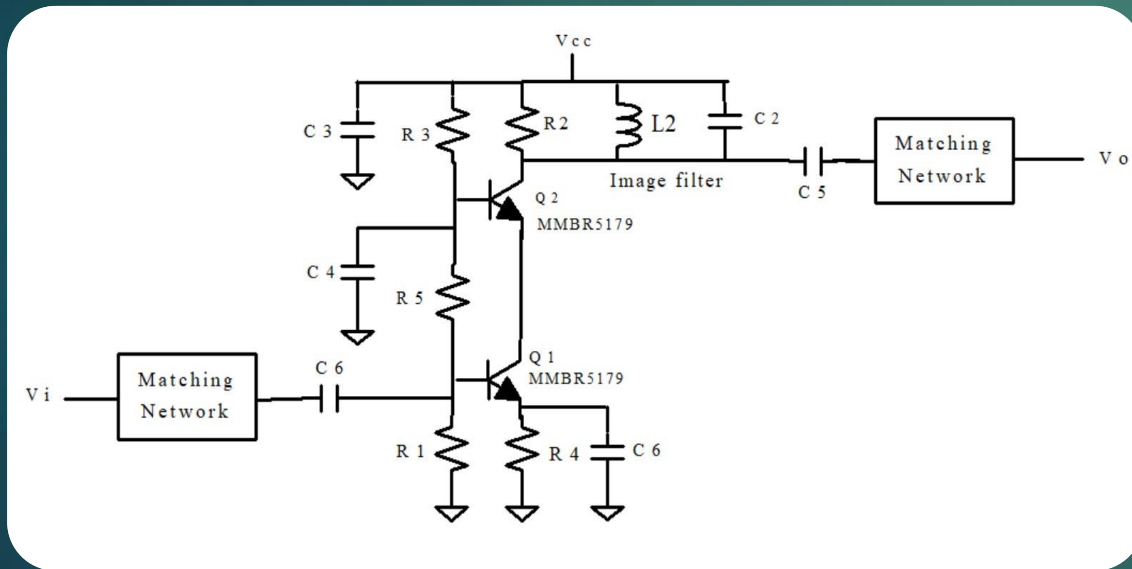Cascode amps with high (and capacitive) Z_{in} :



Converting from Low Z to High Z

L-match network ...

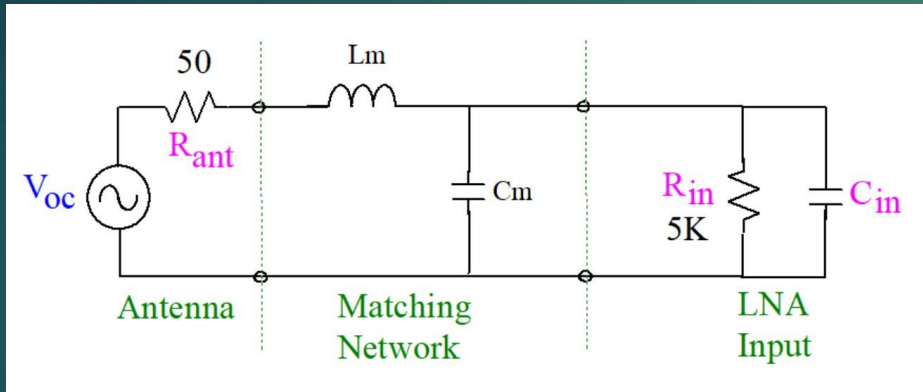


Design Procedure

- Same as before, except
 - Series and parallel sides are reversed
 - C and L are swapped.
- Adjust formulas as appropriate...
- Subtract C_{in} from C_m value

Tuned RF Transformers

Classic transformer design:

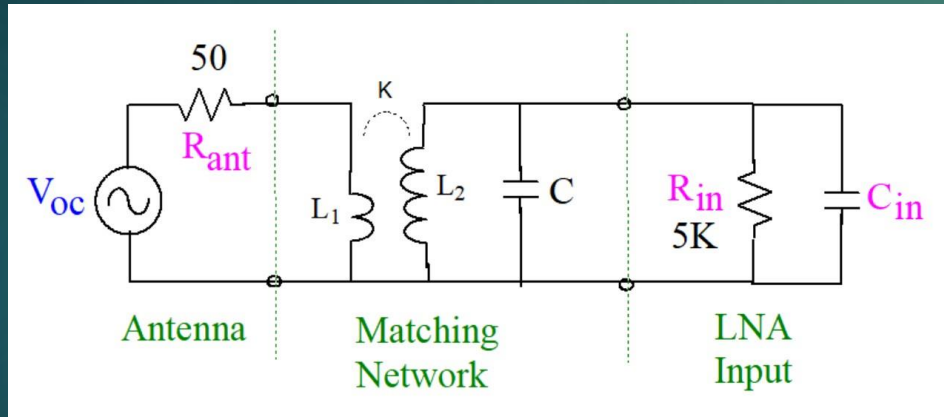

Design Procedure


- L_2 and C form a bandpass filter. Design as in Episode 1
- After determining number of turns N_2 for L_2 , estimate number of turns N_1 for L_1 from:

$$\frac{R_{in}}{R_{ant}} = \frac{L_2}{L_1} = \left(\frac{N_2}{N_1}\right)^2 \quad *$$

- Wind coils so that coupling coefficient $K > 1/Q$

* Assumes $K = 1$

Impedance and Voltage Transformation

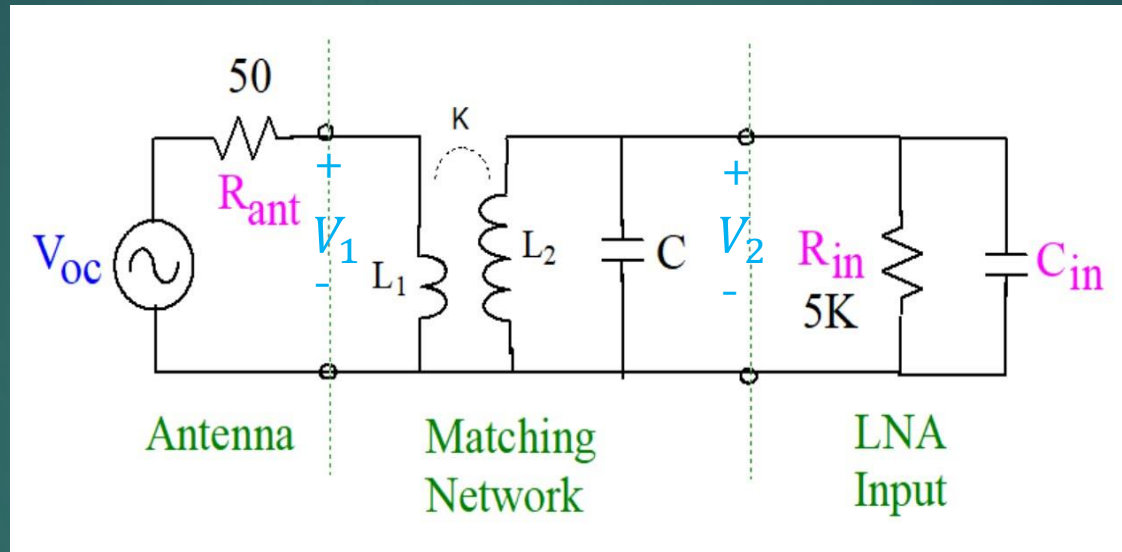


NOTE: Impedance step-up is associated with a voltage gain: 😊

$$\frac{V_2}{V_1} = \sqrt{\frac{R_{in}}{R_{ant}}}$$

← This is true in general for lossless matching, not just in this design !

Tapped LC Resonators

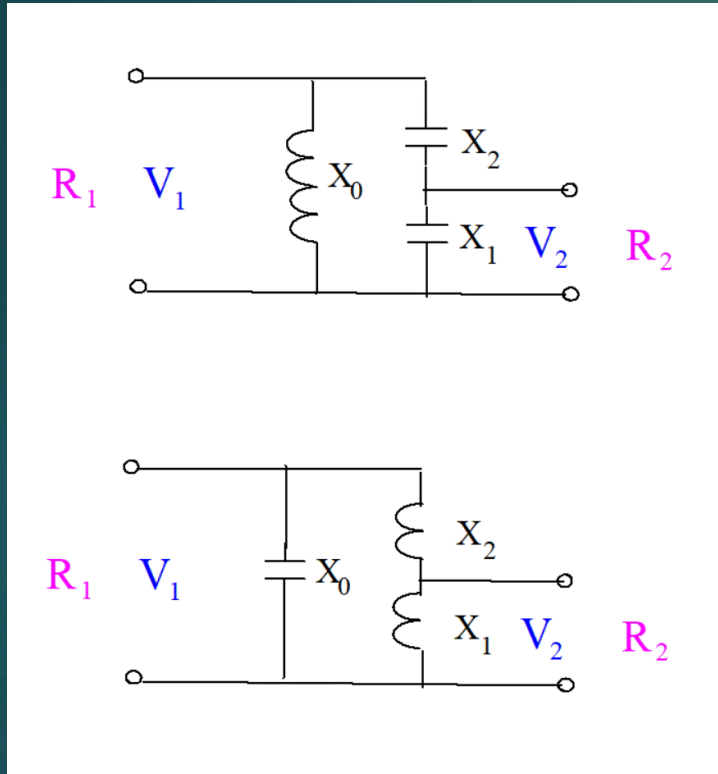

- Shunt L and C form a bandpass filter. Design as in Episode 1

$$Q = \frac{f_0}{B} \quad X_0 = \frac{R_p}{Q} \quad X_1 + X_2 = X_0$$

- Create L or C voltage divider using voltage and impedance relationship from previous slide and V divider

$$\frac{V_2}{V_1} = \sqrt{\frac{R_2}{R_1}} \quad \text{and} \quad \frac{V_2}{V_1} = \frac{X_1}{X_1 + X_2}$$

- Solve for L and C values


NOTES:

- Can use in either direction, to convert up or down
- When finding R_p , need to know if source/load resistances will exist on one side or both...
- If both, then Q is "loaded Q" found from $R_p = R_1 / 2$, else $R_p = R_1$


Additional Options...

To get narrower or wider bandwidths, more realizable L or C values, and to work better in face of component and PC board parasitics, also consider:


- Pi Networks

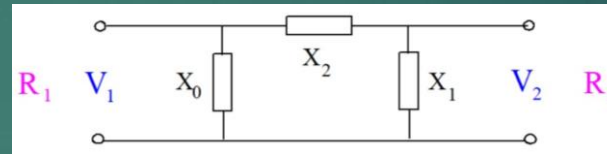


- T Networks

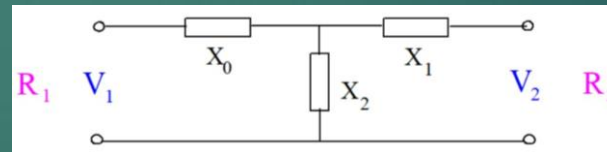

- LL Networks


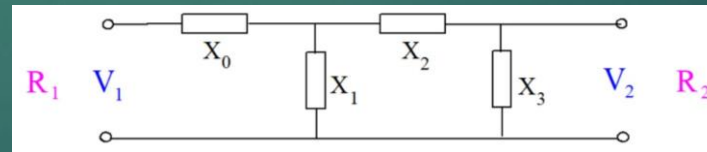


- Microstrip

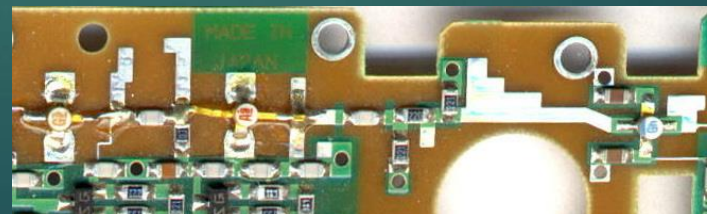

T Matching Network + Filter

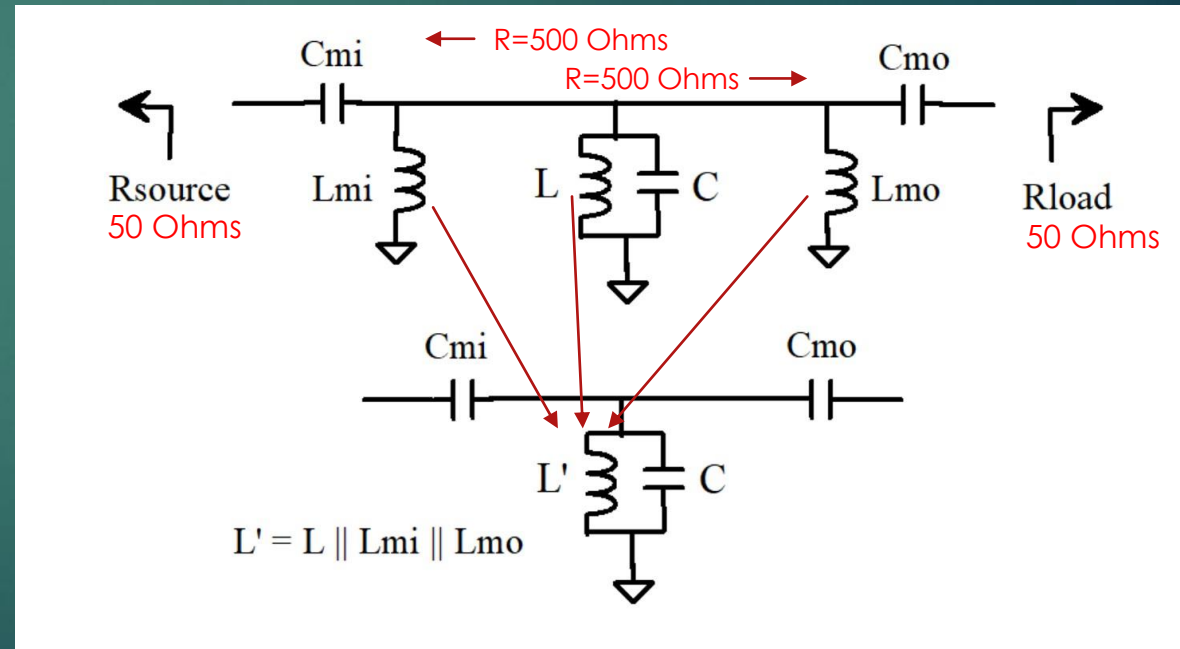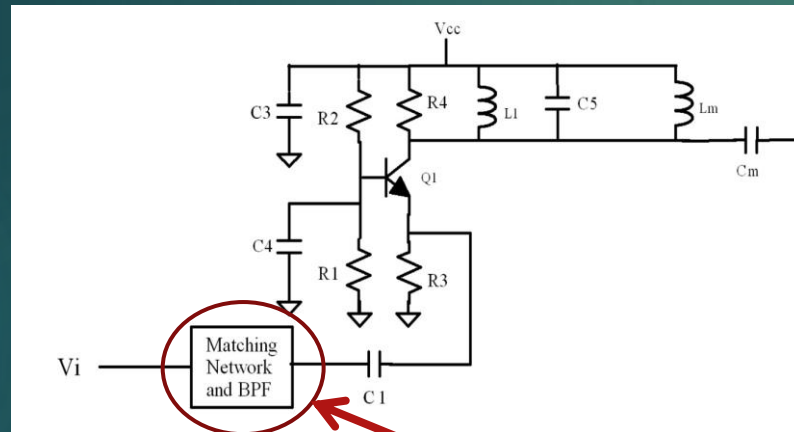Use matching networks to make filters more “realizable”



Take-home assignment:

Combine with (impedance scaled) filter from Episode 1 and build, test 😊

Answer check: L' should come out to 33 nH

Topic Outline

- *Why use matching networks ?*
- *L Matching Networks in Low-Noise Amp*
- *Using NanoVNA to validate design*
- *Other MN circuit topologies*
- *Examples in real-world applications*

Simple “Crystal” Radio



FIGURE 1. This restored crystal radio kit from Allied Radio in Chicago cost \$2.50 in the 1950s and '60s.


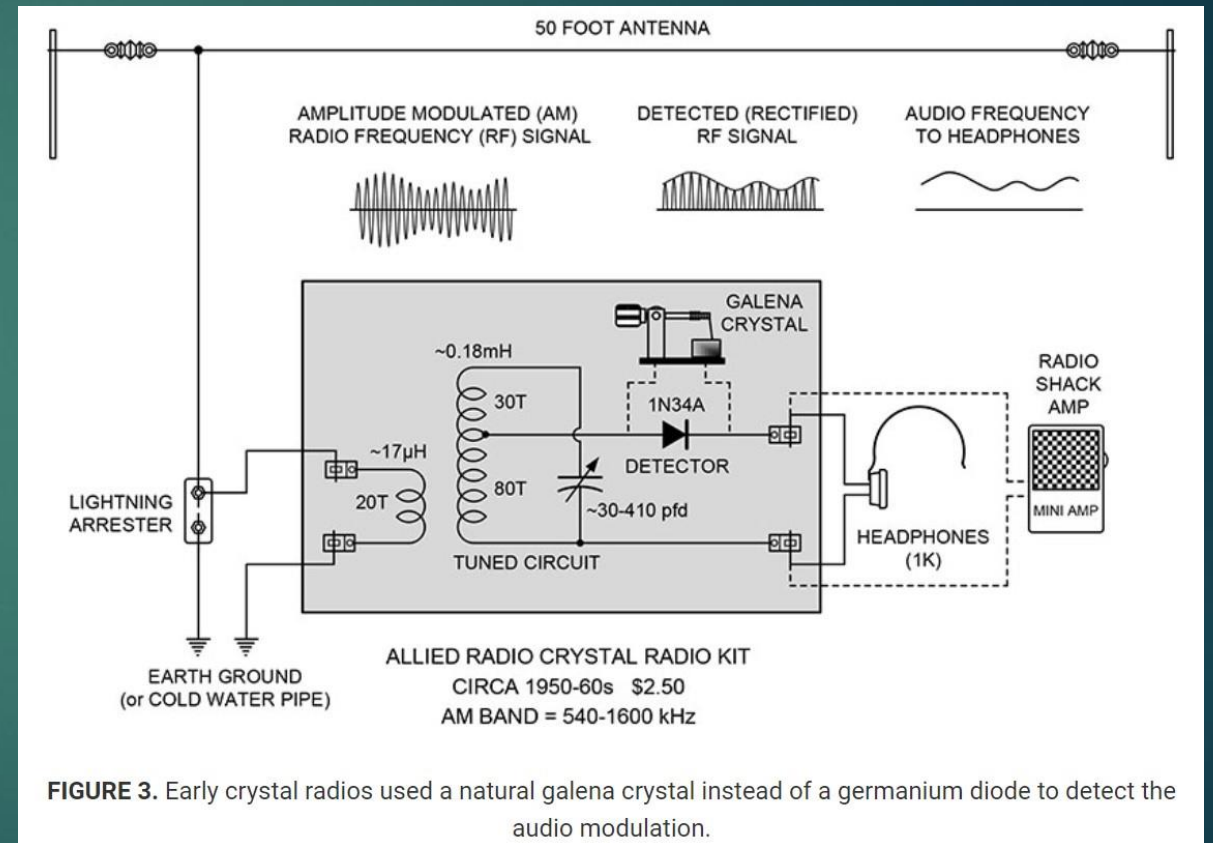
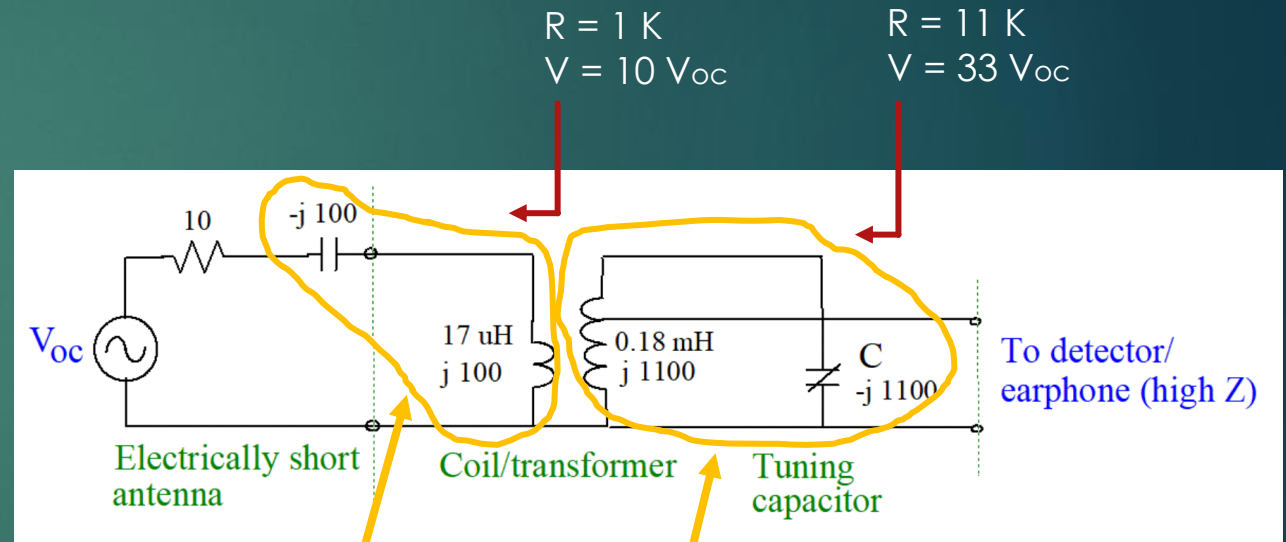


FIGURE 3. Early crystal radios used a natural galena crystal instead of a germanium diode to detect the audio modulation.

Hidden Complexities

(doing more with less)

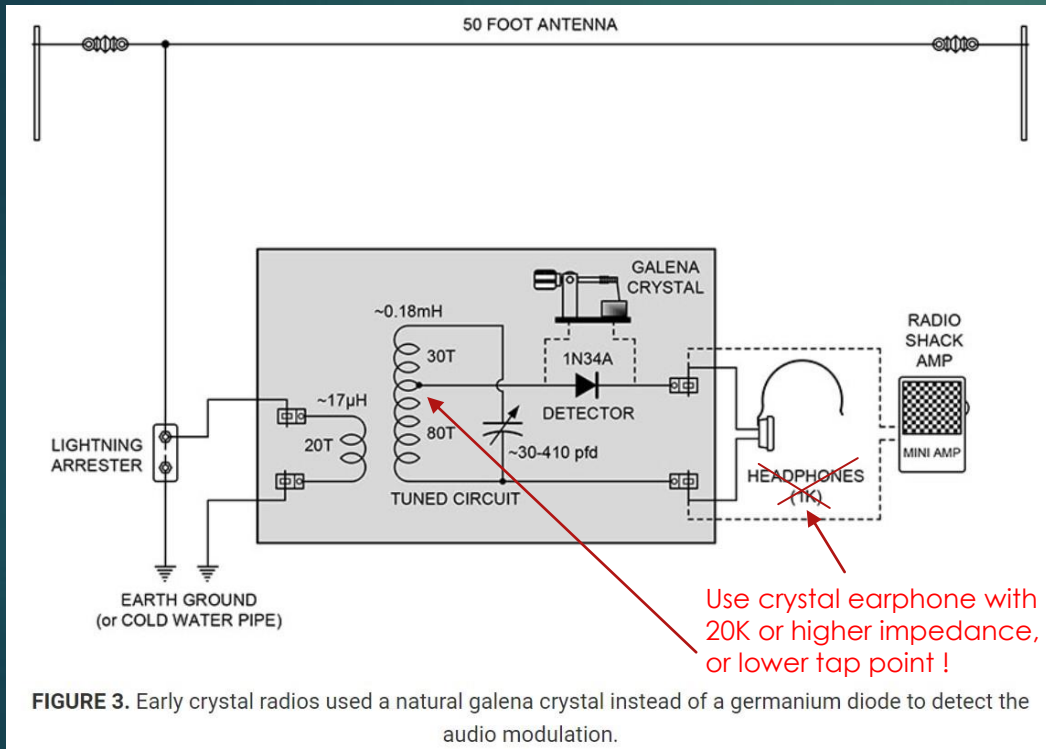

Impedance and voltage step-up, plus (untuned) bandpass filtering

More bandpass filtering
 $Q = R_p/X_o = 10$
 $BW = f_o/Q = 100 \text{ kHz}$


Tuned RF Receiver

(doing more with more)

Same as crystal radio,
but with antenna tuning

RF gain and filtering

Demod and audio amp

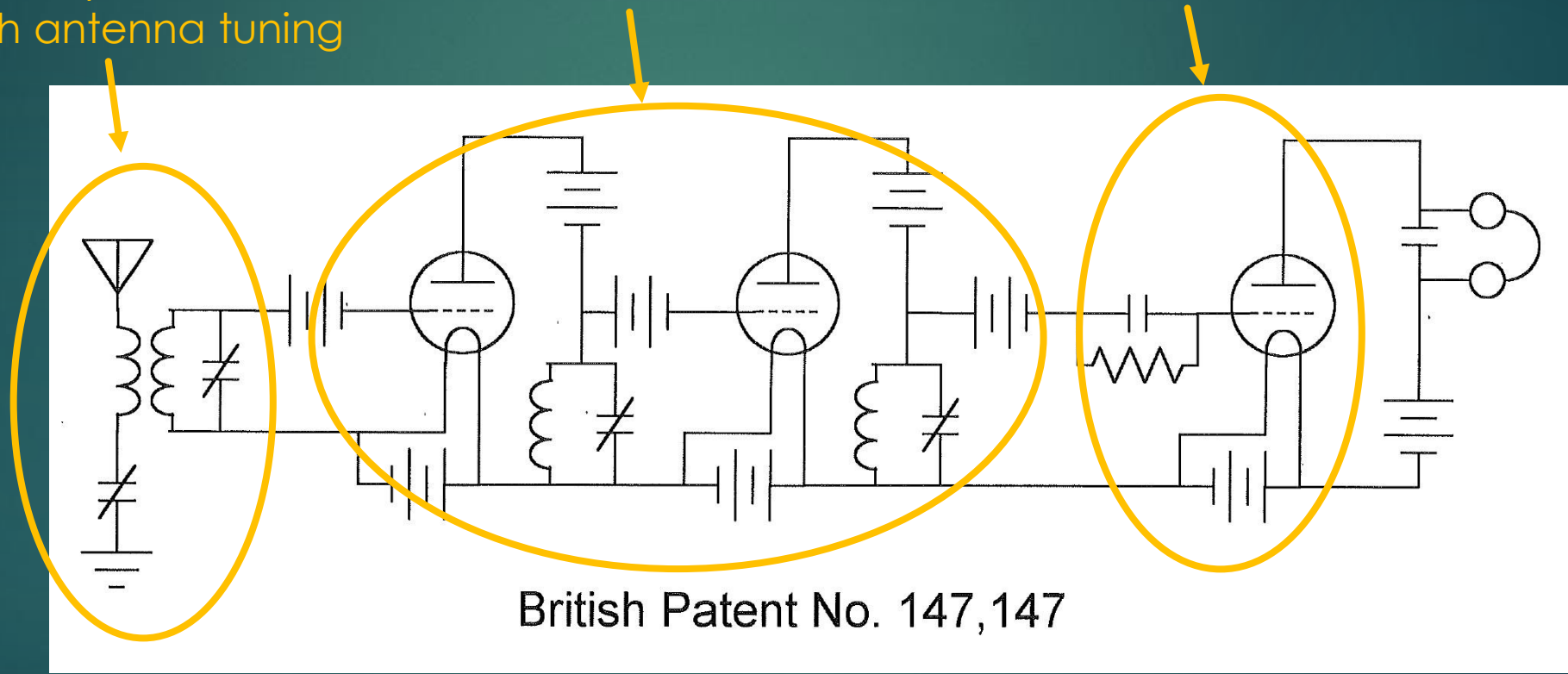

Multi-band Shortwave Receiver



Preselect Filters


Cascade LNA

Image Filters


JFET mixer

IF filter

Antenna Input

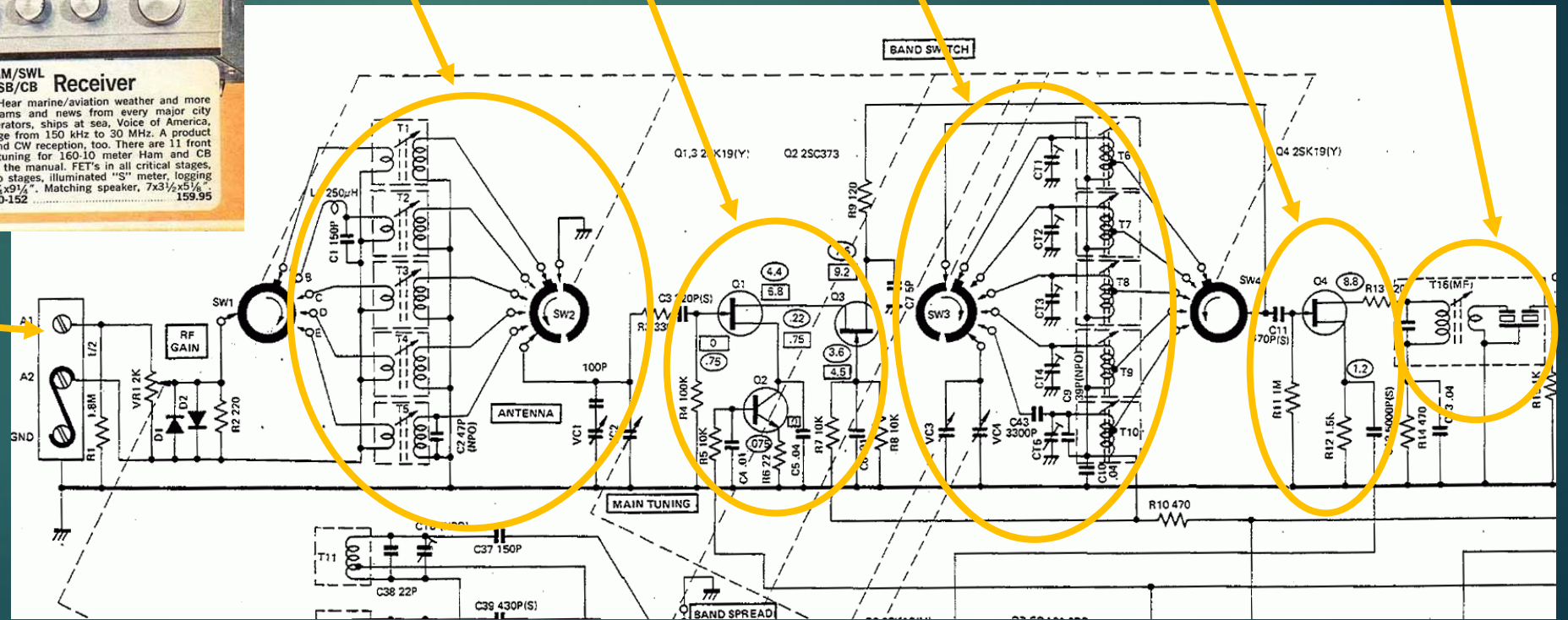





Multi-band VHF/UHF Radio

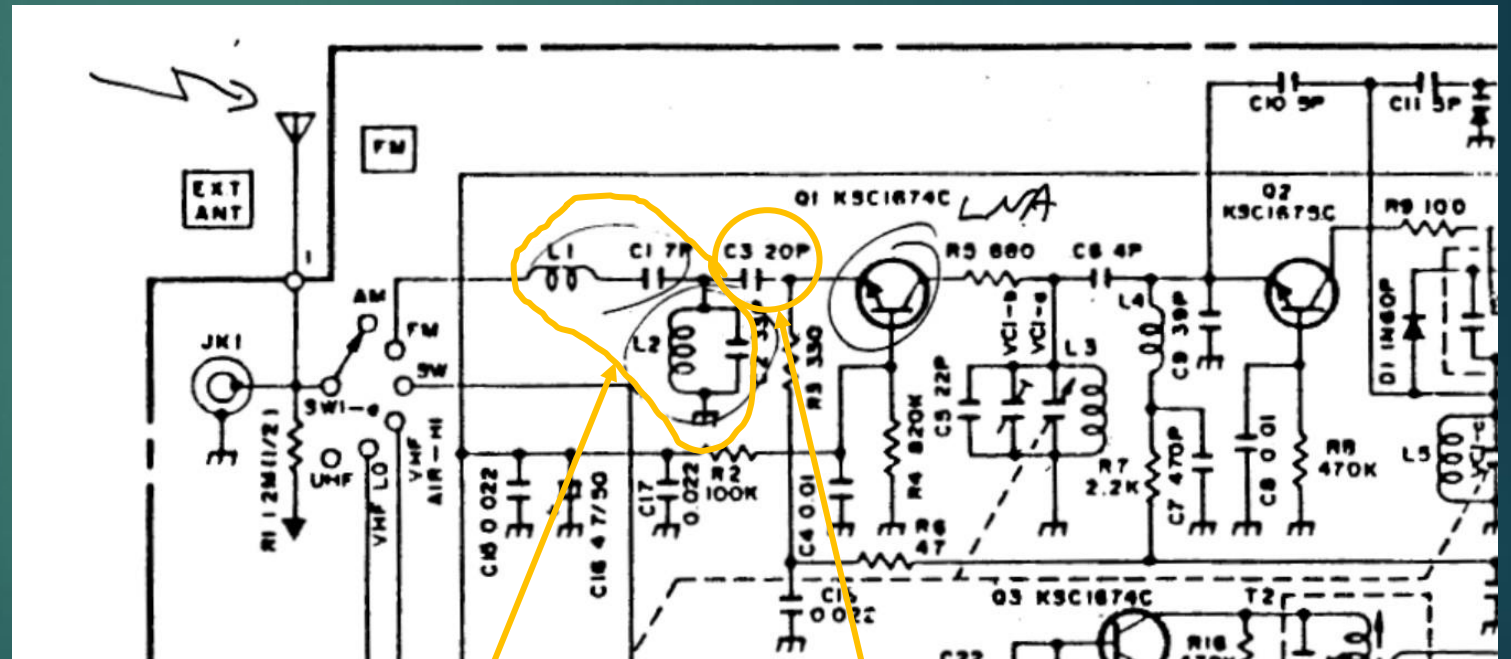

2-pole preselect BPF

$C3 = 20 \text{ pF} \Rightarrow -j 80 \text{ Ohms}$
So P/O matching – not just DC block

UHF Transceiver with Resonant TR Switch

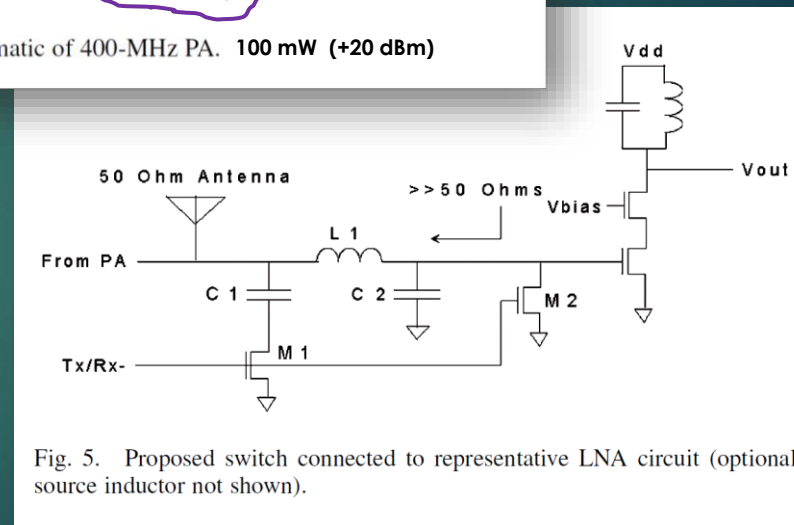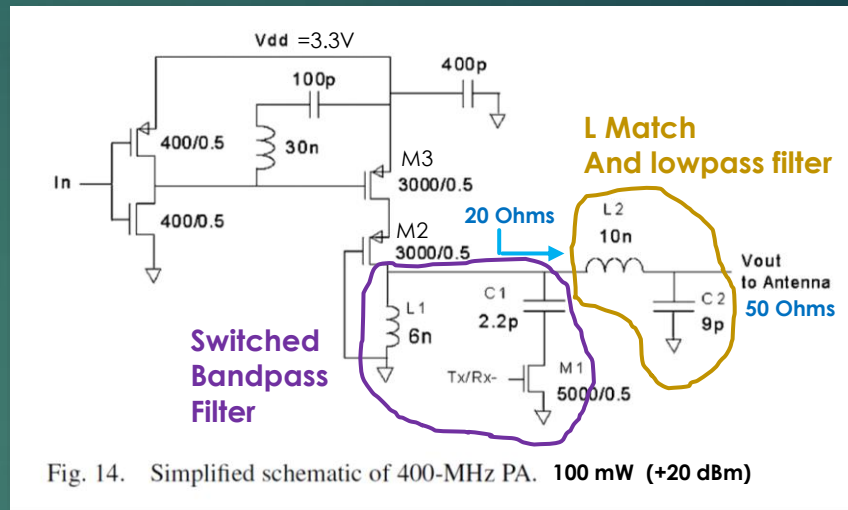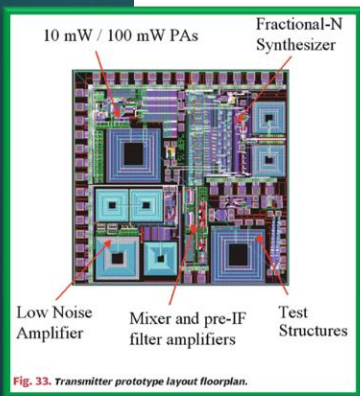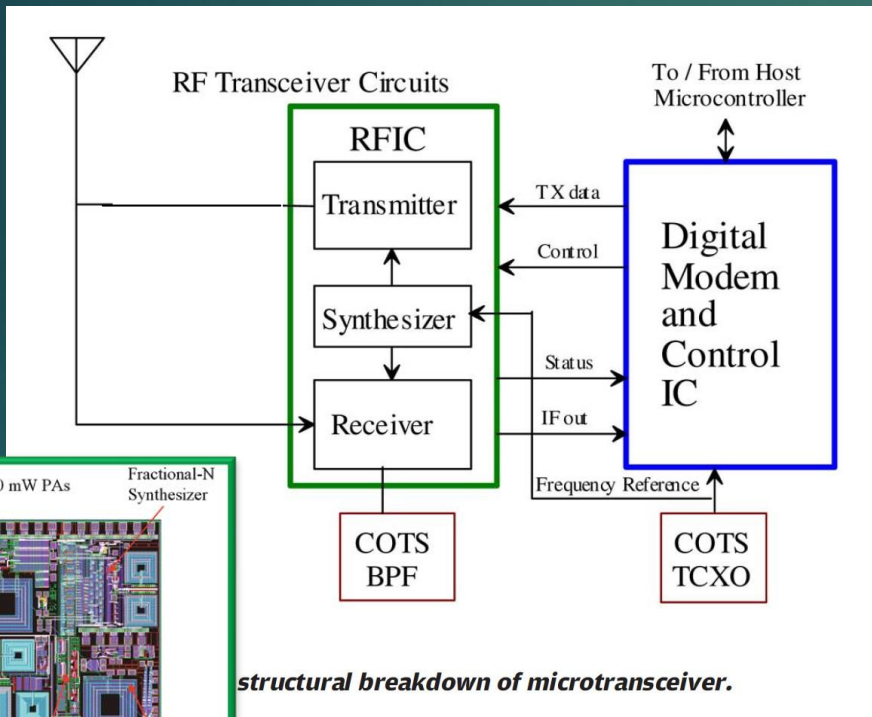

- "A resonant switch for LNA protection in watt-level CMOS transceivers", IEEE Transactions on microwave theory and techniques, 2005.
- "A microtransceiver for UHF proximity links including Mars surface-to-orbit applications", Proceedings of the IEEE, 2007.

Commercial Transceiver IC

Chipcon Products
from Texas Instruments

CC1000 is based on Chipcon's SmartRF[®] technology in 0.35 μm CMOS.



CC1000

Single Chip Very Low Power RF Transceiver

Applications

- Very low power UHF wireless data transmitters and receivers
- 315 / 433 / 868 and 915 MHz ISM/SRD band systems
- RKE – Two-way Remote Keyless Entry
- Home automation
- Wireless alarm and security systems
- AMR – Automatic Meter Reading
- Low power telemetry
- Game Controllers and advanced toys

Chipcon Products
from Texas Instruments

CC1000

5. Circuit Description

Item	315 MHz
C31	8.2 pF, 5%, C0G, 0402
C41	Not used
C42	4.7 pF, 5%, C0G, 0402
C171	18 pF, 5%, C0G, 0402
C181	18 pF, 5%, C0G, 0402
L32	39 nH, 5%, 0402 (Ceramic multilayer)
L41	22 nH, 5%, 0402 (Ceramic multilayer)

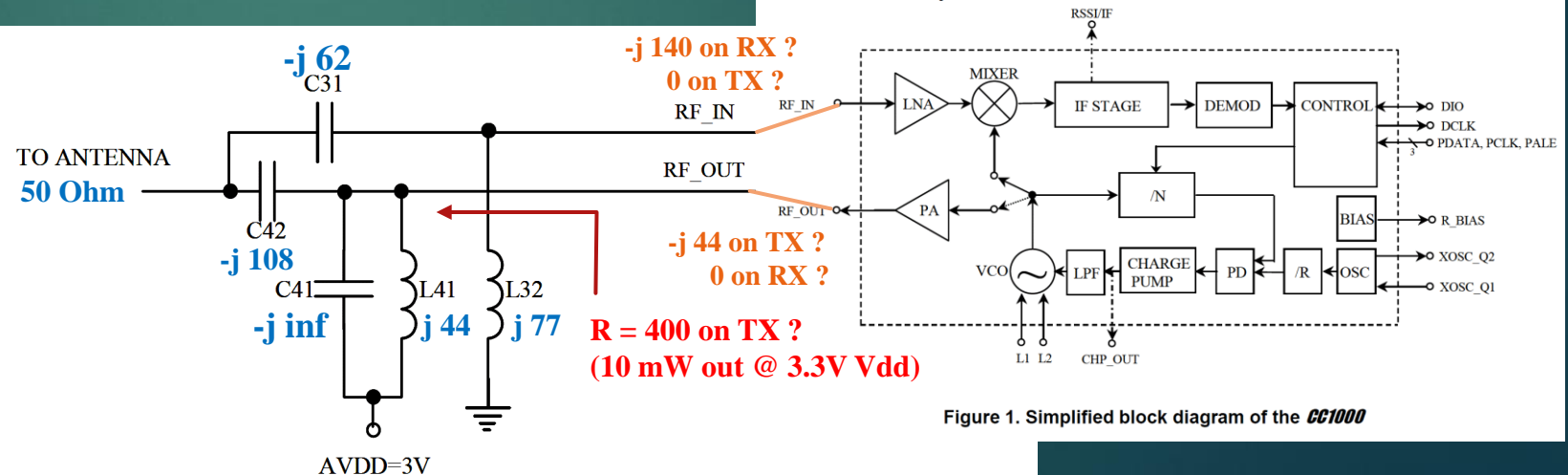




Figure 20. Input/output matching network

Figure 1. Simplified block diagram of the CC1000

Radio Design 101


Future Videos

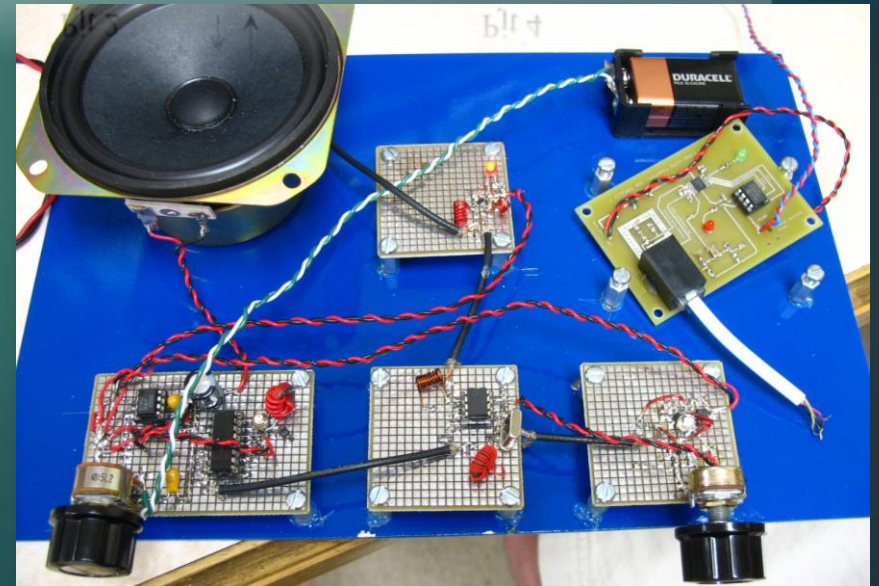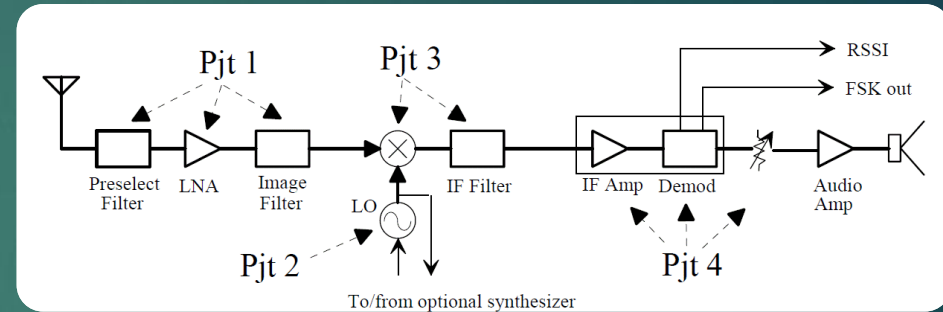- ✓
- ✓
- *Bandpass Filters and Q*
- *Impedance Matching*
- *Amplifiers*
- *Local Oscillators*
- *Mixers*
- *IF Amps / Demodulators*
- *Other (e.g. antennas/synthesizers)*




Additional Resources

American Radio Relay League (ARRL)

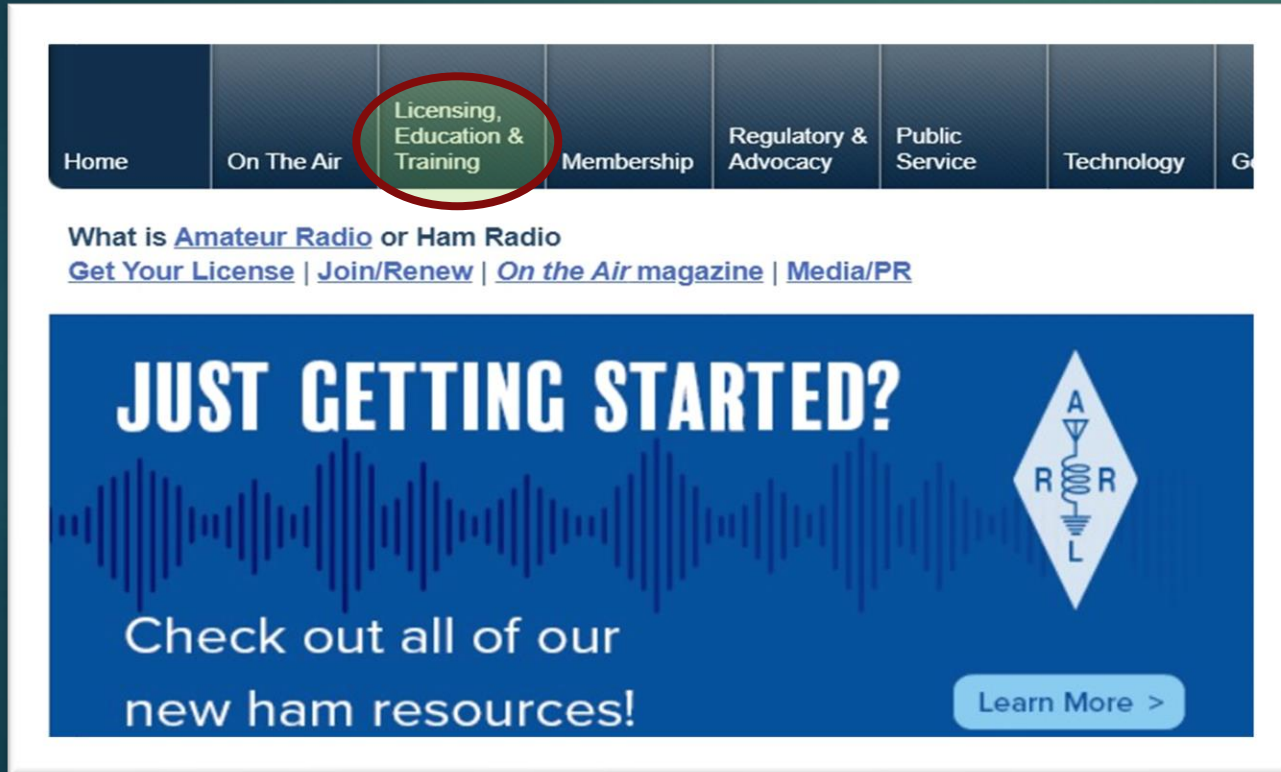

The screenshot shows the ARRL website's navigation menu with the following items: Home, On The Air, **Licensing, Education & Training** (circled in red), Membership, Regulatory & Advocacy, Public Service, Technology, and a partially visible 'G' button. Below the menu is a banner titled "What is Amateur Radio or Ham Radio" with links for "Get Your License", "Join/Renew", "On the Air magazine", and "Media/PR". A large blue banner below that says "JUST GETTING STARTED?" with a radio symbol and the text "Check out all of our new ham resources!" and a "Learn More >" button.

Book Recommended in Course

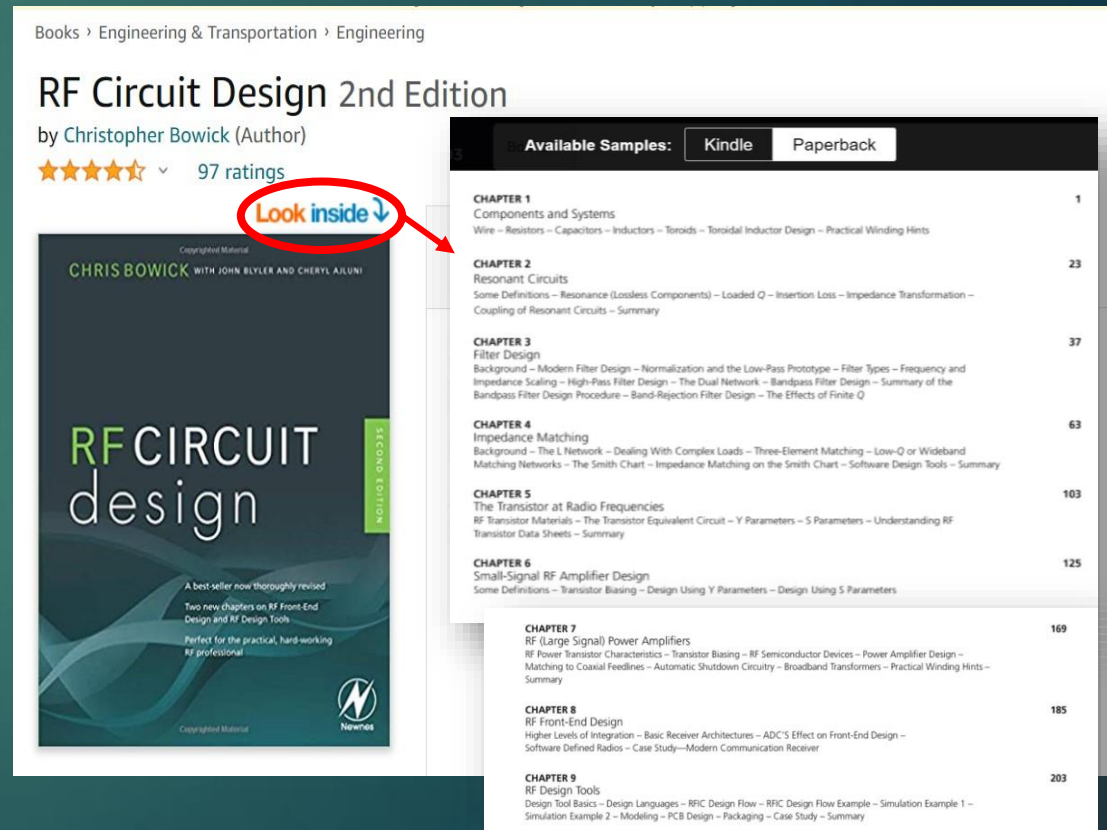

The screenshot shows the Amazon product page for "RF Circuit Design 2nd Edition" by Christopher Bowick. The page includes the book cover, a "Look inside" button (circled in red), and a table of contents. The table of contents lists chapters 1 through 9 with their respective page numbers.

Books > Engineering & Transportation > Engineering

RF Circuit Design 2nd Edition

by Christopher Bowick (Author)

★★★★★ 97 ratings

Available Samples: Kindle Paperback

Look inside ↓

Chapter	Page
CHAPTER 1 Components and Systems Wire – Resistors – Capacitors – Inductors – Toroids – Toroidal Inductor Design – Practical Winding Hints	1
CHAPTER 2 Resonant Circuits Some Definitions – Resonance (Lossless Components) – Loaded Q – Insertion Loss – Impedance Transformation – Coupling of Resonant Circuits – Summary	23
CHAPTER 3 Filter Design Background – Modern Filter Design – Normalization and the Low-Pass Prototype – Filter Types – Frequency and Impedance Scaling – High-Pass Filter Design – The Dual Network – Bandpass Filter Design – Summary of the Bandpass Filter Design Procedure – Band-Rejection Filter Design – The Effects of Finite Q	37
CHAPTER 4 Impedance Matching Background – The L Network – Dealing With Complex Loads – Three-Element Matching – Low-Q or Wideband Matching Networks – The Smith Chart – Impedance Matching on the Smith Chart – Software Design Tools – Summary	63
CHAPTER 5 The Transistor at Radio Frequencies RF Transistor Materials – The Transistor Equivalent Circuit – Y Parameters – S Parameters – Understanding RF Transistor Data Sheets – Summary	103
CHAPTER 6 Small-Signal RF Amplifier Design Some Definitions – Transistor Biasing – Design Using Y Parameters – Design Using S Parameters	125
CHAPTER 7 RF (Large Signal) Power Amplifiers RF Power Transistor Characteristics – Transistor Biasing – RF Semiconductor Devices – Power Amplifier Design – Matching to Coaxial Feedlines – Automatic Shutdown Circuitry – Broadband Transformers – Practical Winding Hints – Summary	169
CHAPTER 8 RF Front-End Design Higher Levels of Integration – Basic Receiver Architectures – ADC'S Effect on Front-End Design – Software Defined Radios – Case Study—Modern Communication Receiver	185
CHAPTER 9 RF Design Tools Design Tool Basics – Design Languages – RFIC Design Flow – RFIC Design Flow Example – Simulation Example 1 – Simulation Example 2 – Modeling – PCB Design – Packaging – Case Study – Summary	203



*Thanks For
Watching !*