

# Radio Design 101





## Episode 3 -- RF Amplifiers

Slides downloaded from: <https://ecefiles.org/rf-design/>

Companion video at: <https://www.youtube.com/watch?v=UUIqW-vSq9M>

This material is **provided by ecefiles.org for educational use only.**




This episode presents a relatively complete discussion of amplifier circuits, including the electronic devices used (tubes/valves, transistors (JFET, BJT, MOSFETs)). It discusses how they're biased, and how the AC behavior is analyzed and understood in terms of gain and input/output impedances. In keeping with previous videos in this series, the focus is on radio-frequency (RF) amps, but much of the theory applies to audio amplifiers as well. A few full-circuit schematics of radios are shown for motivation, and to illustrate variations found in real-world designs.

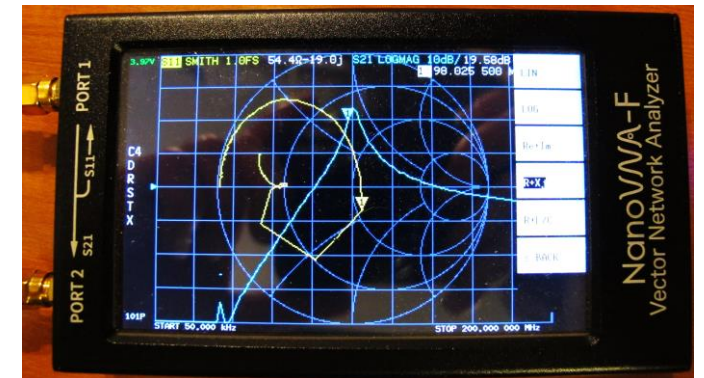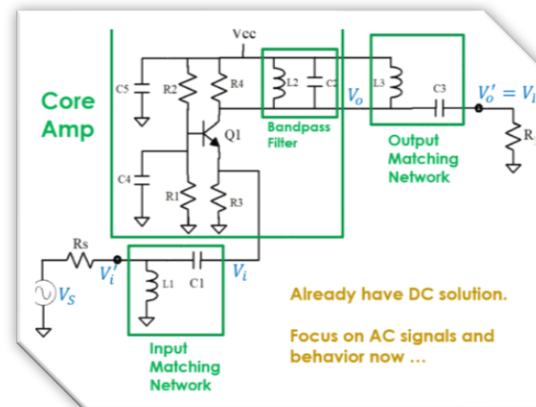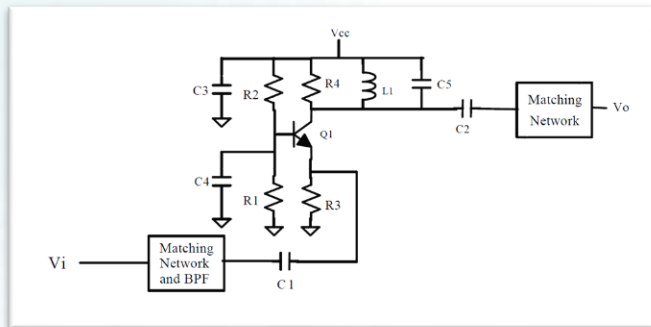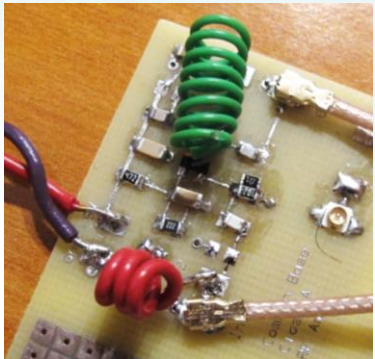


# Radio Design 101

## Episode 3

# RF Amplifiers

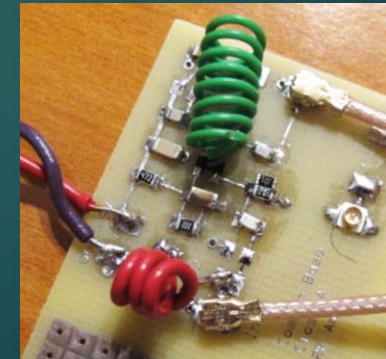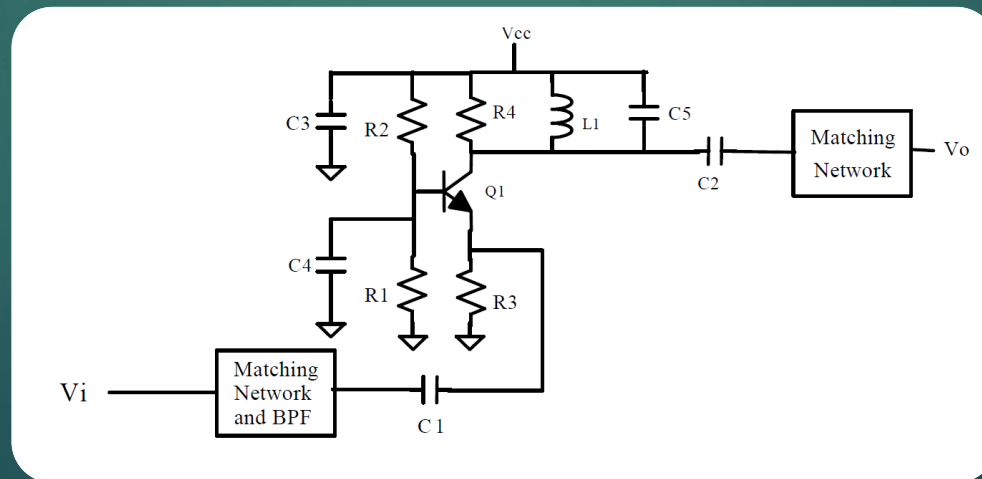
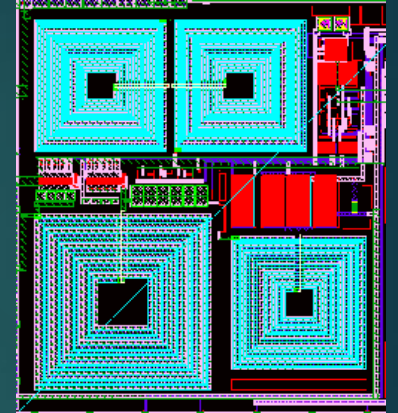


# SB-102 HF SSB Transceiver

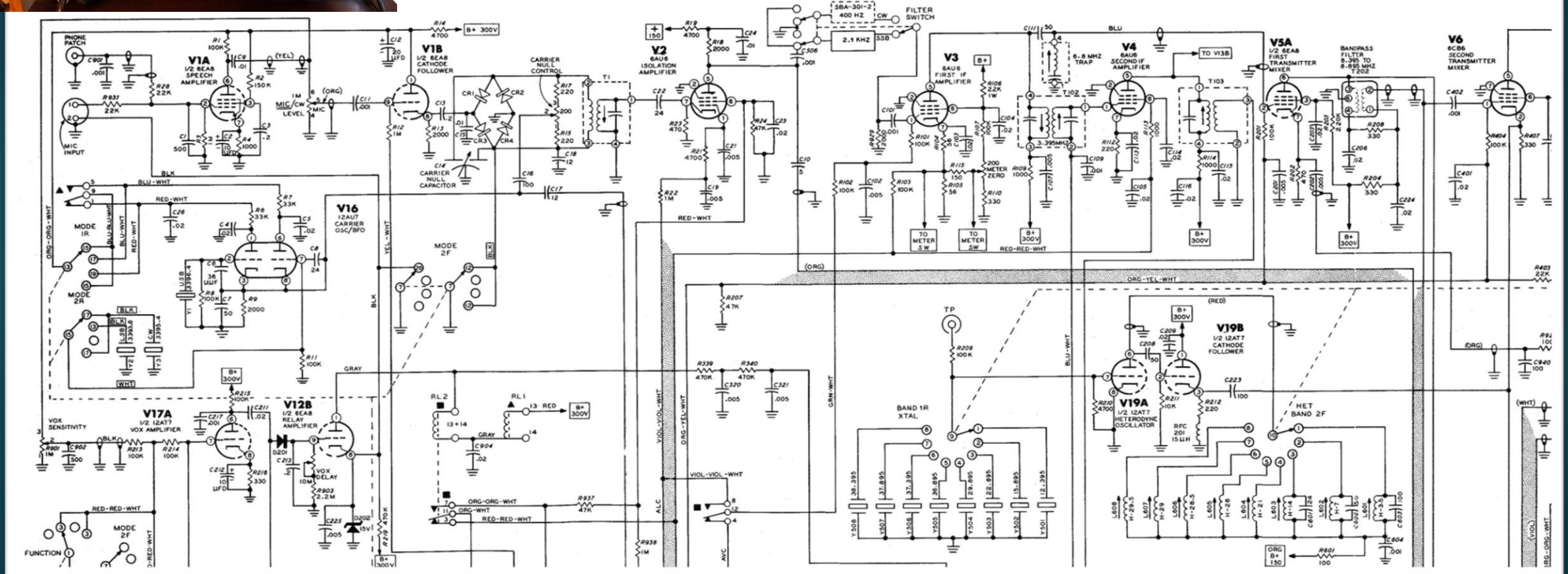



# SX-535 VHF FM Receiver

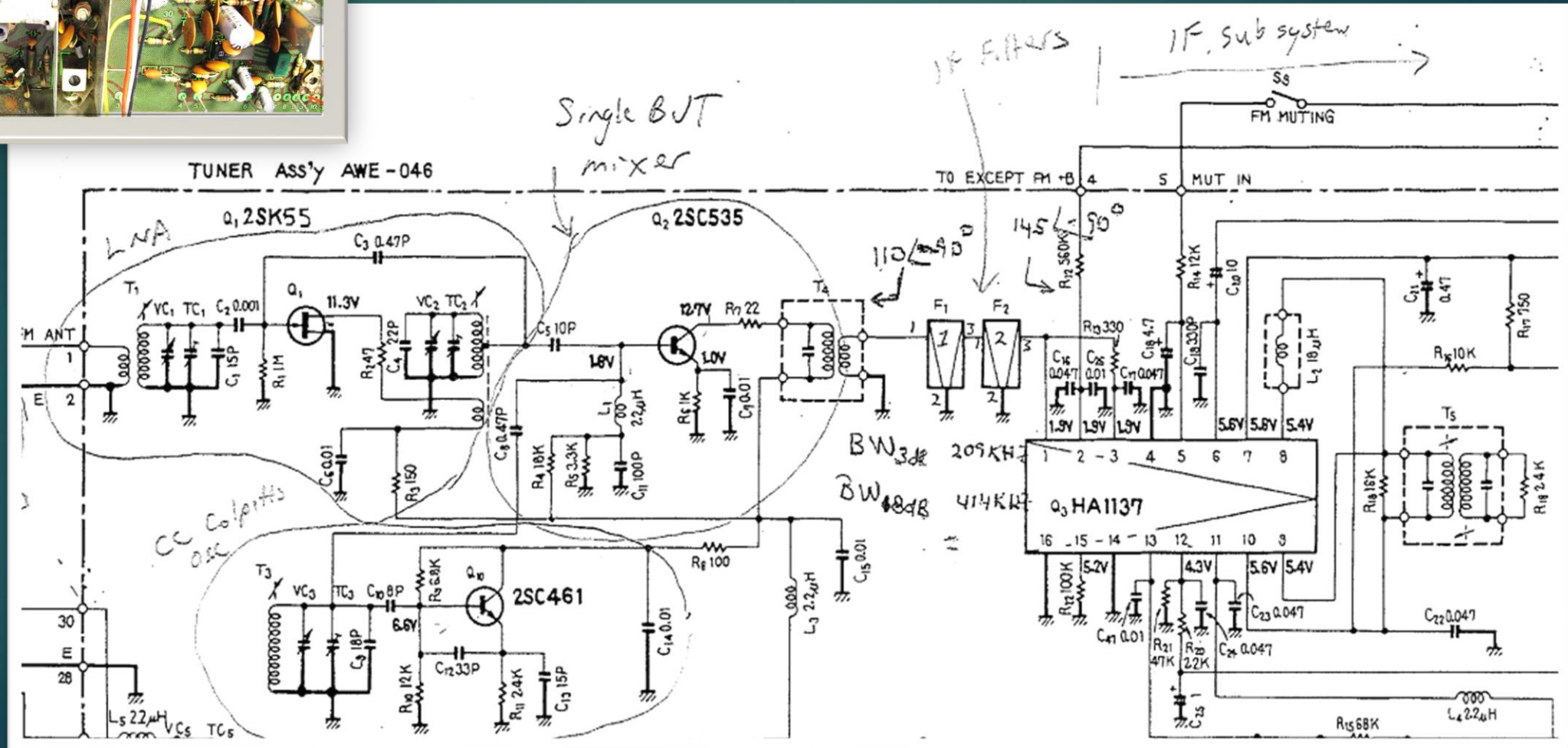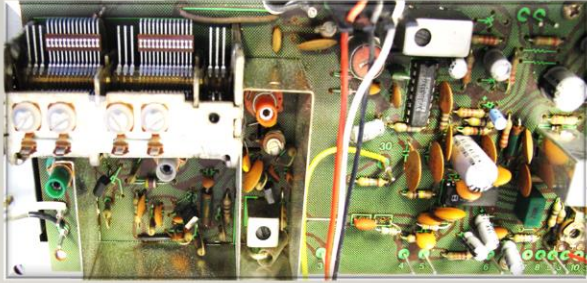

# Single-Chip UHF QPSK Transceiver

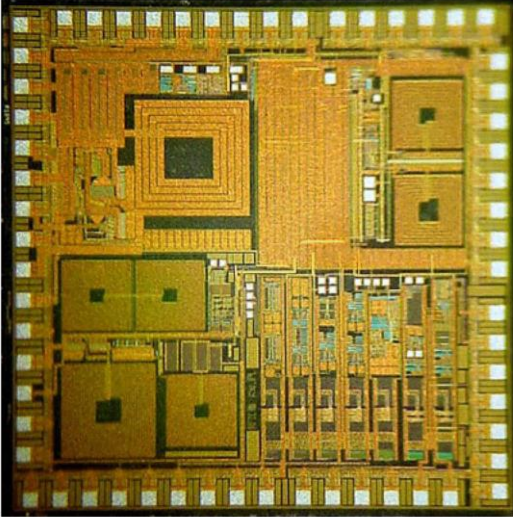


Fig. 39. Die photo of fully integrated single-chip 100-mW transceiver.

Vol. 95, No. 10, October 2007 | PROCEEDINGS OF THE IEEE 2041

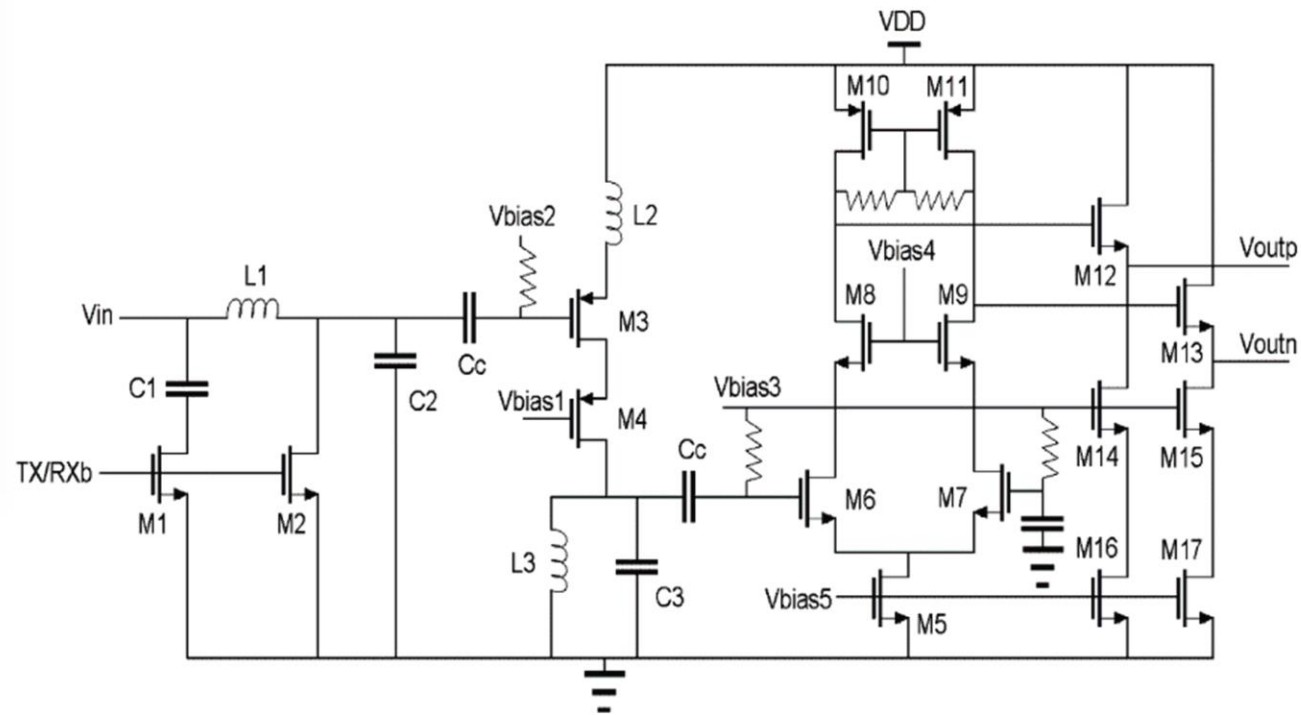


Fig. 23. Schematic diagram of LNA with integrated T/R switch circuits.




2034 PROCEEDINGS OF THE IEEE | Vol. 95, No. 10, October 2007

# Topic Outline



- *Triode Devices*
- *DC Biasing*
- *AC Gain and I/O Impedances*
- *Amplifier Configurations*
- *High Frequency Limitations*
- *Data Sheets and Example Circuits*

# Triode Devices

Vacuum Tube  
(or Valve)

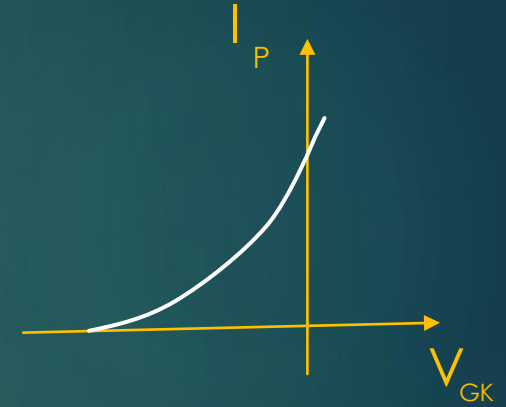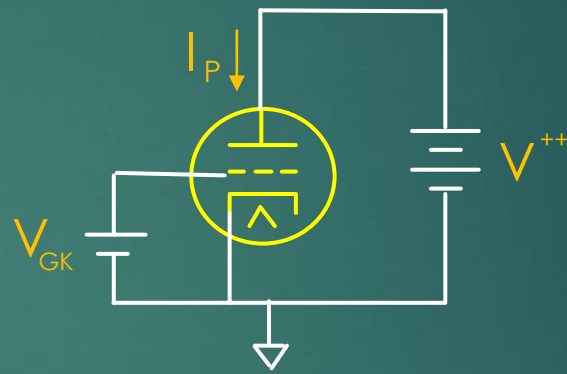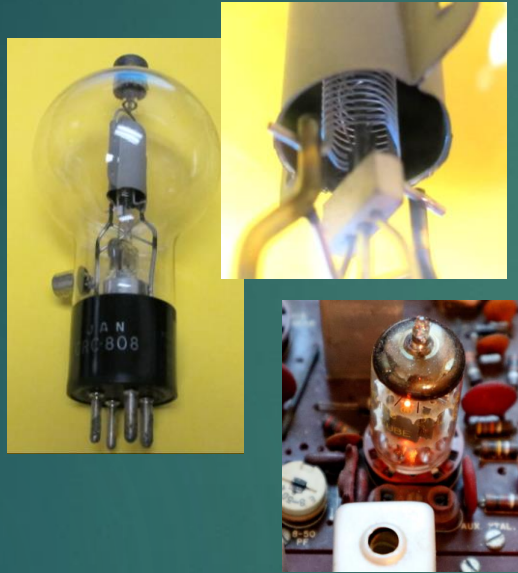




Junction Field  
Effect Transistor

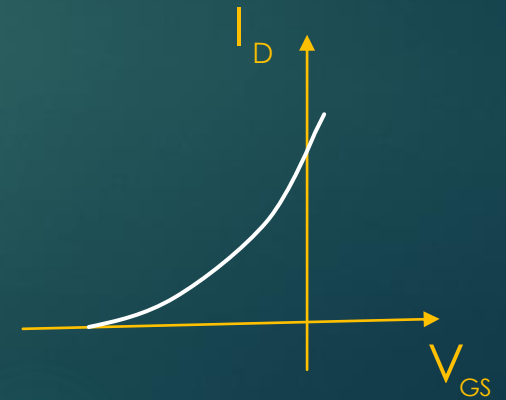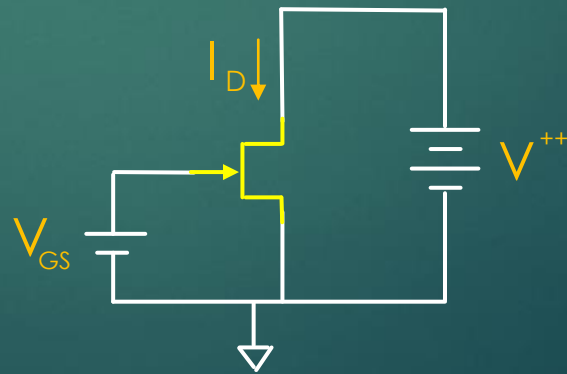






# Triode Devices

## Bipolar Junction Transistor

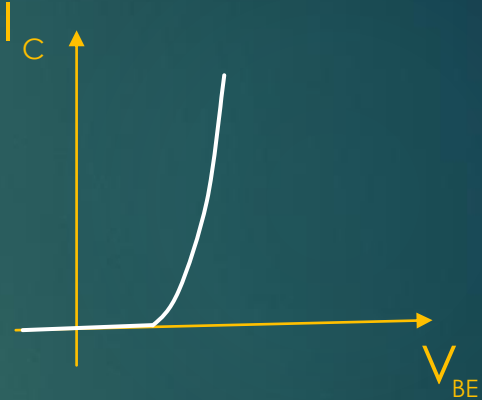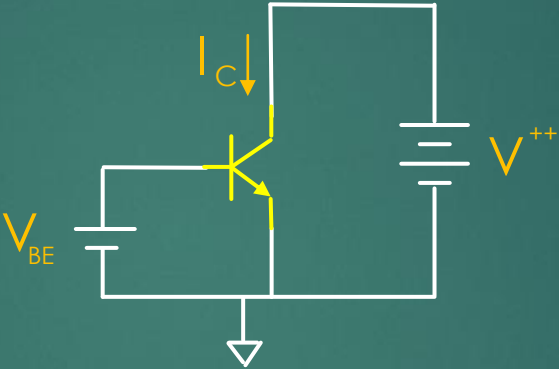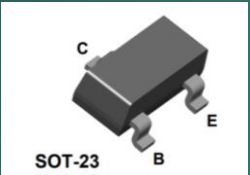


## MOSFET Transistors

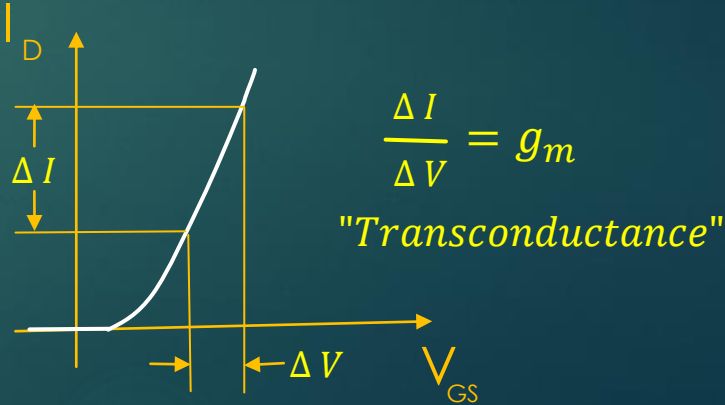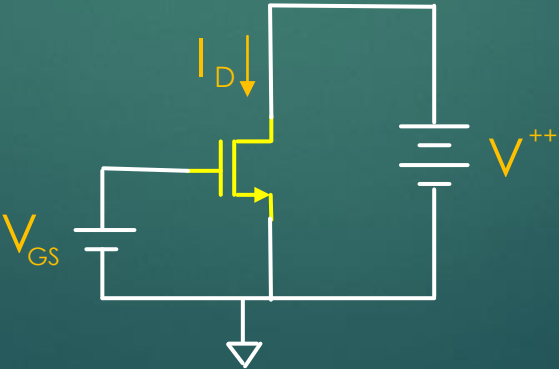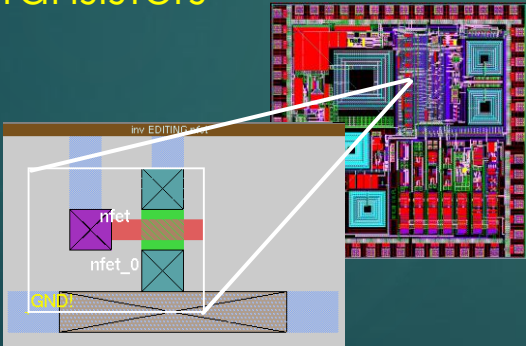




# Basic Amplifier Concept

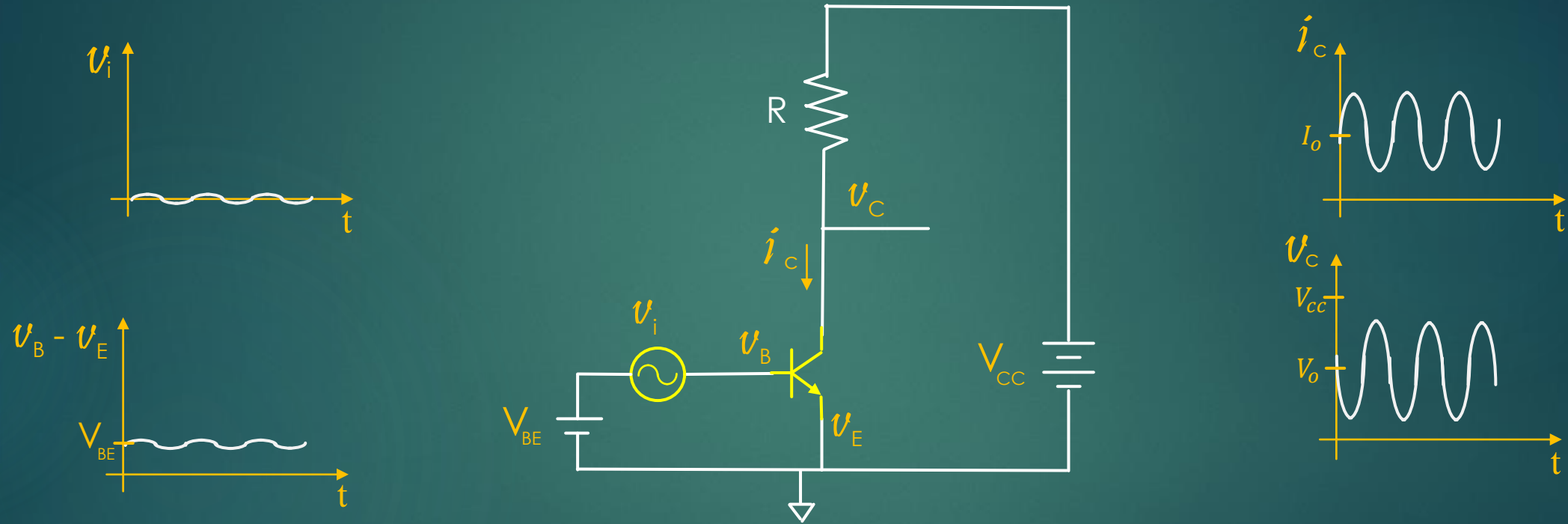

$$A_v = -g_m R$$

"Transconductance"

# Tube-based RF Amplifier

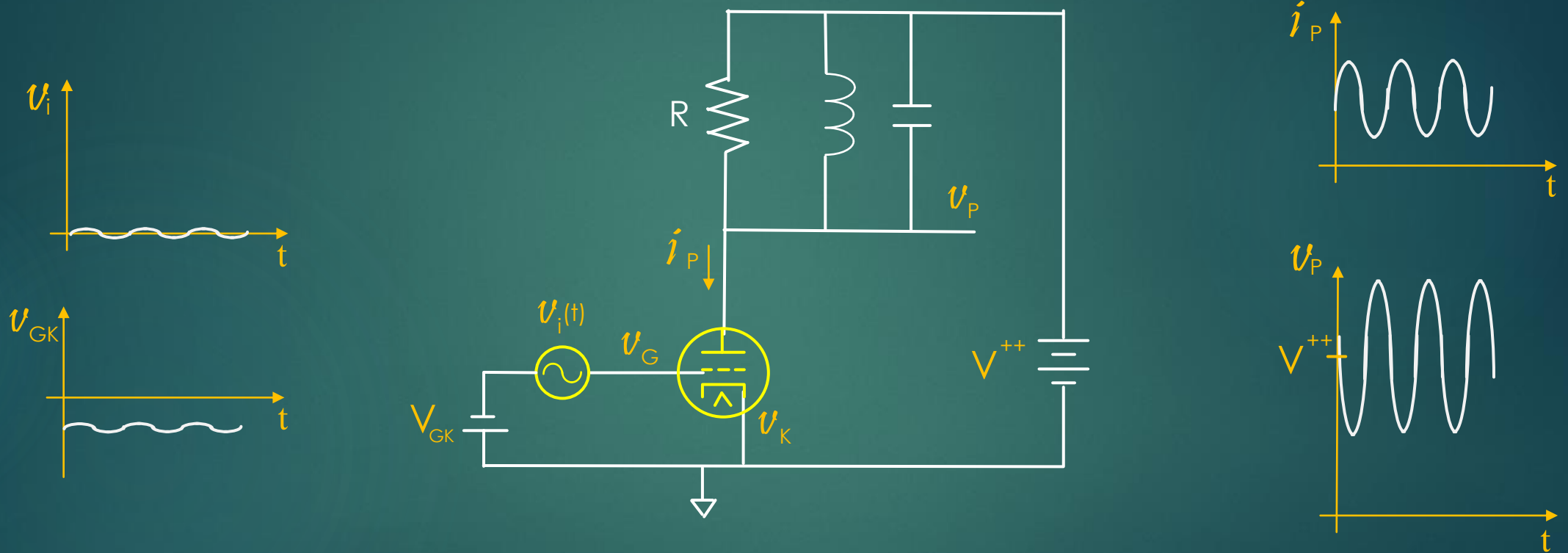

$$A_v = -g_m R \quad @ f_o$$

# Transconductance Values



## DOUBLE TRIODE

MINIATURE TYPE

UNIPOTENTIAL CATHODES


HEATER

SERIES	PARALLEL
12.6 VOLTS 150 MA.	6.3 VOLTS 300 MA.


AC OR DC

FOR 12.6 VOLT OPERATION APPLY HEATER VOLTAGE BETWEEN PINS #4 AND #5. FOR 6.3 VOLT OPERATION APPLY HEATER VOLTAGE BETWEEN PIN #9 AND PINS #4 AND #5 CONNECTED TOGETHER.

ANY MOUNTING POSITION

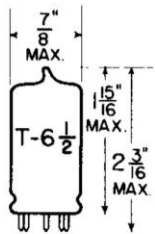

GLASS BULB

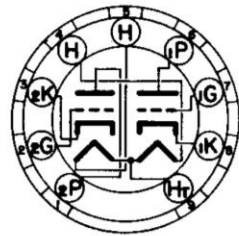

BOTTOM VIEW  
SMALL BUTTON  
9 PIN BASE

THE 12AX7 COMBINES TWO COMPLETELY INDEPENDENT HIGH-MU TRIODES IN THE SMALL 9 PIN BUTTON CONSTRUCTION. IT IS ADAPTABLE TO APPLICATIONS WHERE HIGH VOLTAGE GAIN AND LOW HEATER POWER ARE THE IMPORTANT CONSIDERATION, SUCH AS VOLTAGE AMPLIFIERS, PHASE INVERTERS AND MULTIVIBRATORS. THE CEN-

DISSIPATION

1

WATT

## TYPICAL OPERATING CONDITIONS AND CHARACTERISTICS

### CLASS A<sub>1</sub> AMPLIFIER - EACH TRIODE UNIT

	12.6	6.3	12.6	6.3	
HEATER VOLTAGE	12.6	6.3	12.6	6.3	VOLTS
HEATER CURRENT	150	300	150	300	MA.
PLATE VOLTAGE	100		250		VOLTS
GRID VOLTAGE	-1		-2		VOLTS
PLATE CURRENT	0.2		1.2		MA.
PLATE RESISTANCE	80 000		62 500		OHMS
TRANSCONDUCTANCE	1 250		1 600		μMHOS
AMPLIFICATION FACTOR	100		100		



*SIMILAR TYPE REFERENCE: Characteristics somewhat similar to types 6SL7GT and 12SL7GT.*

COPYRIGHT 1947 BY TUNG-SOL LAMP WORKS INC. ELECTRONIC TUBE DIVISION NEWARK, NEW JERSEY, U. S. A.

$$A_v = -g_m R = -(1250 \times 10^{-6})(80,000) = -100$$



# BJT Transconductance

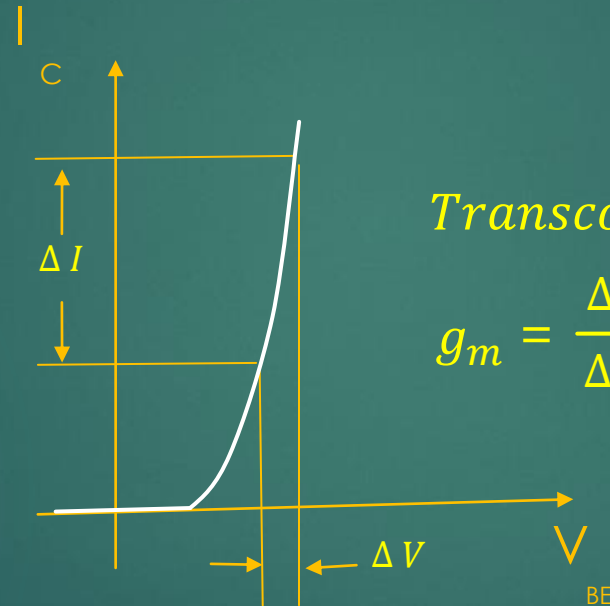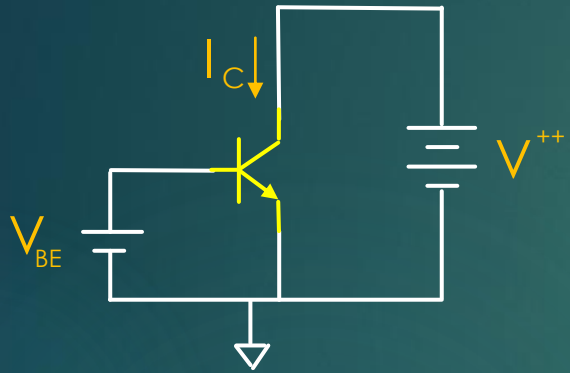

*Transconductance*

$$g_m = \frac{\Delta I}{\Delta V}$$

*$g_m$  varies with bias current*

For a BJT device:

$$g_m = \frac{I_c}{nV_T} \approx \frac{I_c}{0.04}$$

# Amplifier Design Basics are Device-Independent

(but bias circuits and details vary)

## Tube Amp



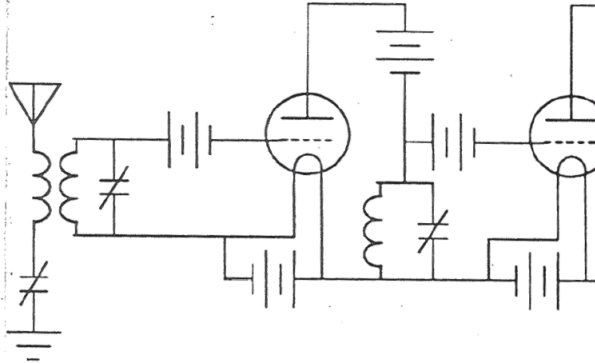
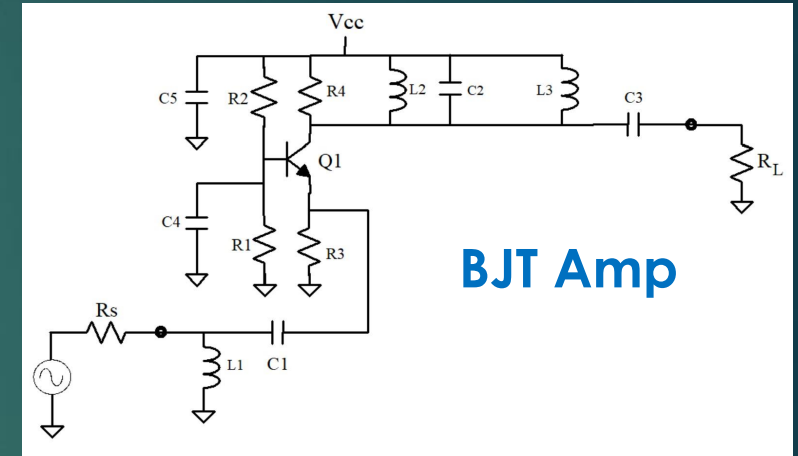


Figure 4.2: Early tuned-RF receiver

## JFET Amp

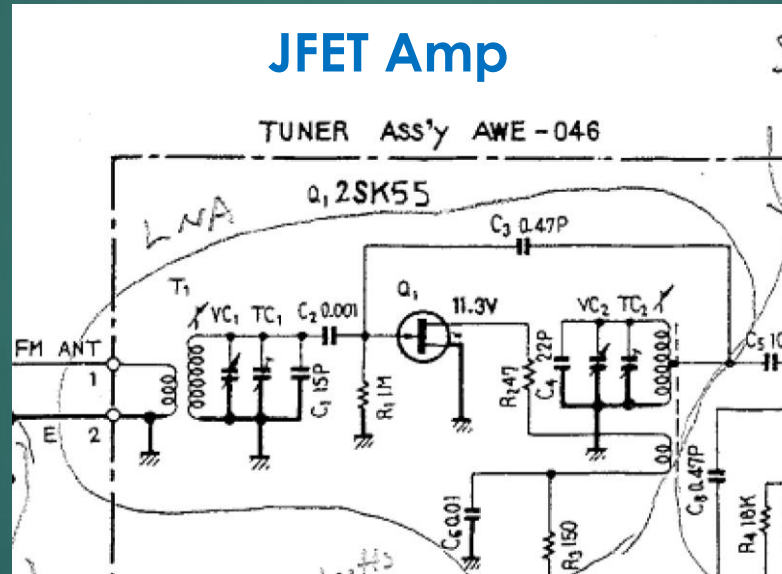

## BJT Amp

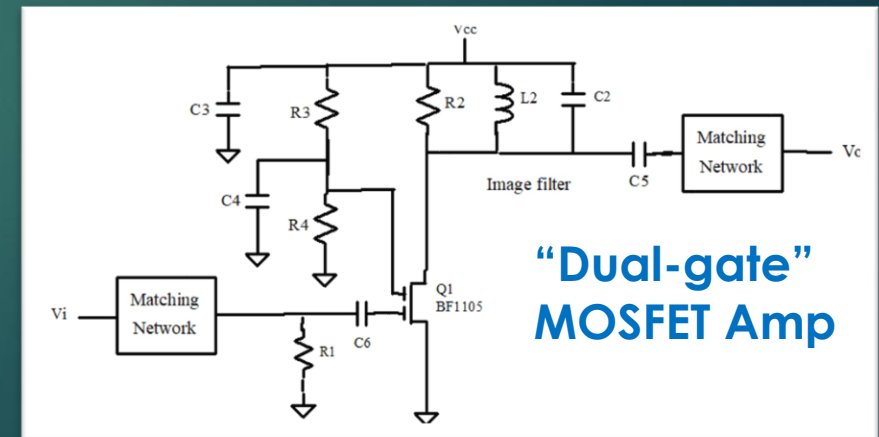


## "Dual-gate" MOSFET Amp

# Topic Outline

- *Triode Devices*
- *DC Biasing*
- *AC Gain and I/O Impedances*
- *Amplifier Configurations*
- *High Frequency Limitations*
- *Data Sheets and Example Circuits*



# Recall Amplifier Concept

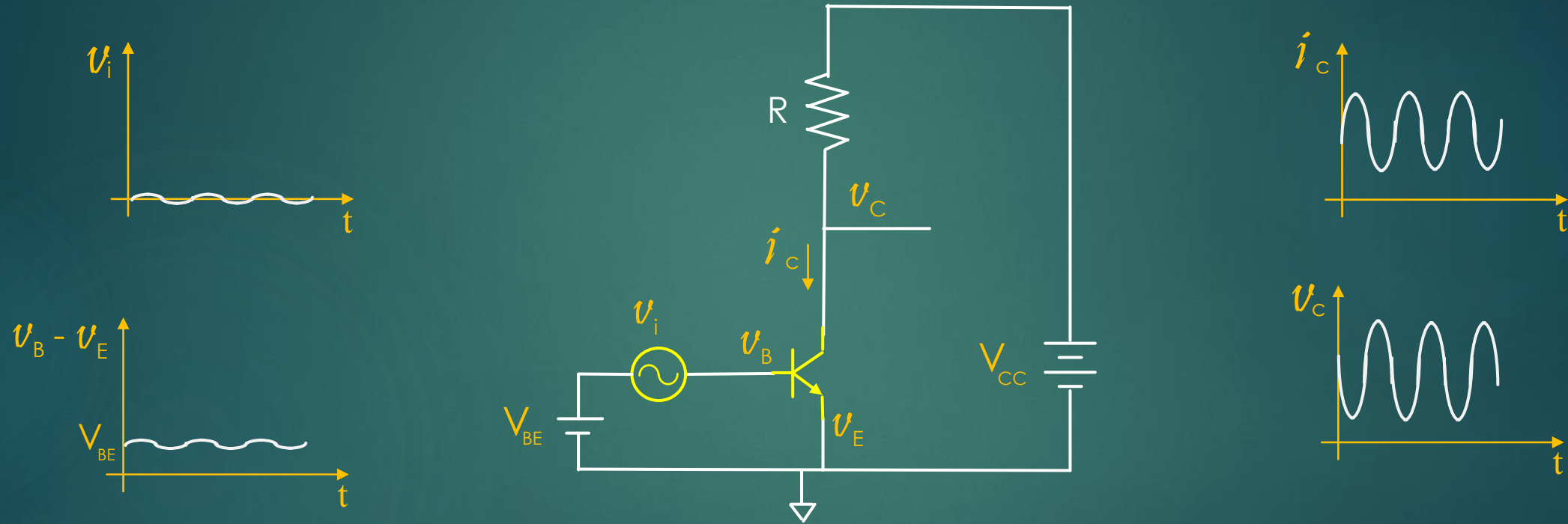


Requires multiple batteries ☹

Bias current is not stable in this circuit ☹

Input source isn't ground referenced ☹


# Practical BJT Biasing Circuit

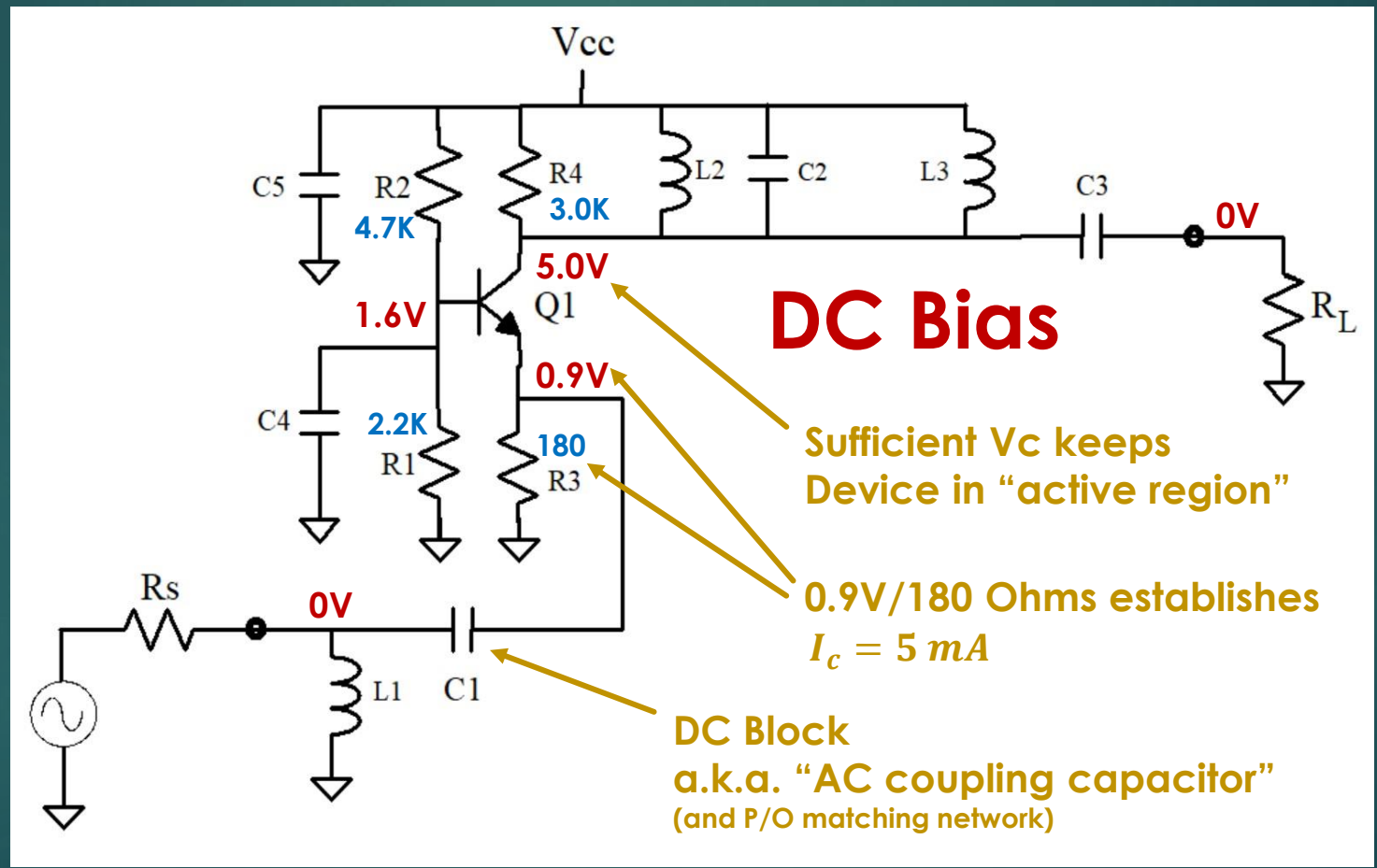

# BJT Bias Circuit Analysis
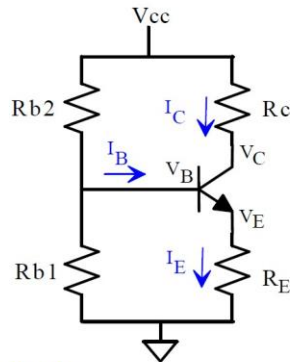
## DC Biasing of Class A BJT Amplifiers

A traditional "4-resistor bias circuit" is shown below.



### Bias circuit analysis

Assume the transistor is operating in the active region, and that Beta or  $h_{FE}$  is "large". Then,  $I_B$  will be approximately zero (relative to the current in  $R_{b1}$ ,  $R_{b2}$ ), and we can use the simple voltage divider formula at the base to get,

$$V_B \approx V_{cc} \frac{R_{b1}}{R_{b1} + R_{b2}}$$

If the transistor is in the active region, the BE junction is forward biased and  $V_{BE_{on}} \approx 0.7V$ . Hence,

$$V_E \approx V_B - 0.7$$

The emitter current is then,

$$I_E = \frac{V_E}{R_E}$$

and the collector current is,

$$I_C \approx I_E$$

Finally, the collector voltage can be found from the IR drop in  $R_c$  as,

$$V_C = V_{cc} - I_C R_C *$$

Note that these equations are reasonably independent of the transistor gain  $h_{FE}$ , provided the current through  $R_{b1}$  and  $R_{b2}$  is  $\gg I_B$ . Hence, the bias voltages and currents should not change significantly with changes in  $h_{FE}$

Note also that the bias current and DC voltages will be relatively insensitive to small variations in  $V_{BE}$  caused by temperature or manufacturing, provided that  $V_E$  is greater than about 0.5 to 1 volt.

\* For an RF amplifier with LC across  $R_c$ ,  $V_c$  will be equal to  $V_{cc}$



# BJT Bias Circuit Design

## *Bias Circuit Design*

The following procedure is based on the simplified analysis on the previous page.

- Pick  $V_E > 0.5$  V to swamp  $V_{BE}$  variations due to manufacturing and temperature changes. (But not so high that it significantly degrades the output signal swing you can achieve.)
- Pick  $R_E$  to give the desired  $I_E$ . (Hence the desired  $I_C$  since the two are approximately equal).
- Find  $V_B$  from  $V_B \approx V_E + 0.7$ .
- Find  $I_{Bmax}$  from  $I_C$  and the ***minimum*** transistor  $h_{FE}$  value in the datasheet.
- Find  $R_{b1}$  and  $R_{b2}$  to produce the value of  $V_B$  above, subject to the constraint that the current in  $R_{b1}$ ,  $R_{b2}$  is much greater than  $I_{Bmax}$ . (Typically 5 to 10 times  $I_{Bmax}$  is used, but this could be relaxed some since we're already using the worst-case  $I_B$ .)

- Fine-tune  $R_{b1}$  and  $R_{b2}$  if desired to account for the (small) lowering of  $V_B$  due to the non-zero base current expected (use the *typical*  $h_{FE}$  here to provide good “design-centering”).
- Find  $R_c$  to produce a desired  $V_C$  and to satisfy other design constraints such as the amplifier gain.
- Convert resistors to available values.
- Check to be sure the transistor is operating comfortably in the active region !!






\* *NOTE: For small current circuits, we can stop here, but in general you should consider power dissipations in the transistor and resistors and be sure you don't approach or exceed the limits...*

\* For an RF amplifier with LC across  $R_c$ ,  $V_c$  can reach  $2 \times V_{cc}$ , so need to check  $V_{CE}$  breakdown spec also

# Some Additional Bias Circuits

## Class C Power Amplifier



Typical Circuit

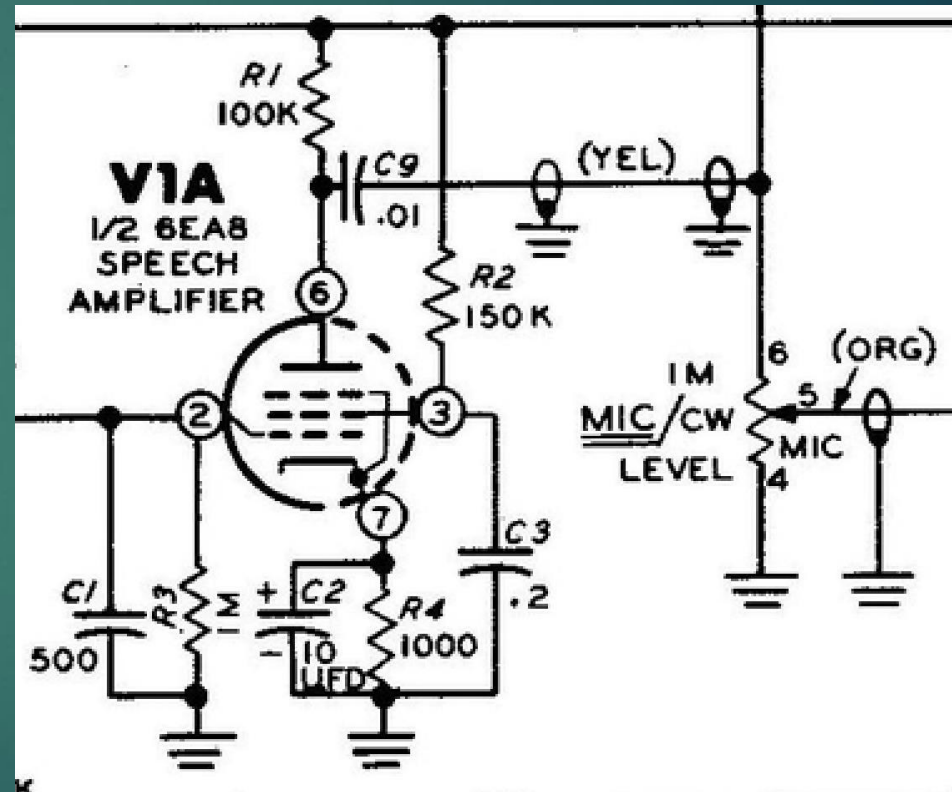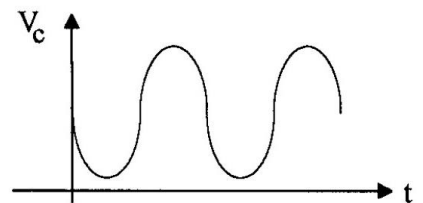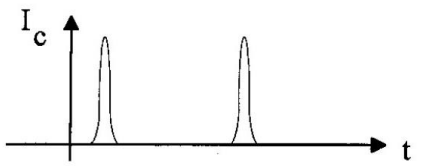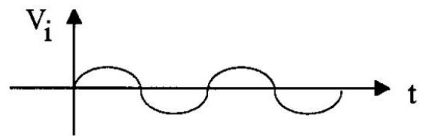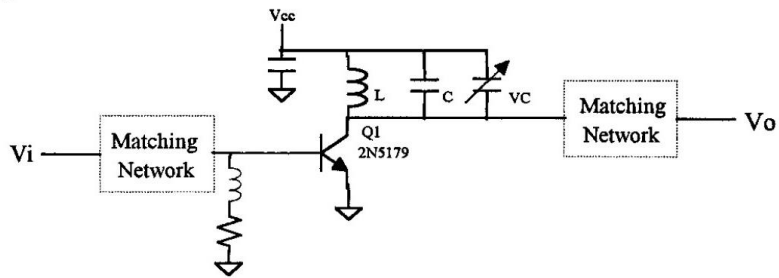



# Topic Outline

- *Triode Devices*
- *DC Biasing*
- *AC Gain and I/O Impedances*
- *Amplifier Configurations*
- *High Frequency Limitations*
- *Data Sheets and Example Circuits*

# Full Circuit Behavior

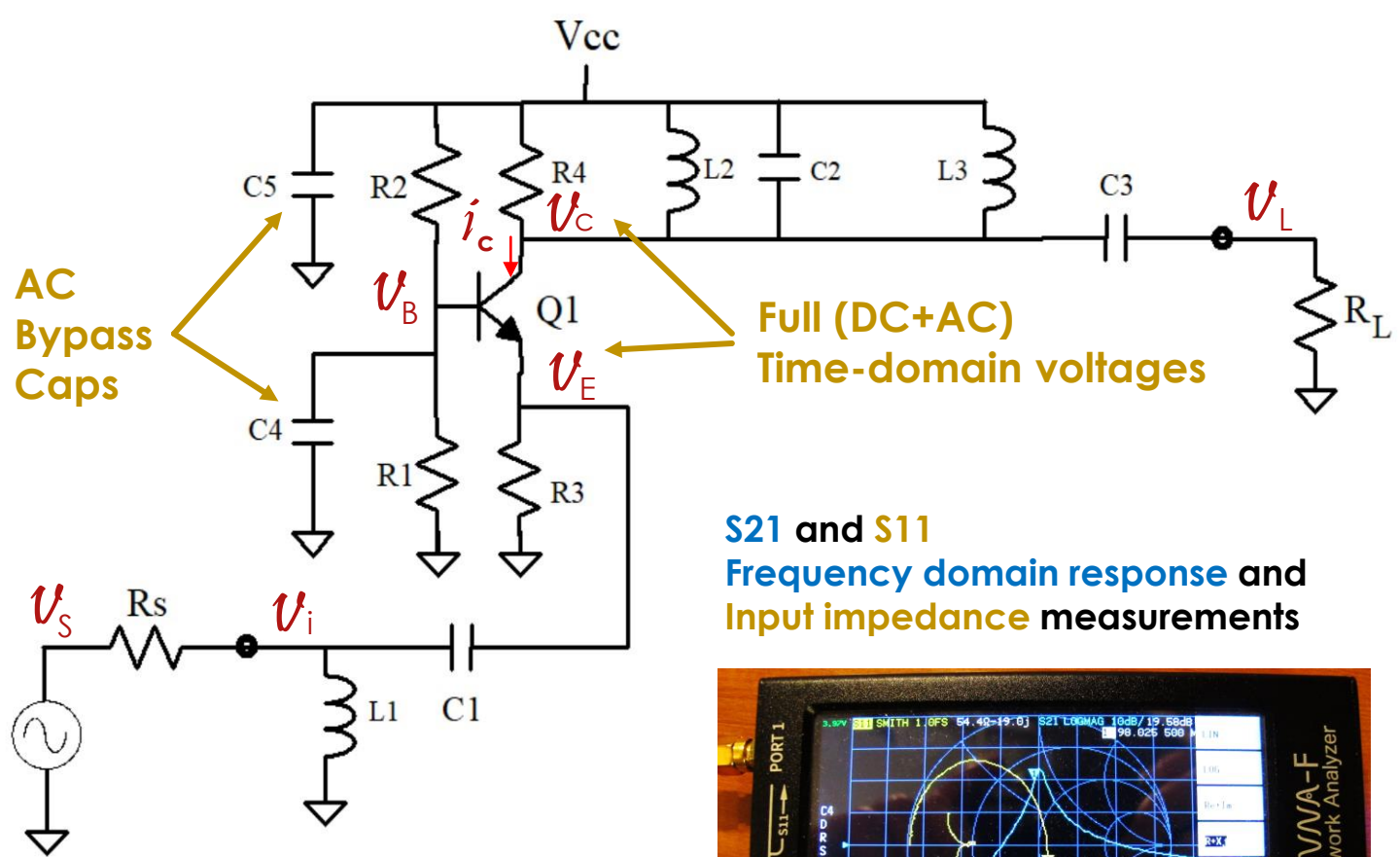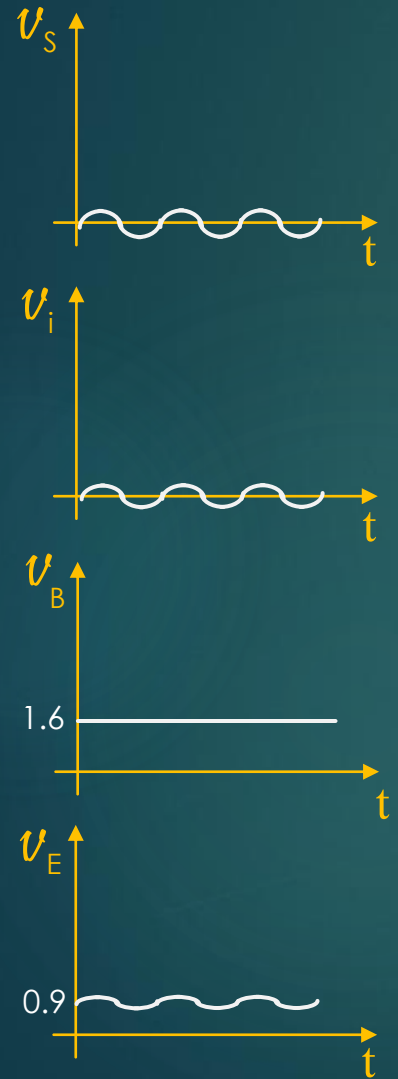


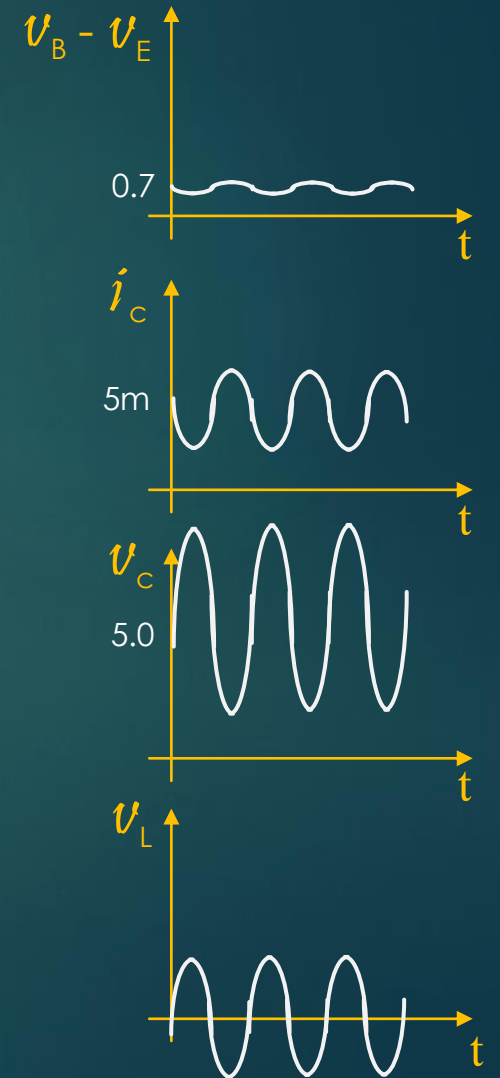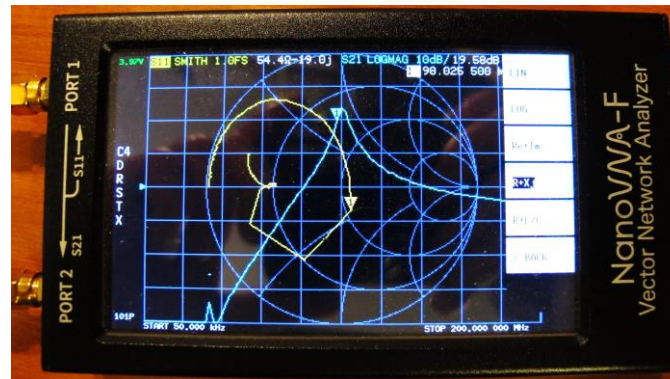**S21 and S11**  
**Frequency domain response and**  
**Input impedance measurements**







# Circuit Understanding

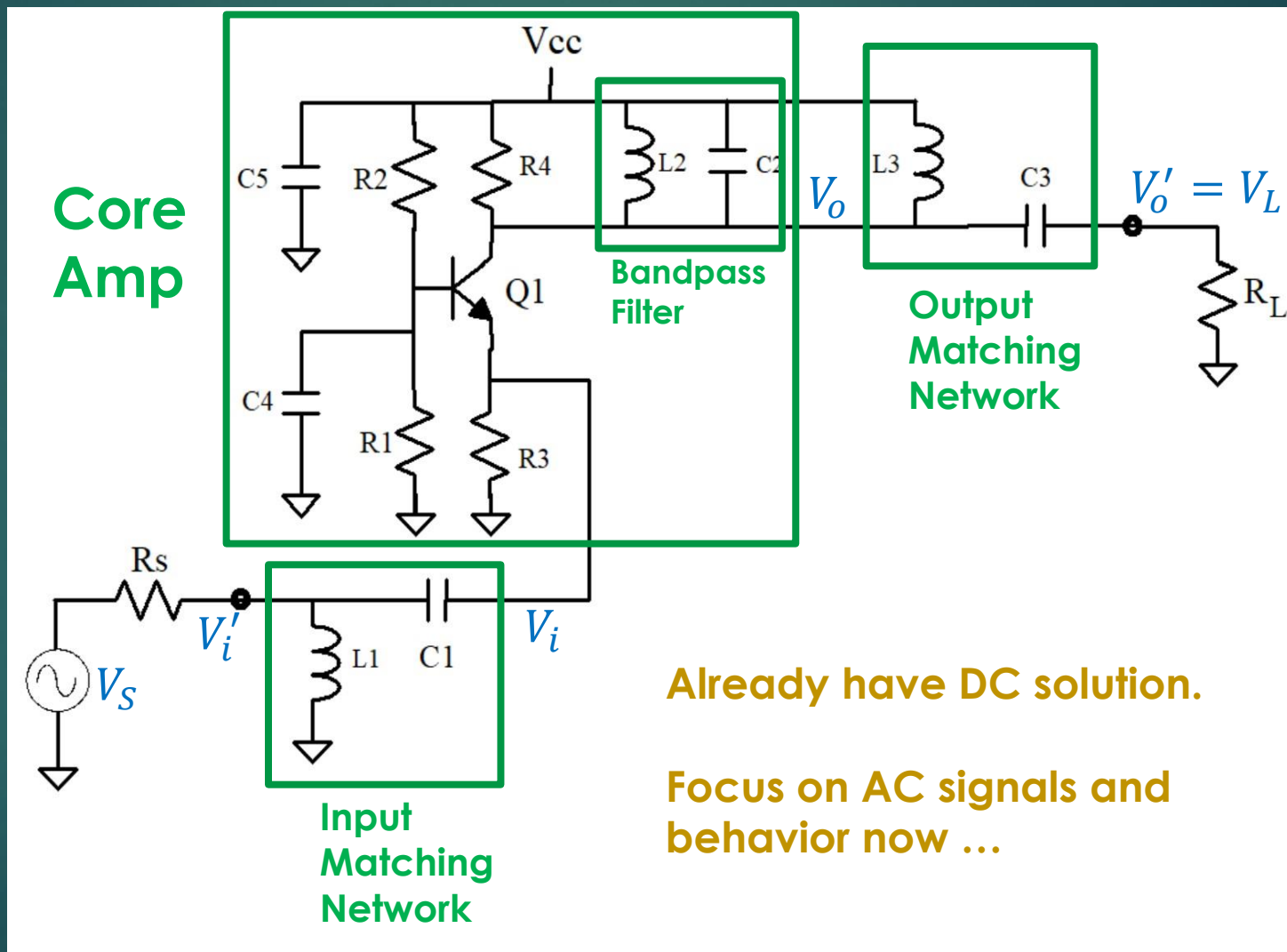

# Core Amp AC Small Signal Model

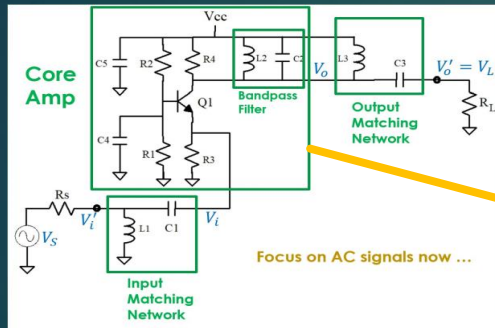

@  $f_o$

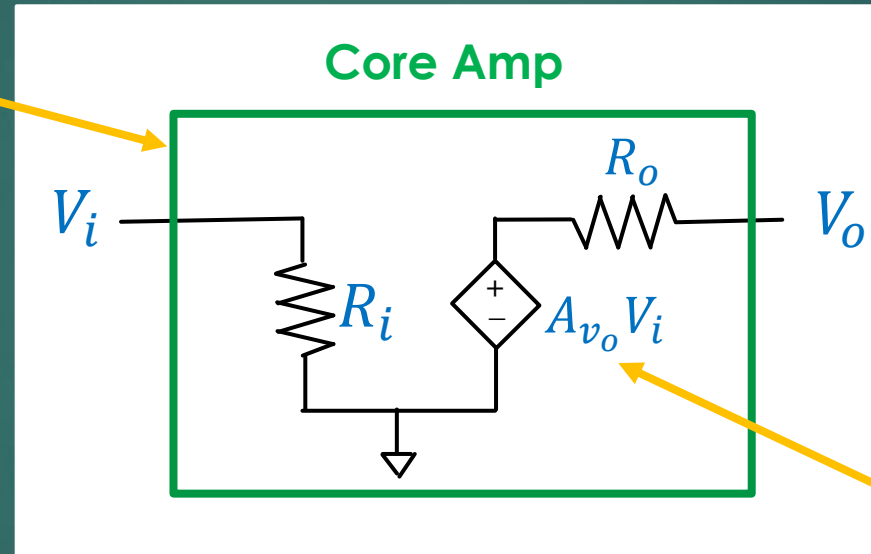



Simplified equivalent circuit  
of Core Amp (@  $f_o$ )

Based on Thevenin's theorem  
and linear systems theory


$$A_{v_o} = \frac{V_o}{V_i} \quad \text{with no loading}$$

- $R_i$ ,  $R_o$ , and  $A_{v_o}$  depend on amplifier device, circuit configuration, and biasing
- In general, we should use  $Z_i$ ,  $Z_o$ , and complex frequency-dependent gain, but this simplified treatment is sufficient for this particular Radio 101 video...

# Using the Model

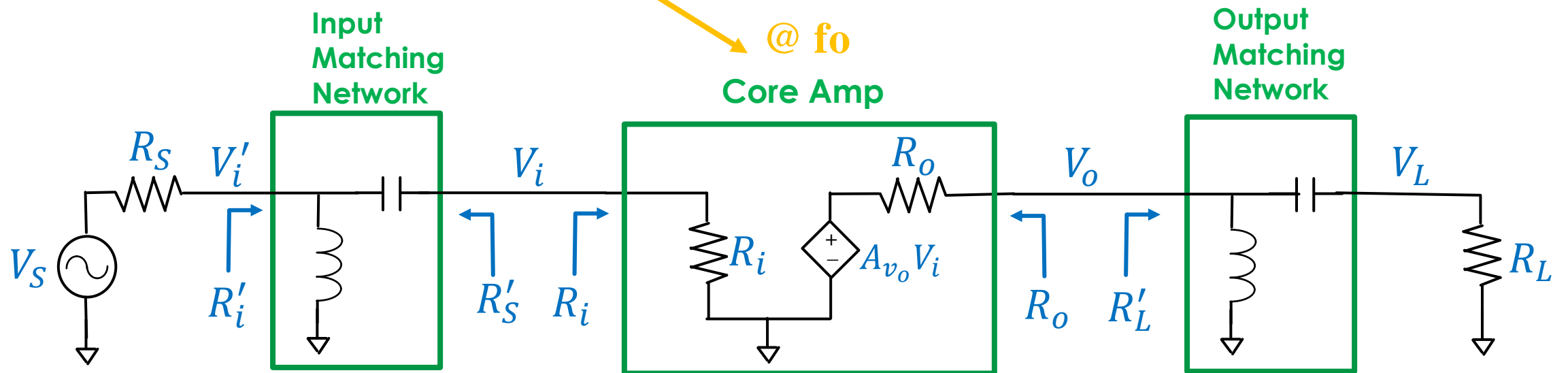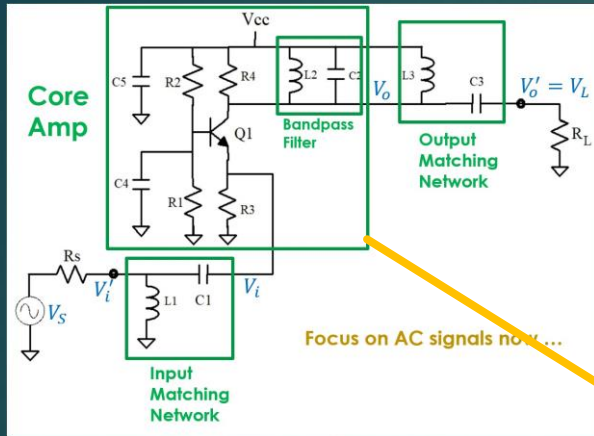


# Concentrating on the Core

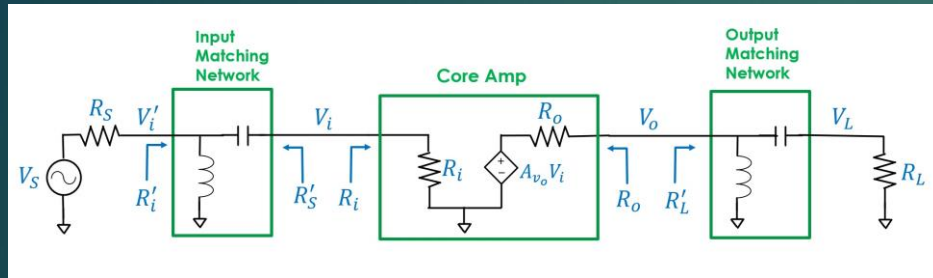

Knowing  $R_i$ ,  $A_{v_o}$ , and  $R_o$  is critical to:

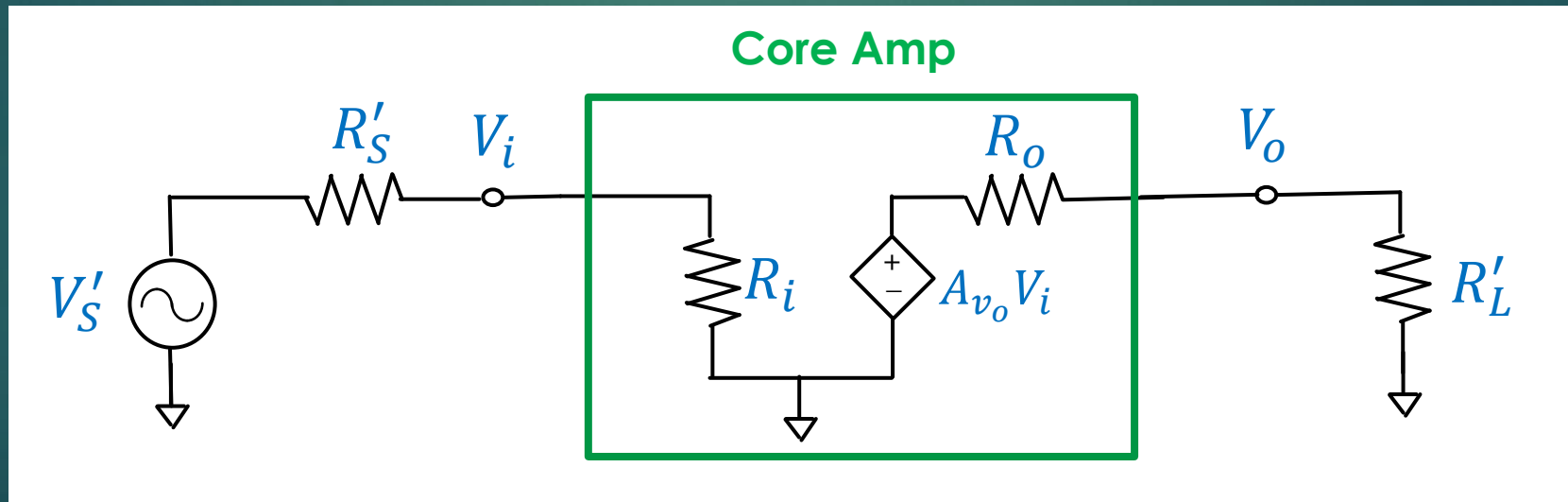- Interfacing with source and load
- Calculating voltage division factors
- Matching for maximum power gain
- **Understanding analog/RF circuits !**





# Overview of Part 2

- *Triode Devices*
- *DC Biasing*
- *AC Gain and I/O Impedances*
- *Amplifier Configurations*
- *High Frequency Limitations*
- *Data Sheets and More Example Circuits*

Part 2



# Amplifier Configurations Preview

## BJT Amplifier Configurations

Configuration	Representative Circuit	Approx. Formulas	$A_{V_{no-load}}$	$R_i$	$R_o$
Common Emitter		$A_{V_{no-load}} = -g_m (R_c \parallel r_o)$ $R_i = r_\pi \parallel R_{b1} \parallel R_{b2}$ where $r_\pi = h_{fe}/g_m$ $R_o = R_c \parallel r_o$	High	Med	Med
Common Base		$A_{V_{no-load}} = +g_m (R_c \parallel r_o)$ $R_i = 1/g_m \parallel R_E \parallel r_\pi$ $R_o = R_c \parallel r_o$	High	Low	Med
Common Collector (Emitter follower)		$A_{V_{no-load}} \approx 1$ $R_i = R_{b1} \parallel R_{b2} \parallel r_\pi (1 + g_m R_E)^*$ $R_o = 1/g_m^{***}$	Unity	High	Low


\* Assumes unloaded output

\*\* Assumes low source R

# Amplifier Configurations Preview

Configuration	Representative Circuit	Approx. Formulas	$A_{v_{no-load}}$	$R_i$	$R_o$
---------------	------------------------	------------------	-------------------	-------	-------

Common Emitter with Emitter Resistor

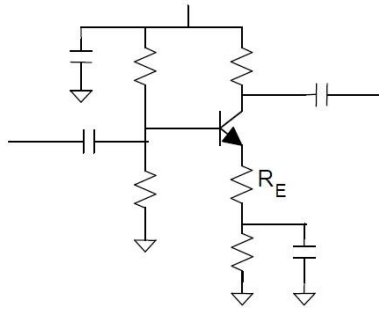


$$A_{v_{no-load}} = -g_m R_c / (1 + g_m R_E) \quad \text{Med} \quad \text{High} \quad \text{Med}$$

$$R_i = R_{b1} \parallel R_{b2} \parallel r_{\pi}(1 + g_m R_E)$$

$$R_o = R_c \parallel r_o$$

Cascode (CE + CB)

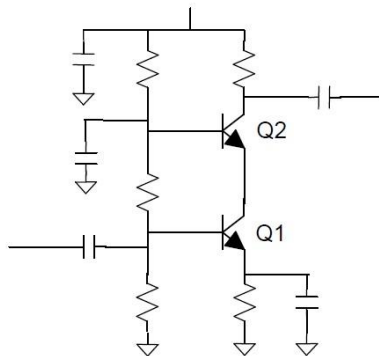


$$A_{v_{no-load}} = -g_m R_c \quad \text{High} \quad \text{Med} \quad \text{Med/High}$$

$$R_i = R_{b1} \parallel R_{b2} \parallel r_{\pi}$$

$$R_o = R_c \parallel (r_{o1} + r_{o2}(1 + g_m r_{o1}))$$





# Example Circuit 1

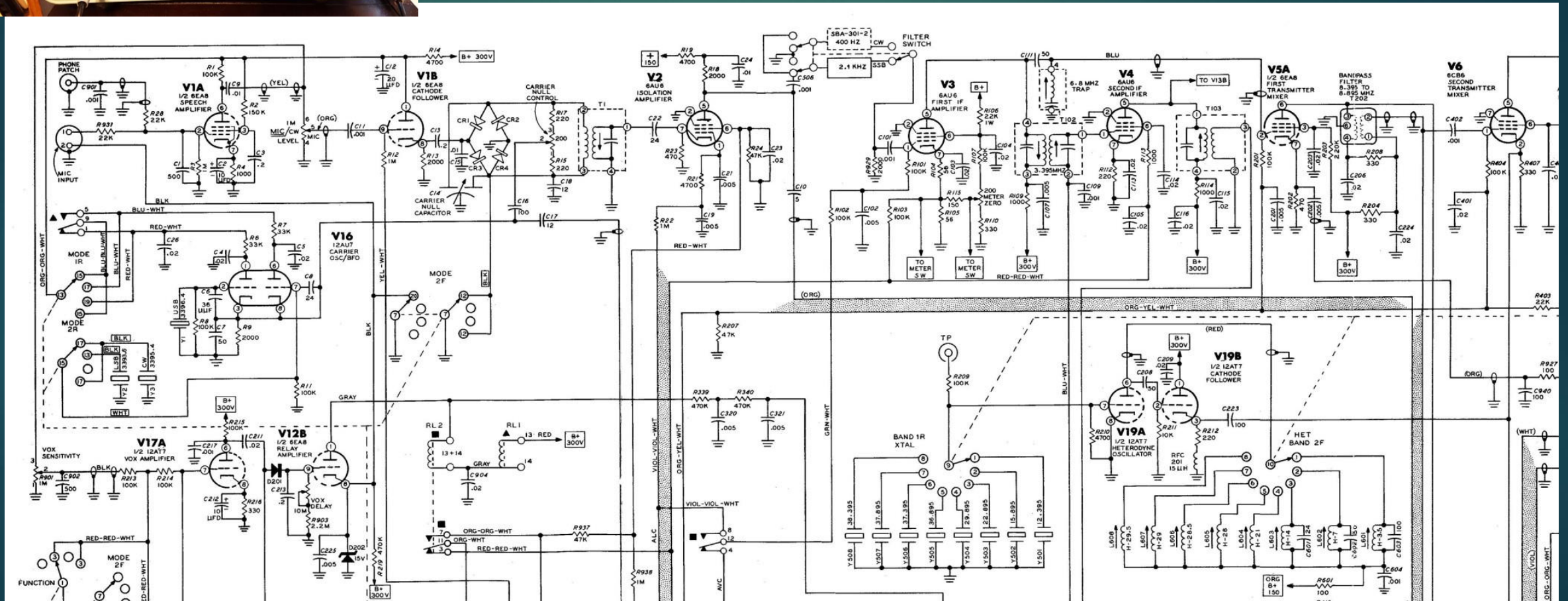



# Example Circuit 2

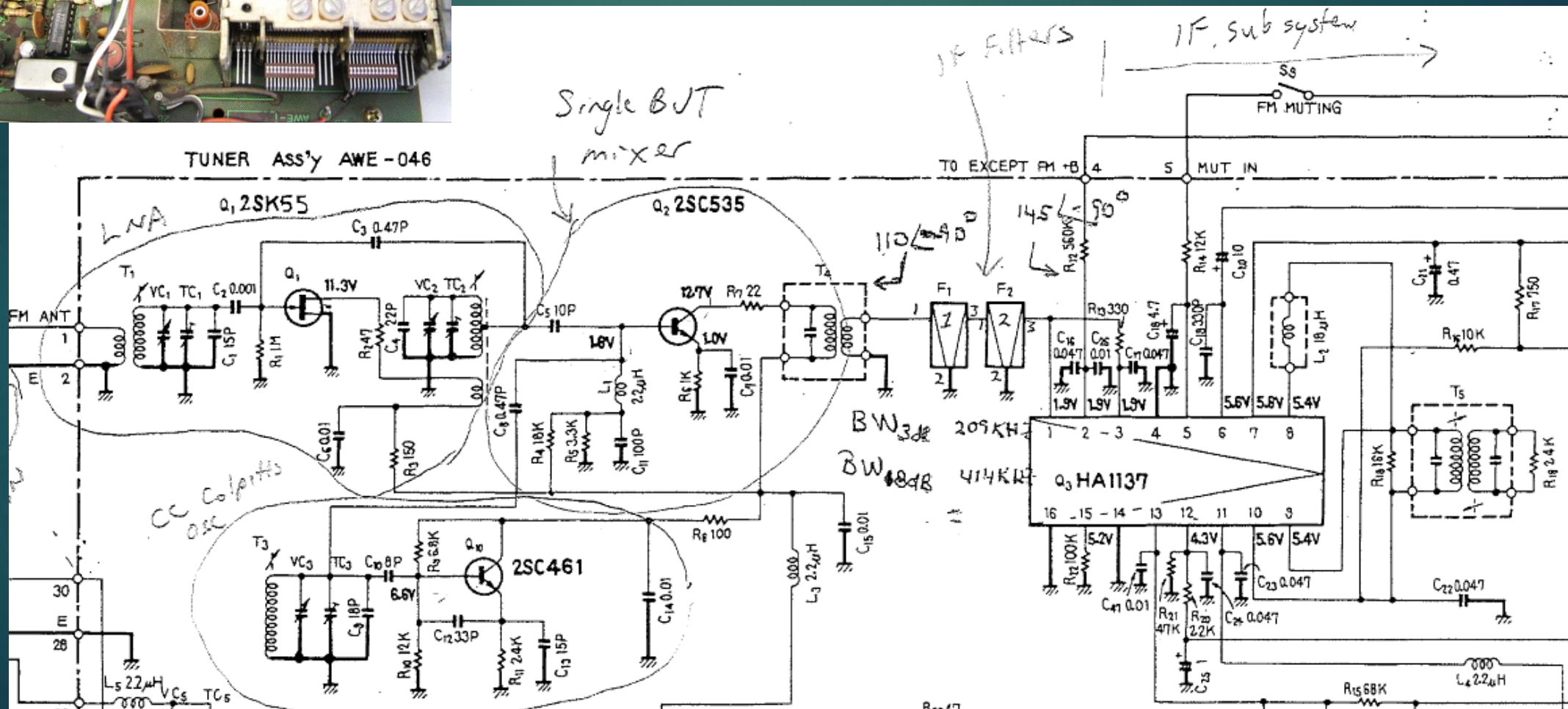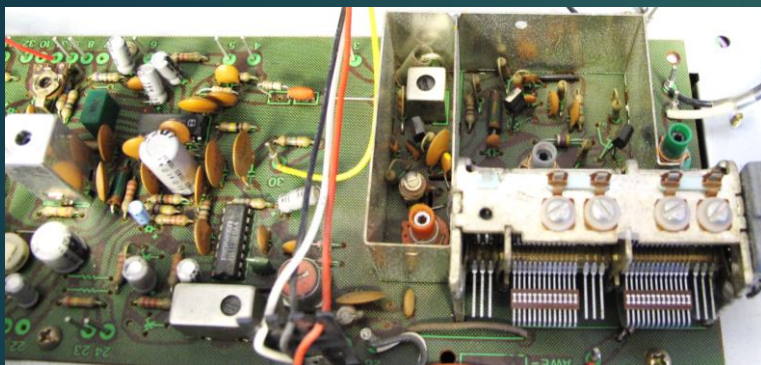

# Example Circuit 3

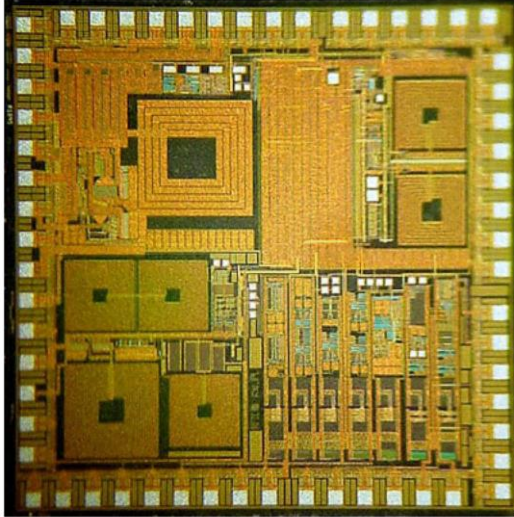


Fig. 39. Die photo of fully integrated single-chip 100-mW transceiver.

Vol. 95, No. 10, October 2007 | PROCEEDINGS OF THE IEEE 2041


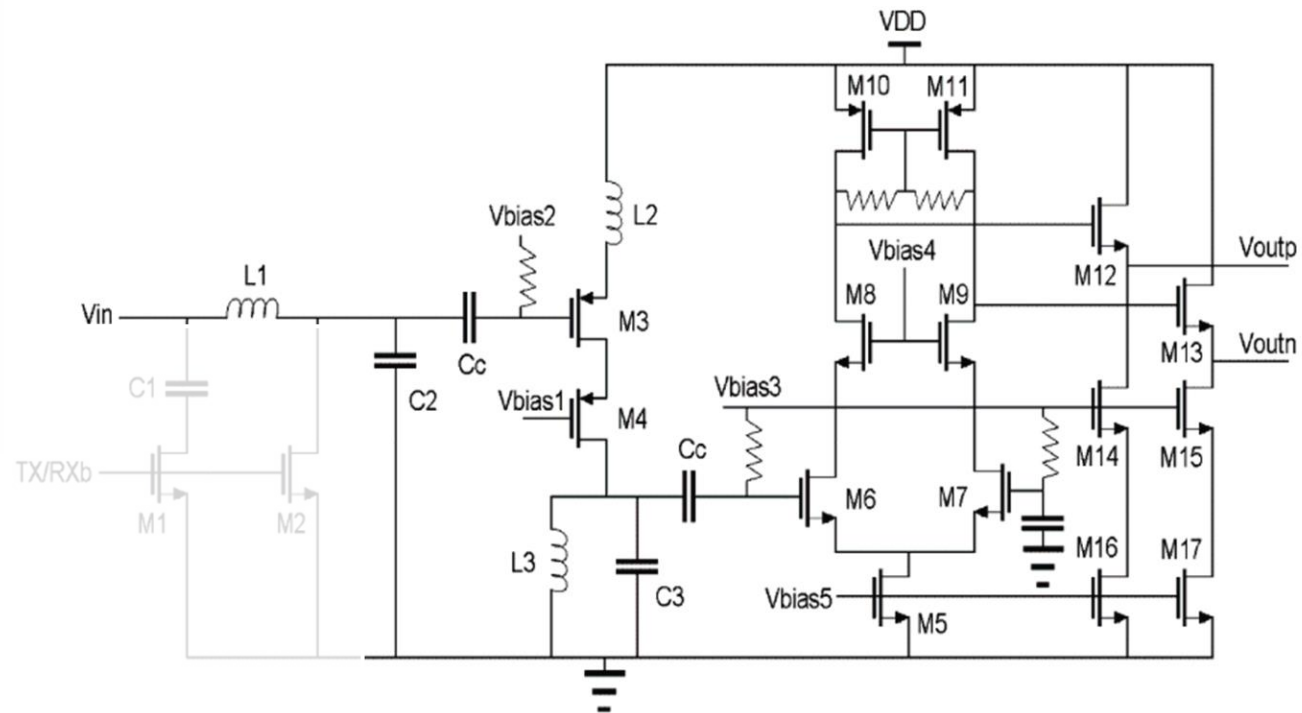


Fig. 23. Schematic diagram of LNA with integrated T/R switch circuits.


# High-Frequency Behavior

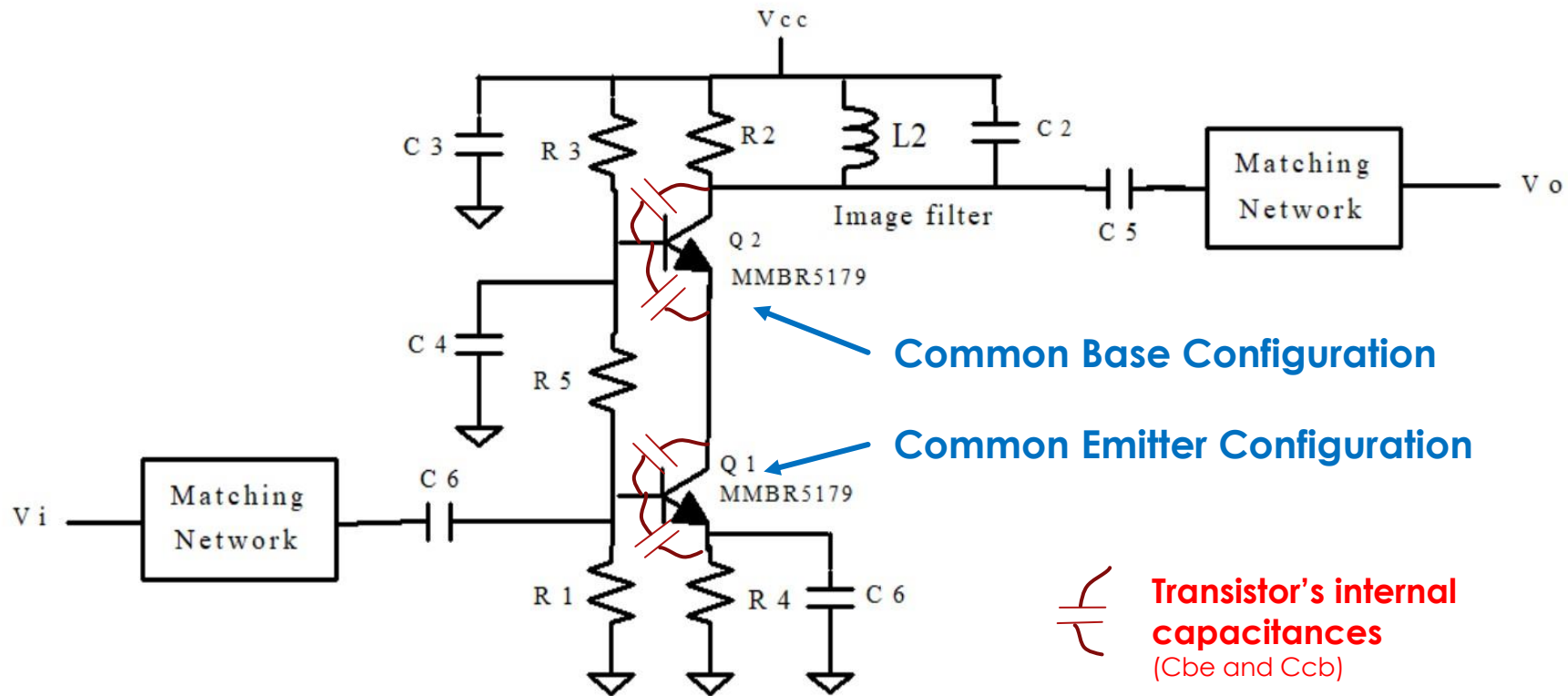


# Example Datasheet




## MPS5179

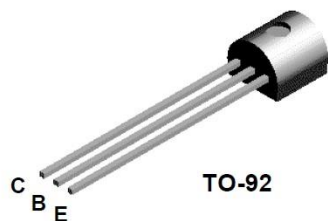

## MMBT5179

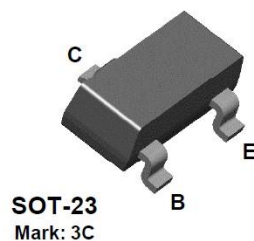

## PN5179

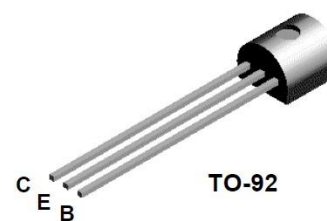

MPS5179 / MMBT5179 / PN5179

### NPN RF Transistor

This device is designed for use in low noise UHF/VHF amplifiers with collector currents in the 100  $\mu$ A to 30 mA range in common emitter or common base mode of operation, and in low frequency drift, high output UHF oscillators. Sourced from Process 40.

### Absolute Maximum Ratings\* TA = 25°C unless otherwise noted

Symbol	Parameter	Value	Units
$V_{CE0}$	Collector-Emitter Voltage	12	V
$V_{CBO}$	Collector-Base Voltage	20	V
$V_{EBO}$	Emitter-Base Voltage	2.5	V
$I_C$	Collector Current - Continuous	50	mA



# Tabular Data

## NPN RF Transistor (continued)

### Electrical Characteristics

TA = 25°C unless otherwise noted


Symbol	Parameter	Test Conditions	Min	Max	Units
<b>OFF CHARACTERISTICS</b>					
$V_{CE(sus)}$	Collector-Emitter Sustaining Voltage*	$I_C = 3.0 \text{ mA}, I_B = 0$	12		V
$V_{(BR)CBO}$	Collector-Base Breakdown Voltage	$I_C = 1.0 \text{ }\mu\text{A}, I_E = 0$	20		V
$V_{(BR)EBO}$	Emitter-Base Breakdown Voltage	$I_E = 10 \text{ }\mu\text{A}, I_C = 0$	2.5		V
$I_{CBO}$	Collector Cutoff Current	$V_{CB} = 15 \text{ V}, I_E = 0$ $V_{CB} = 15 \text{ V}, T_A = 150^\circ\text{C}$		0.02 1.0	$\mu\text{A}$ $\mu\text{A}$
<b>ON CHARACTERISTICS</b>					
$h_{FE}$	DC Current Gain	$I_C = 3.0 \text{ mA}, V_{CE} = 1.0 \text{ V}$	25	250	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 10 \text{ mA}, I_B = 1.0 \text{ mA}$		0.4	V
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C = 10 \text{ mA}, I_B = 1.0 \text{ mA}$		1.0	V
<b>SMALL SIGNAL CHARACTERISTICS</b>					
$f_T$	Current Gain - Bandwidth Product	$I_C = 5.0 \text{ mA}, V_{CE} = 6.0 \text{ V},$ $f = 100 \text{ MHz}$	900	2000	MHz
$C_{cb}$	Collector-Base Capacitance	$V_{CB} = 10 \text{ V}, I_E = 0,$ $f = 0.1 \text{ to } 1.0 \text{ MHz}$		1.0	pF
$h_{fe}$	Small-Signal Current Gain	$I_C = 2.0 \text{ mA}, V_{CE} = 6.0 \text{ V},$ $f = 1.0 \text{ kHz}$	25	300	
$rb'C_c$	Collector Base Time Constant	$I_C = 2.0 \text{ mA}, V_{CE} = 6.0 \text{ V},$ $f = 31.9 \text{ MHz}$	3.0	14	ps
NF	Noise Figure	$I_C = 1.5 \text{ mA}, V_{CE} = 6.0 \text{ V},$ $R_S = 50\Omega, f = 200 \text{ MHz}$		5.0	dB
<b>FUNCTIONAL TEST</b>					
$G_{pe}$	Amplifier Power Gain	$V_{CE} = 6.0 \text{ V}, I_C = 5.0 \text{ mA},$ $f = 200 \text{ MHz}$	15		dB
$P_O$	Power Output	$V_{CB} = 10 \text{ V}, I_E = 12 \text{ mA},$ $f \geq 500 \text{ MHz}$	20		mW

MPS5179 / MMBT5179 / PN5179


# Graphs and Formulas

2N5179

FIGURE 6 - CURRENT-GAIN-BANDWIDTH PRODUCT

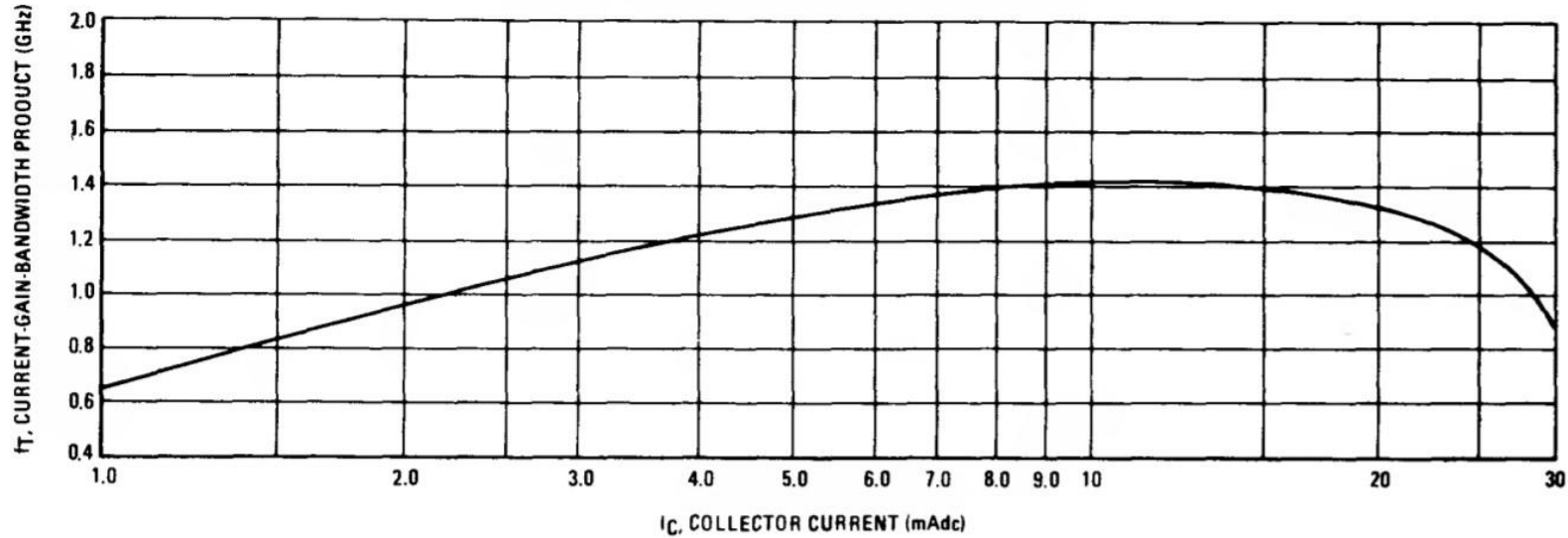

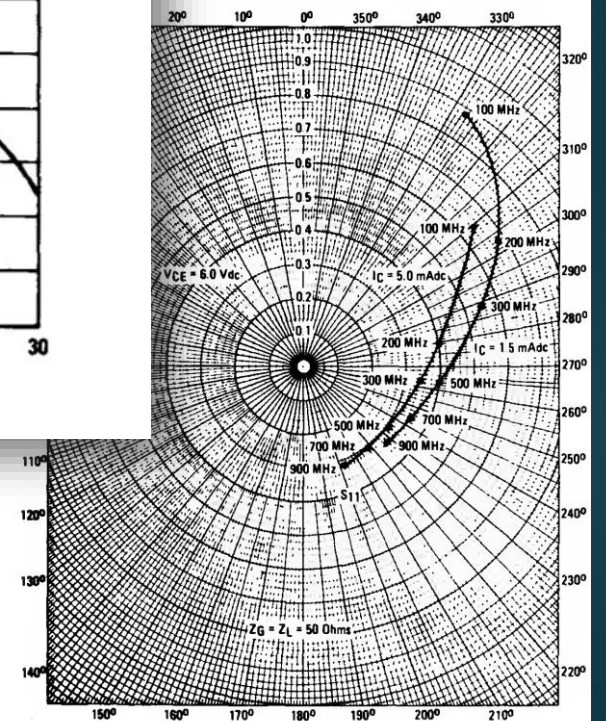11 - S<sub>11</sub>, INPUT REFLECTION COEFFICIENT



$$C_{be} \approx \frac{1}{2\pi \frac{1}{g_m} f_T} - C_{cb}$$

$$r_{\pi} = \frac{1}{g_m} h_{fe}$$

$$g_m = \frac{I_C}{nV_T}$$



*Thanks For  
Watching !*