

Radio Design 101




Episode 4 – RF Oscillators

Slides downloaded from: <https://ecefiles.org/rf-design/>

Companion video at: <https://www.youtube.com/watch?v=oJQONLdFC20>

This material is **provided by ecefiles.org for educational use only.**

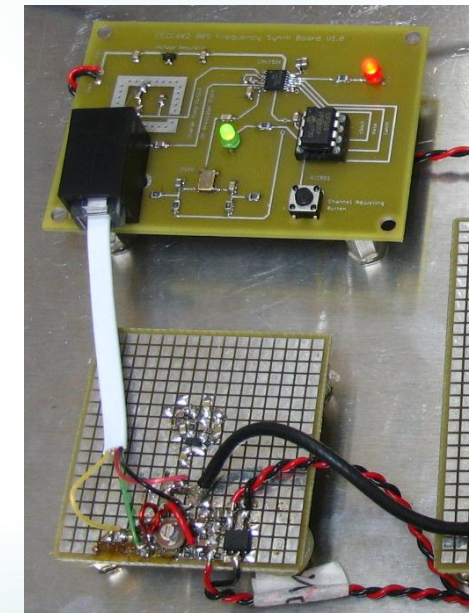
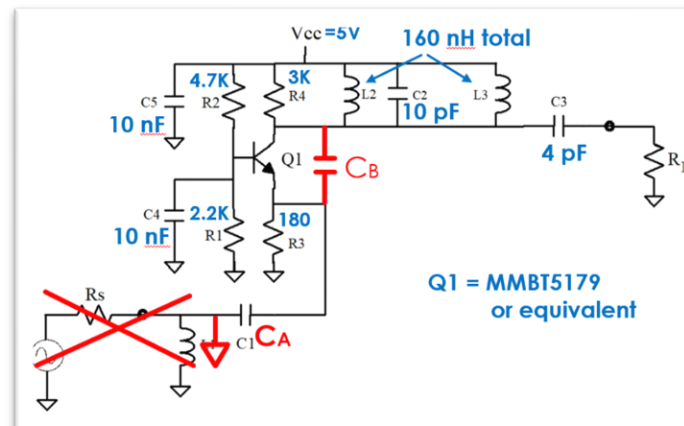
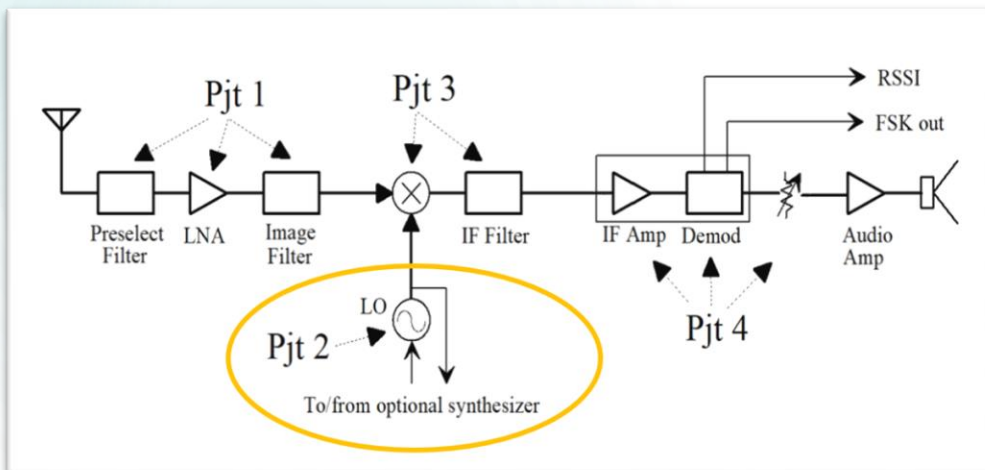
This episode covers radio frequency oscillator circuits, ranging from discrete designs through modern integrated circuit architectures. Associated topics include oscillator types (Hartley vs Colpitts), tuning using varactor diodes, and achieving frequency stability using crystals and PLL frequency synthesizers.



Radio Design 101


Episode 4

RF Oscillators

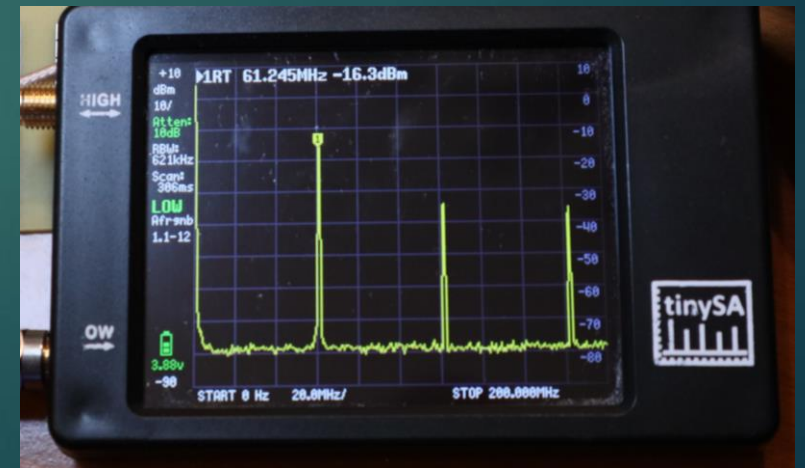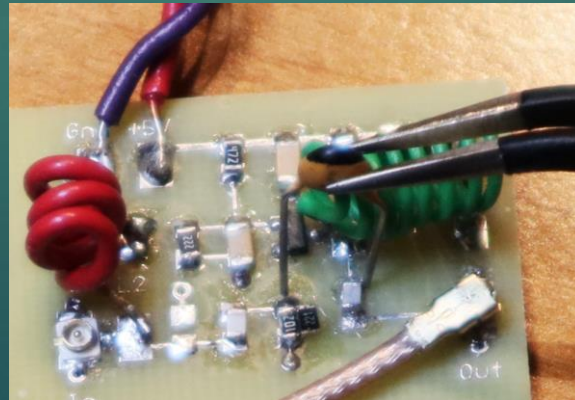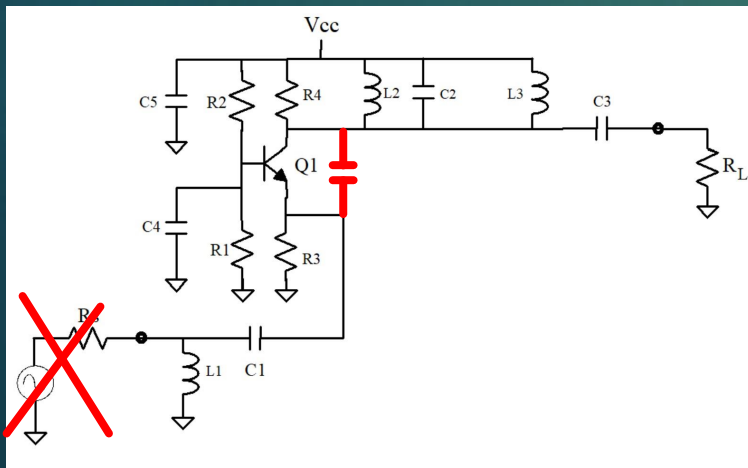


System Context

Frequency Synthesized Transmitter*

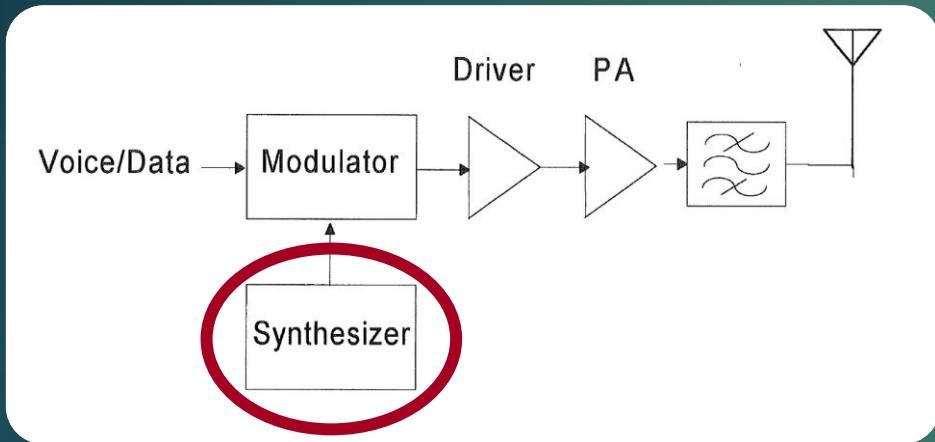

Superheterodyne Receiver

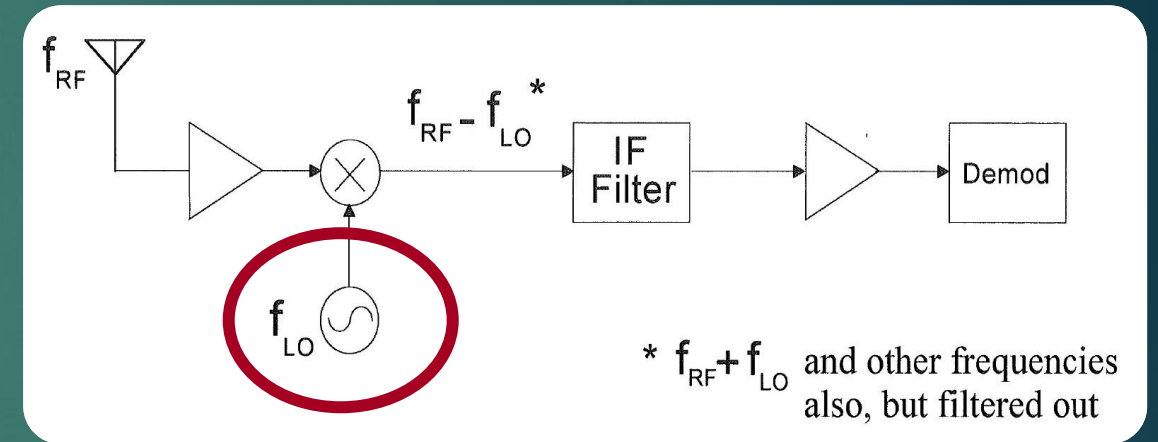

***WARNING:** Transmitting requires license and proper frequency control

Radio Design 101 “Semester Projects”



Radio Design 101 - Episode 3 - Amplifi...
A relatively complete discussion of amplifier circuits, including the electroni...



Radio Design 101 - Episode 2 - Impeda...
Impedance Matching networks. This is the second half of episode 2 in the Radi...



Radio Design 101 - Episode 2 - Impeda...
Impedance Matching networks. This is episode 2 in the Radio Design 101 series...




Radio Design 101 - Episode 1 - Transc...
This video covers the design of bandpass filters, including the concept of quality...




Radio Design 101 - Episode 1 - Transc...
This video overviews radio / wireless transmitters and receivers, circuit...



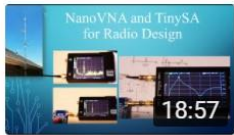
NanoVNA - Antennas and Tuners
Using the NanoVNA to illustrate the operation of antennas and antenna...



NanoVNA and TinySA for Radio Design
Using the NanoVNA and TinySA to illustrate how radio / wireless devices...


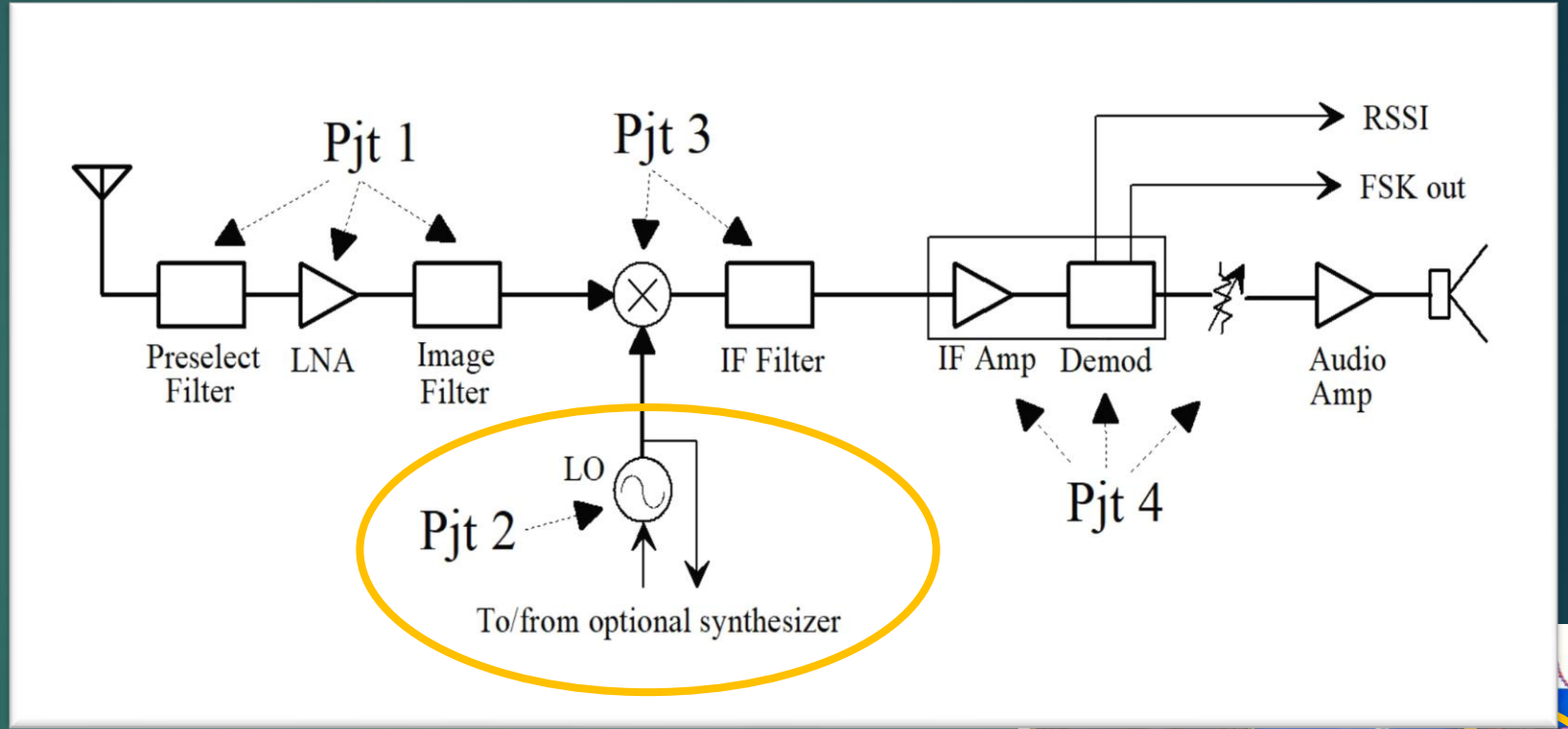


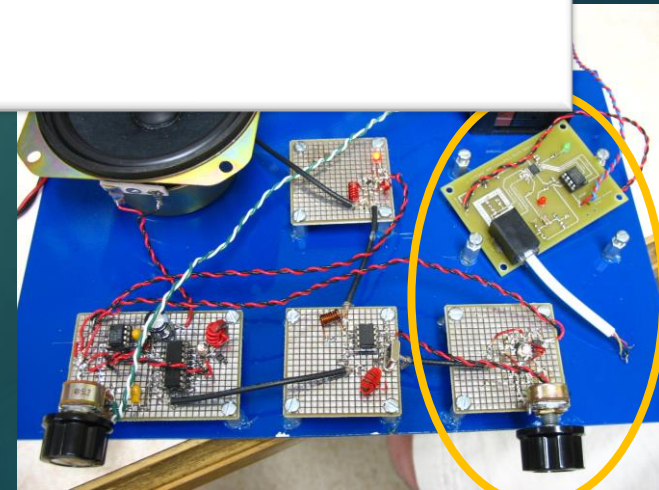Project 2 – Local Oscillator (This Video)



Overview

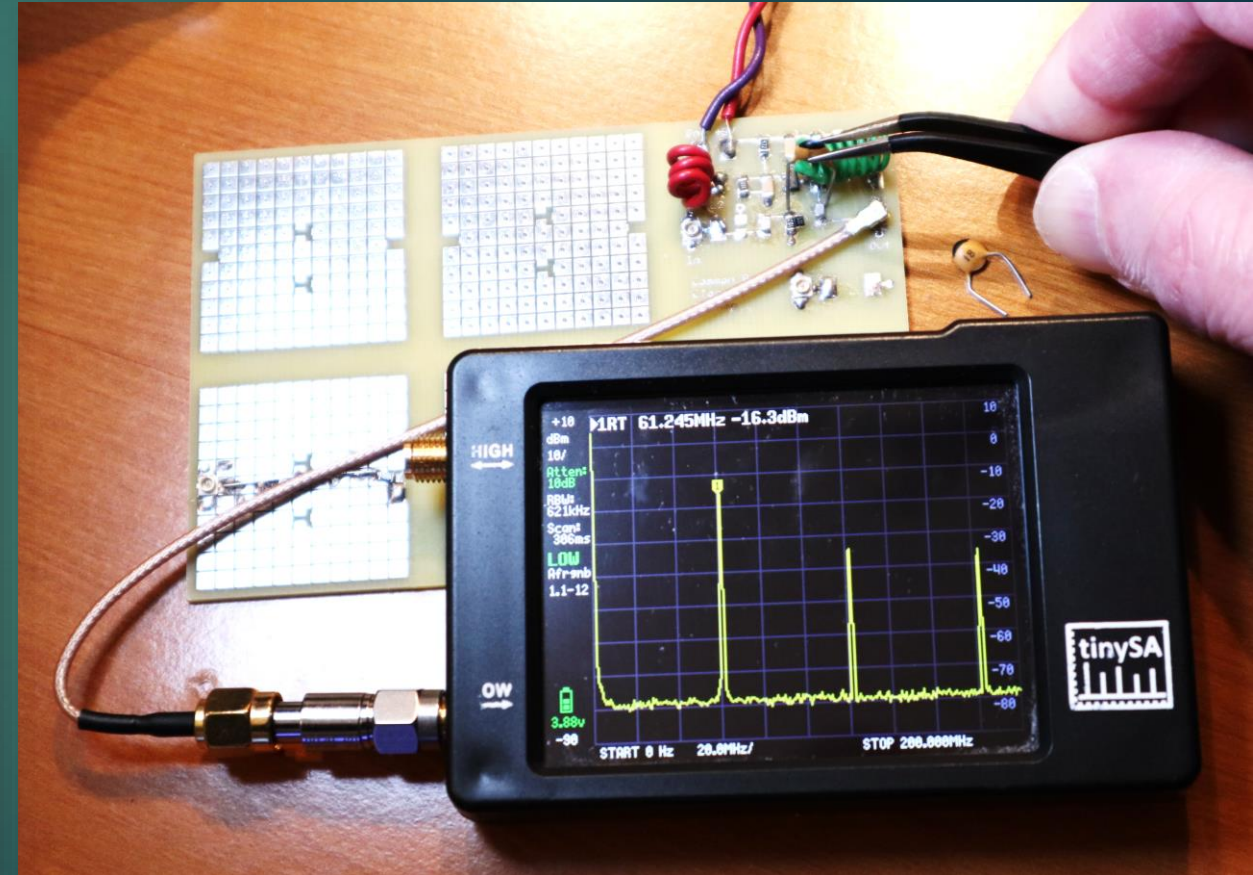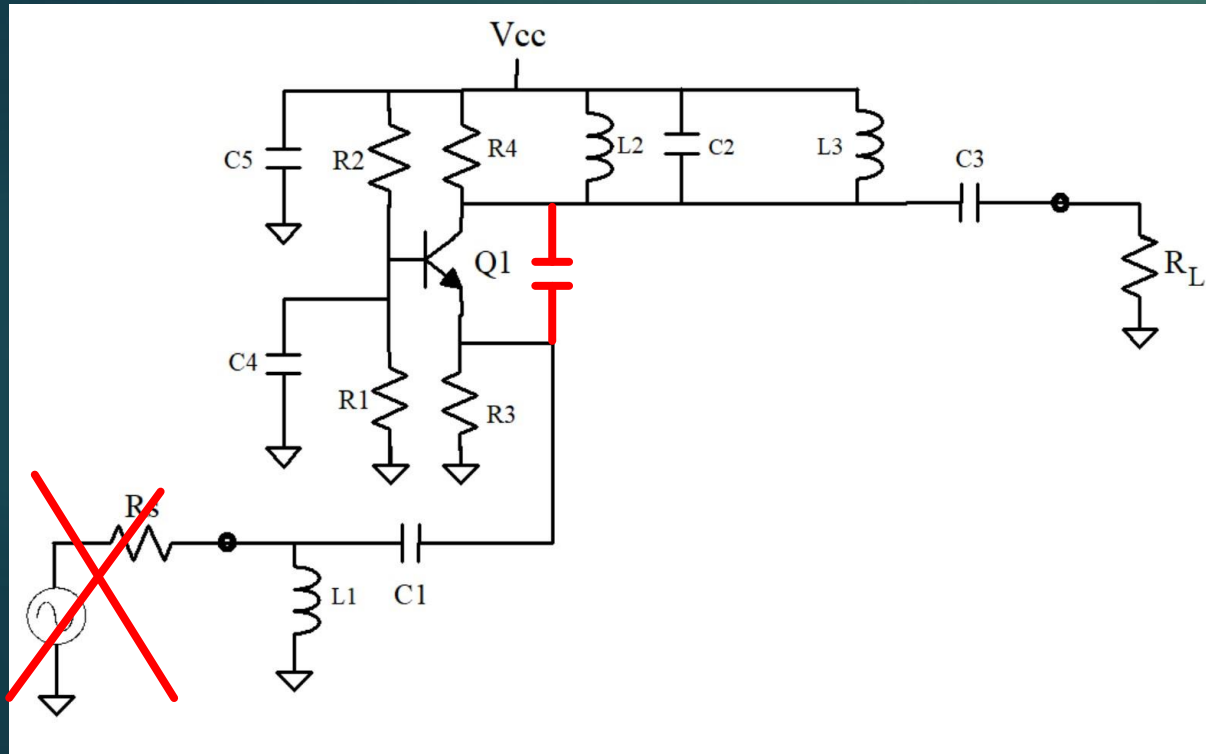Amplifier + (Positive) Feedback = Oscillator




Topic Outline

- *LC Oscillator Basics*
- *Hartley and Colpitts circuits*
- *Voltage Controlled Oscillators*
- *Crystal Oscillators and Synthesizers*


How to Make an LC Oscillator

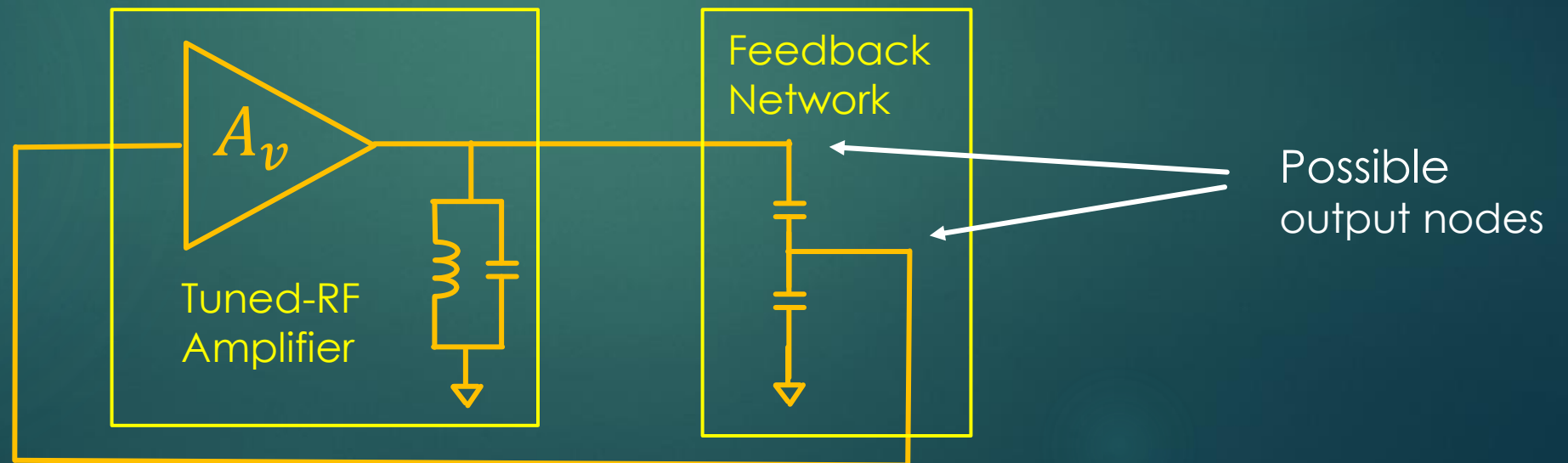- Design a tuned-RF amplifier
- Add positive (in-phase) feedback
- Select output node and assess loading and inductor-Q effects on gain
- Verify “loop gain” is > 1 at center frequency
- See also: https://en.wikipedia.org/wiki/Barkhausen_stability_criterion




Leveraging our Existing Work

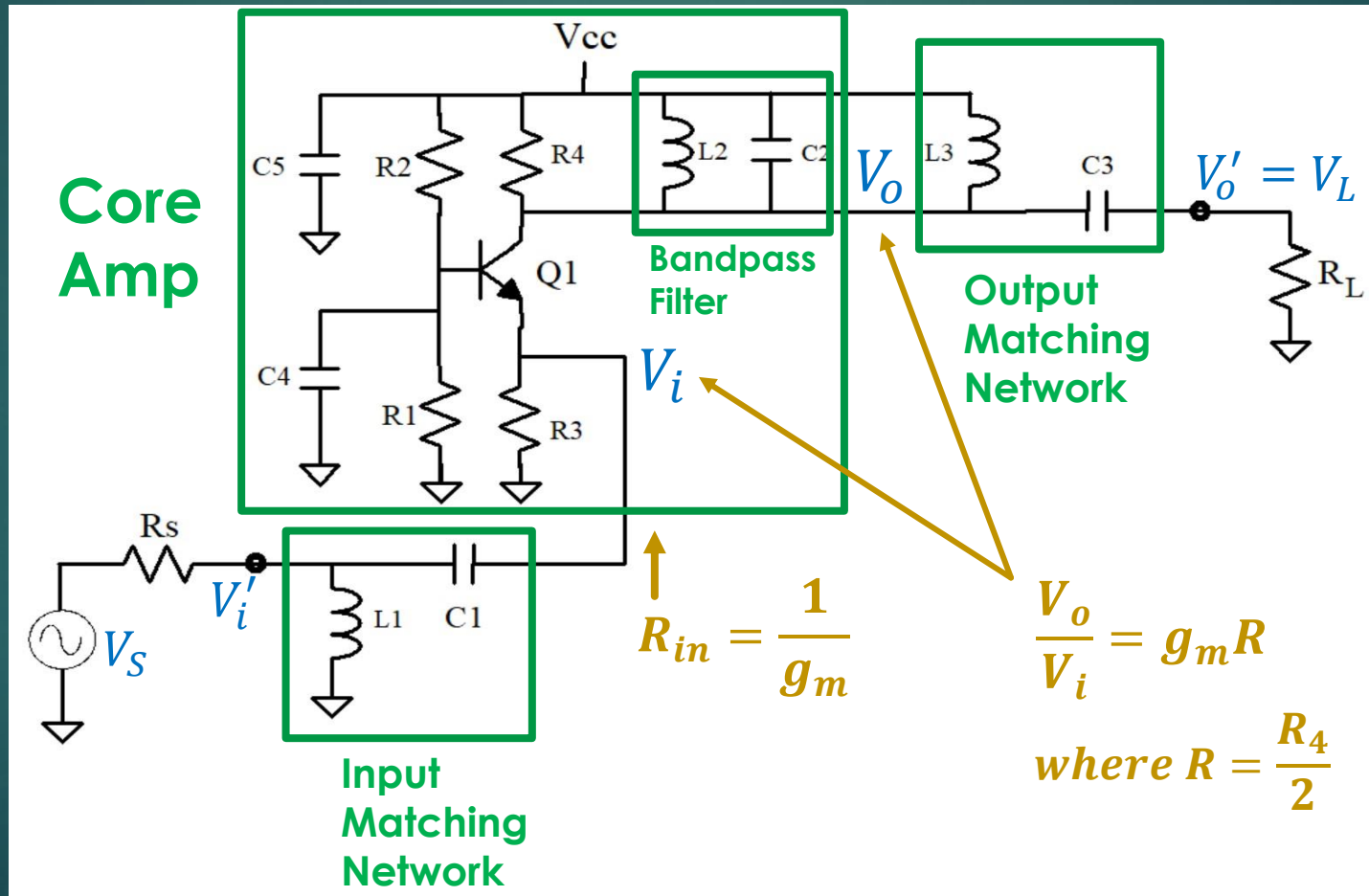Recall our Common-Base amplifier from Episode 2:



Modify to Create Oscillation

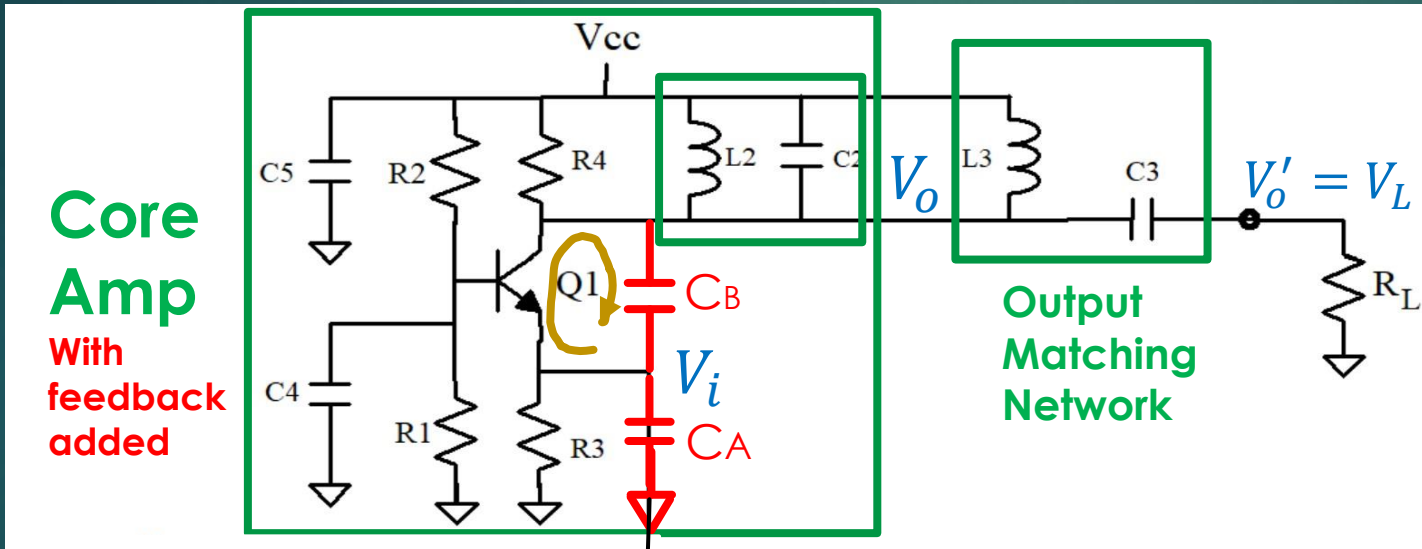- Delete input port and input matching network (and optionally R4)
- Add feedback network and adjust L2, C2 to get desired frequency



Core
Amp
With
feedback
added

Output
Matching
Network


- Voltage divider C_A , C_B feeds output back to input
- Oscillates if “loop gain” from V_i to V_o and back to V_i
 A_{v-loop} is > 1 and the reactance of C_A is $X_{C_A} < R_{in}$
- Typically, $C_B = C_A$ to $C_B = C_A / 4$ will make $A_{v-loop} > 1$

NOTE:


If $X_{C_A} \ll R_{in}$ then $C_A C_B$

is part of a tapped – capacitor impedance matching network that transforms R_{in} to R_{in}' seen by the collector node.

Why Did This Work Without C_A ?

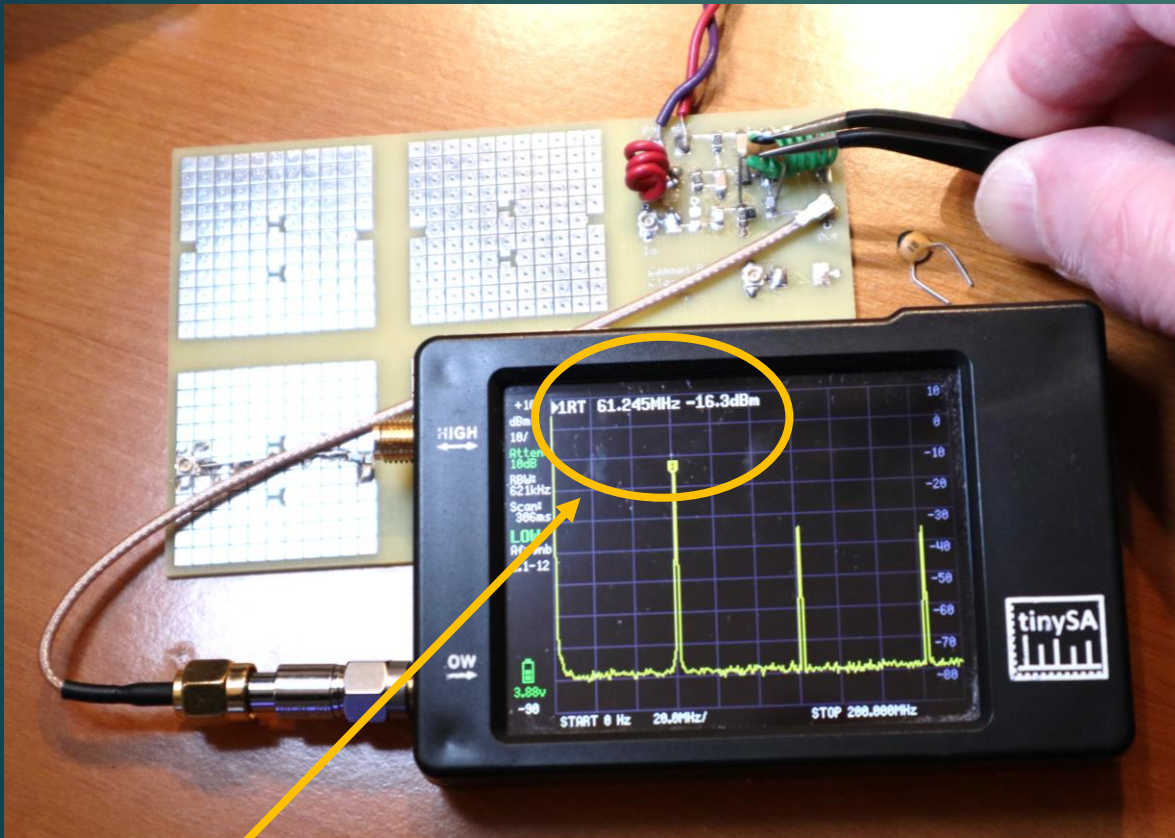


$f_o = 61 \text{ MHz}$

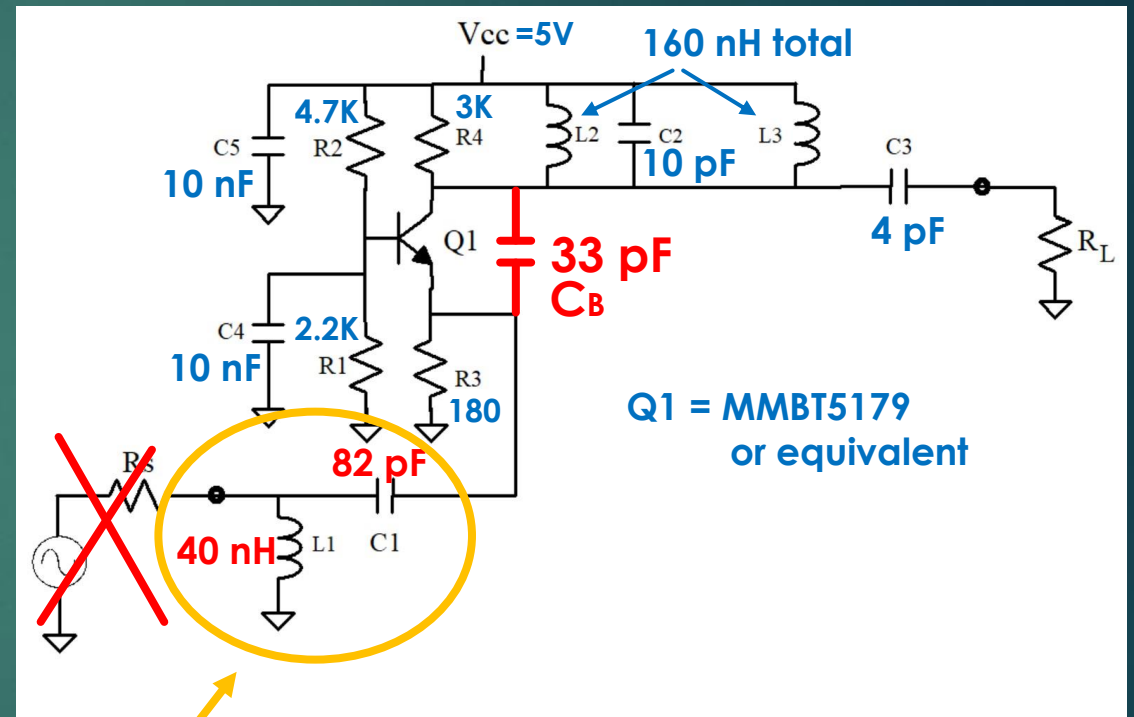

Looks like 160 pF at 61 MHz
(@ 61 MHz $Z_{c1} = -j 31$ and $Z_{L1} = +j 15$)

ALSO – C_{be} inside Q1 is 15 pF @ $I_c = 5\text{mA}$

Project 2 “Homework” 😊

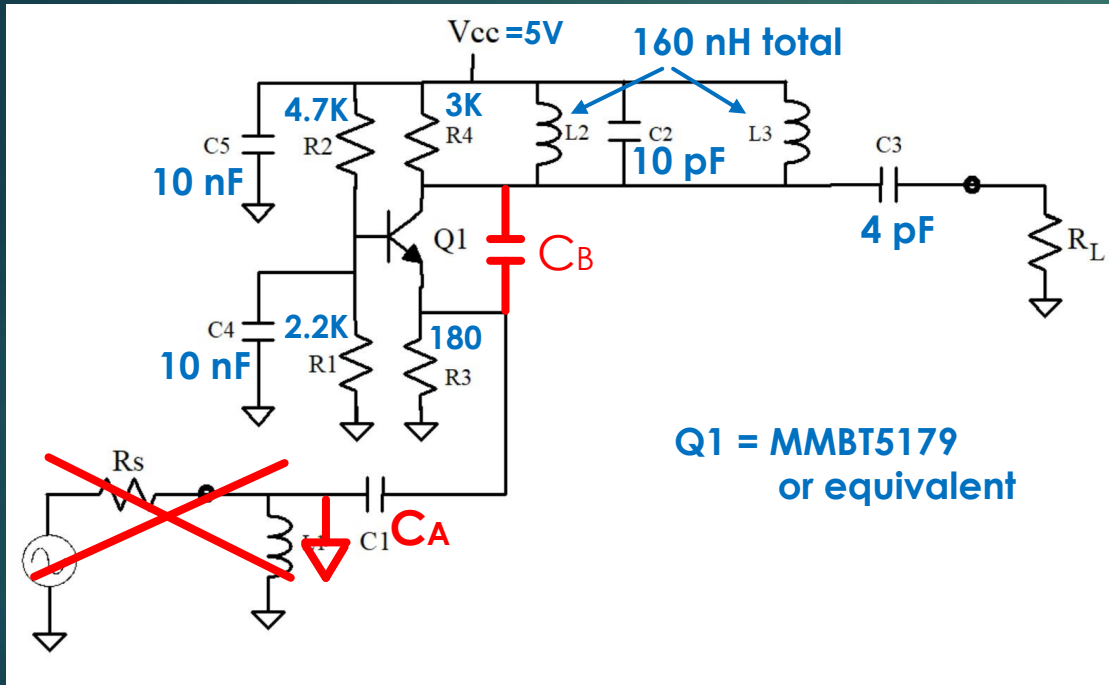

Redesign this for use in FM receiver

PROCEDURE :

- Delete L1 and ground C1 (now labeled C_A)
- Increase R3 to 360 to raise R_{in} from 10 to 20 Ohms
- Find C_A to give $X_{C_A} = 20$ at 87 MHz
- Find C_B as 1/3 of C_A
- Adjust L total to resonate at 87 MHz*
- Build and test
- Add varactor tuning to cover 77.2 to 97.2 MHz**
- Refine and retest

* Total C to ground at collector of Q1 is $C_2 + C_3 + C_{bc} + (C_B - - C_A)$,
 where C_{bc} collector-base C inside Q1 (about 1 pF) and $(C_B - - C_A)$ is the series combination of C_B and C_A


** To tune FM broadcast receiver with 10.7 MHz IF. See varactor diode discussion coming up

Topic Outline

- *LC Oscillator Basics*
- *Hartley and Colpitts circuits*
- *Voltage Controlled Oscillators*
- *Crystal Oscillators and Synthesizers*

1915 Hartley Patent

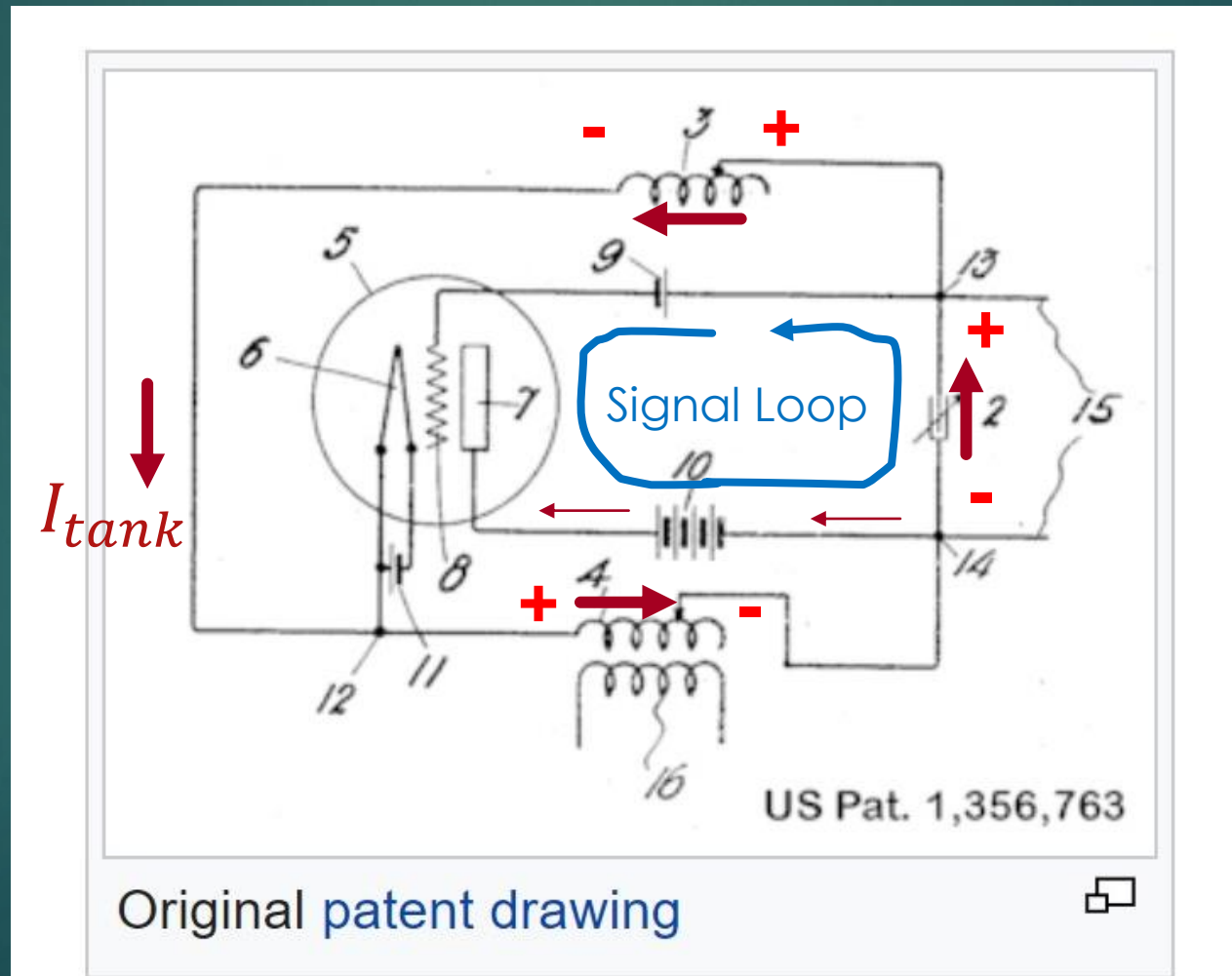
https://en.wikipedia.org/wiki/Hartley_oscillator



Modern Hartley Designs


Common-emitter Hartley
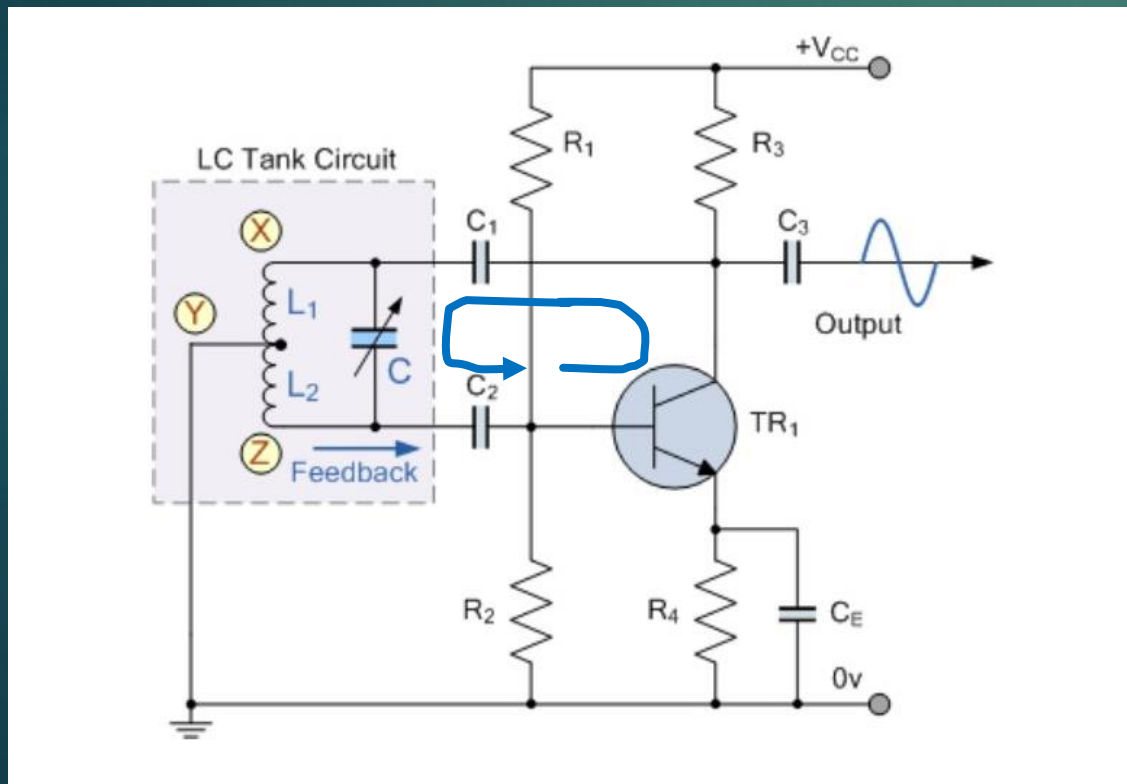
<https://www.electronics-tutorials.ws/oscillator/hartley.html>



Simple Common-drain Hartley

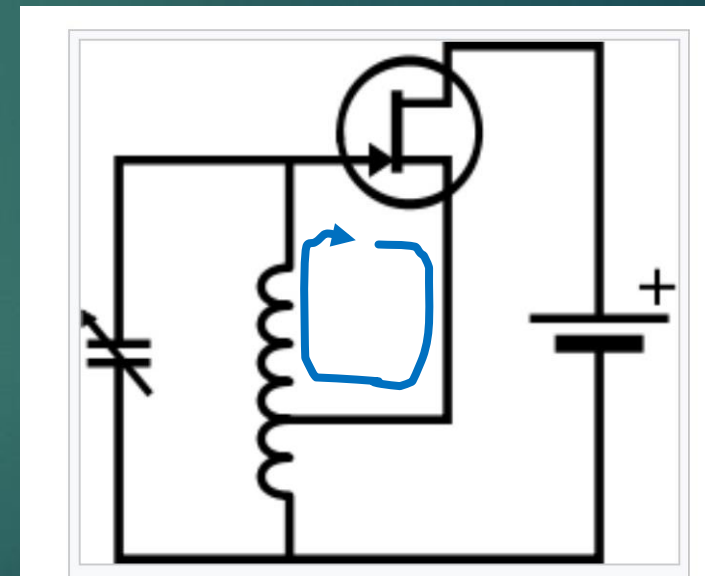
https://en.wikipedia.org/wiki/Hartley_oscillator



Requires two inductors (or tapped inductor) ☹️

Modern Colpitts Designs


Common-base Colpitts

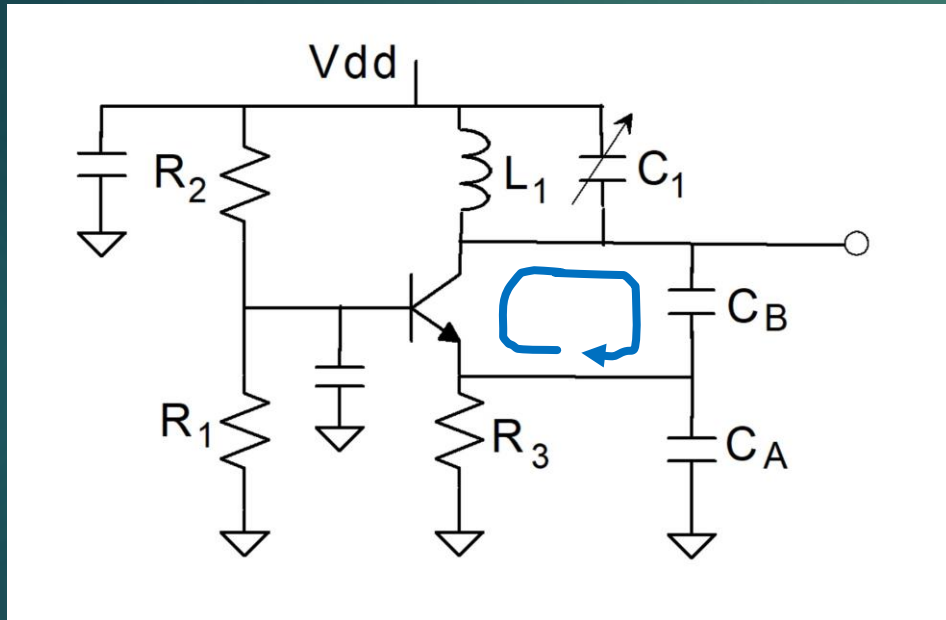

$$A_{v-open-loop} = +g_m R$$

Voltage/impedance step – down in capacitors


Common-collector Colpitts

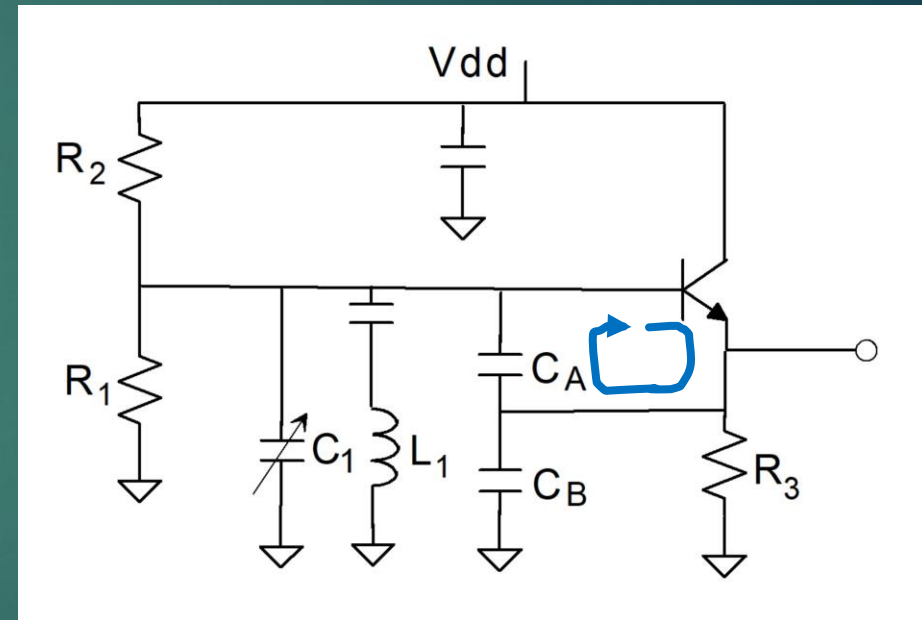

$$A_{v-open-loop} = +1$$



*Voltage/impedance step – up in capacitors
(due to resonance with L1,C1)*

Example 1 – Ham Radio VFO

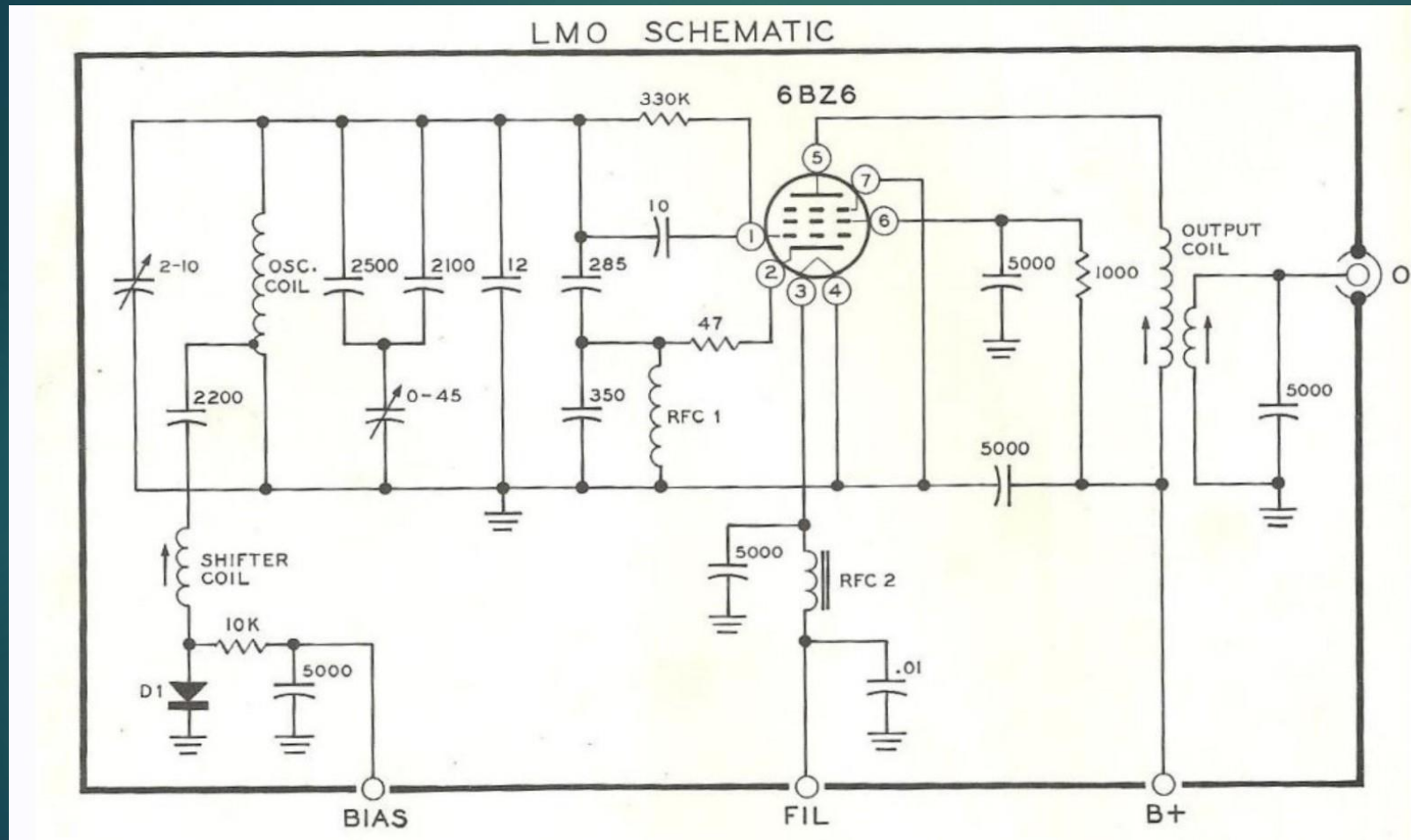

<https://forums.qrz.com/index.php?threads/heathkit-trw-110-48-lmo.747520/>

Example 2 – FM Broadcast Receiver

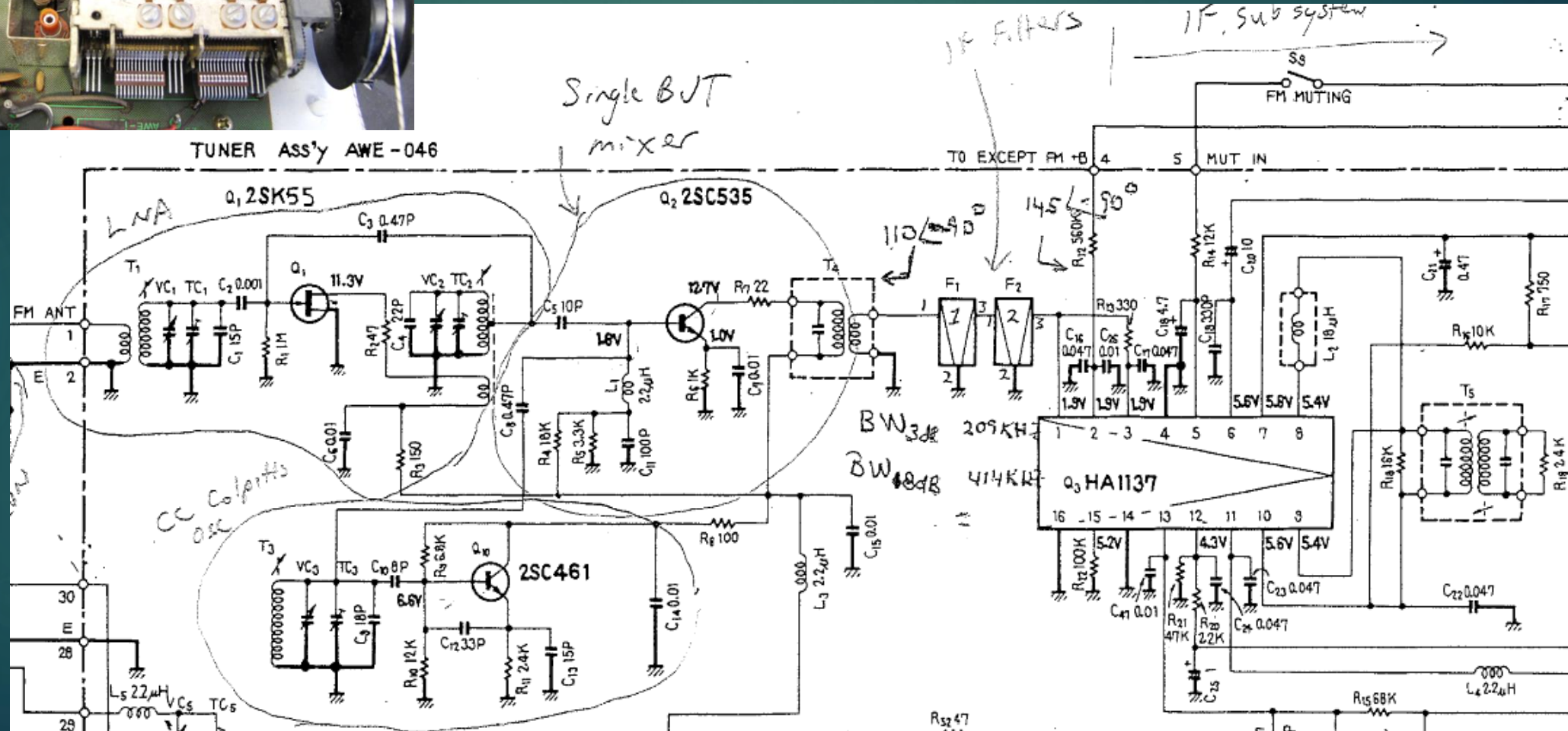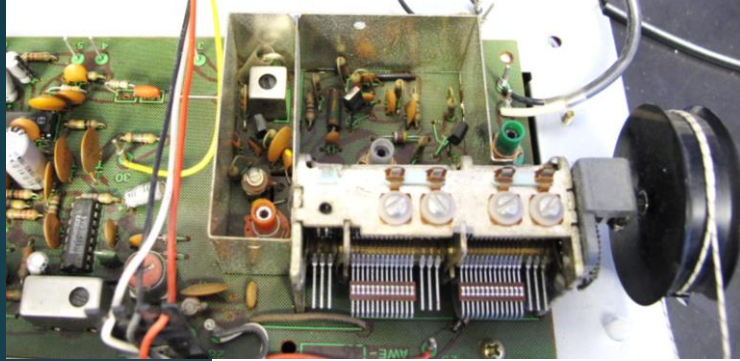

Topic Outline


- *LC Oscillator Basics*
- *Hartley and Colpitts circuits*
- *Voltage Controlled Oscillators*
- *Crystal Oscillators and Synthesizers*

Varactor Diode

MMBV609LT1

ON Semiconductor Preferred Device

DUAL
VOLTAGE VARIABLE
CAPACITANCE DIODE

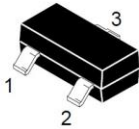

CASE 318-08, STYLE 9
SOT-23 (TO-236AB)

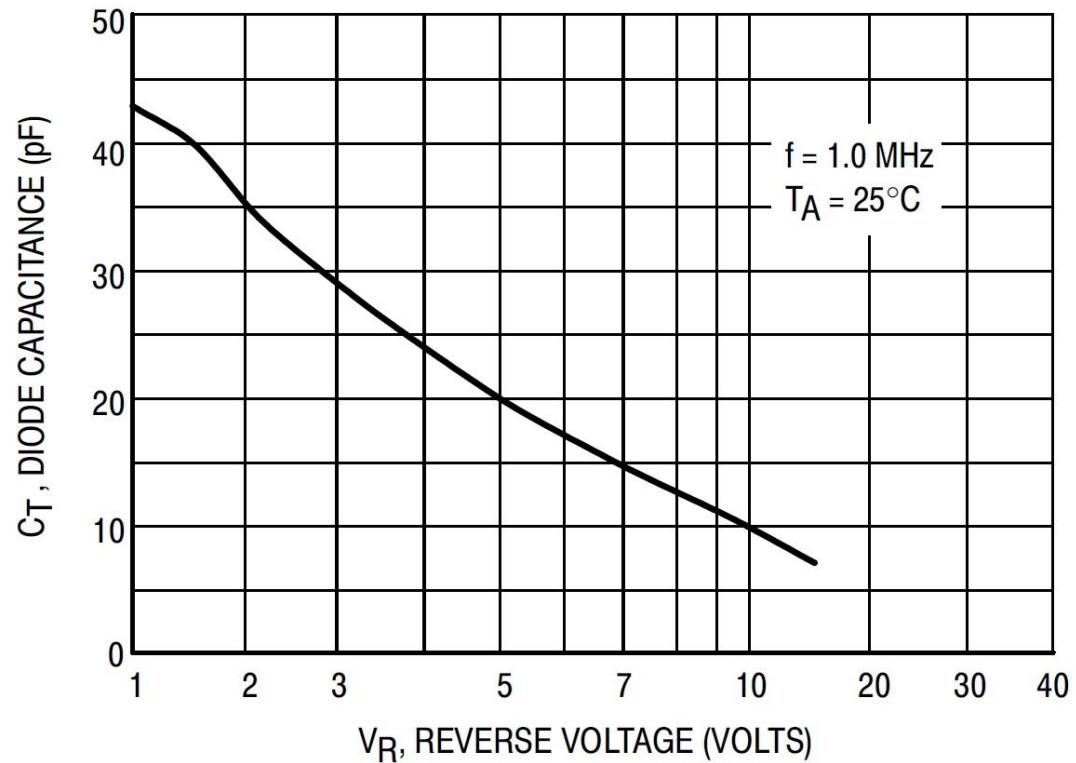
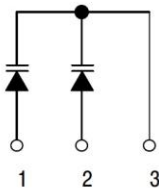


Figure 1. Diode Capacitance

CC Colpitts VCO


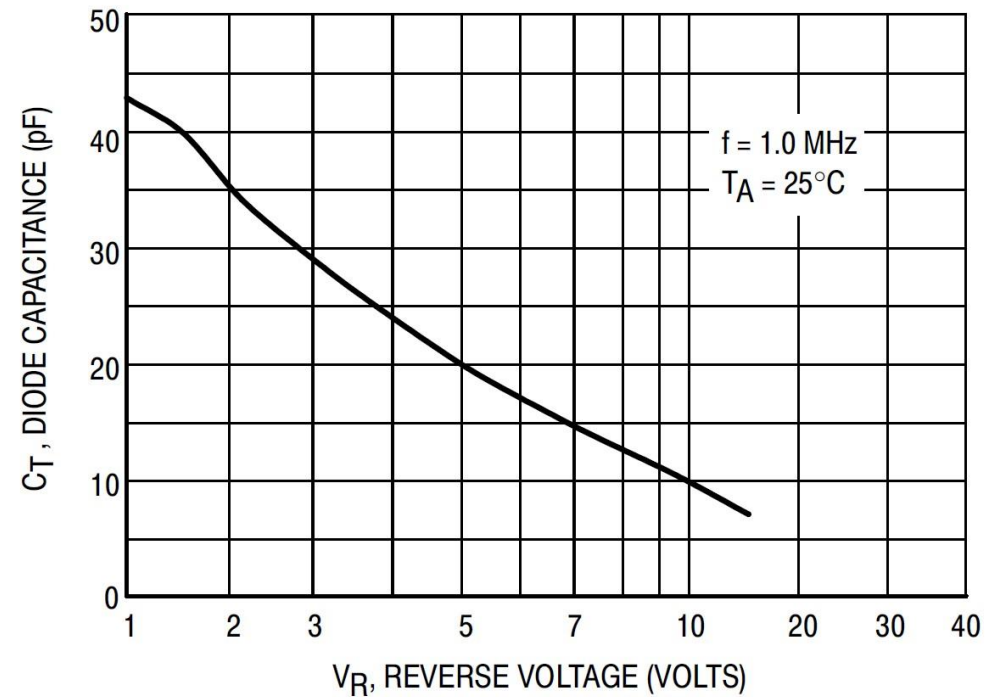
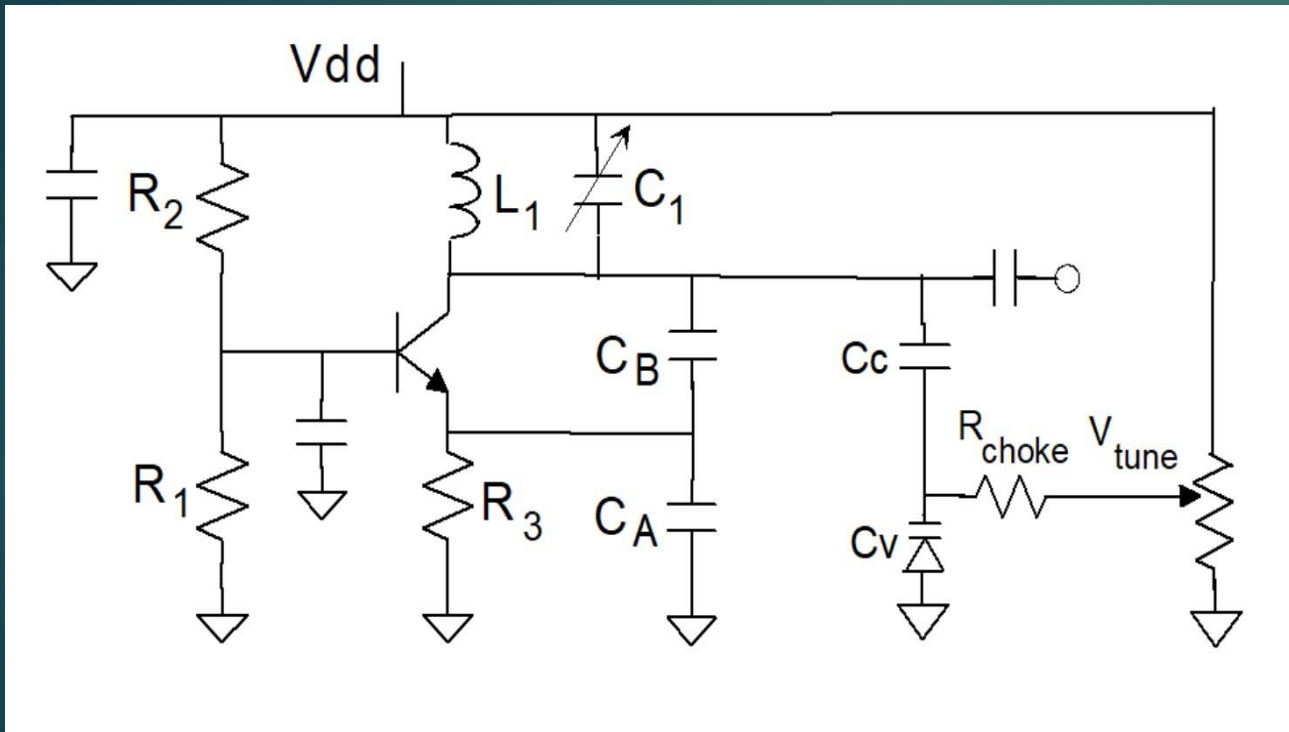
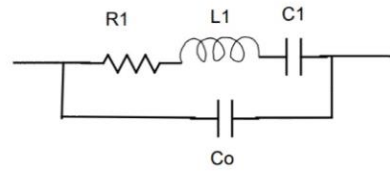


Figure 1. Diode Capacitance


Topic Outline

- *LC Oscillator Basics*
- *Hartley and Colpitts circuits*
- *Voltage Controlled Oscillators*
- *Crystal Oscillators and Synthesizers*

Colpitts Crystal Oscillators

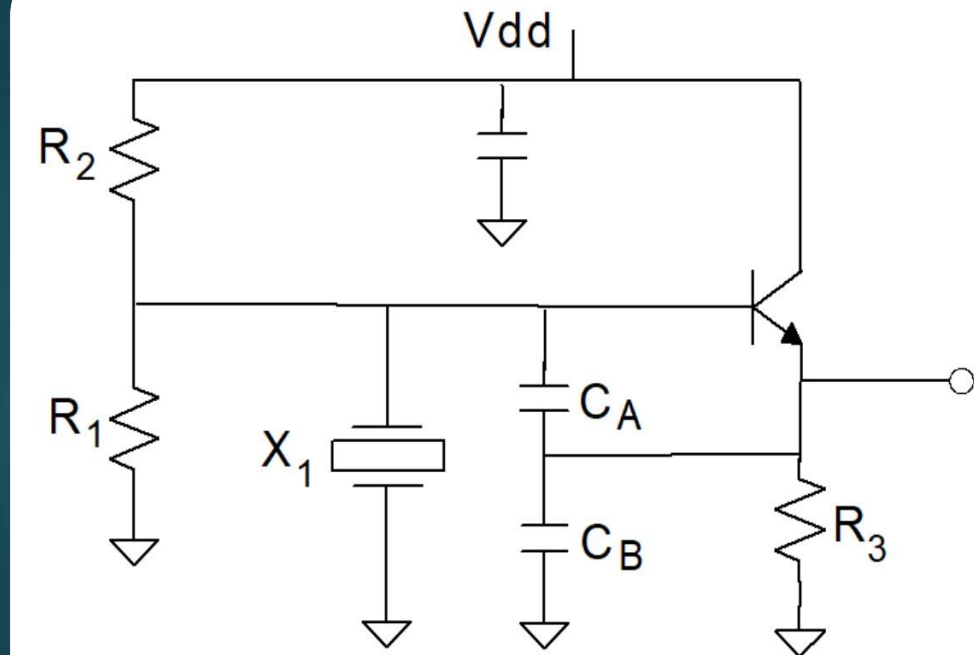

Crystal Reactance v/s Frequency

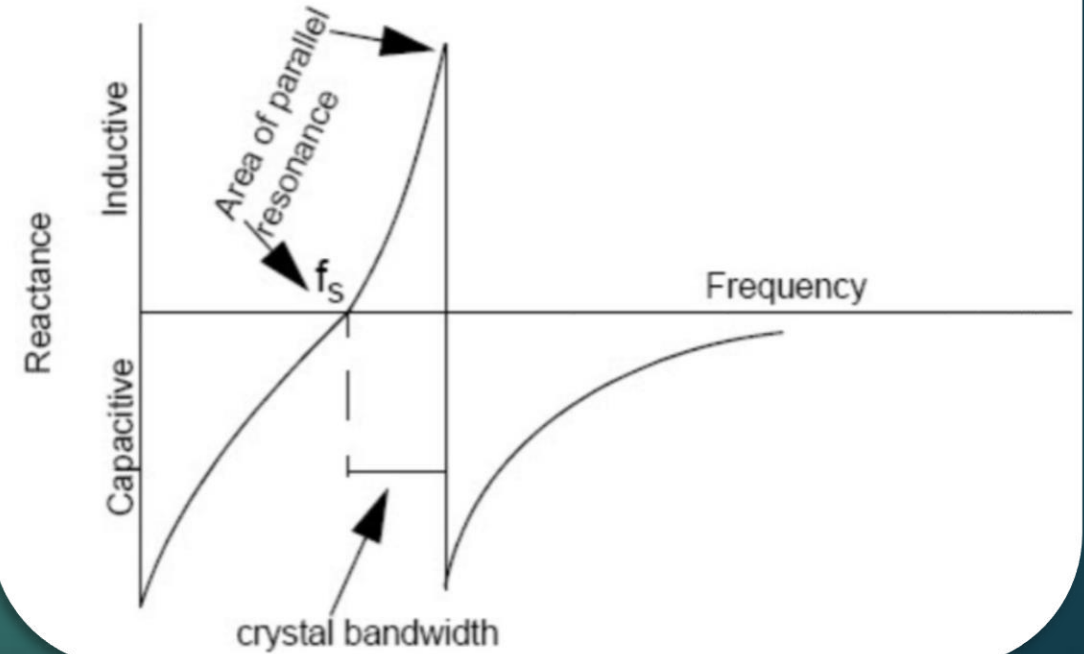

TCXOs

HCMOS OUTPUT SMD TCXO

ASTX-H11



ESD Sensitive



RoHS/RoHS II compliant



3.2 x 2.5 x 1.0mm

Moisture Sensitivity Level (MSL)-1

FEATURES:

- HCMOS Output
- Compact and low in height
- Low current consumption; IR reflow possible
- Suitable for high-density SMT

APPLICATIONS:

- Cellular and cordless phones
- Standard OSC for exact equipment
- Mobile communication equipment
- Portable radio equipment and music player

STANDARD SPECIFICATIONS:

Parameters	Minimum	Typical	Maximum	Units	Notes
Frequency Range	2.500		55.000	MHz	
Standard Frequencies	5, 10, 12, 16, 20, 24, 32, 40, 44			MHz	
Operating Temperature	-30		+75	°C	
Storage Temperature:	-40		+125	°C	
Frequency Stability $\Delta f/f_0$ vs Tolerance (@+25°C)	-2.0		+2.0		1 hr after reflow
vs Temperature (ref. to +25°C)	-2.5		+2.5		See option (Table 1)

Fully Integrated Transceiver



Si4430/31/32-B1

Si4430/31/32 ISM TRANSCEIVER

Features

- Frequency Range
 - 240–930 MHz (Si4431/32)
 - 900–960 MHz (Si4430)
- Sensitivity = -121 dBm
- Output power range
 - +20 dBm Max (Si4432)
 - +13 dBm Max (Si4430/31)
- Low Power Consumption
 - 18.5 mA receive
 - 30 mA @ +13 dBm transmit
 - 85 mA @ +20 dBm transmit
- Data Rate = 0.123 to 256 kbps
- FSK, GFSK, and OOK modulation
- Power Supply = 1.8 to 3.6 V
- Ultra low power shutdown mode
- Digital RSSI
- Wake-up timer
- Auto-frequency calibration (AFC)
- Power-on-reset (POR)
- Antenna diversity and TR switch control
- Configurable packet handler
- Preamble detector
- TX and RX 64 byte FIFOs
- Low battery detector
- Temperature sensor and 8-bit ADC
- -40 to +85 °C temperature range
- Integrated voltage regulators
- Frequency hopping capability
- On-chip crystal tuning
- 20-Pin QFN package
- Low BOM

Applications

- Remote control
- Home security & alarm
- Telemetry
- Personal data logging
- Toy control
- Tire pressure monitoring
- Wireless PC peripherals
- Remote meter reading
- Remote keyless entry
- Home automation
- Industrial control
- Sensor networks
- Health monitors
- Tag readers


Description

Silicon Laboratories' Si4430/31/32 devices are highly integrated, single chip wireless ISM transceivers. The high-performance EZRadioPRO® family includes a complete line of transmitters, receivers, and transceivers allowing the RF system designer to choose the optimal wireless part for their application.



Ordering Information:
See page 67.


Pin Assignments

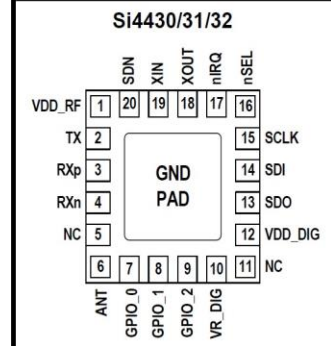

Patents pending

Si4430/31/32-B1


Functional Block Diagram

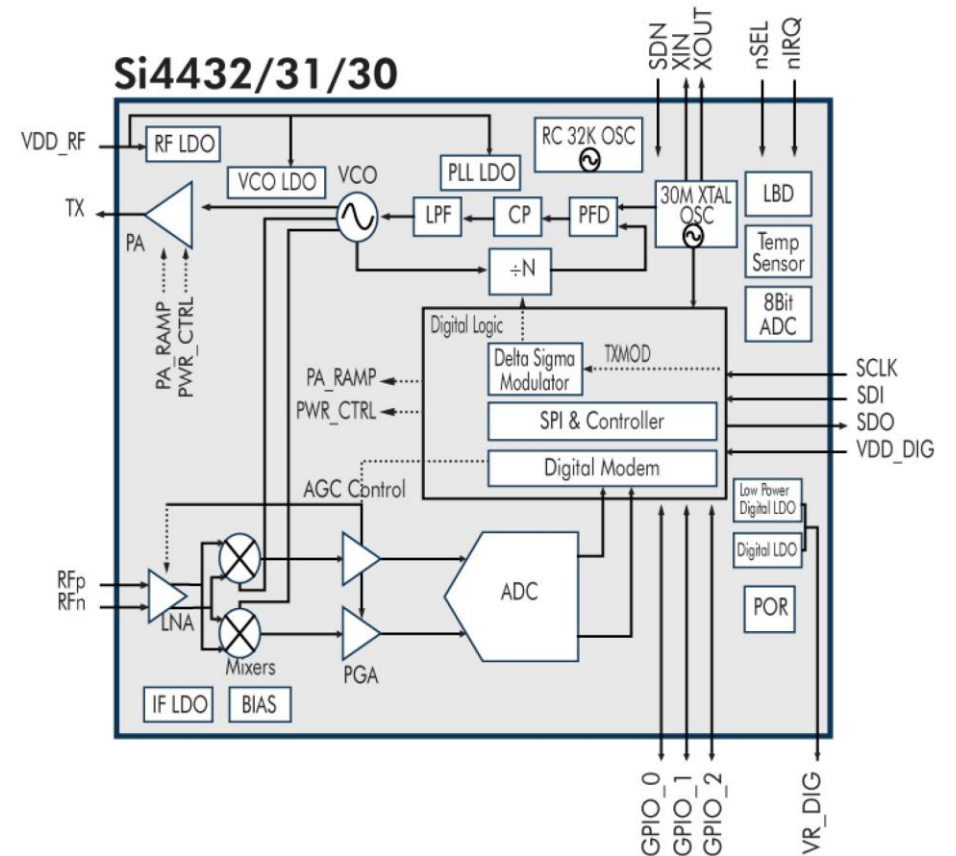



Phase-Locked Loop Synthesizer

$$f_{out} = N f_{ref}$$

“Fractional-N”
Architecture

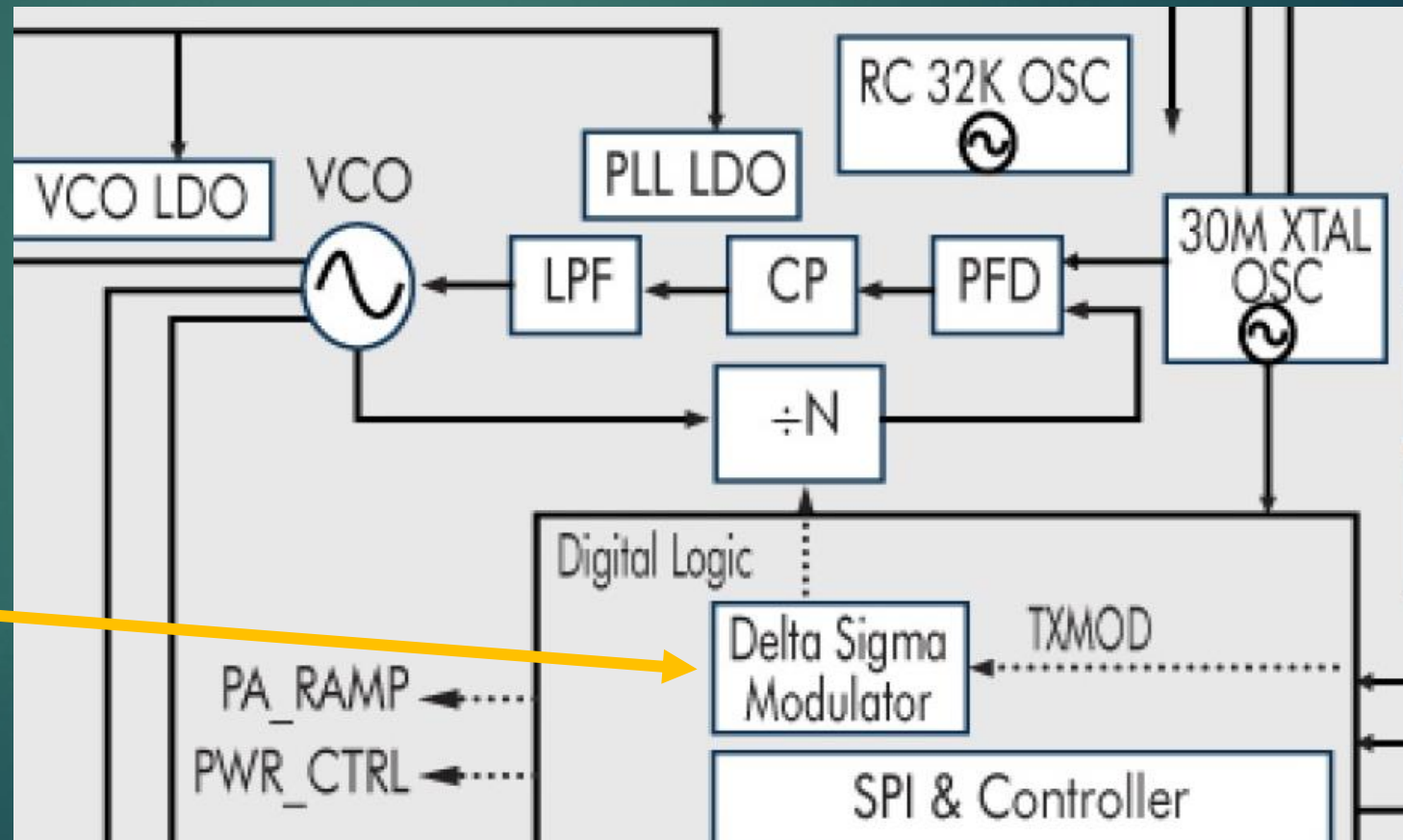

Class FM Receiver Synthesizer

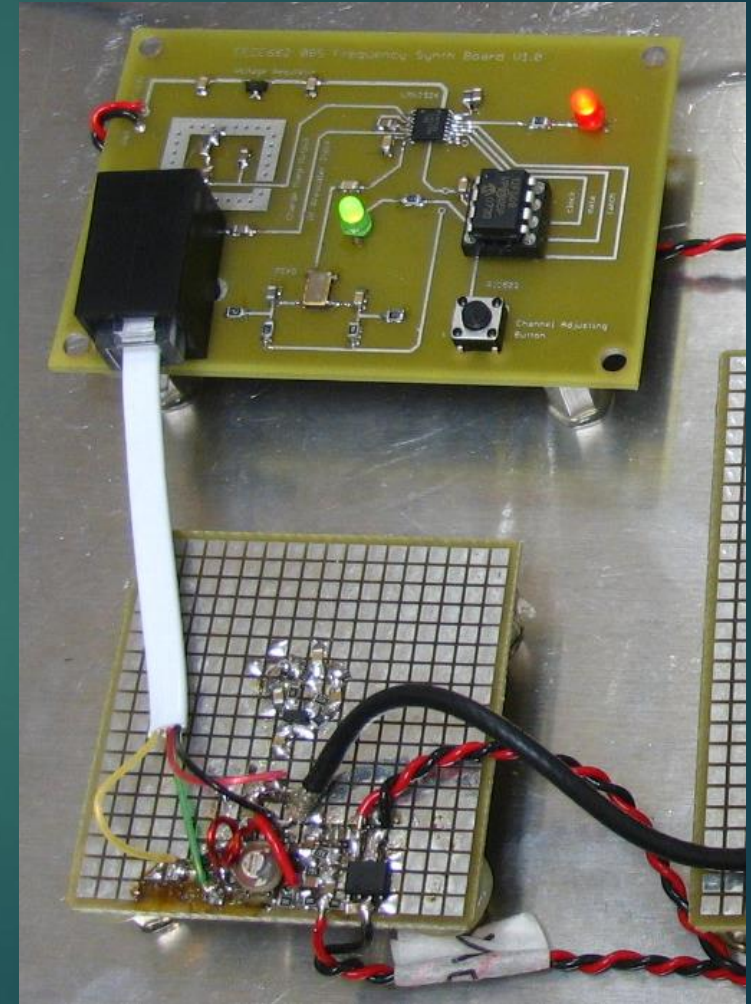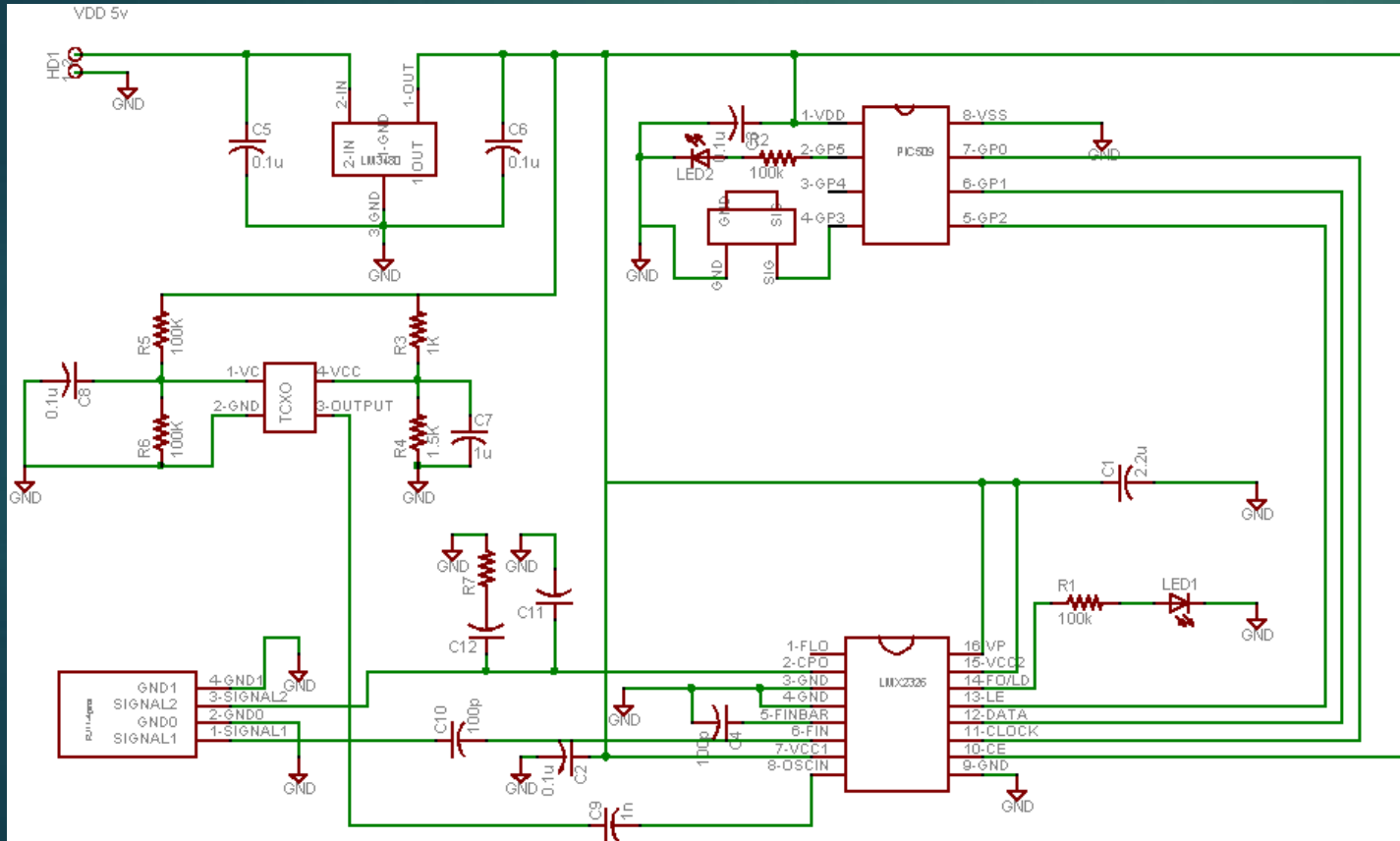

Topic Review

- *LC Oscillator Basics*
- *Hartley and Colpitts circuits*
- *Voltage Controlled Oscillators*
- *Crystal Oscillators and Synthesizers*

Radio Design 101 “Semester Projects”



Radio Design 101 - Episode 3 - Amplifi...
A relatively complete discussion of amplifier circuits, including the electroni...



Radio Design 101 - Episode 2 - Impeda...
Impedance Matching networks. This is the second half of episode 2 in the Radi...



Radio Design 101 - Episode 2 - Impeda...
Impedance Matching networks. This is episode 2 in the Radio Design 101 series...




Radio Design 101 - Episode 1 - Transc...
This video covers the design of bandpass filters, including the concept of quality...




Radio Design 101 - Episode 1 - Transc...
This video overviews radio / wireless transmitters and receivers, circuit...



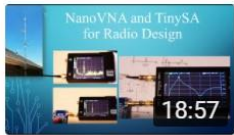
NanoVNA - Antennas and Tuners
Using the NanoVNA to illustrate the operation of antennas and antenna...



NanoVNA and TinySA for Radio Design
Using the NanoVNA and TinySA to illustrate how radio / wireless devices...

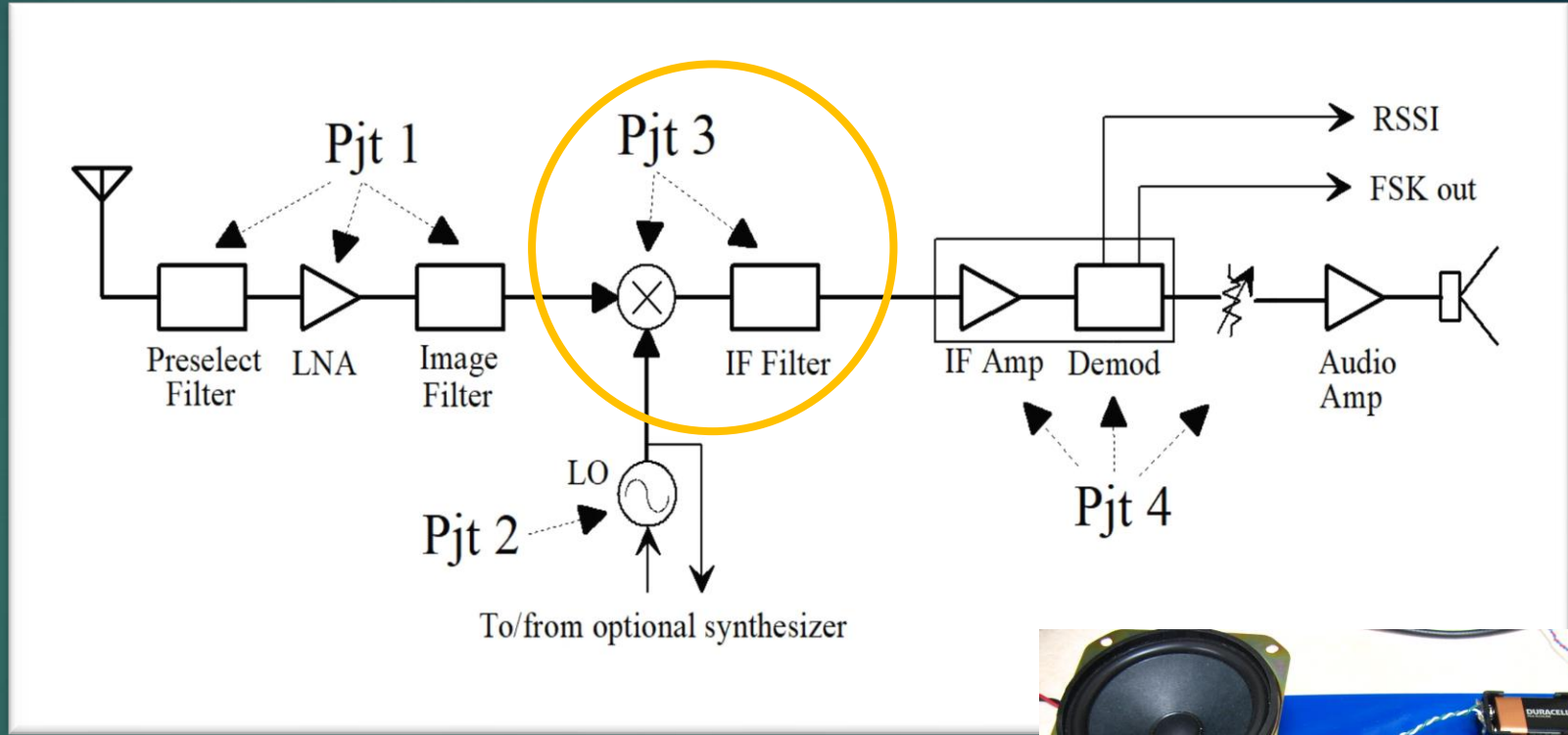

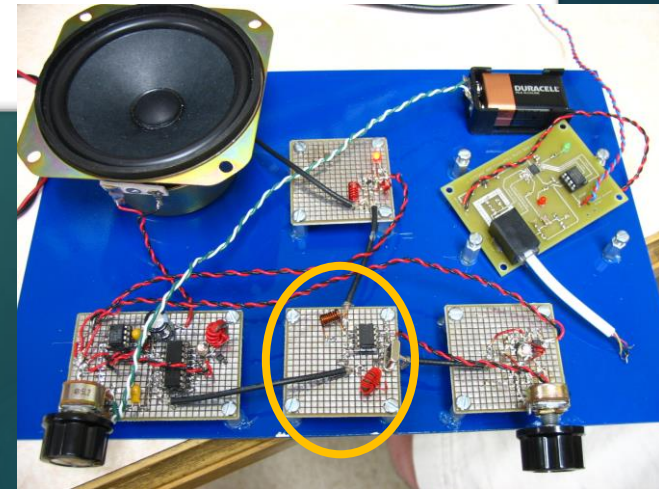Project 3 – Mixer / IF Filter (Next Video)





*Thanks For
Watching !*