

# Radio Design 101



## Episode 6 – Finishing the Receiver

Slides downloaded from: <https://ecefiles.org/rf-design/>

Companion video at: <https://www.youtube.com/watch?v=jwbYQUTUEmE>

This material is [provided by ecefiles.org](https://ecefiles.org) for educational use only.



In this episode we finish the receiver design by creating an IF amplifier and demodulator, and then assemble and demonstrate the final product. A limiting IF amplifier is used to address the 100 dB dynamic range of signals typical at a receiver's antenna input. The demod is a classic quadrature architecture that uses a mixer and phase shifter, and leverages what we learned in episode 5. Details of design, construction, and testing are presented, together with comments on how the overall Radio Design 101 course material is applicable to virtually all radio design work, including modern RF integrated circuits.

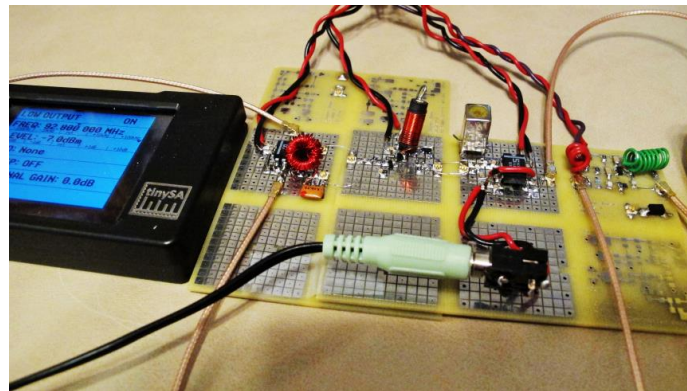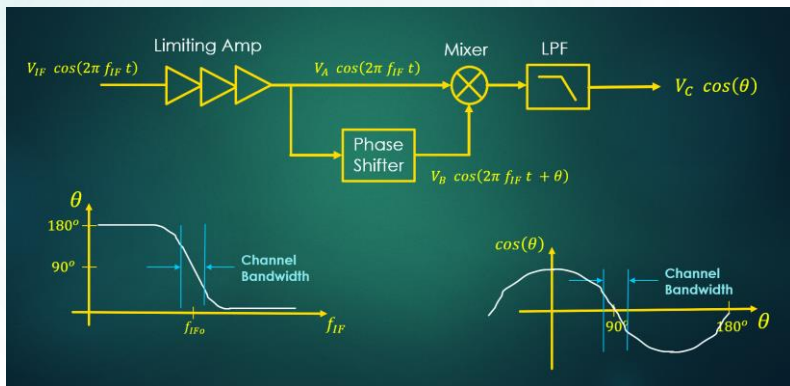


# *Radio Design 101*

## *Episode 6*


# *Finishing the Receiver*

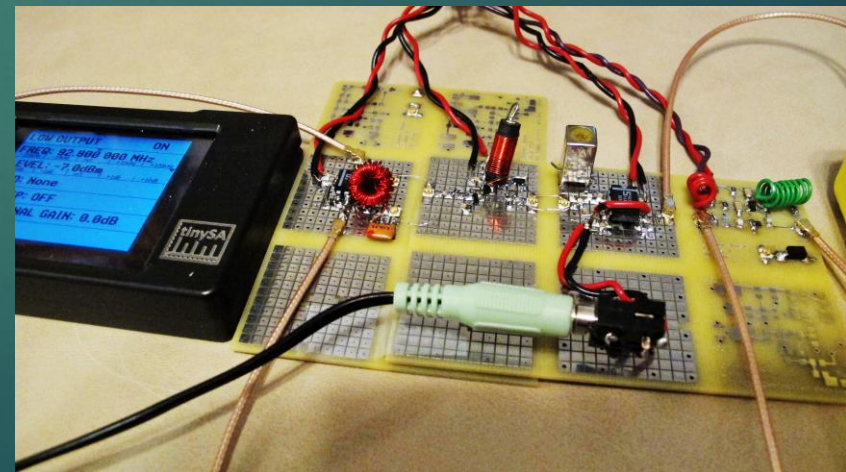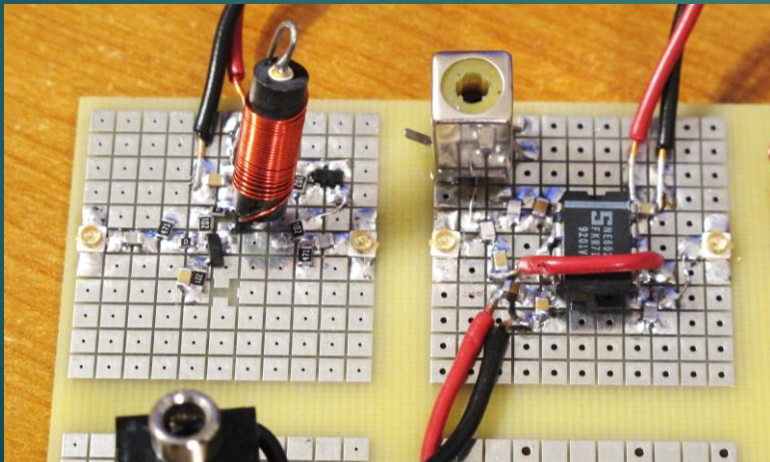

# Class Projects

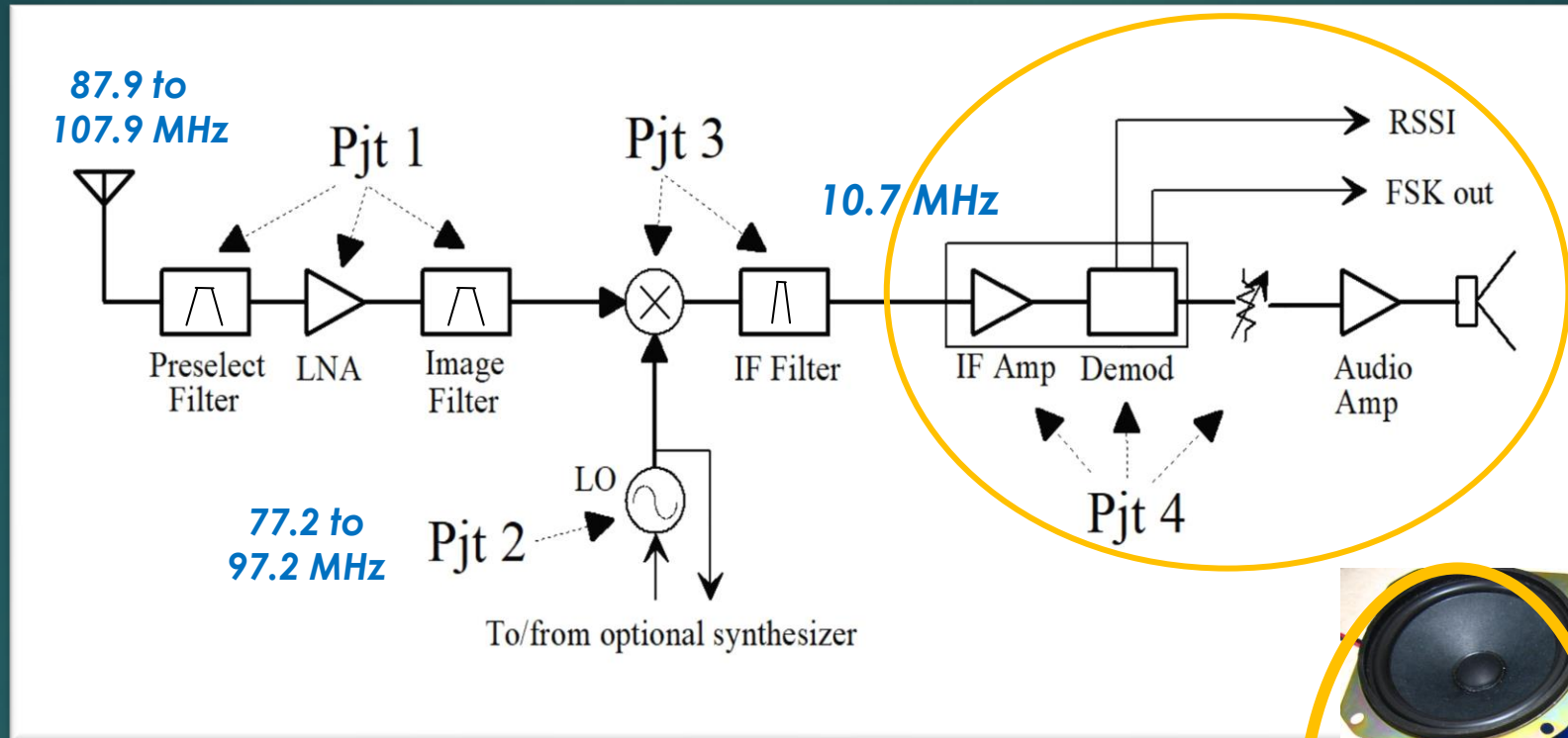

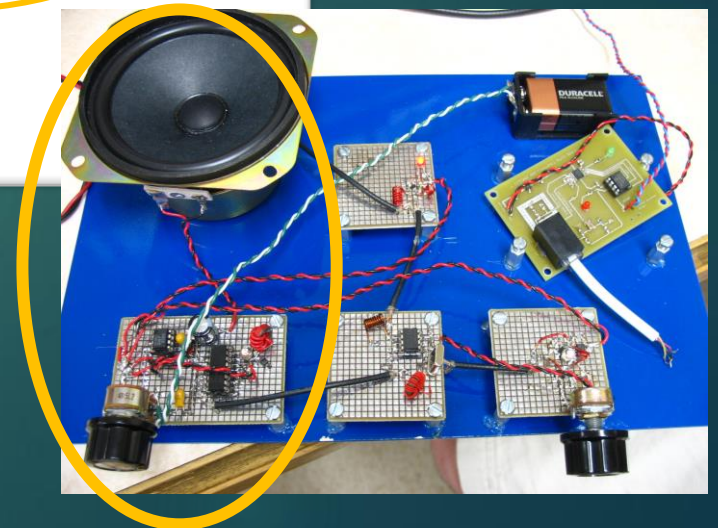**Pjt 4: IF Amplifier, Demod/Audio  
(This Episode)**




# *Debugging => Learning and Success*




# Today's Topics

- *Superhet receiver architecture review*
- *IF limiting amplifier design*
- *Quadrature FM demod*
- *Receiver assembly and demonstration*
- *Modern radio chipsets*

# Superhet Receiver Spectrums

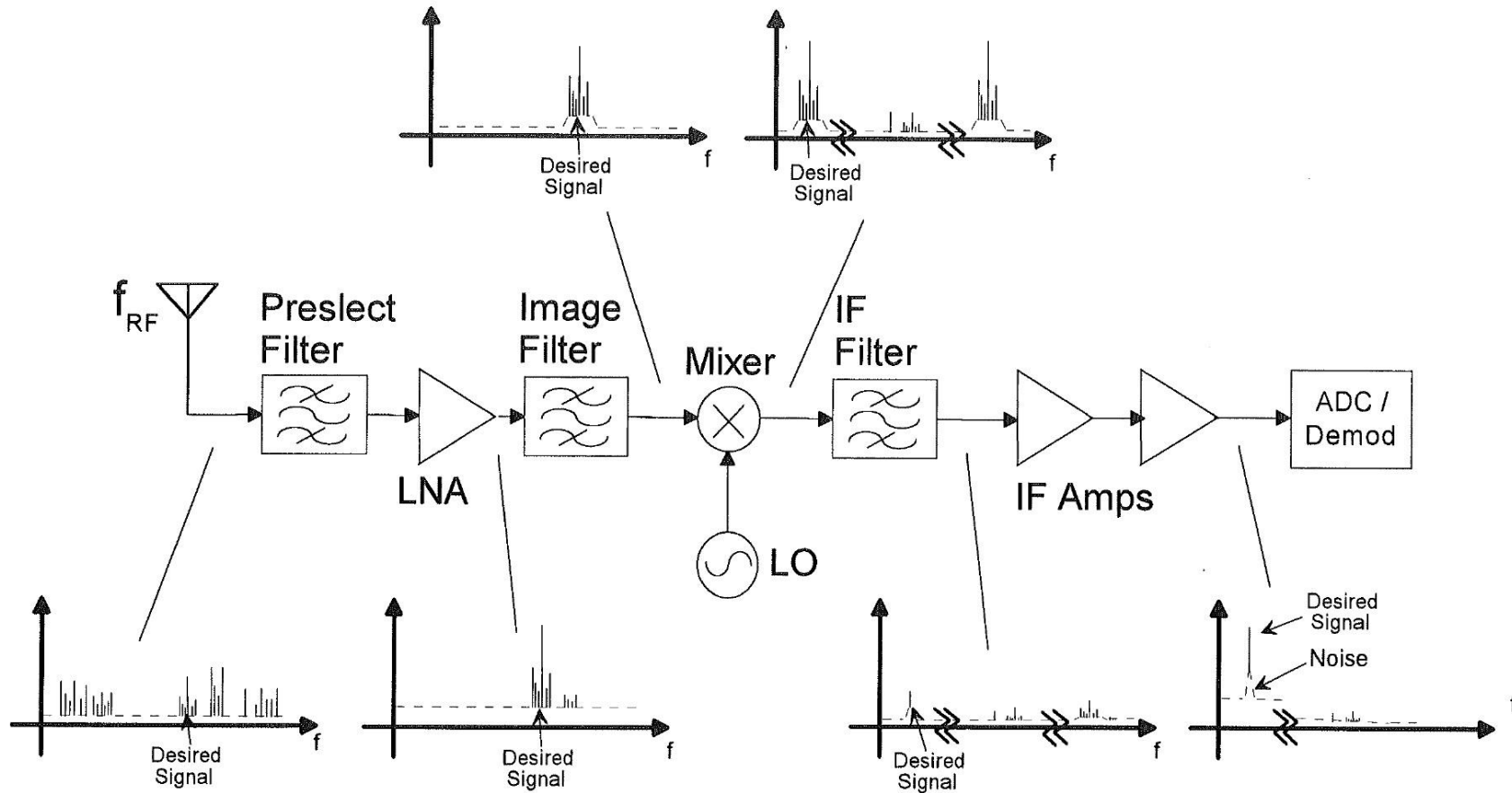

# Signal Levels and IF Amp Gain

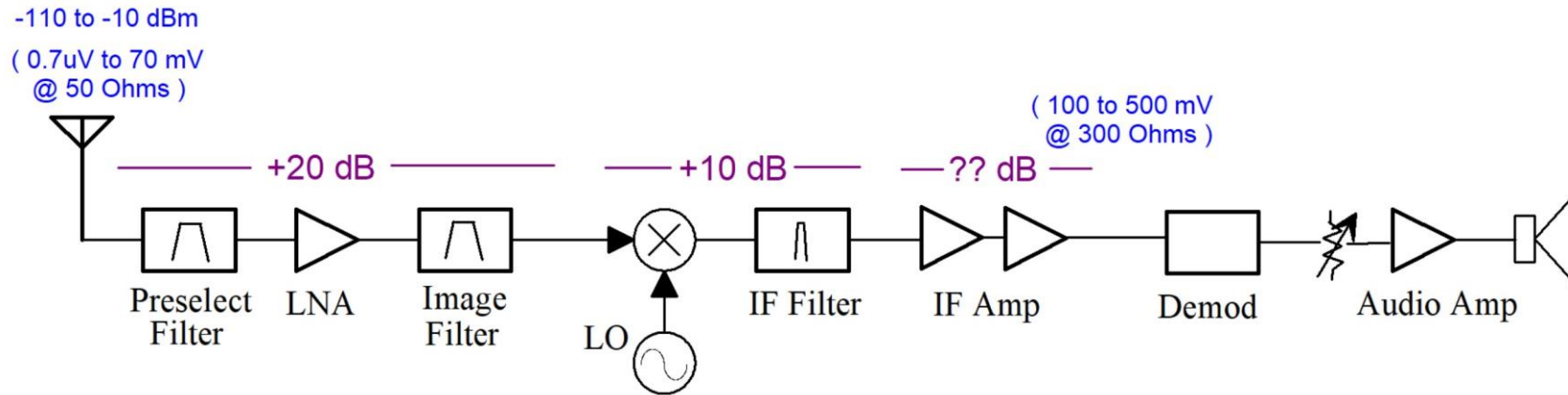

**Minimum IF Amplifier gain needed (with this frontend):**


$$20 \log_{10} \left( \frac{100 \text{ mV}}{0.7 \text{ uV}} \right) - 20 - 10 - 20 \log_{10} \left( \sqrt{\frac{300}{50}} \right) = \underline{\underline{65 \text{ dB}}}$$

# Episode 6 Topics

- *Superhet receiver architecture review*
- *IF limiting amplifier design*
- *Quadrature FM demod*
- *Receiver assembly and demonstration*
- *Modern radio chipsets*





# IF Amp Design and AC Sim

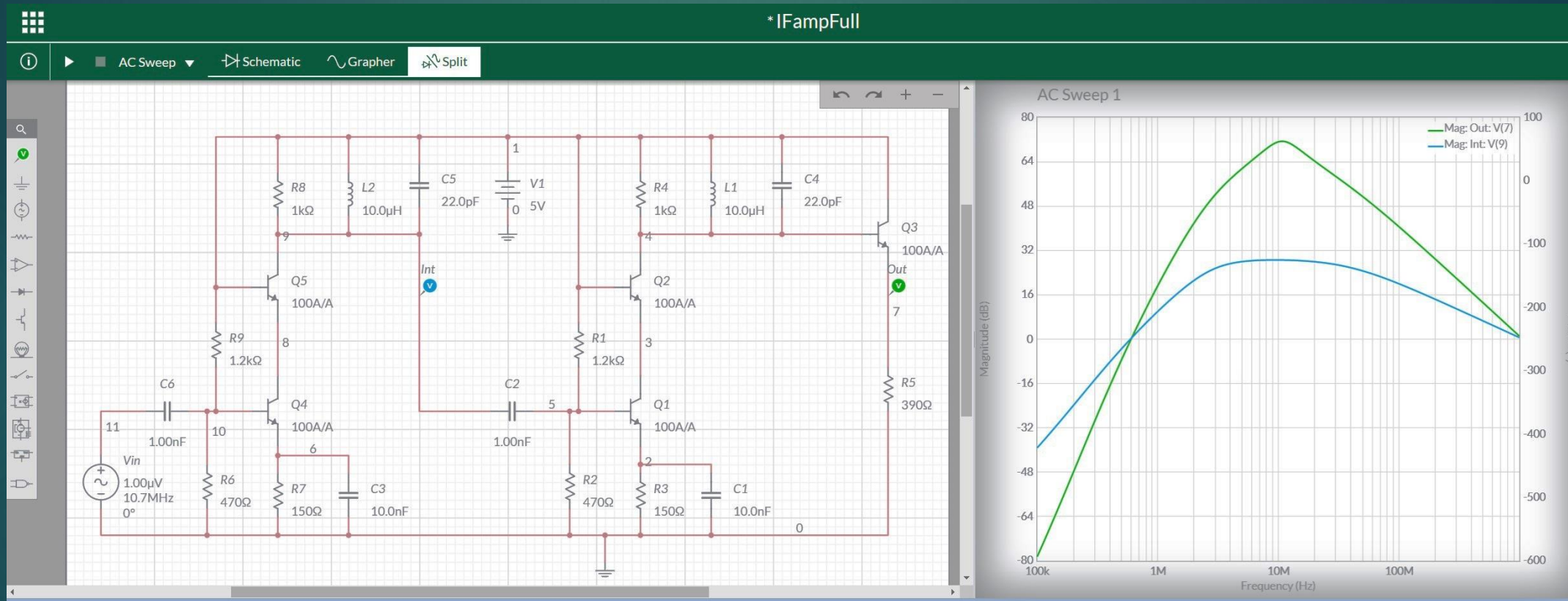


Drawn and simulated with free version of National Instruments' "**Multisim Live**" web-based tool

# Transient Analysis and Limiting

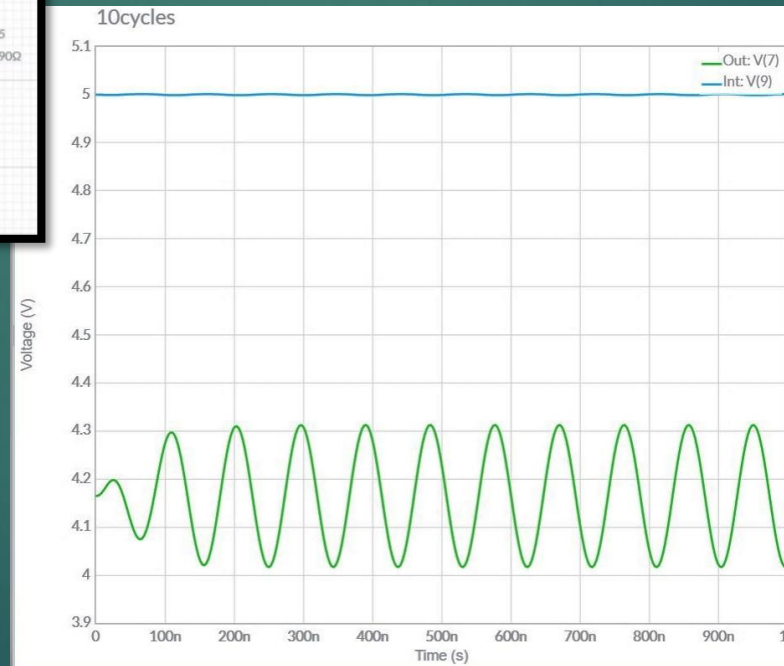
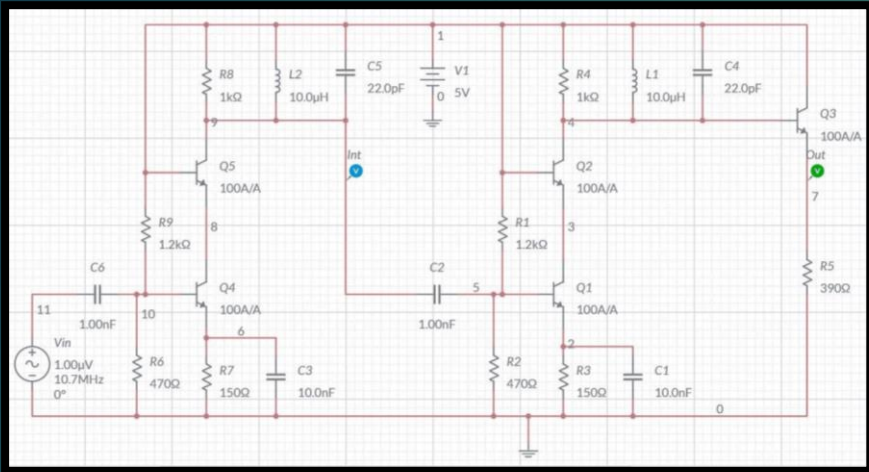


40  $\mu\text{V}$  Input

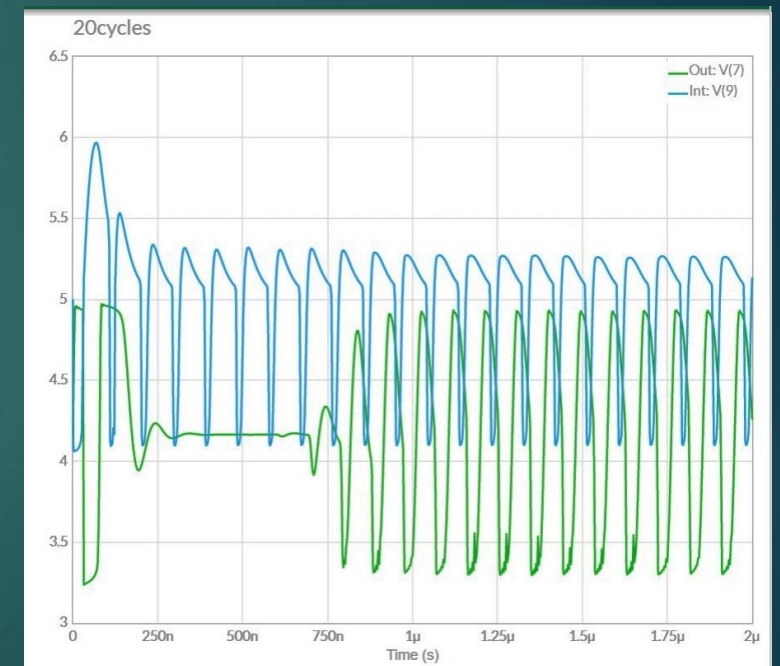


1.0 V Input

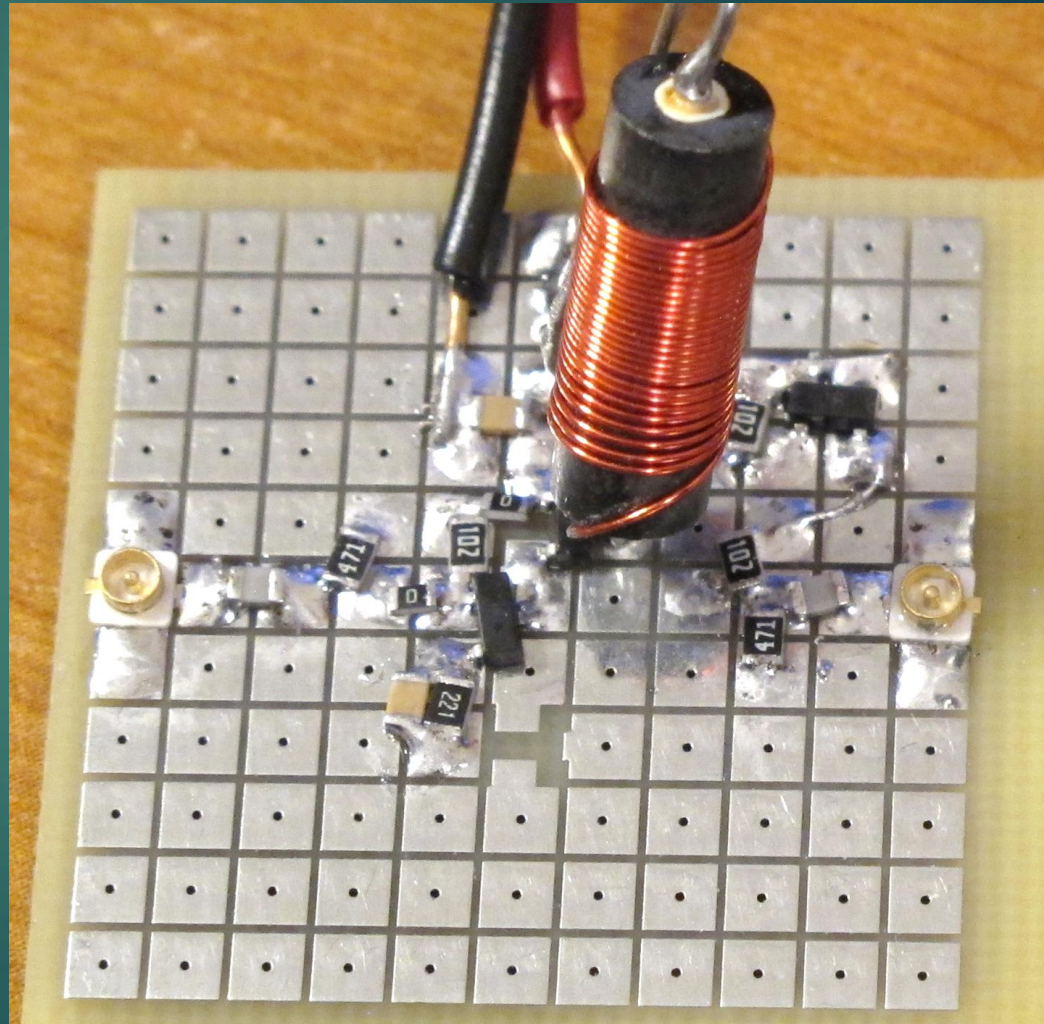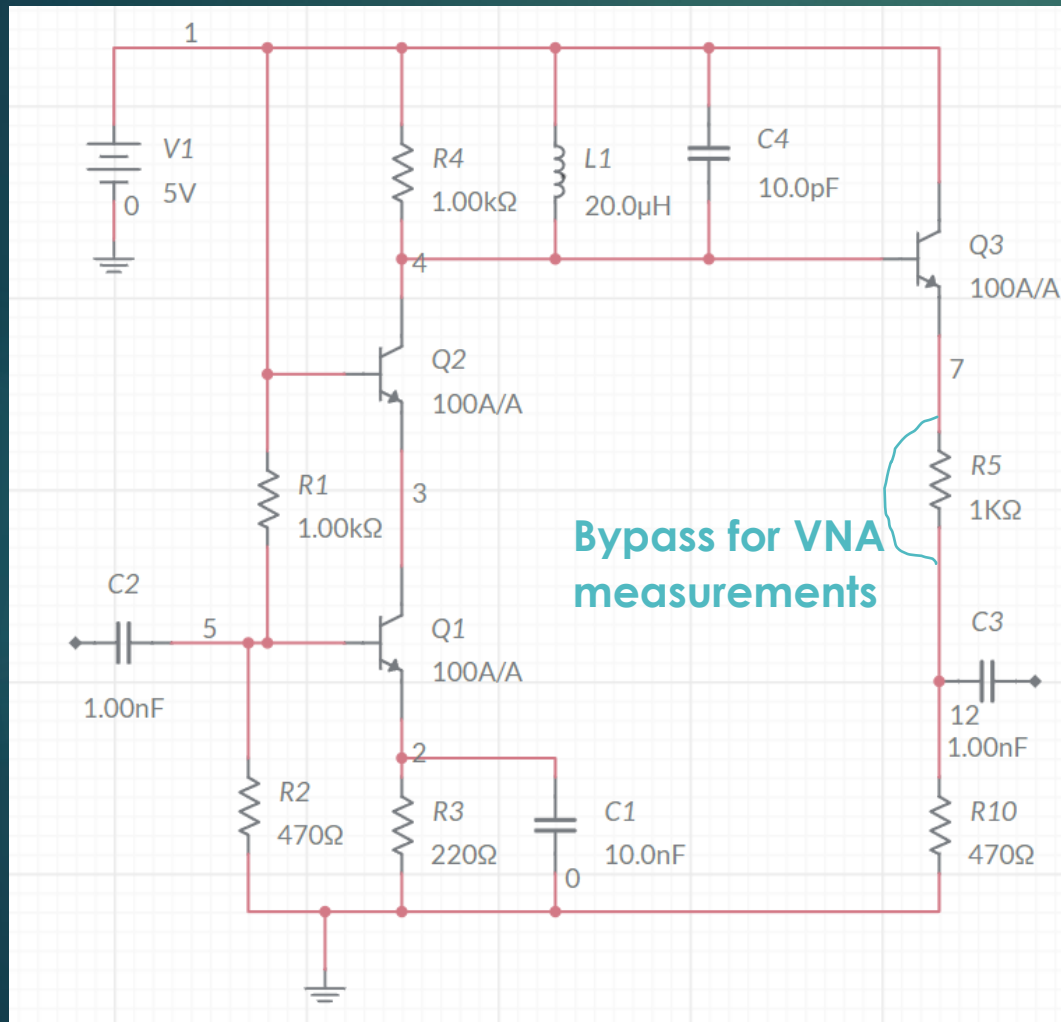
# Construction (2<sup>nd</sup> Stage Only)



# Testing

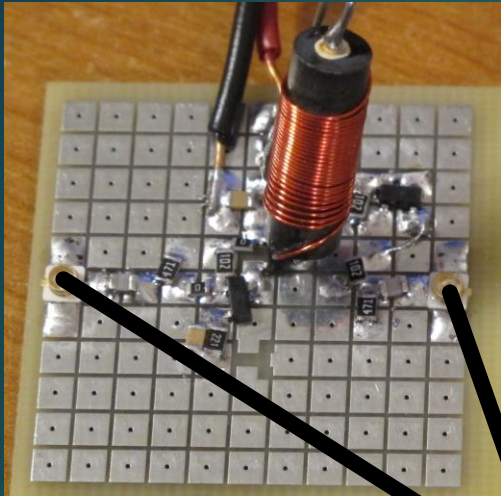


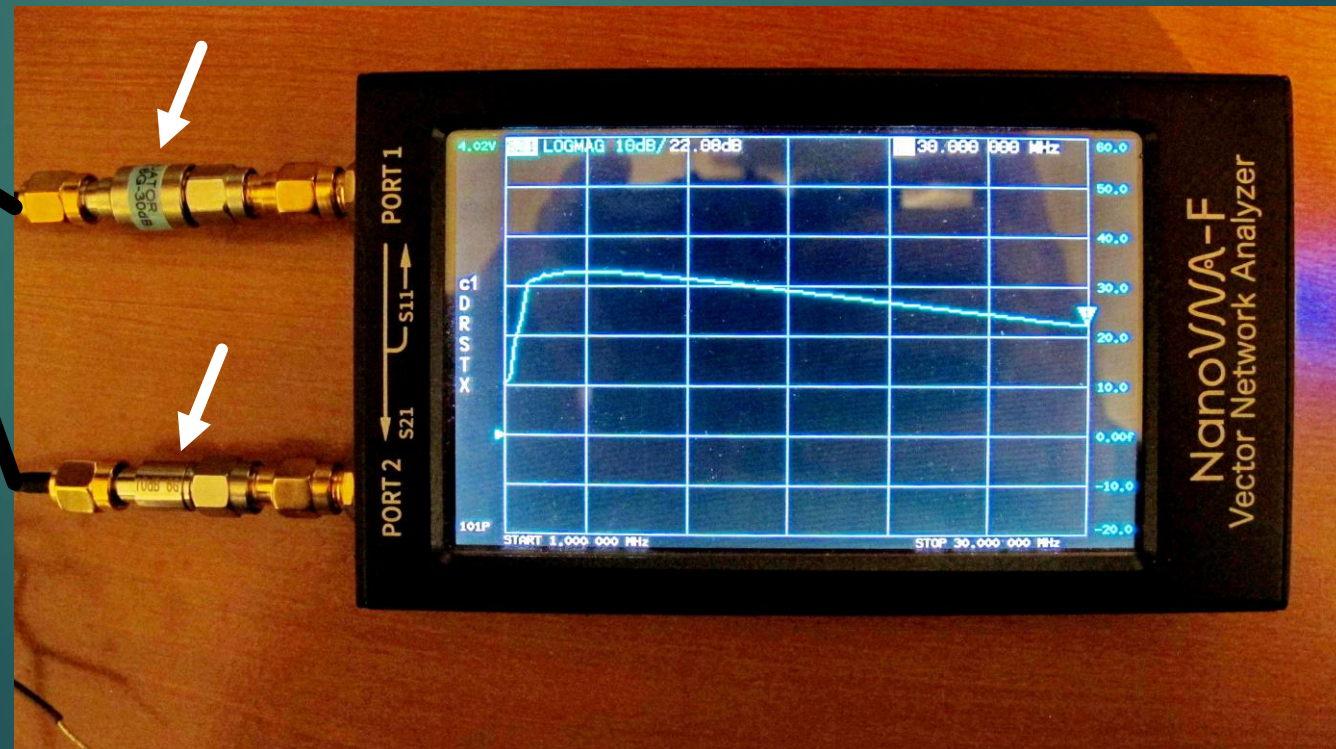- 30 dB and 10 dB attenuators on ports 1 and 2 respectively
- Calibrated with these in place
- R5 bypassed for testing (due to 50 Ohm Rin of VNA)
- 32 dB gain at 10.7 MHz (low due to limiting)


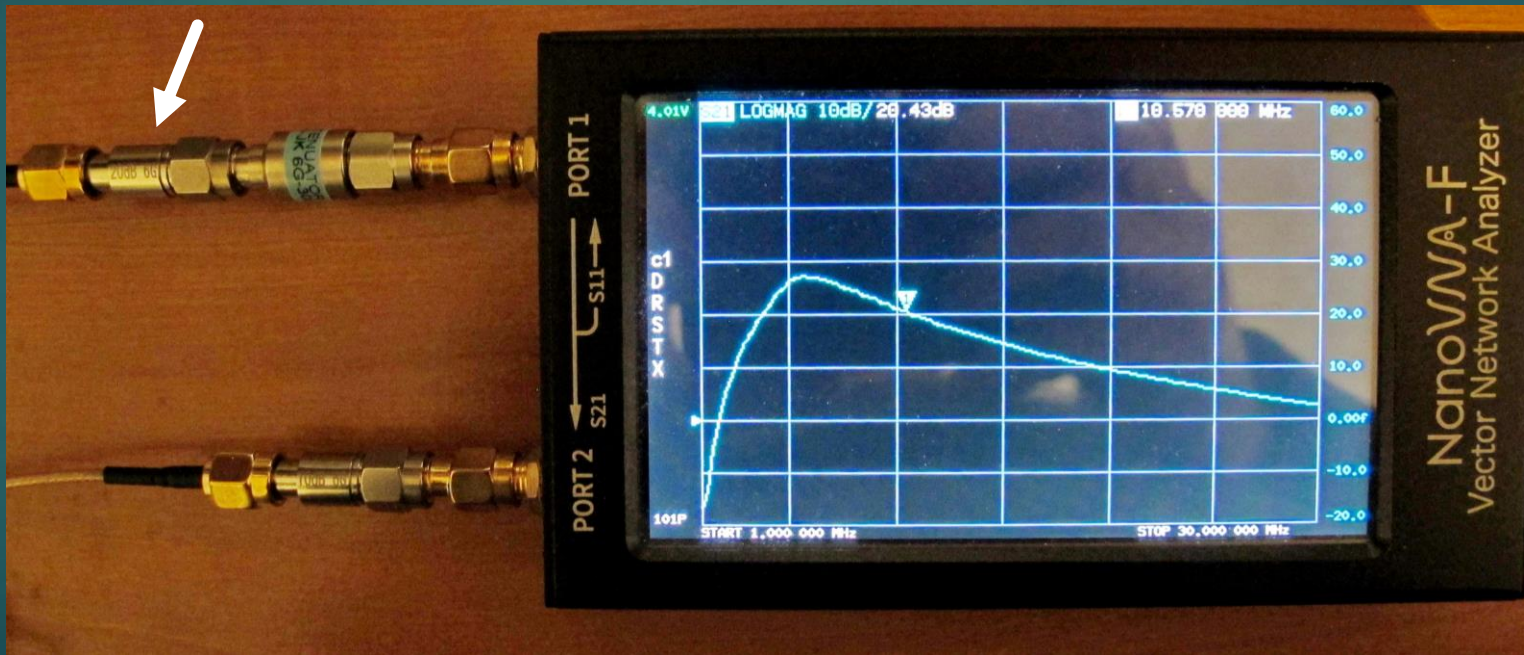
# Testing (2<sup>nd</sup> Stage Only)




- Added extra 20 dB attenuator to port 1, but did NOT recalibrate
- So, displayed gain is 20 dB lower than actual
- No gain compression this time ☺
- **40 dB gain at 10.7 MHz. 46 dB at 6 MHz**
- Needs some tweaking, and/or addition of first IF amp stage ...




# Episode 6 Topics

- *Superhet receiver architecture review*
- *IF limiting amplifier design*
- *Quadrature FM demod*
- *Receiver assembly and demonstration*
- *Modern radio chipsets*

# Classic FM Quadrature Subsystem

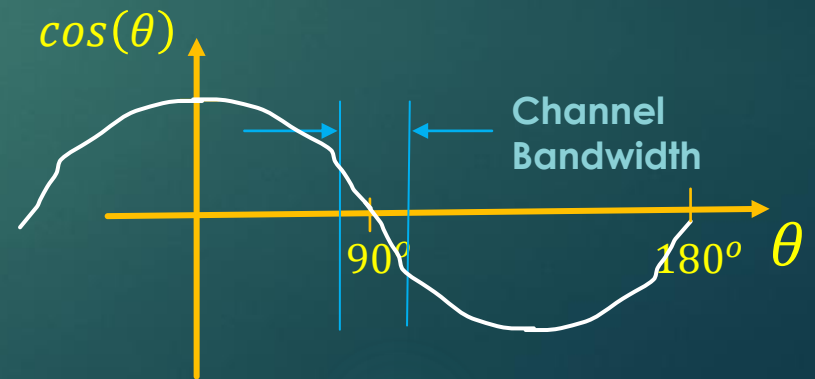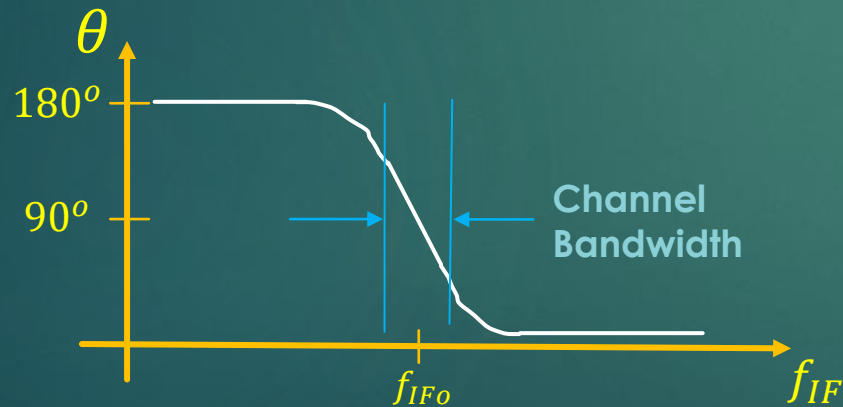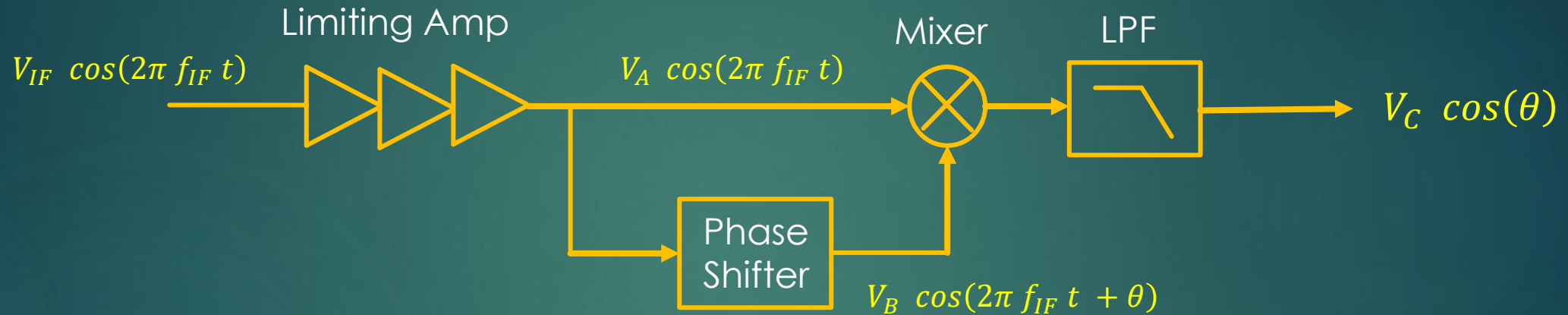


# Phase Shifter Network

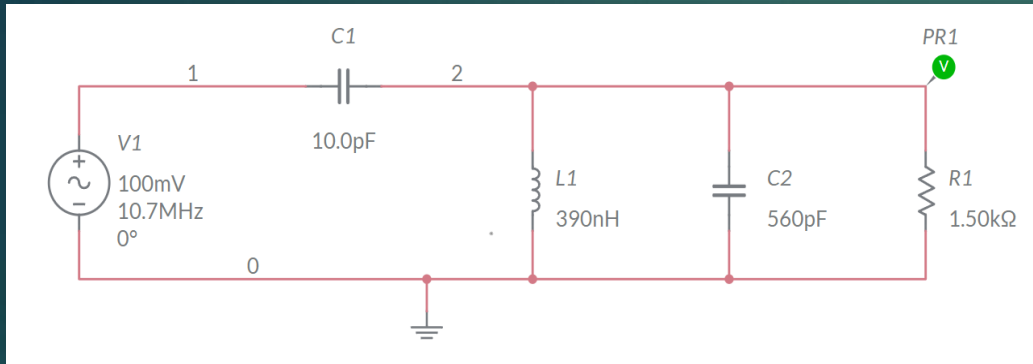

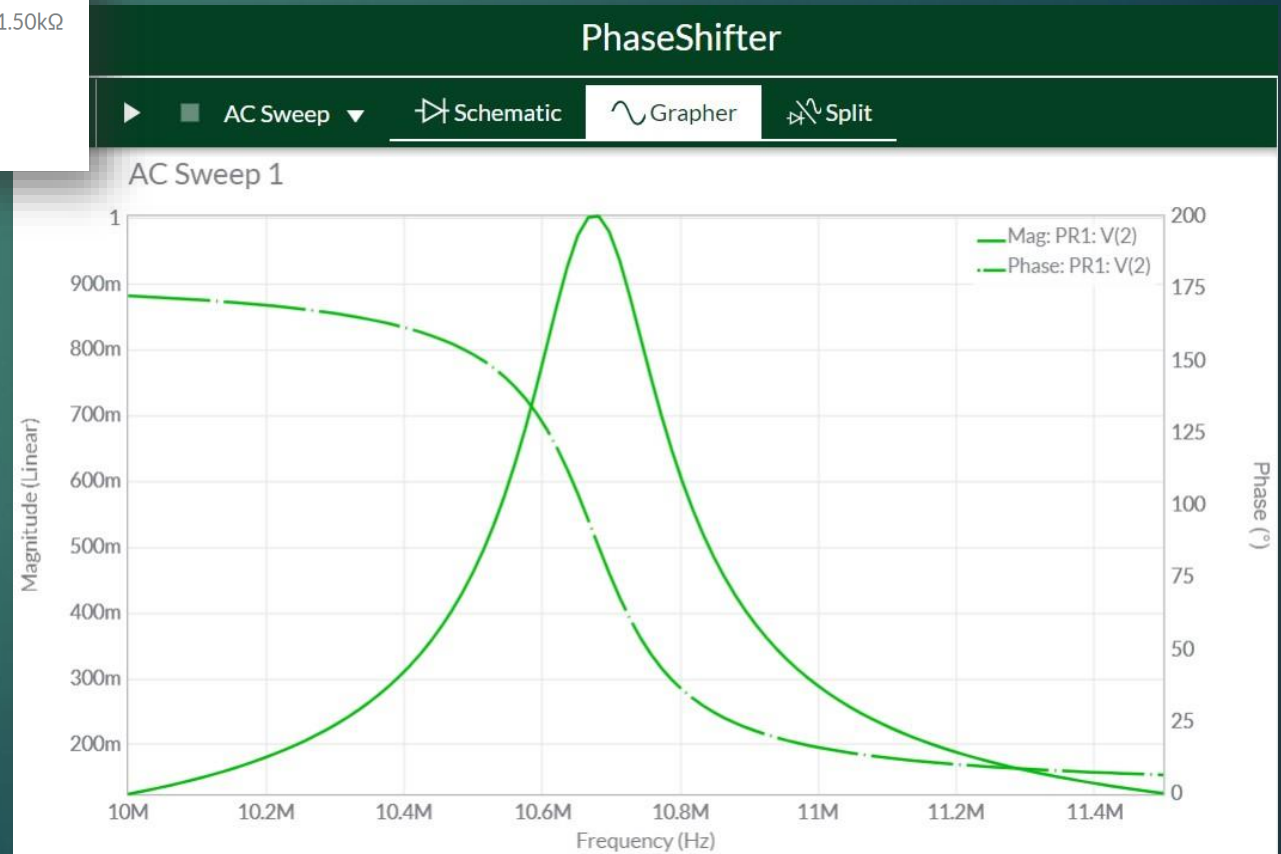
## Analysis / Design:

- Use Norton equivalent for V1, C1 to understand behavior vs frequency
- Consider Q of L1 when making real-world circuits
- R1 is input R of mixer (together with parallel-form parasitic R of L1 and any physical resistor used)
- Q is high, so requires good quality inductor and alignment after build







# Demod Schematic Design

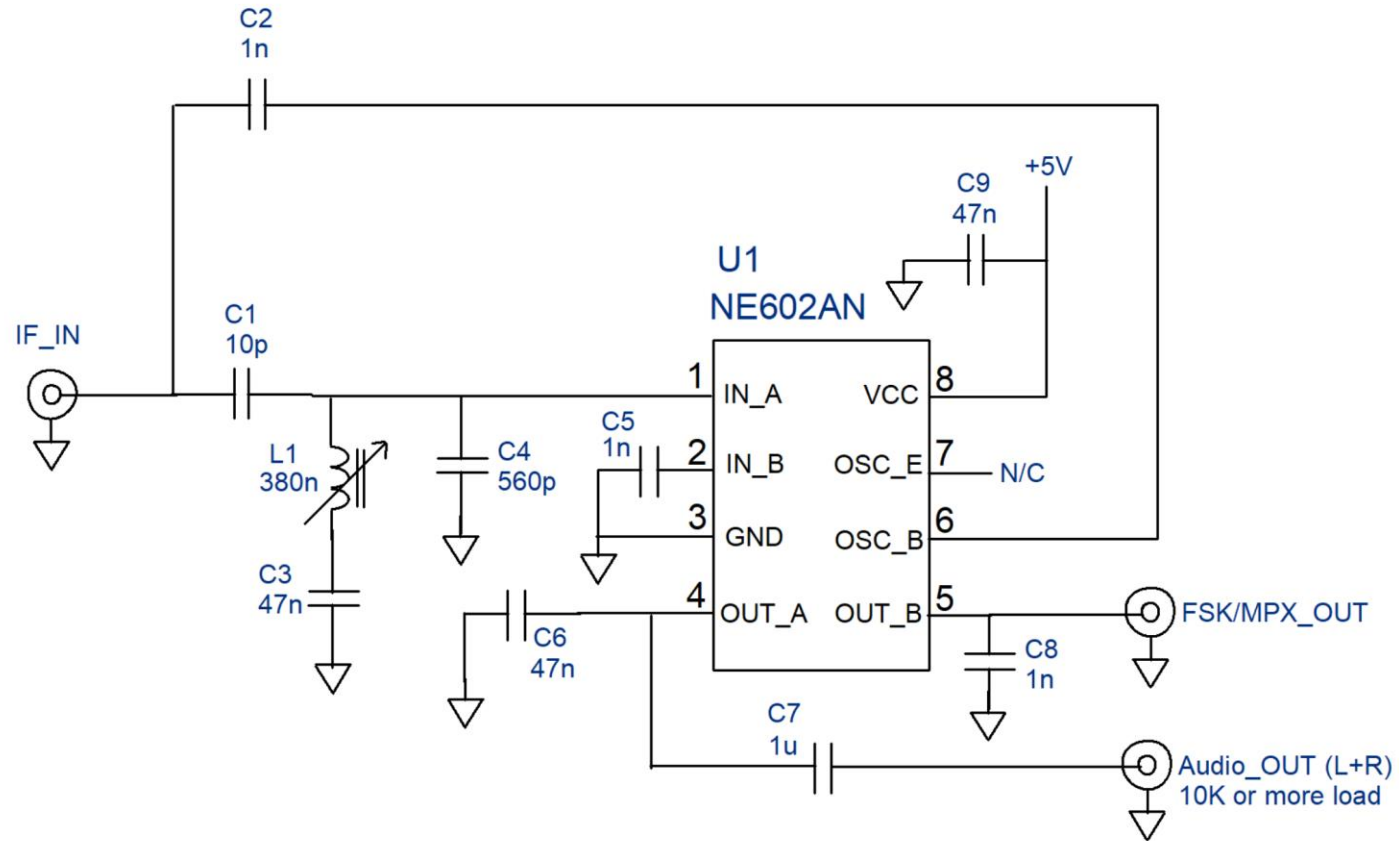

# Construction

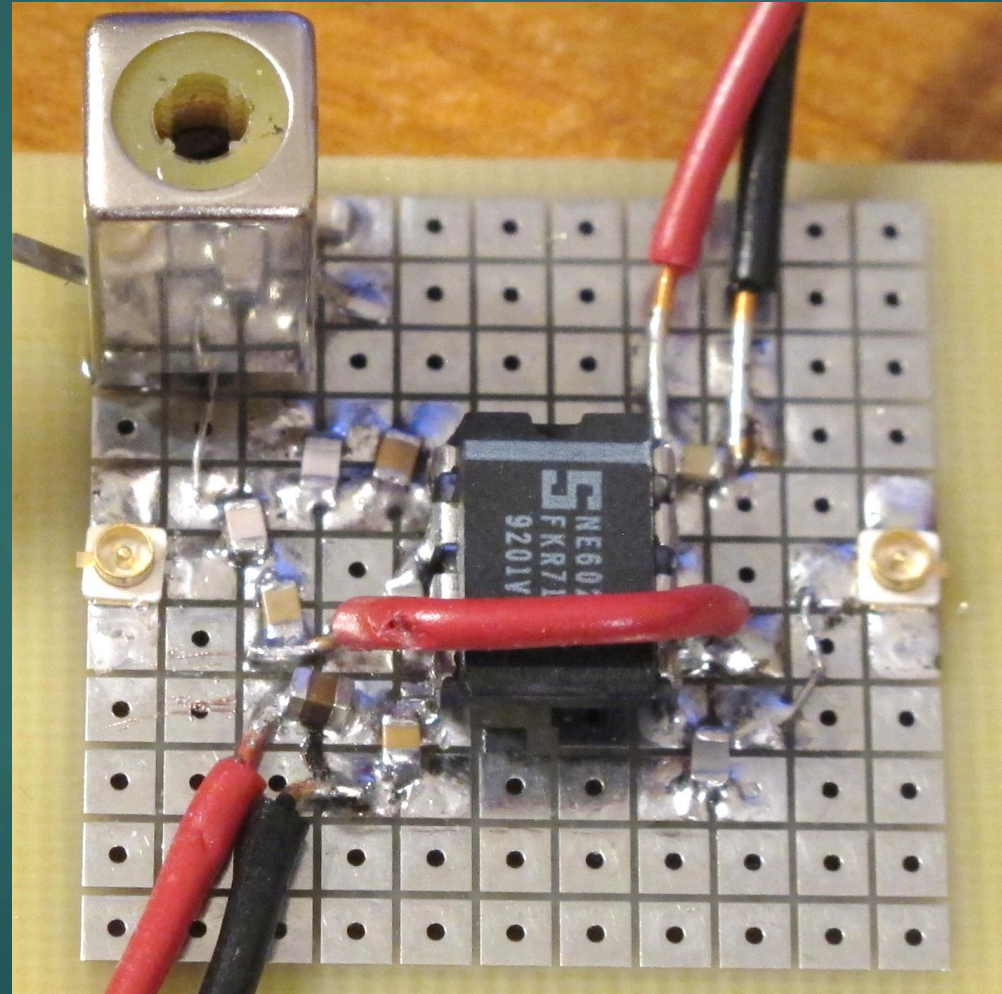


# Testing

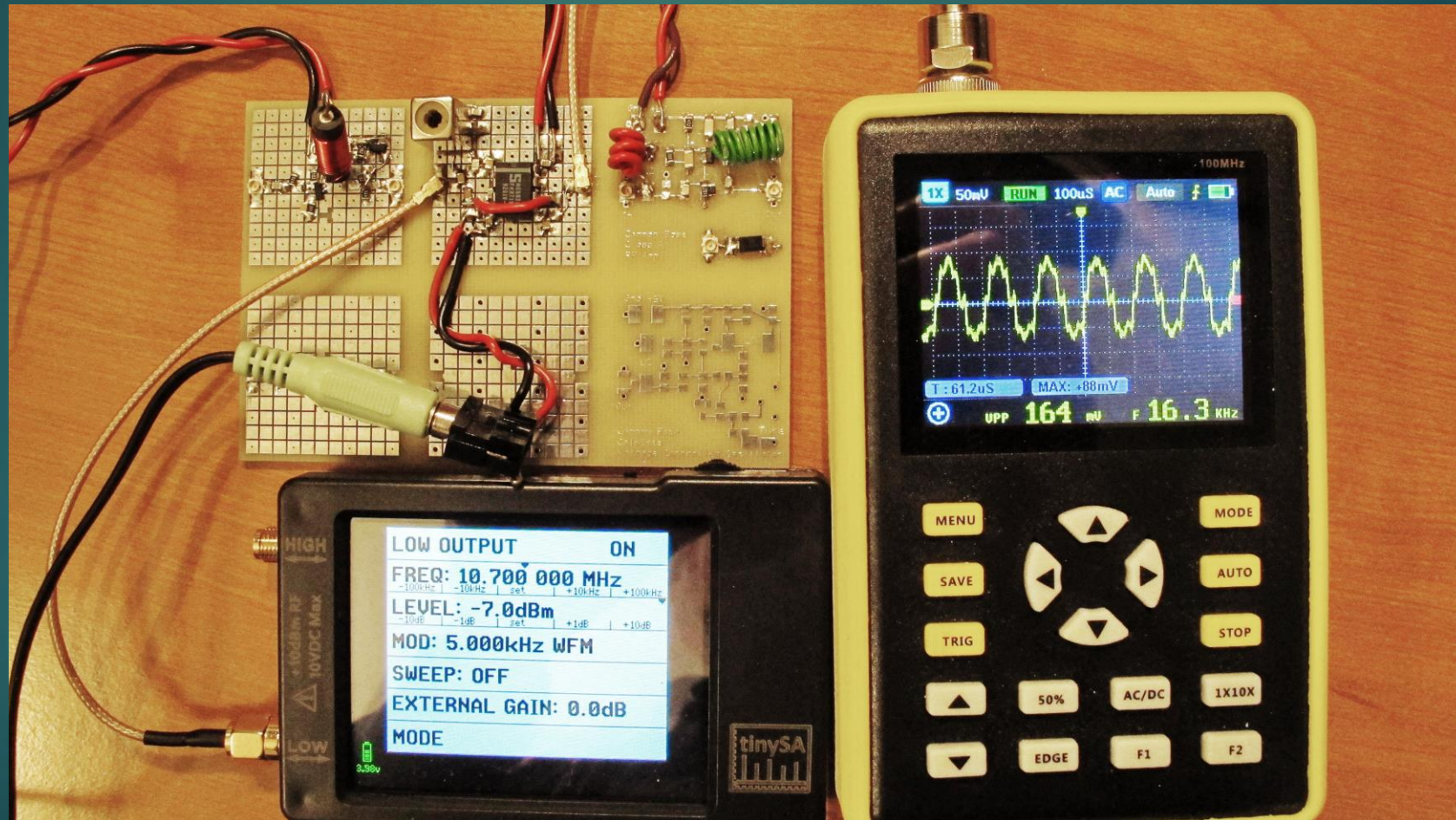


# Episode 6 Topics

- *Superhet receiver architecture review*
- *IF limiting amplifier design*
- *Quadrature FM demod*
- *Receiver assembly and demonstration*
- *Modern radio chipsets*


# Final Assembly

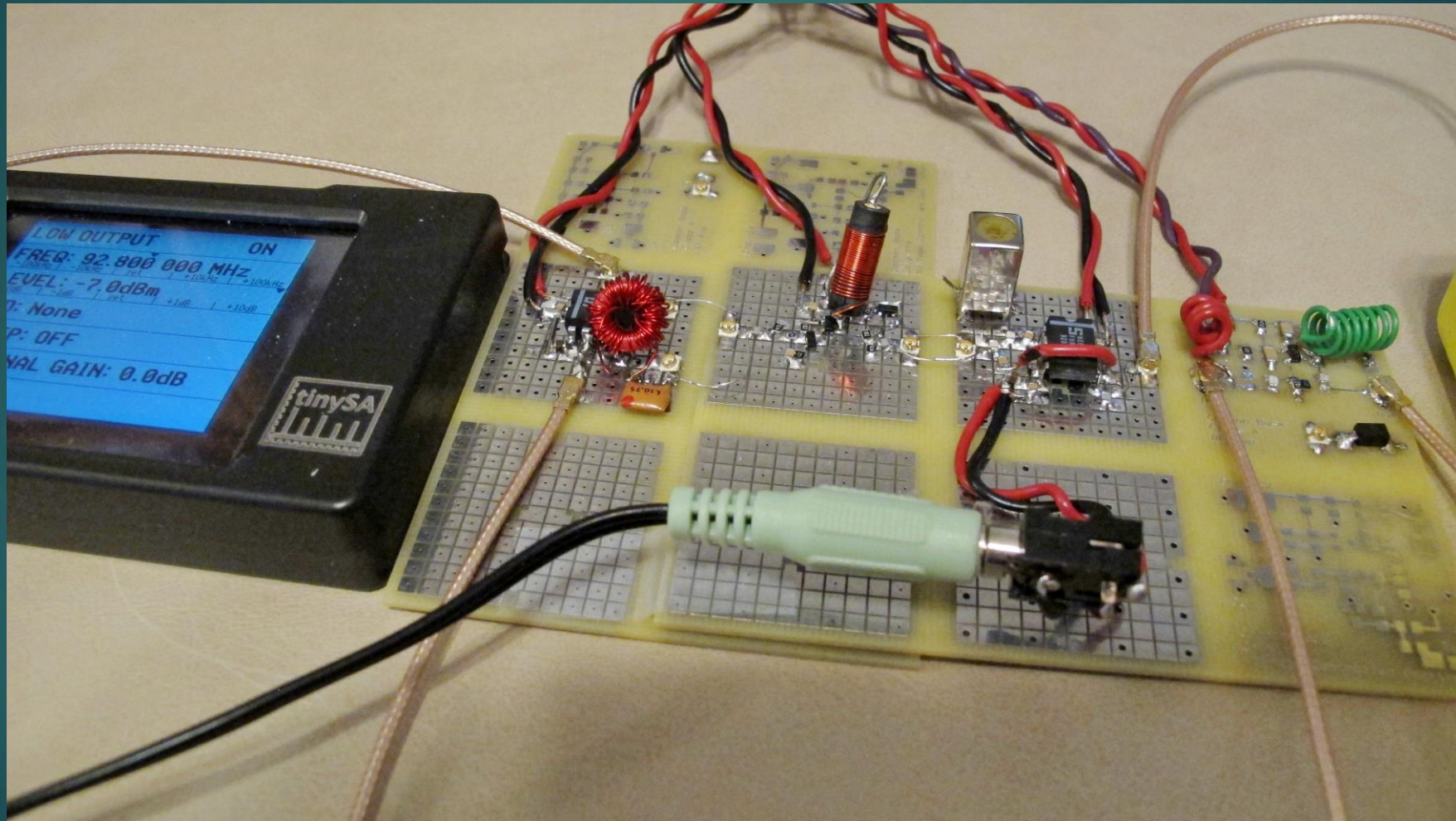

# First Sound

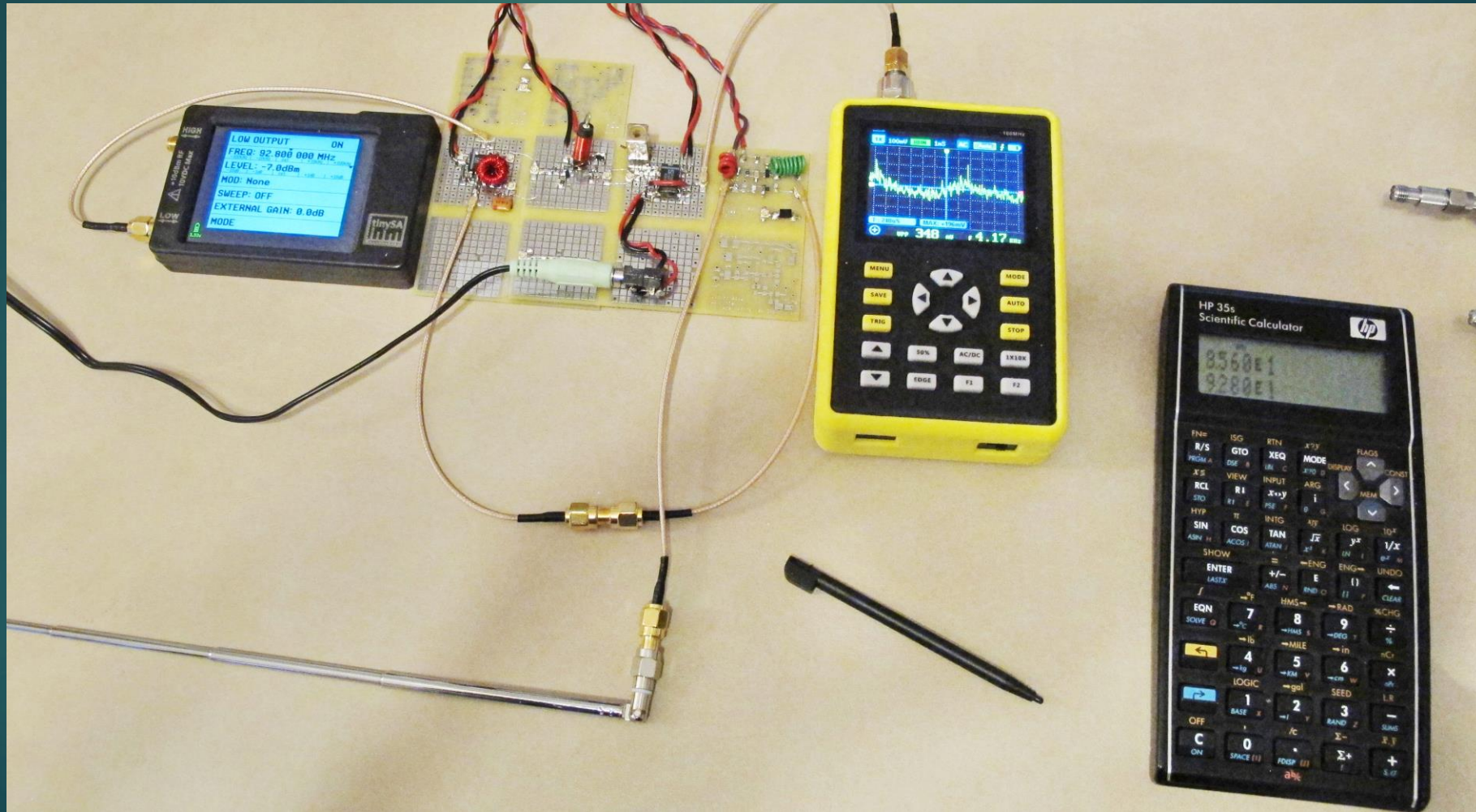

# Optional Audio Amp

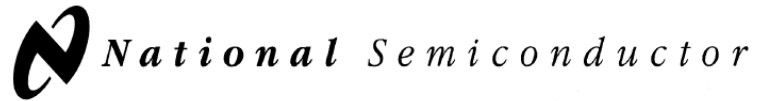

August 2000

## LM386 Low Voltage Audio Power Amplifier

### General Description

The LM386 is a power amplifier designed for use in low voltage consumer applications. The gain is internally set to 20 to keep external part count low, but the addition of an external resistor and capacitor between pins 1 and 8 will increase the gain to any value from 20 to 200.


The inputs are ground referenced while the output automatically biases to one-half the supply voltage. The quiescent power drain is only 24 milliwatts when operating from a 6 volt supply, making the LM386 ideal for battery operation.

### Features

- Battery operation
- Minimum external parts
- Wide supply voltage range: 4V–12V or 5V–18V
- Low quiescent current drain: 4mA
- Voltage gains from 20 to 200
- Ground referenced input
- Self-centering output quiescent voltage
- Low distortion: 0.2% ( $A_v = 20$ ,  $V_s = 6V$ ,  $R_L = 8\Omega$ , 125mW,  $f = 1\text{kHz}$ )
- Available in 8 pin MSOP package

## Typical Applications

### Amplifier with Gain = 20 Minimum Parts

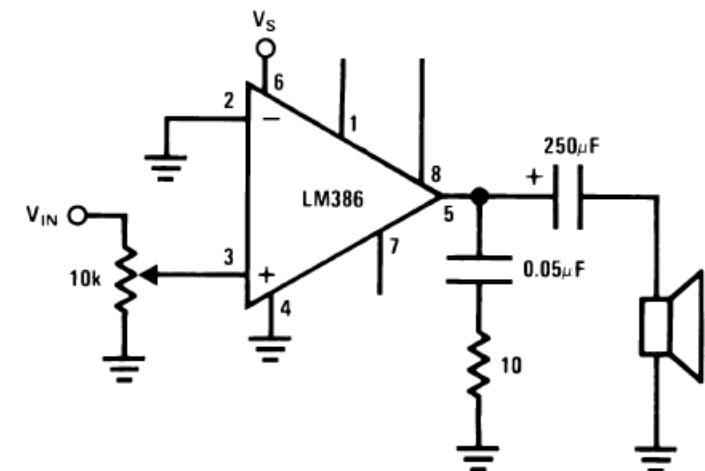


DS006976-3

# Episode 6 Topics

- *Superhet receiver architecture review*
- *IF limiting amplifier design*
- *Quadrature FM demod*
- *Receiver assembly and demonstration*
- *Modern radio chipsets*



# Other Options for FM IF Subsystem

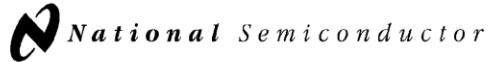

April 1987

LM3189 FM IF System

## LM3189 FM IF System


### General Description

The LM3189N is a monolithic integrated circuit that provides all the functions of a comprehensive FM IF system. The block diagram of the LM3189N includes a three stage FM IF amplifier/limiter configuration with level detectors for each stage, a doubly balanced quadrature FM detector and an

### Features

- Exceptional limiting sensitivity: 12  $\mu$ V typ at  $-3$  dB point
- Low distortion: 0.1% typ (with double-tuned coil)
- Single-coil tuning capability
- Improved (S + N)/N ratio

### Block Diagram

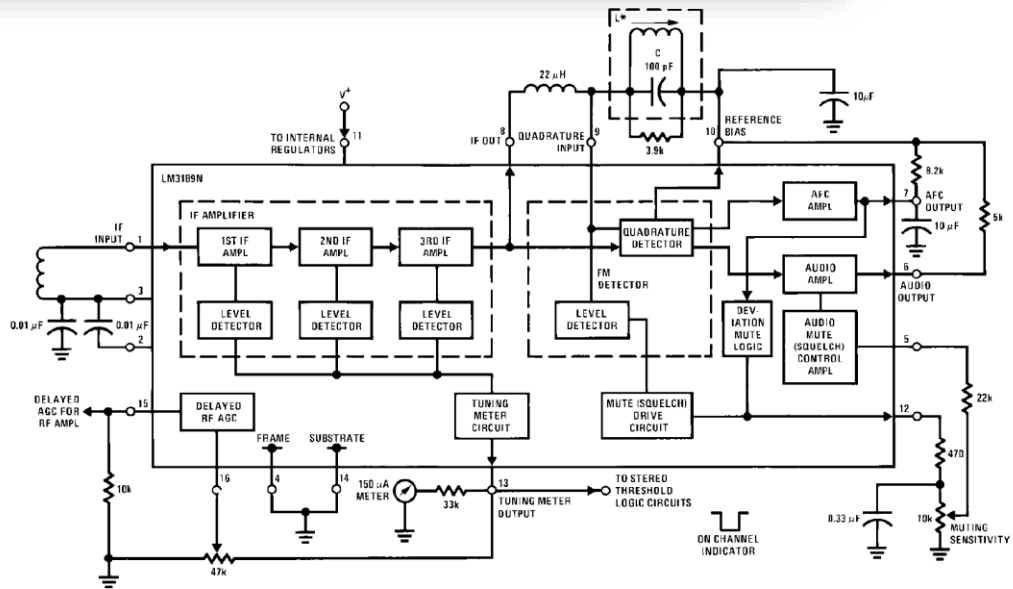

TL/H/7960-1

All resistance values are in  $\Omega$


\*L tunes with 100 pF (C) at 10.7 MHz,  $Q_0 \approx 75$   
(Toko No. KACS K586HM or equivalent)

### Complete FM IF System for High Quality Tuners

The circuit provides a complete FM IF system for a high quality receiver. Either one or two stages of amplification and bandpass filtering may be desired, depending on the

receiver requirements. See graph for Typical Limiting and Noise Characteristics for each circuit configuration which can be compared to the LM3189N alone.
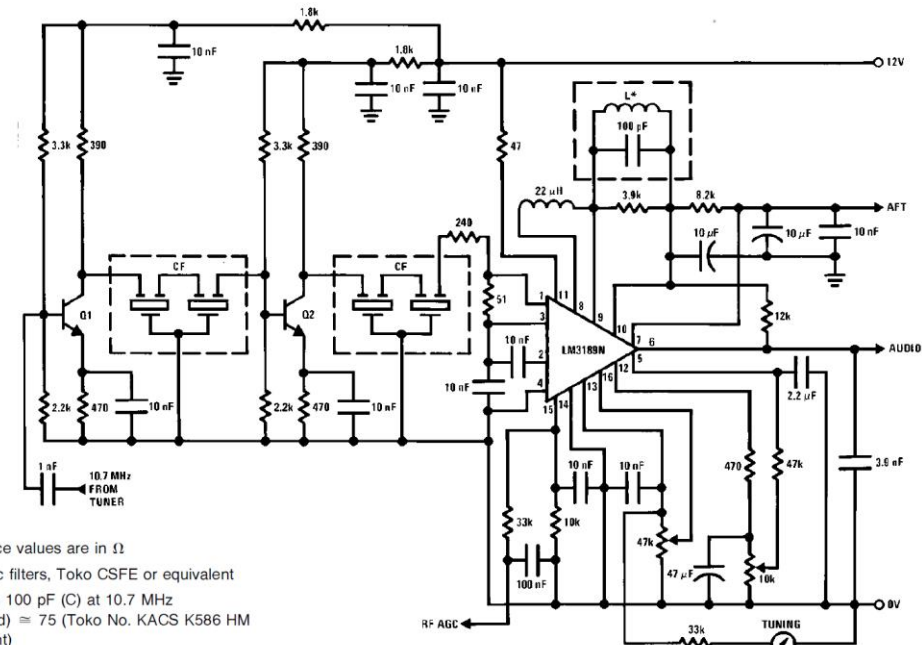
### Complete FM IF System for High Quality Receivers



All resistance values are in  $\Omega$

CF: Ceramic filters, Toko CSFE or equivalent

\*L tunes with 100 pF (C) at 10.7 MHz

$Q_0$ (unloaded)  $\approx 75$  (Toko No. KACS K586 HM or equivalent)

TL/H/7960-5

# Other Options for FM IF Subsystem

NXP Semiconductors

SA604A

High-performance low-power FM IF system

## 5. Block diagram

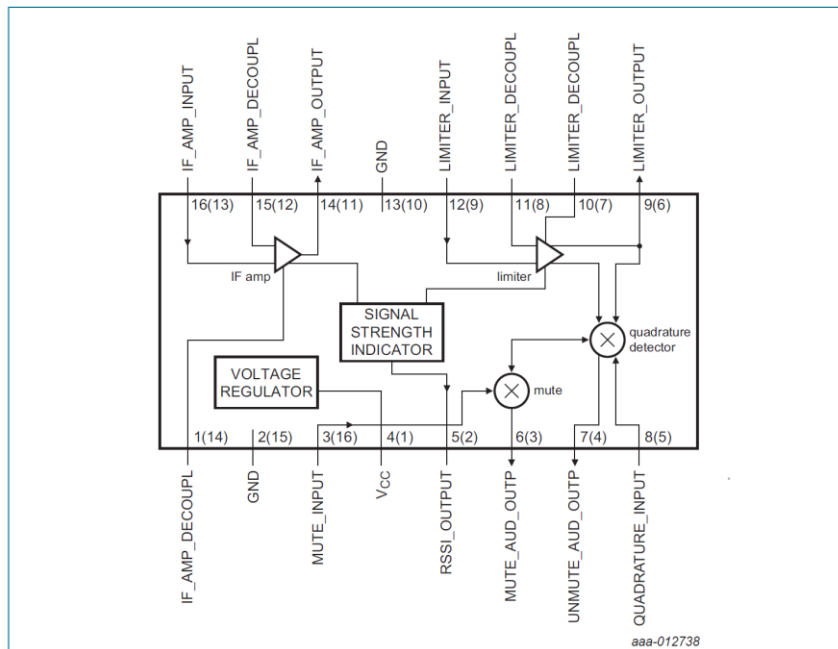



Fig 1. Block diagram of SA604A

NXP Semiconductors

SA604A

High-performance low-power FM IF system

## 13. Application information

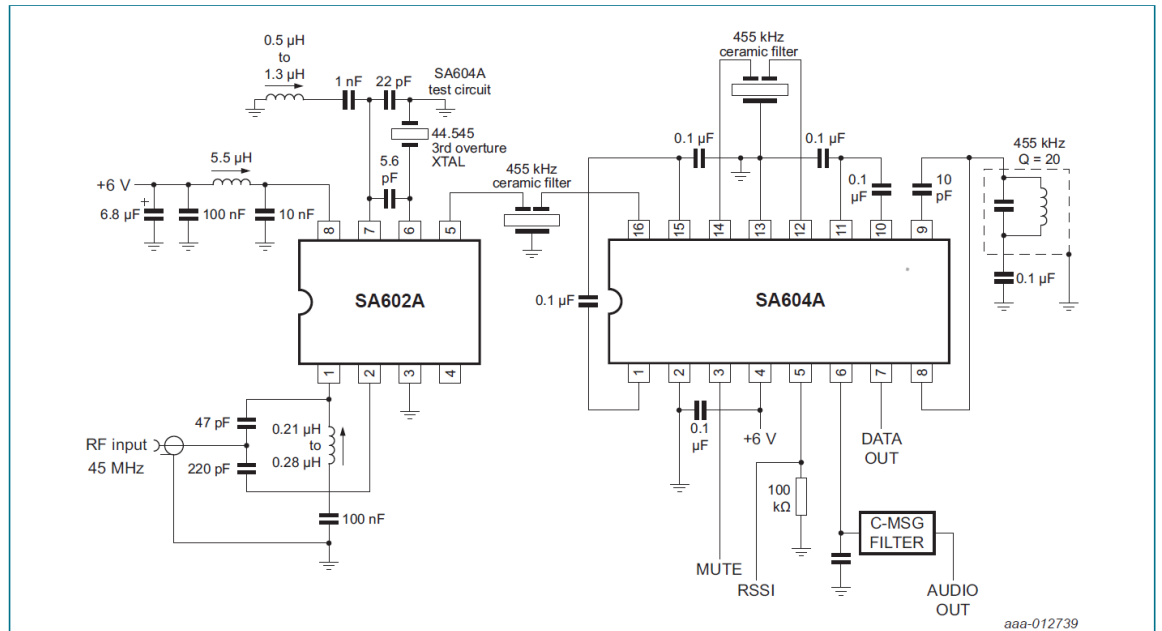

# Full Receivers on a Chip




SILICON LABORATORIES

## Si4700/01 Broadcast FM Radio Tuner for Portable Applications
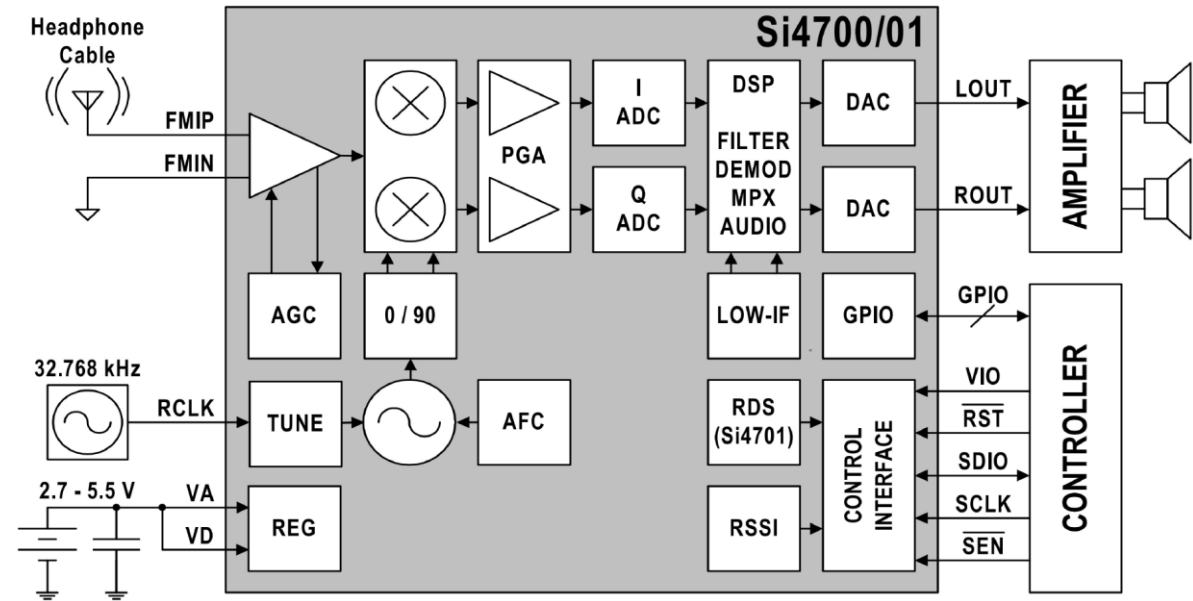
### Description

The Si4700 is the industry's first FM radio tuner IC to leverage digital integration and 100% CMOS process technology, resulting in a completely integrated solution that requires only one external supply bypass capacitor and less than 20 mm<sup>2</sup> of board space. Offering unmatched integration, the Si4700 allows FM radio reception to be added to a variety of portable devices where board space, performance, low power consumption, and ease of use are essential.




# Performance Issues

(possible future videos)

- ◆ Selectivity and Image Rejection
- ◆ Weak Signal Performance
- ◆ Strong Signal Performance
- ◆ Dynamic Range and Power Consumption

# Preview

## *The Intermod Problem*

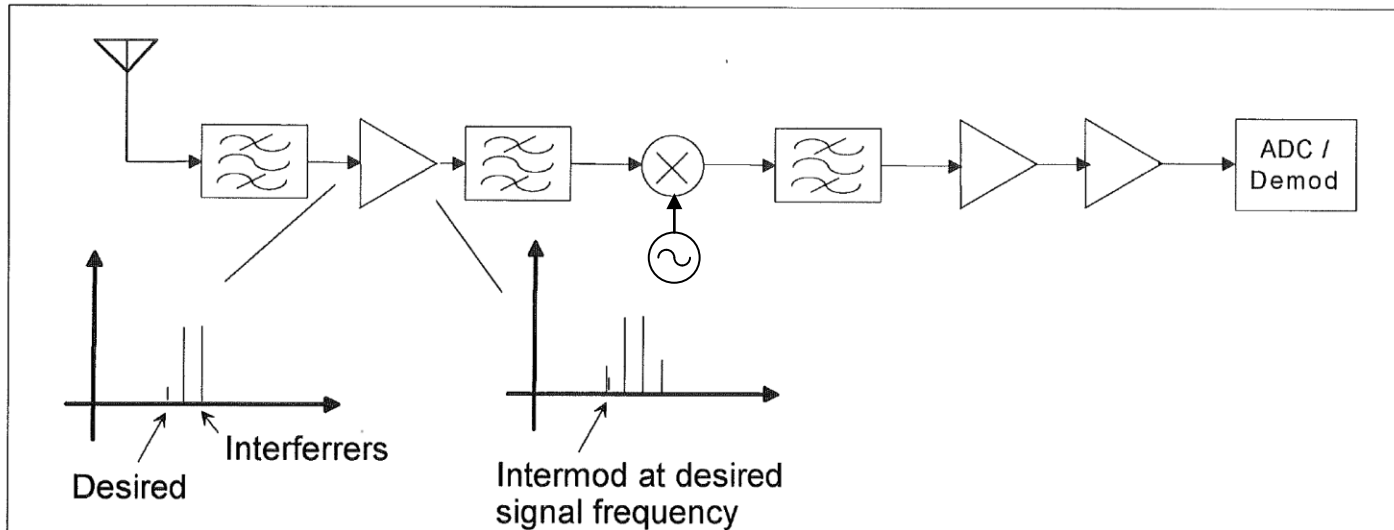

Can occur in any circuits up to last IF filter.

Typically occurs at lower power than blocking problems.

Can be mitigated with good preselect filters if interferrers are out-of-band

Cannot be filtered if interferrers are close to desired signal frequency .

Requires higher power LNA, mixer, etc.



*Thanks For  
Watching !*