

ECE Topics #1 -- Voltage, Current, Resistance, and Power

Slides downloaded from: <https://ecefiles.org/ece-topics/>

Companion video at: https://www.youtube.com/watch?v=2kJbzG6z_tU

This material is [provided by ecefiles.org](https://ecefiles.org) for educational use only.

This first video in the ECE Topics Series provides an introduction to what voltage, current, power, and resistance are. Going beyond basic theory, we present real-world examples of each. In addition to classic topics like Ohm's Law, we introduce device datasheets and show how such information can be used to design, build, and test a simple circuit.

What is Current "I" ?

The flow-rate of electric charge:

Application	Current I
Flashlight Bulb	0.3 A
Red LED	0.005 Amps (5 mA)
USB Charger	0.5 to 2+ A
Electric Vehicle	0 to 200+ A

Circuit Analysis and Design

5V supply minus 1.8V across LED leaves 3.2V across R, So...

$$R = \frac{V}{I} = \frac{3.2}{0.005} = 640 \Omega$$

Use $R = 680 \Omega$ (Standard value)



Check power dissipations I (Recall: $P = IV$)

Construction / Testing

WARNING
Electricity can be dangerous! High voltages like those in home electrical systems can force enough current through the body to **KILL** you. Even low-voltage sources with high-energy like car batteries can cause sparks, fires, and/or explosions. In Lab 1, we will use only low voltage, low-energy circuits to avoid danger. **DO NOT** extrapolate what you learn here to ANY other voltage or power sources until you know what you are doing!

Topics in ECE #1

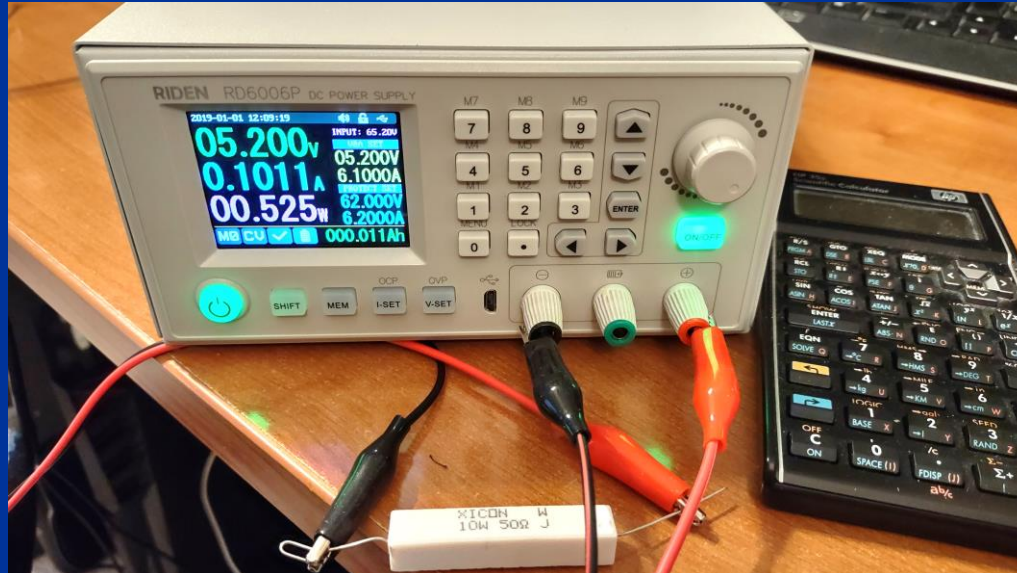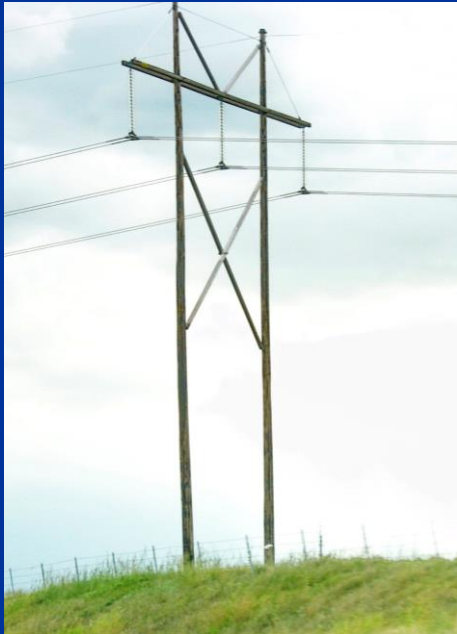Voltage, Current, and Power *Resistance,*



Based on University Courses

Intro EE, Lab 1



This lab is designed to introduce you to many important Electrical Engineering concepts including:

- Schematics and wiring diagrams
- Electrical circuit construction and soldering
- Use of digital multimeters to measure voltage and current
- Series versus parallel circuits, and Kirchoff's voltage and current laws
- Difference between shorts and opens
- Battery performance, including voltage versus time and load

In addition, the lab will introduce you to some basic issues, such as engineering units and "**significant digits**" in reporting results.

WARNING


Electricity can be dangerous! *High voltages* like those in home electrical systems can force enough current through the body to **INJURE** or **KILL** you. Even low-voltage sources with *high-energy* like car batteries can create sparks, fires, and/or explosions. In Lab 1, we will use only low voltage, low-energy circuits to avoid danger. **DO NOT** extrapolate what you learn here to **ANY** other voltage or power sources until you know what you are doing!

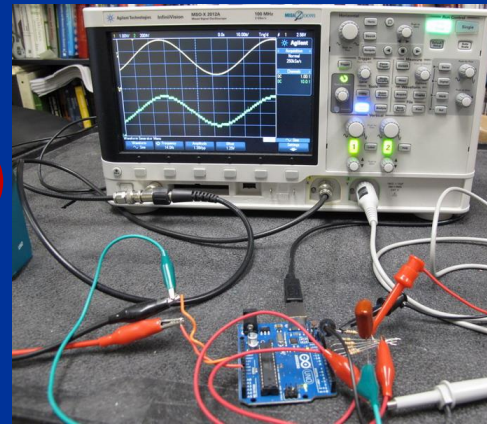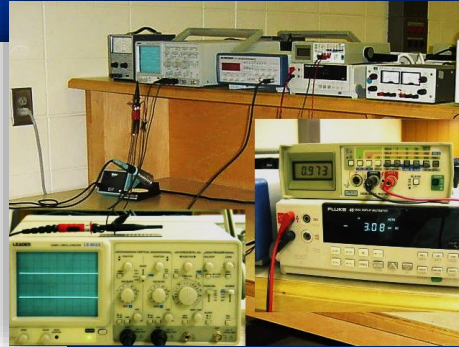

Electronics 2 Design Project

Due Friday, Dec 7, 2018 (Preliminary designs due Monday, Nov 12, 2018)

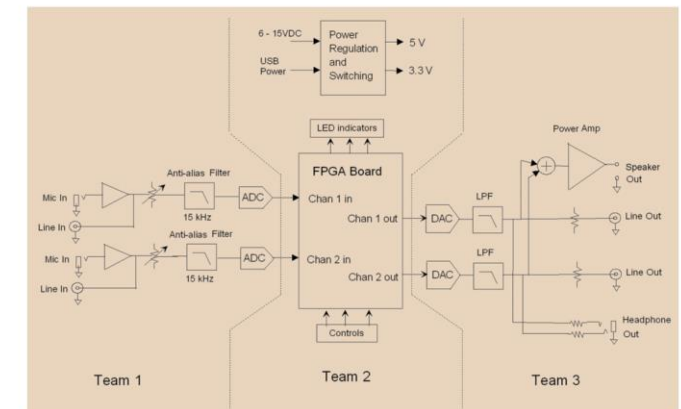See Gantt chart for additional task breakdown and scheduling detail.



Project Overview

Our project this semester is the design of a Digital Signal Processing (DSP) based audio effects board. It is intended to implement a guitar-pedal effects box, but the block diagram (above) is general enough to allow development of many future products as well. Since the design centers around an FPGA board¹, this can be as simple as reprogramming and building new packaging. The basic functions of the board you are to design are implied in the block diagram above. Additional specification details will be provided in class discussions.



We will work in "companies" comprised of 6 engineers each, and you will be required to turn in a company report. Most of the "deliverables" however are individual so that each engineer must pull their own weight. Each company will consist of 3 teams, each having one circuit designer and one layout engineer. Your combined report should be broken into 3 core sections with separate circuit schematics and separate layouts for each team, plus an introduction and a conclusion. For a good score, you will need to do your own design and writeup well, but coordinate with your teammate and company to provide a coherent design/report.

Episode 1 Topics

- **The Basics**
 - What are current, voltage, and power ?
 - Real world applications and example values
- **Ohms Law vs Device IV Curves**
- **Circuit Analysis and Design**
- **Protoboard Construction / Testing**

What is Current "I" ?

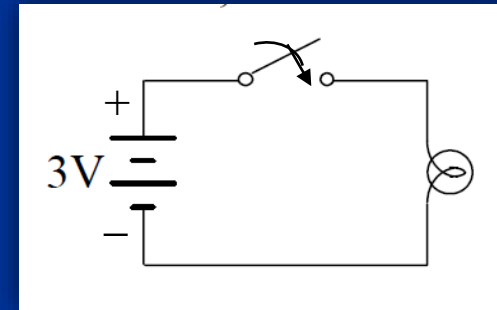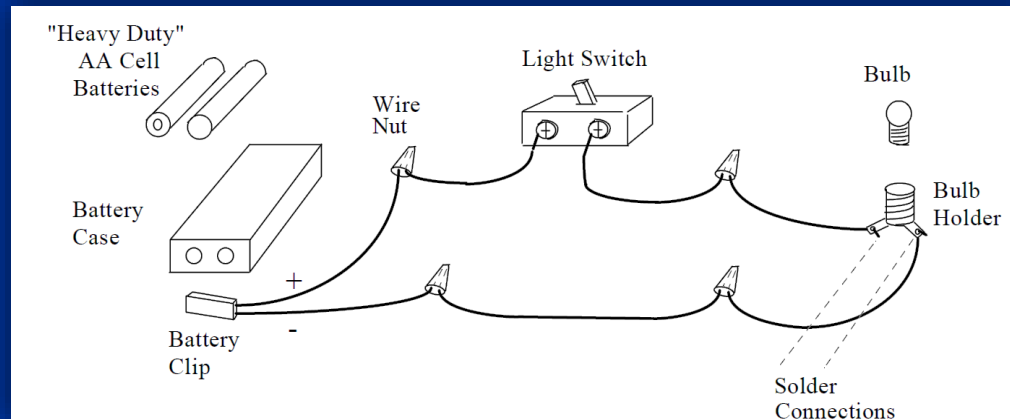The flow-rate of electric charge in Amperes



Charge in Coulombs

$$I = \frac{Q}{t}$$



or $I = \frac{\Delta Q}{\Delta t}$

or $i(t) = \frac{dq}{dt}$

Time in seconds

What is Current “I” ?

The flow-rate of electric charge:

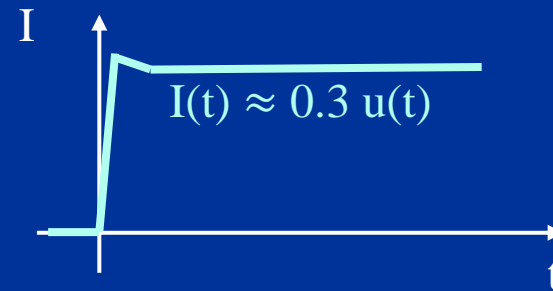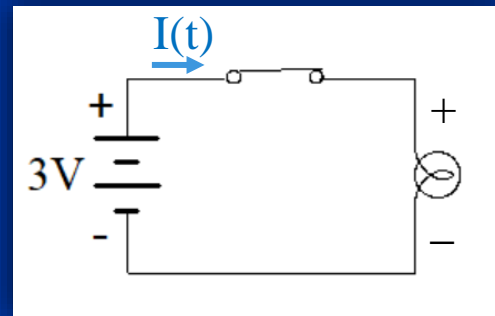


Application	Current I
Flashlight Bulb	0.3 A
Red LED	0.005 Amps (5 mA)
USB Charger	0.5 to 2+ A
Electric Vehicle	0 to 200+ A

OK – So what is Voltage ?

This is more complicated...

It's kinda like the “pressure” behind the flow...

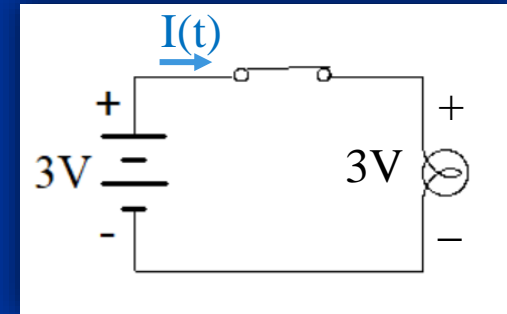But actually, it's energy (a.k.a. work) per unit charge, in Volts



Work (energy) in Joules

$$V = \frac{W}{Q}$$

or

$$V = \frac{\Delta W}{\Delta Q}$$

Charge in Coulombs

Application	Voltage V
Flashlight Bulb	3 Volts
Red LED	1.8 V
USB Charger	5 V (5-20V for PD)
Electric Vehicle	200 to 800 V

Measuring I and V


Small Currents

III. Measuring Current

Recall from class that current is a “through variable”, whereas voltage is an “across variable”. To measure voltage, all we needed to do was place the DMM test leads “across” the battery. **To measure current, we must put the meter in the path of the current so that the current passes through the DMM.** The following steps will walk you through this procedure.

1. It is almost always good practice to “de-energize” a circuit before working on it. To do this here, disconnect the clip from the battery holder.
2. Undo the connection between the switch and the bulb (at the wire nut).
3. “Hook-up” the meter as shown in the figure below to measure current. **Be sure to use the 10A current input on the meter**, and to configure the meter to read DC amps (ask your instructor if you are not sure!).
4. With the switch off, re-energize your circuit (hook up the batteries again).

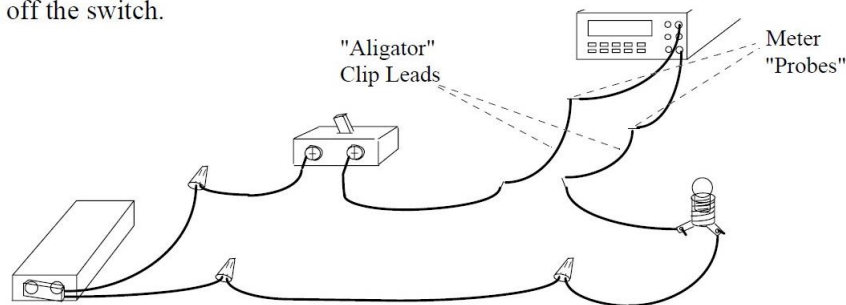8. Note that there is a “voltage drop” from the battery to the bulb due to the DMM that is measuring the current. **This is an example of an important issue in taking measurements. The measurement equipment itself can affect the quantity being measured, to some degree.**
9. Turn off the switch.



Hooking up meter to measure current (meter terminals may not be shown accurately).

Voltages and Large Currents



WARNING

Electricity can be dangerous! *High voltages* like those in home electrical systems can force enough current through the body to **INJURE** or **KILL** you. Even low-voltage sources with *high-energy* like car batteries can create sparks, fires, and/or explosions. In Lab 1, we will use only low voltage, low-energy circuits to avoid danger. **DO NOT** extrapolate what you learn here to **ANY** other voltage or power sources until you know what you are doing!

How Are V&I Related ?

Through Power (P) in Watts

$$V I = \frac{\Delta W}{\Delta Q} \frac{\Delta Q}{\Delta t} = \frac{\Delta W}{\Delta t} = P \quad \text{or} \quad P = VI$$

Application	Voltage	Current	Power
Flashlight Bulb	3 V	0.3 A	0.9 W
Red LED	1.8 Volts	0.005 Amps	0.009 Watts (9 mW)
USB	5 V	2 A	10 W
Electric Vehicle	800 V	200 A	160 kW (215 HP)

How Are V&I Related ?

Through Power (P) in Watts

$$V I = \frac{\Delta W}{\Delta Q} \frac{\Delta Q}{\Delta t} = \frac{\Delta W}{\Delta t} = P \quad \text{or} \quad P = VI$$


Application	Voltage	Current	Power
Flashlight Bulb	3 V	0.3 A	0.9 W
Red LED	1.8 Volts	0.005 Amps	0.009 Watts (9 mW)
USB	5 V	2 A	10 W
Electric Vehicle	800 V	200 A	160 kW (215 HP)

Oh yeah, and thru “Ohms Law”...


$$I = \frac{V}{R} \Rightarrow P = \frac{V^2}{R} \quad P = I^2 R$$

Resistance in Ohms

50 Ohm Resistor (actually 51.4 Ω)

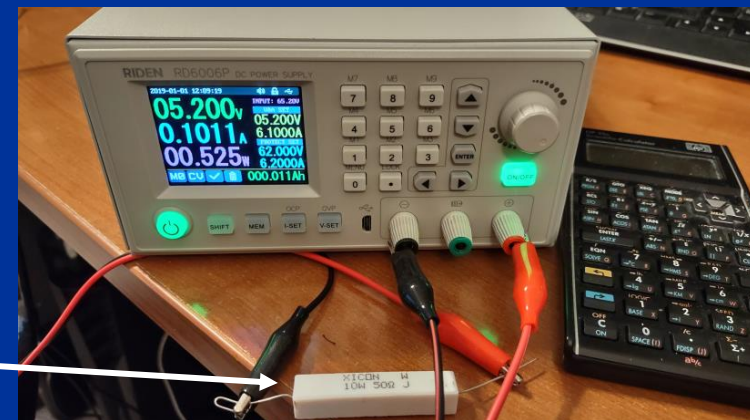

Ohms Law vs Device IV Curves

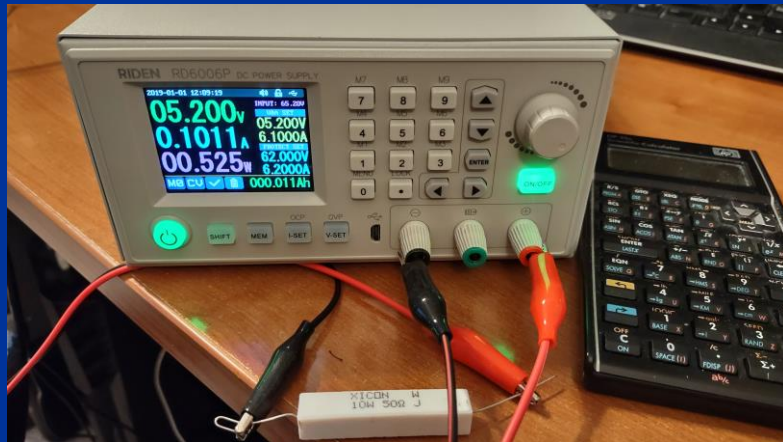


$$I = \frac{V}{R}$$

$$R = \frac{V}{I} \quad V = IR$$

ROHM SEMICONDUCTOR SLR-56x

■ **Features**

- Viewing angle 2θ 1/2 : 40°

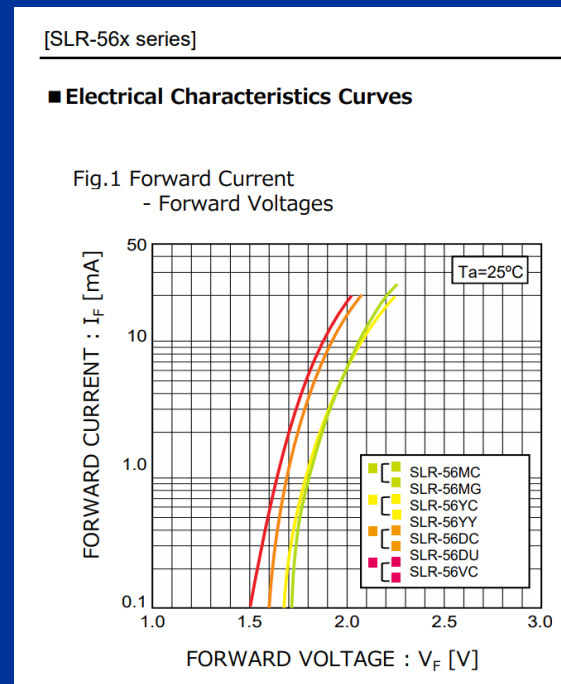


Data Sheet

■ **Outline**

Fig.3 Luminous Intensity - Forward Current

Fig.4 Derating

Circuit Analysis and Design

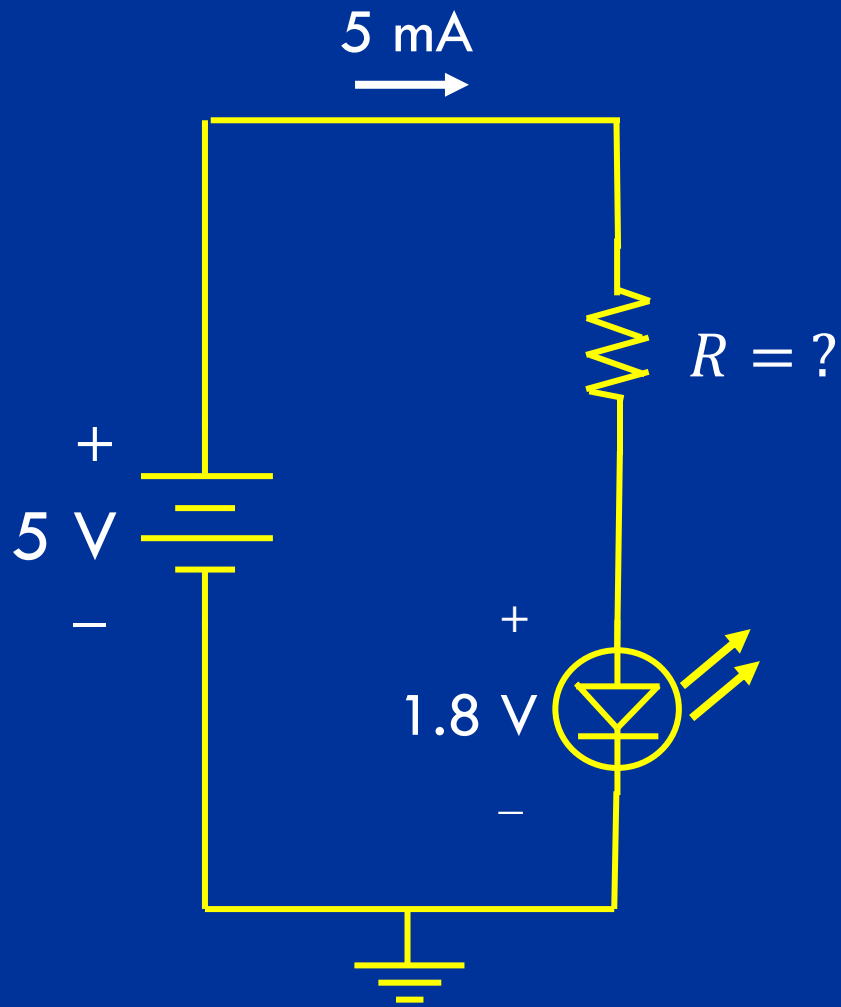


If $I = 5 \text{ mA}$
flows
through
LED

[SLR-56x series]

■ Electrical Characteristics Curves


Fig.1 Forward Current
- Forward Voltages

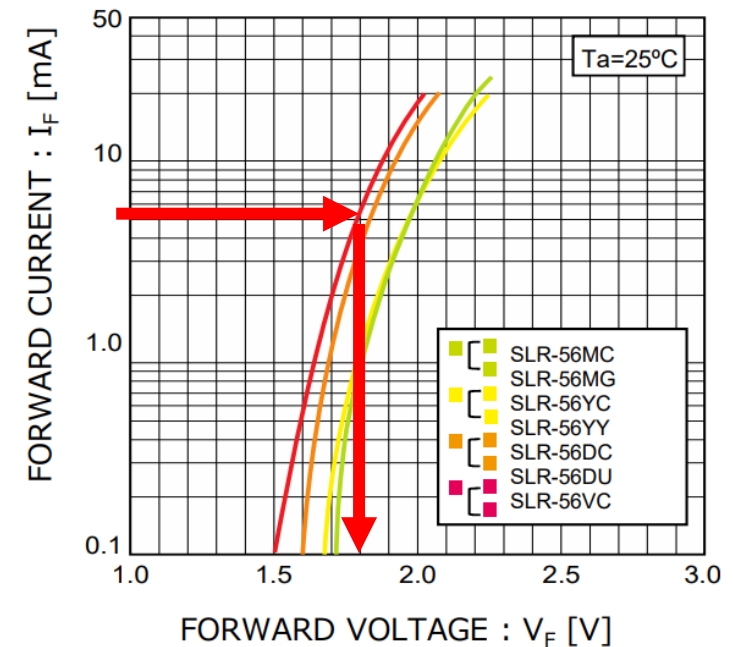

LED will have $V = 1.8 \text{ V}$ across it

Circuit Analysis and Design

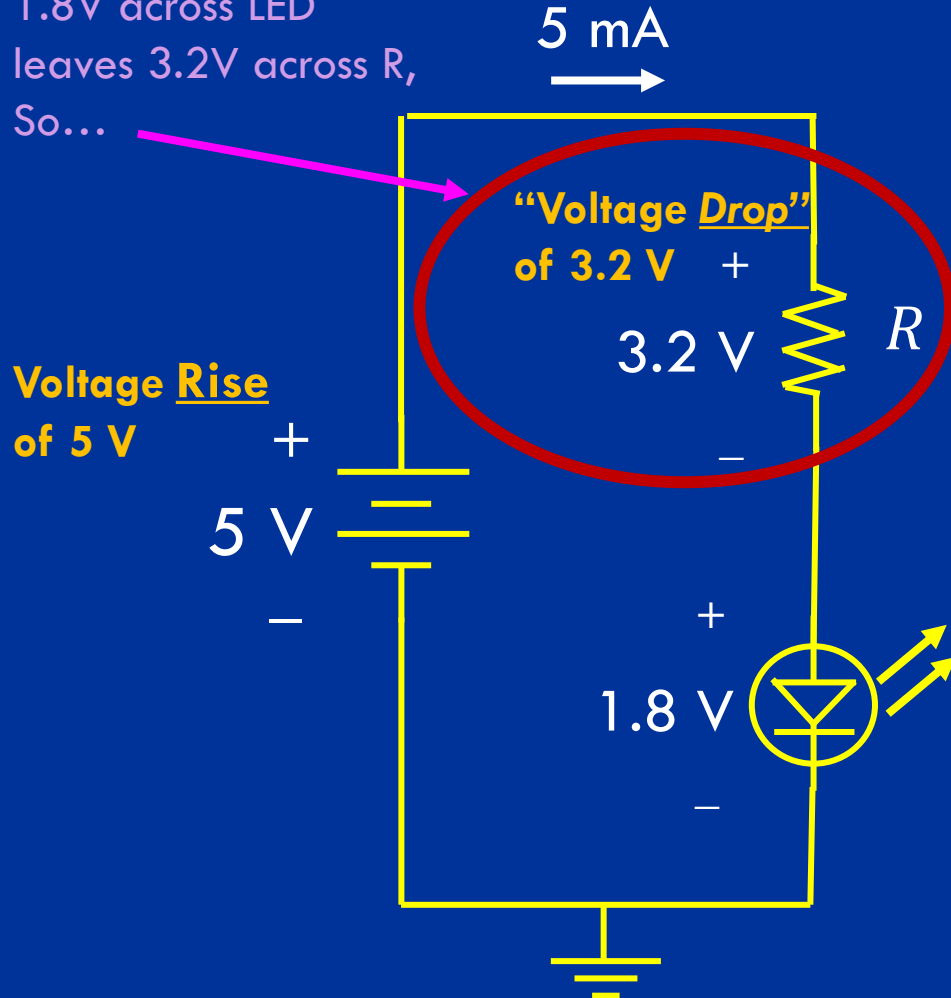5V supply minus
1.8V across LED
leaves 3.2V across R,
So...



$$R = \frac{V}{I} = \frac{3.2}{0.005}$$

$$= 640 \Omega$$


Use $R = 680 \Omega$
(Standard value)

Check power
dissipations !
(Recall: $P = IV$)



[SLR-56x series]

Electrical Characteristics Curves

Fig.1 Forward Current
- Forward Voltages

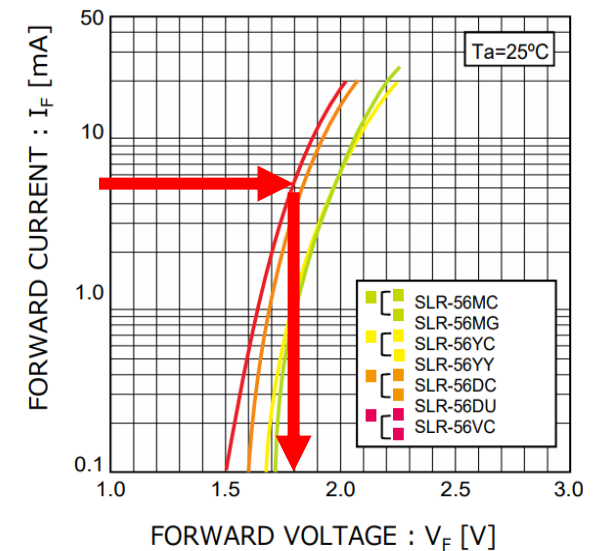


Construction / Testing

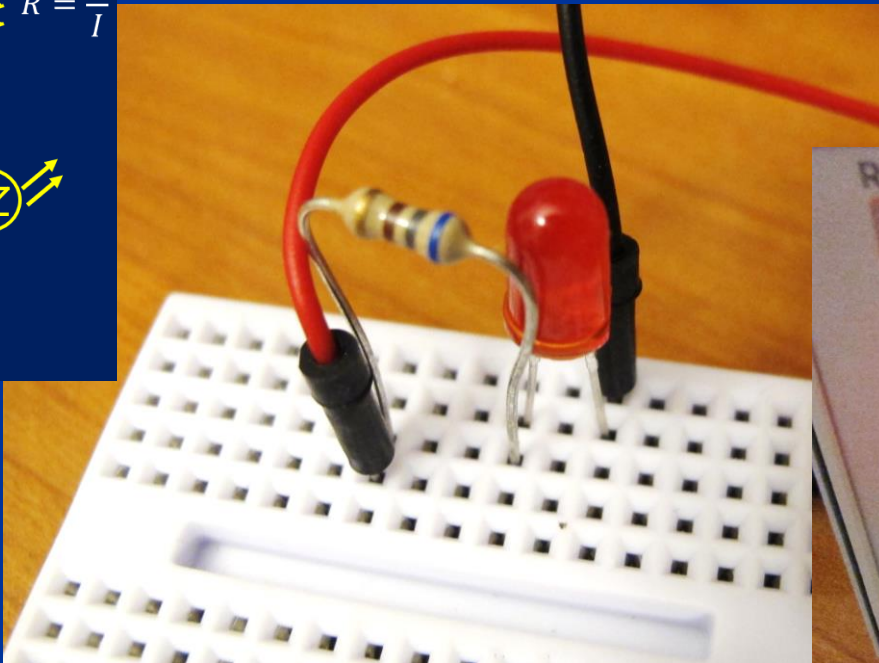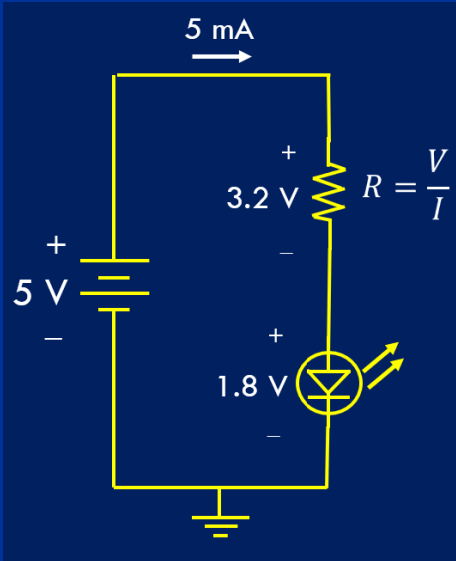

WARNING

Electricity can be dangerous! *High voltages* like those in home electrical systems can force enough current through the body to **INJURE** or **KILL** you. Even low-voltage sources with *high-energy* like car batteries can create sparks, fires, and/or explosions. In Lab 1, we will use only low voltage, low-energy circuits to avoid danger. **DO NOT** extrapolate what you learn here to **ANY** other voltage or power sources until you know what you are doing!

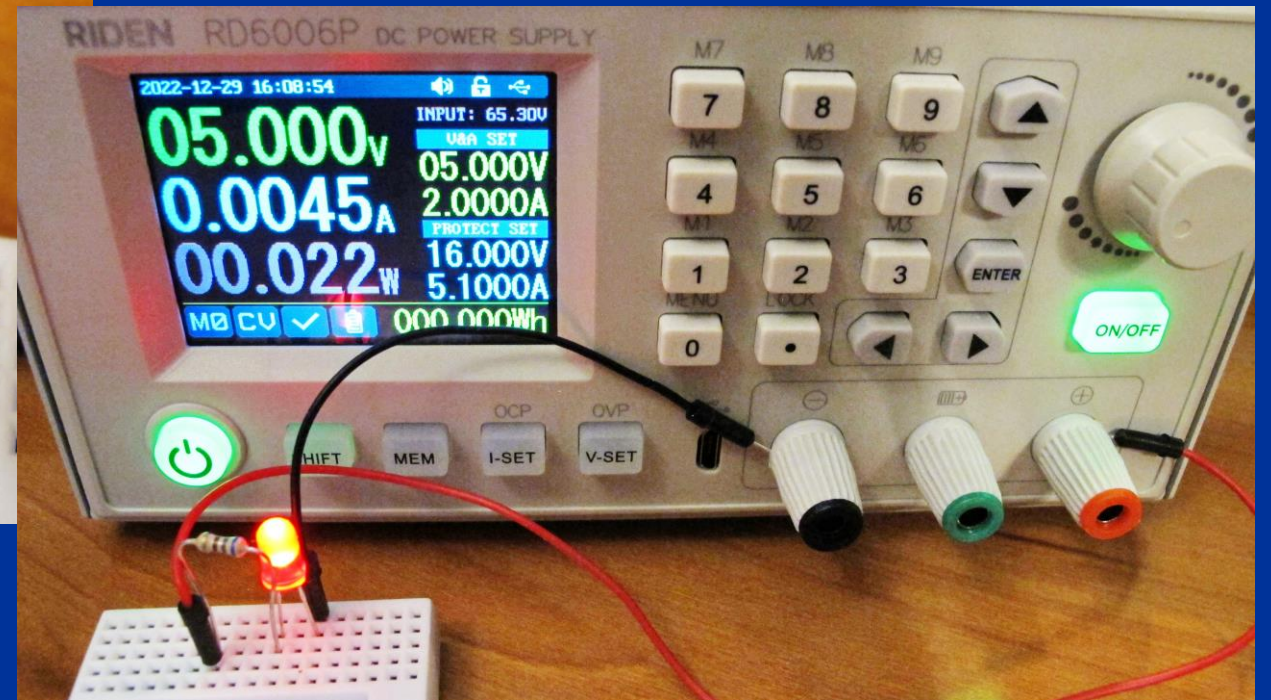

A Little More Theory ...

Ohm's Law $I = \frac{V}{R}$
 $V = IR$
 $R = \frac{V}{I}$


Kirchoff's Current Law
At a "node":

$$\sum I_{entering} = \sum I_{leaving}$$


Kirchoff's Voltage Law
Around a loop:

$$\sum V_{rises} = \sum V_{drops}$$


In this lab, we will build 3 simple circuits, shown in the 3 schematics below.

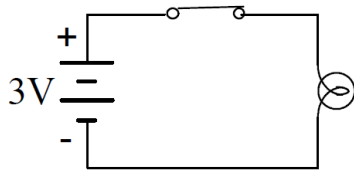

Schematic 1
Ohm's Law Demo

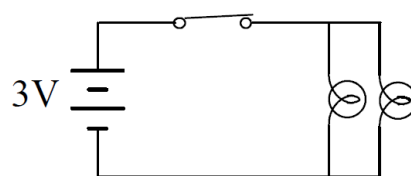

Schematic 2
KCL Demo

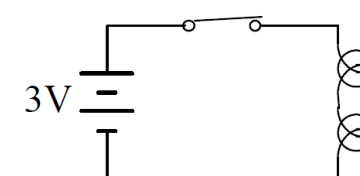

Schematic 3
KVL Demo

Suggested References

The screenshot shows the Amazon product page for the book "Practical Electronics for Inventors, Fourth Edition" by Paul Scherz and Simon Monk. The page includes the Amazon Prime logo, delivery location (Manhattan 66503), search bar, and navigation menu. The book cover features a lightbulb and a circuit board. The price is listed as \$26.72 - \$33.79 for paperback. The book is part of the "Electronics (18 books)" series and is a "#1 Best Seller in Integrated Circuits".

Practical Electronics for Inventors, Fourth Edition 4th Edition
by Paul Scherz (Author), Simon Monk (Author)
★★★★★ 1,775 ratings
Part of: Electronics (18 books)
#1 Best Seller in Integrated Circuits

Paperback
\$26.72 - \$33.79 ✓prime
20 Used from \$22.75
26 New from \$29.45

Publisher's Note: Products purchased from Third Party sellers are not guaranteed by the publisher for quality, authenticity, or access to any online entitlements included with the product.

A Fully Updated, No Nonsense Guide to Electronics
Read more
Report incorrect product information.

https://www.amazon.com/Practical-Electronics-Inventors-Fourth-Scherz/dp/1259587541/ref=asc_df_1259587541

The screenshot shows a YouTube video titled "The Map of Engineering" by the channel "Domain of Science". The video thumbnail is a colorful infographic map of engineering disciplines. The video has 789K views and was uploaded 2 months ago. The video player shows a progress bar at 22:09. Below the video, there are chapter markers for "Civil Engineering" (11 chapters) and "Aerospace Engineering 13:38 Marine Engineering 14:18 Electrical E...".

The Map of Engineering
789K views • 2 months ago
Domain of Science ✓
... Aerospace Engineering 13:38 Marine Engineering 14:18 Electrical E...
Civil Engineering 11 chapters

<https://youtu.be/pQgxiQAMTTo?t=858>

This screenshot shows the YouTube video player interface for "The Map of Engineering". The video is at the 20:03 mark of a 22:09 duration. The video title and channel name "Domain of Science" are visible. The video has 34K likes and 1.11M subscribers. The description includes a link to a Brilliant.org subscription and a link to a store for posters.

The Map of Engineering
Domain of Science 1.11M subscribers
34K likes
789K views 2 months ago
Visit <https://brilliant.org/dos/> to get started learning STEM for free, and the first 200 people will get 20% off their annual premium subscription.
And grab your posters here: <https://store.dftba.com/collections/d> Show more

Future Episodes ?

<i>Lecture Topics</i>	<i>Labs</i>
Voltage, current, nodes, batteries, resistance,	None
KVL, KCL, Ohm's law, power, AC, peak vs RMS	Circuit construction, V, I measurements with DMM
Circuit analysis and applications	Resistance Measurements, AC Signals, Function generators.
Electricity&magnetism, Faraday's law, applications	Resistor circuits (volume controls, input/output impedance)
Inductors and application circuits	Magnetism, transformers, relays, motors and generators
Capacitors and application circuits	Inductor and capacitor circuits
Frequency response, dB, and sinusoidal circuit analysis	Kit Construction
Semiconductors, diodes and application circuits	Kit Construction
Transistors and amplifier/switching applications	Diodes, rectifiers, transistors and applications
Introduction to Systems (esp. renewable energy)	Project work with solar-cell panels and renewable energy sy
Introduction to complex numbers and impedance	Project work with solar-cell panels and renewable energy sy

From Intro EE Course Syllabus (Fall 2010 offering)

Topics covered include:

Part I (The big picture)

- ◆ Review of “signals” and amplifiers. Frequency domain concepts (Fourier theory)
- ◆ Mathematical models, including Thevenin models and loading effects
- ◆ Opamp review, including application circuits and real-world performance issues
- ◆ Additional analog ICs (comparitors, switches, regulators, etc.)
- ◆ Systems that include amplifiers, ADCs, DACs, and digital signal processing (DSP).
- ◆ Circuit board layout

Part 2 (The details of discrete devices and their applications, and circuits inside ICs)

- ◆ Diodes, classic power supplies, and modern switching supplies
- ◆ MOSFET structure and operation and switching and amplifier applications
- ◆ Amplifier configurations (e.g. CS, CG, CD, and high-frequency behavior)
- ◆ Multi-transistor amplifiers, Miller's theorem, and cascoding.
- ◆ Comparison of MOSFETs and BJTs.
- ◆ Differential amplifiers, power-amp stages, and basics of op-amp internal designs
- ◆ Two-port network representations, feedback, and stability

Additional topics will be interwoven as time permits (e.g. Simulators, filter design, noise and coupling)

From Electronics 2 Course Syllabus (Fall 2015 offering)

THANKS FOR WATCHING !

