



Radio Design 401 Episode 1 – Low-power Receivers in Crowded Spectrum Environments (a White Paper)

Slides downloaded from: <https://ecefiles.org/>

Companion videos at: <https://www.youtube.com/playlist?list=PL9Ox3wpmB0krNexW2k5JMCaewXN7LoRXd>

This material is **provided by ecefiles.org for educational use** .

This is the first episode in our follow-on to the Radio Design 101 series. In RD401, we will be covering more advanced topics including fundamental research into how to improve the performance of receivers in dense spectrum environments. In keeping with RD101 series, we will be using the FM broadcast band for our demonstrations - but the material and circuit technologies are applicable to all radio receivers.

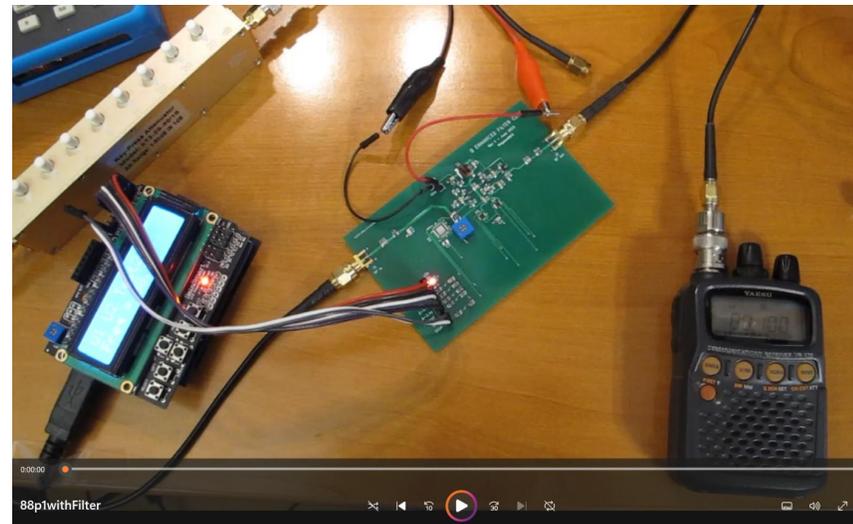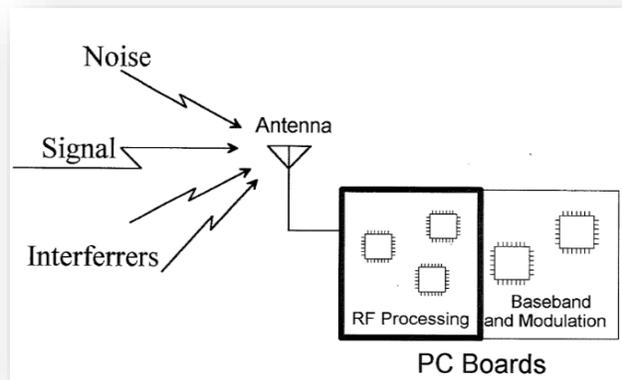




Radio Design 401

Episode 1


Low-power Receivers in Crowded Spectrum Environments

(An Advanced “Course” & “White Paper”)

“Prereq”: Radio Design 101 ☺

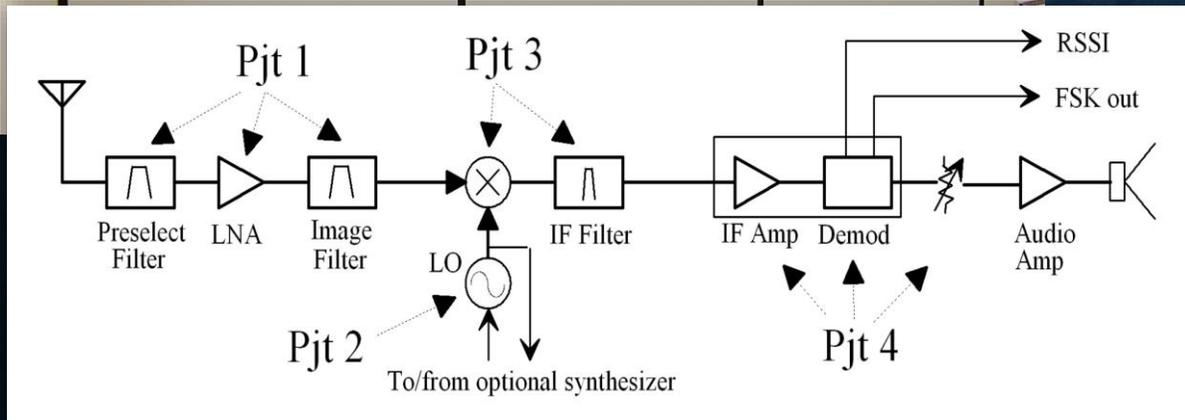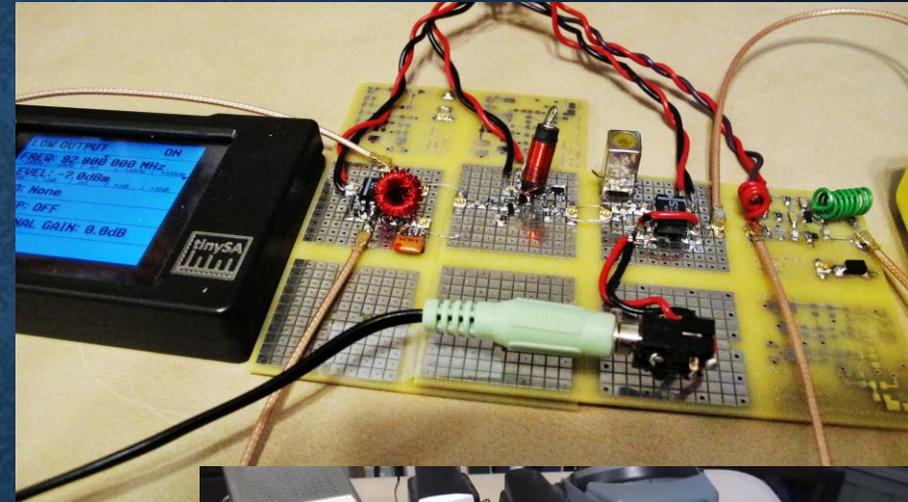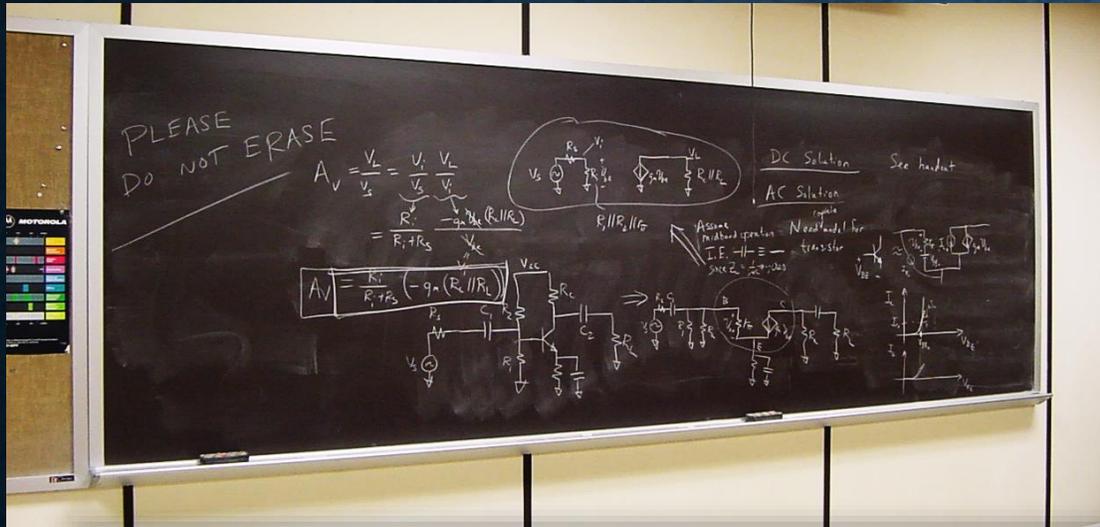

What's a "White Paper"

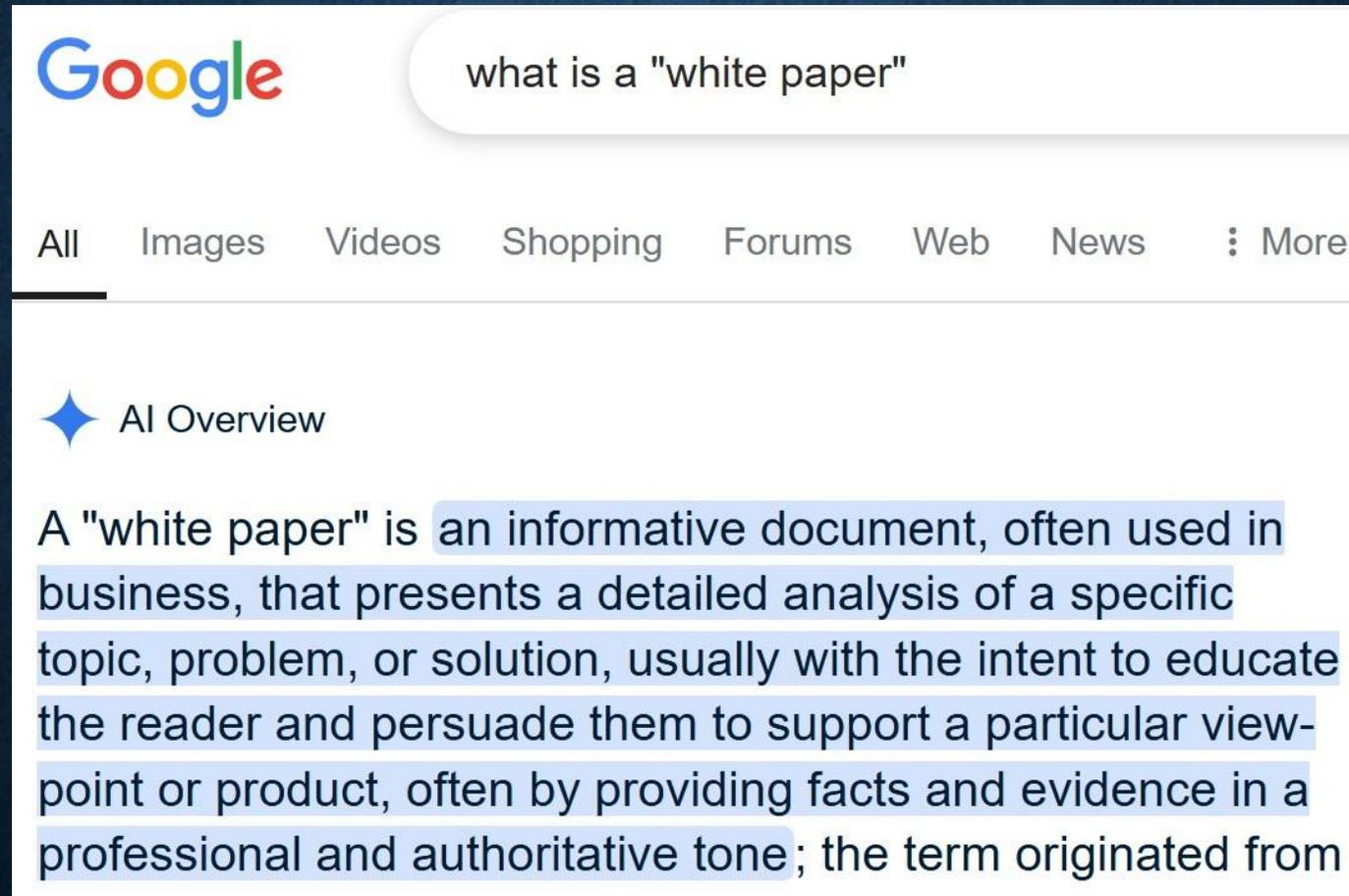

The image shows a Google search interface. At the top left is the Google logo. To its right is a search bar containing the text "what is a 'white paper'". Below the search bar are navigation tabs: "All", "Images", "Videos", "Shopping", "Forums", "Web", "News", and "More". The "All" tab is selected. Below the tabs is an "AI Overview" section, indicated by a blue star icon. The text in this section defines a white paper as an informative document used in business for detailed analysis, education, and persuasion, often providing facts and evidence in a professional tone.

Google

what is a "white paper"

All Images Videos Shopping Forums Web News : More

◆ AI Overview

A "white paper" is an informative document, often used in business, that presents a detailed analysis of a specific topic, problem, or solution, usually with the intent to educate the reader and persuade them to support a particular viewpoint or product, often by providing facts and evidence in a professional and authoritative tone; the term originated from



First Day Review



NanoVNA and TinySA for Radio Design



MegawattKS
9.99K subscribers

Analytics

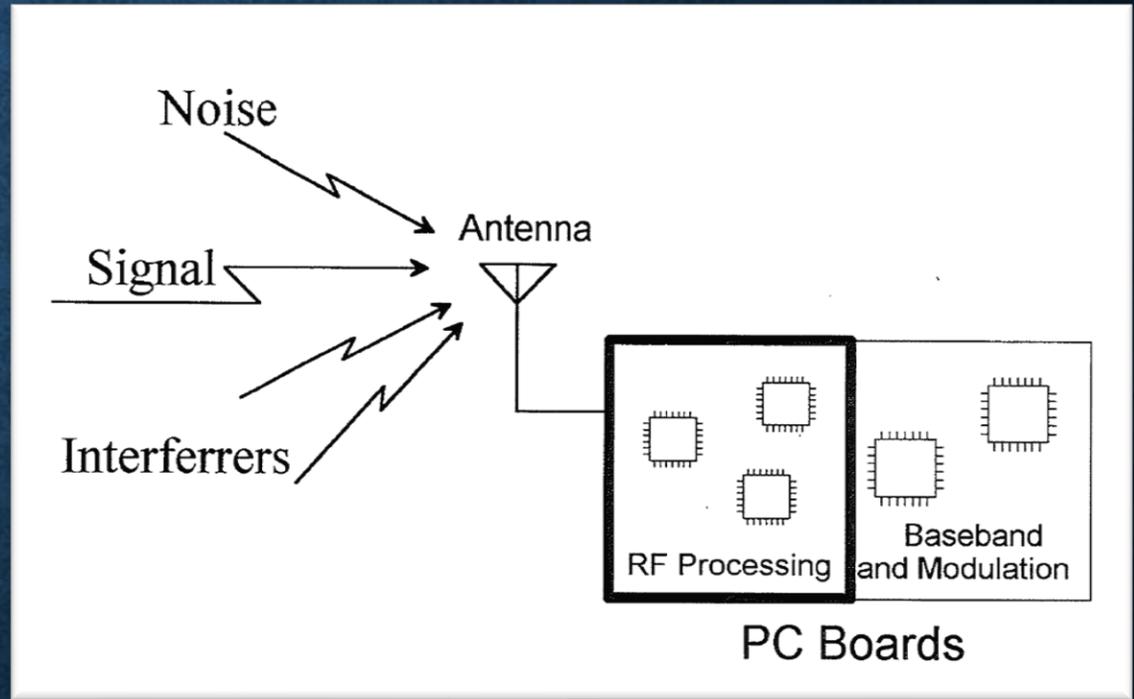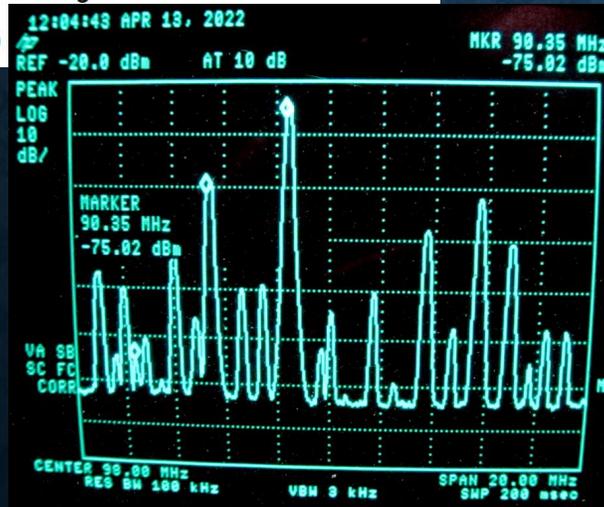

Radio Performance Testing

(From Radio Design 101 – Epilogue 1)

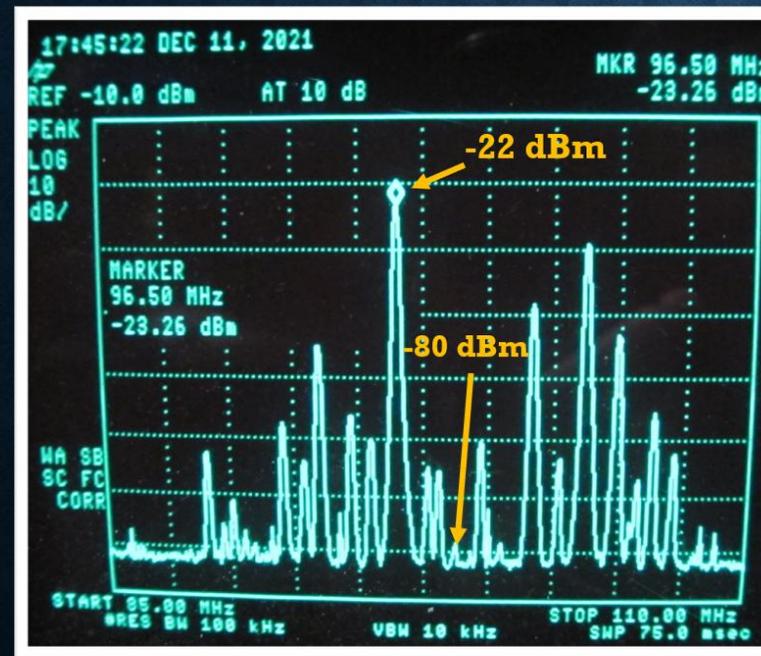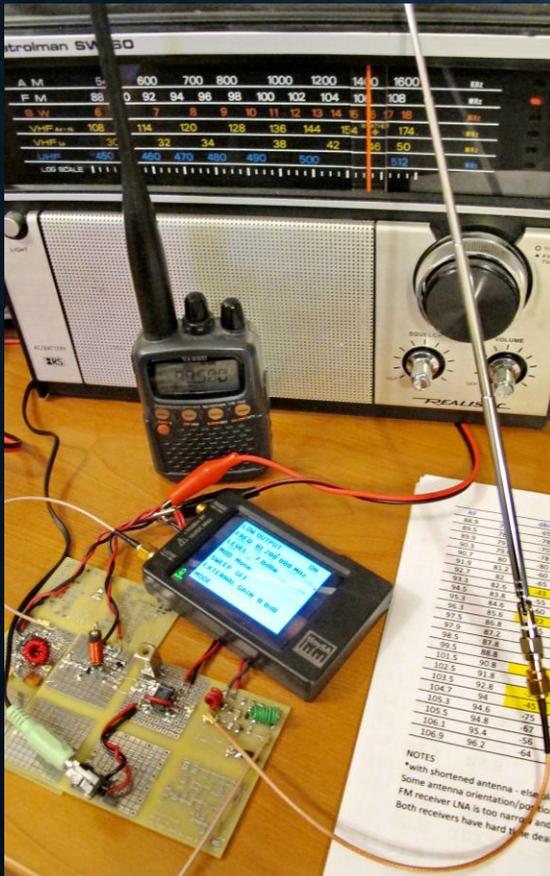


RF	LO	dBm	FMrx	FMrxFixed	VR120	VR120atten	Old Radio
88.9	78.2	-65				yes	yes
89.5	78.8	-78			yes		yes
89.9	79.2	-70	quiet	quiet	yes	yes	yes
90.3	79.6	-78		quiet		yes	yes
90.7	80	-80					yes
91.9	81.2	-60	quiet	good	yes	yes	yes
92.7	82	-65		good		yes	yes
93.3	82.6	-43	excellent	excellent	yes	yes	yes
94.5	83.8	-55	quiet	good	yes	yes	yes
95.3	84.6	-60	quiet	good	yes	yes	yes
96.3	85.6	-22	excellent	excellent	yes	yes	yes
97.5	86.8	-65		good		yes	yes
97.9	87.2	-67	quiet	quiet	yes	yes	yes
98.5	87.8	-80					?
99.5	88.8	-61	?	excellent*		yes	yes
101.5	90.8	-40	excellent	excellent	yes	yes	yes
102.5	91.8	-62					yes
103.5	92.8	-30	excellent	excellent	yes	yes	yes
104.7	94	-45	good	excellent	yes	yes	yes
105.3	94.6	-75					yes
105.5	94.8	-67				yes	yes
106.1	95.4	-56		very quiet		yes	yes
106.9	96.2	-64				yes	yes

Today's Topic – The Intermod Problem

Two strong signals at 96.3 and 93.3 MHz 'mix' and block weaker (-75 dBm) signal at 90.3 MHz



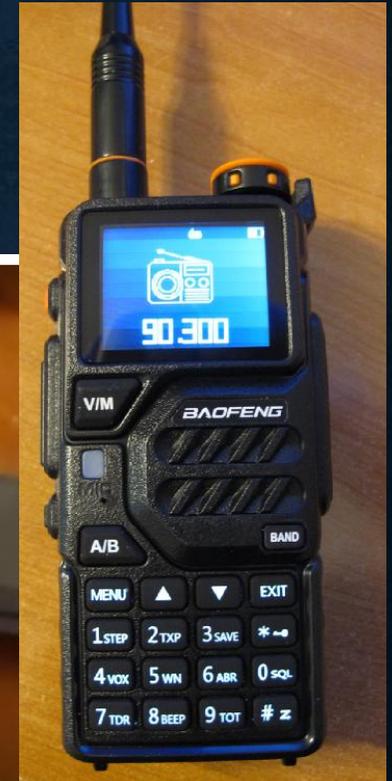A YouTube video player interface. The video shows a Yaesu Communications Receiver VR 120 with a digital display showing 90.300. The video title is "Receiver Architectures - Radio Design 101 Final Epilogue" and the timestamp is 7:43. The channel is MegawattKS with 9.87K subscribers. The video has 148 likes and options for Analytics, Edit video, Share, and Promote.



Result – Using New Technology

RD101 Radio Out-performed all 3 Commercial Ones !


(when using 200 kHz bandwidth Q-enhanced Front-End filter)



88.1 MHz



Station	dBm	ATS 25	VR-120	SW-60	RD-101*
88.1	-96				
88.9	-58				
89.5	-75				
89.9	-61				
90.3	-77				
90.5	-85				
90.7	-71				
91.3	-80				
91.9	-55				
92.5	-82				
92.7	-70				
93.3	-41				
94.5	-63				
95.3	-60				
96.3					
97.5					
97.9					

With Q-enhanced filter front-end added

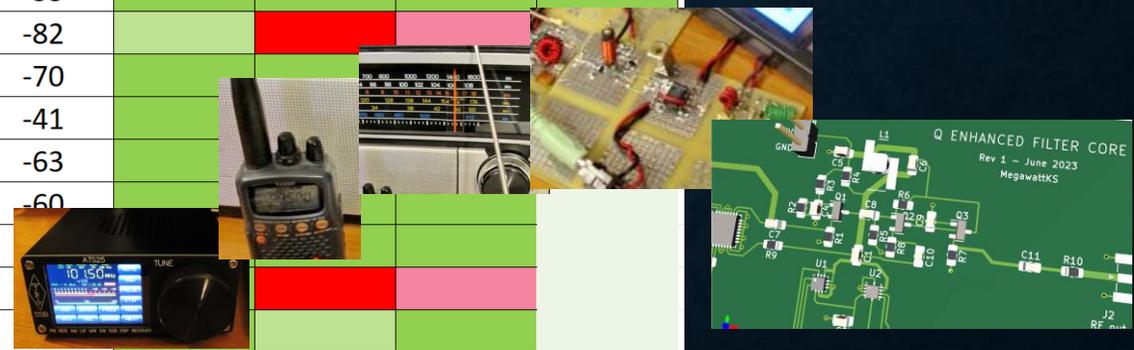


New Q-Enhanced LNA


From Radio Design 101 – Epilogue 3

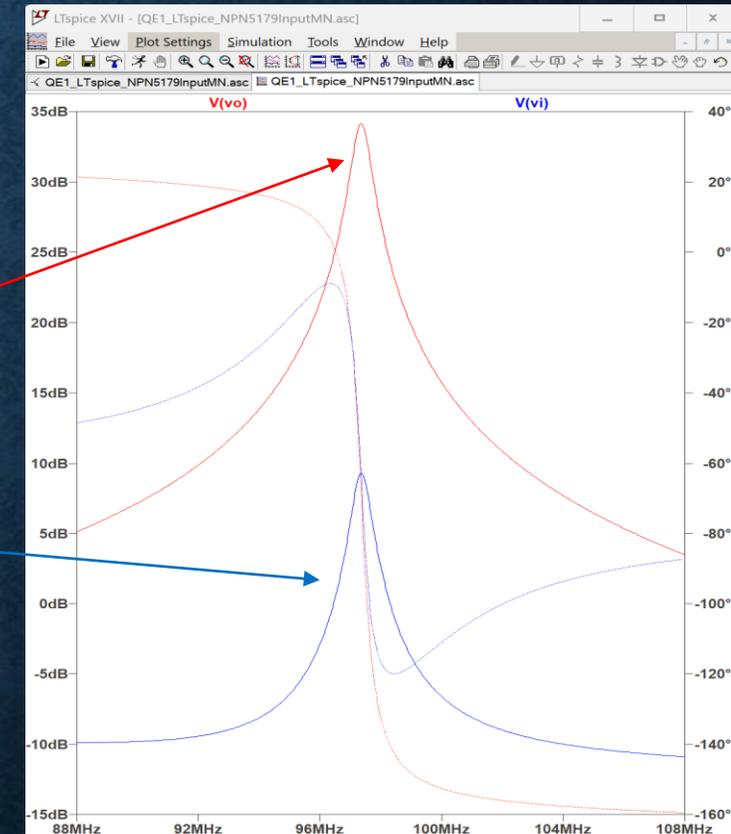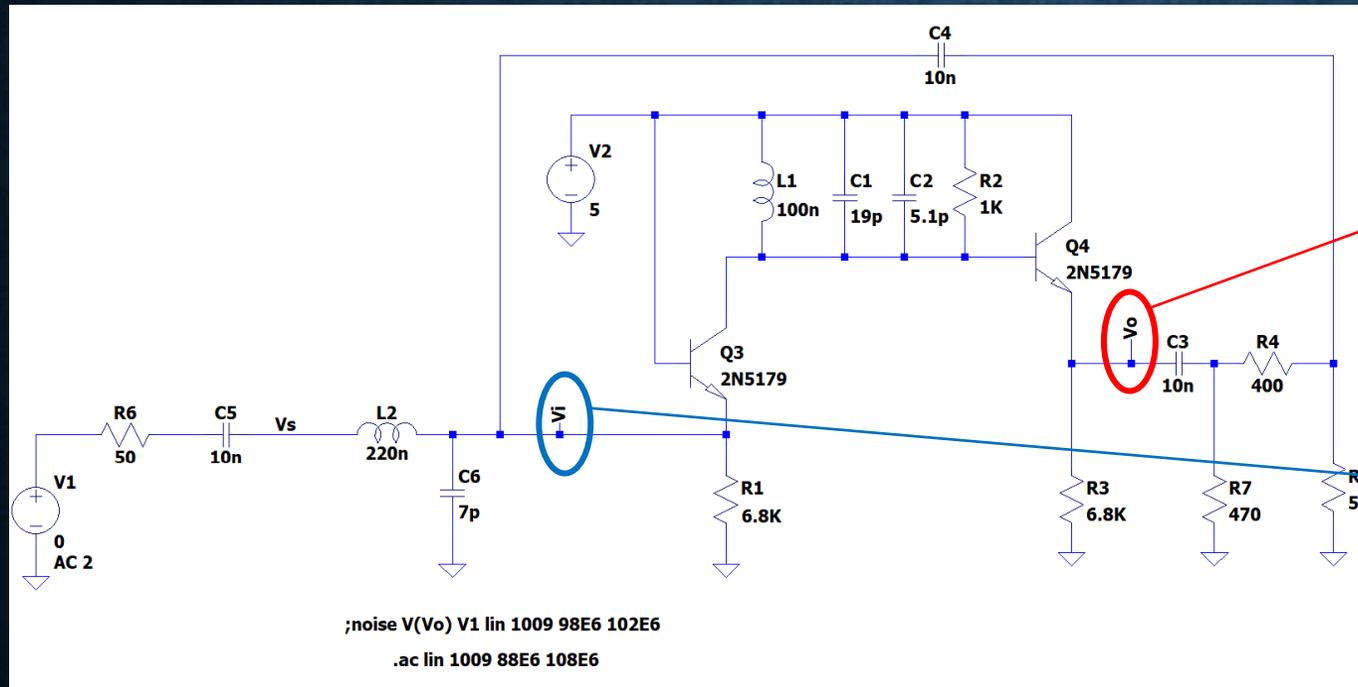

Intermodod and Noise Figure Sims

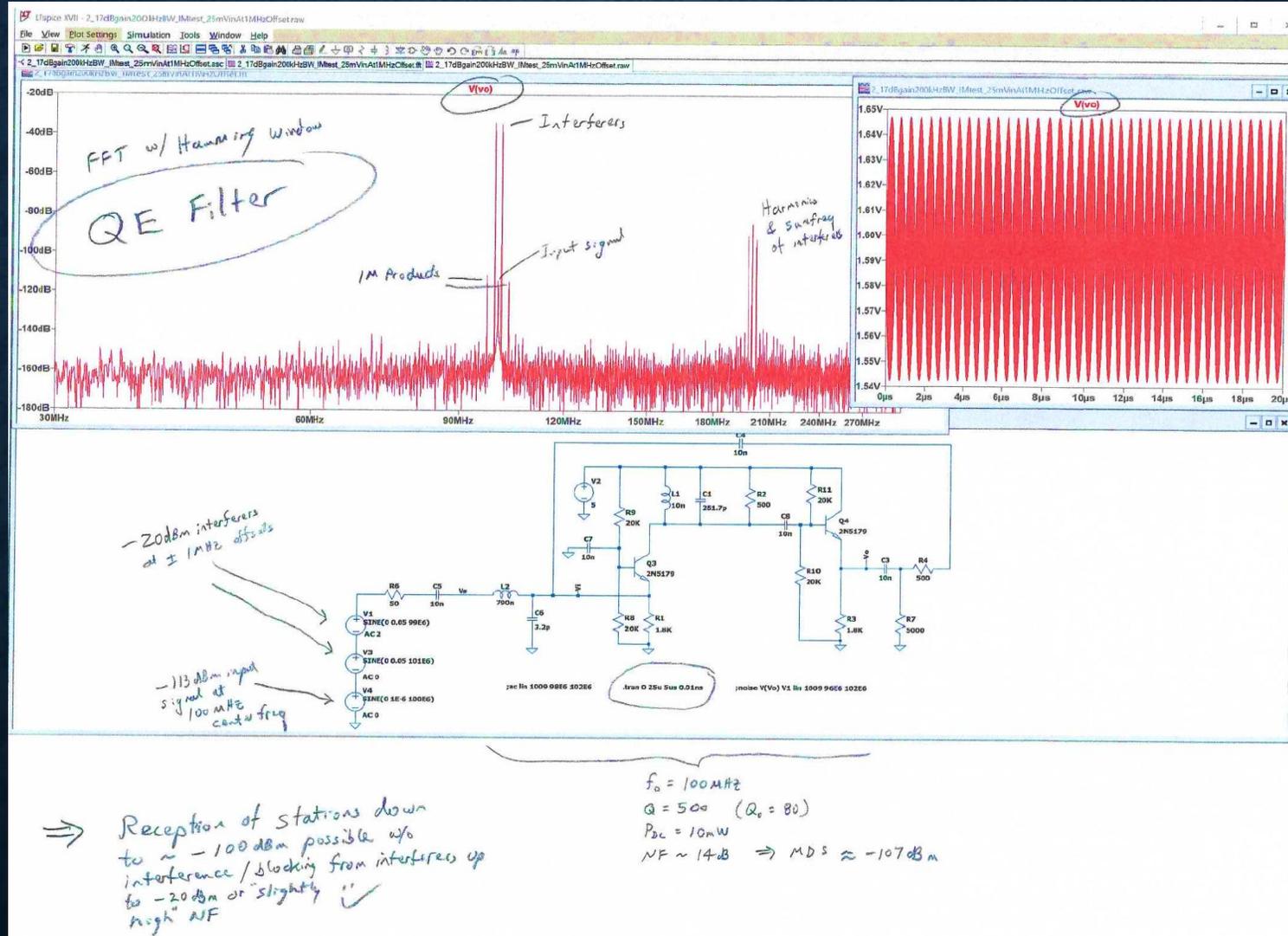


vs Traditional Low-Power LNA

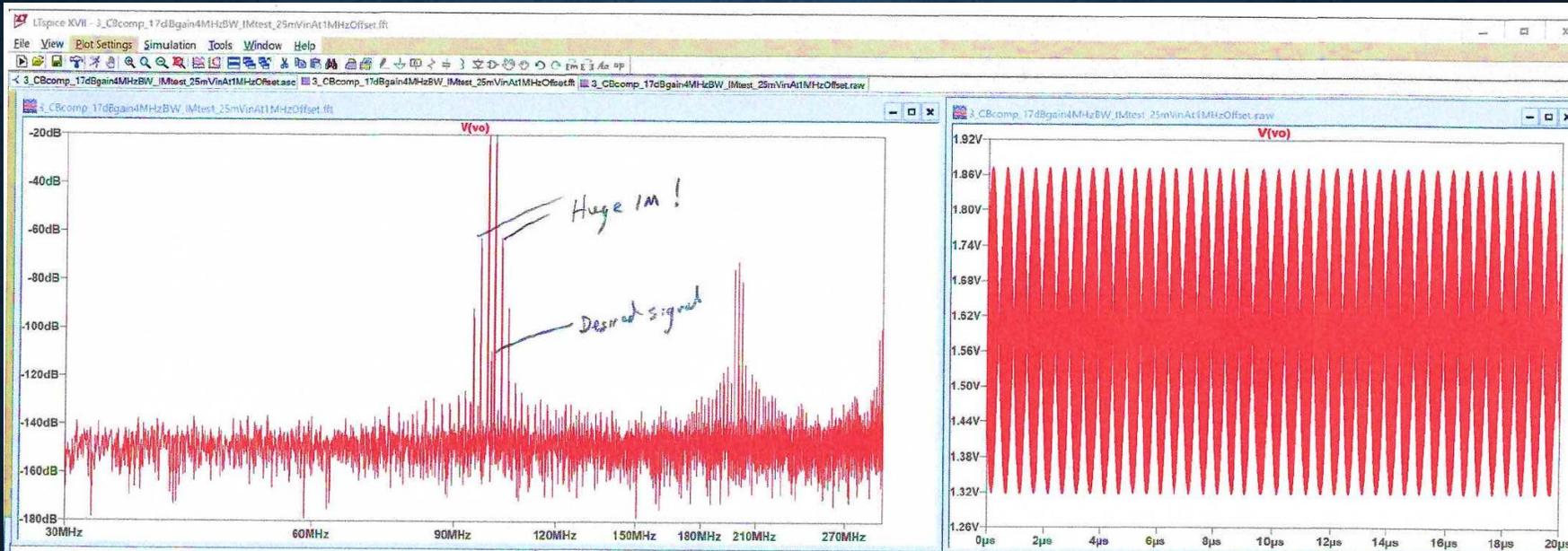


Basic CB Amp w/
Same LC & biasing but no QE

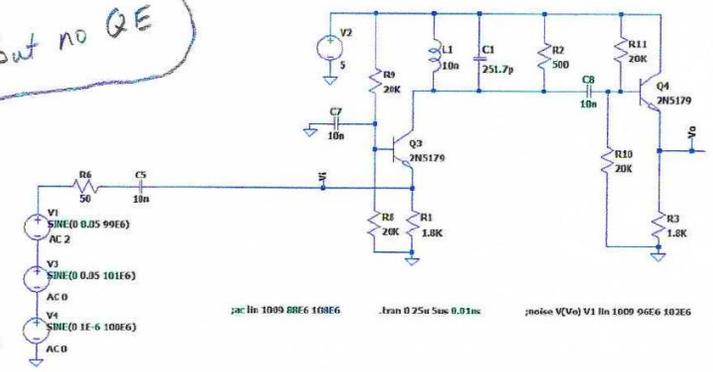NF = 4dB,
but doesn't matter
IM products are
60dB higher
in QE Filter!



Radio Design 401

Episode 1 *Part 2*

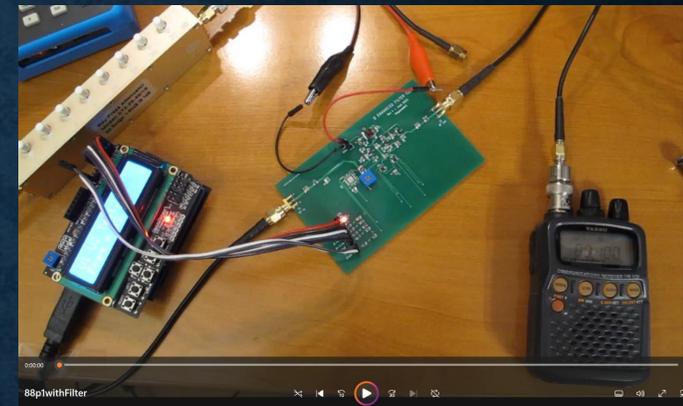


Low-power Receivers in Crowded Spectrum Environments

Today's Outline

- • *Intermodulation Problems and Solutions*
- *Basic Research in Low Power Receivers*
- *Circuit-level Solution Examples*
- *Future Episodes in This Series*

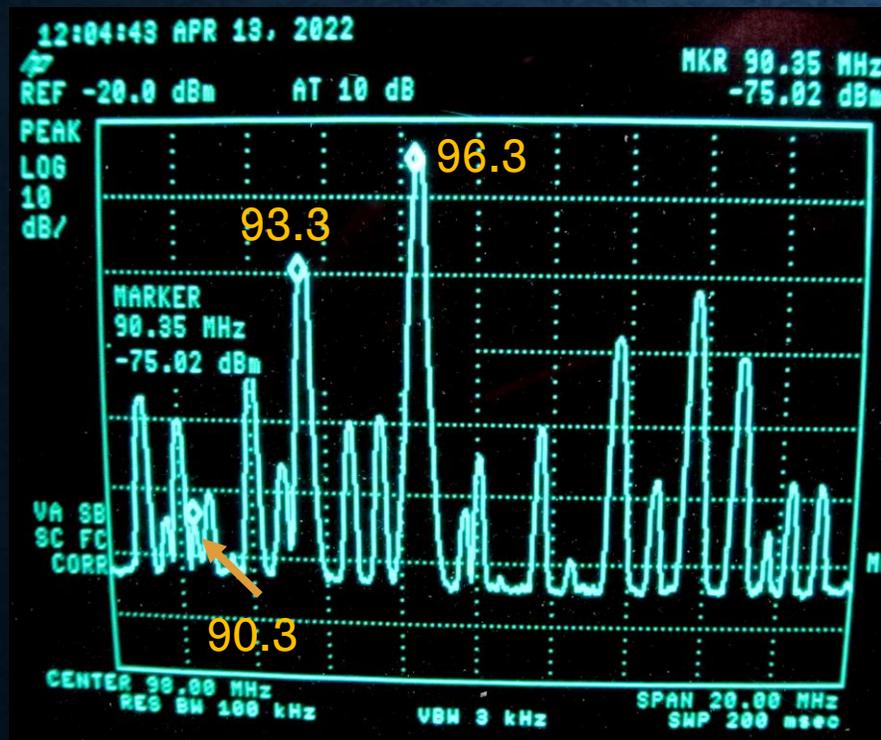
Part 1 Review – The Intermod Problem

*Two strong signals at 96.3 and 93.3 MHz ‘mix’
and block weaker (-75 dBm) signal at 90.3 MHz*




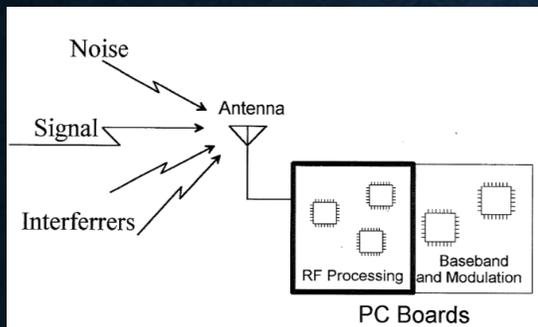Problem Origins

Strong signals inside preselect filter passband can overwhelm weak ones !



Blocking Problem

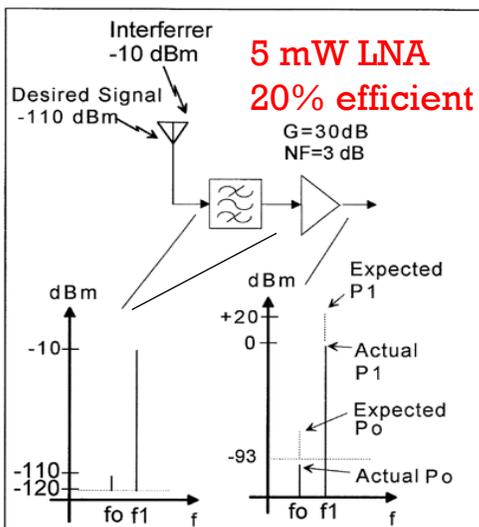

Effects

Gain compression
Desired signal below noise floor at output


Solutions

Use higher power LNA
Decrease LNA gain
Filter out f_1

NOTE

Could occur in later stages
also **Like Mixer !!**

Intermod Problem

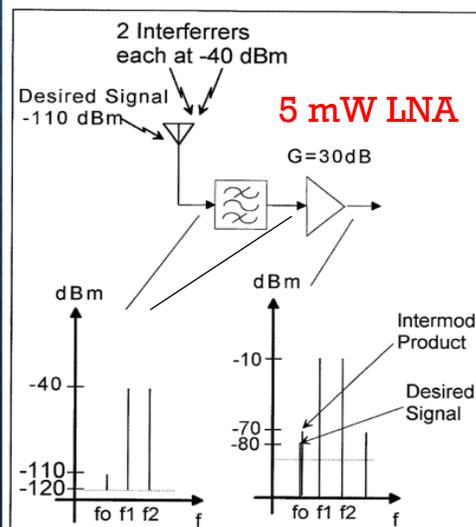

Effects

LNA generates “intermod products” at $2f_2-f_1$ & $2f_1-f_2$.
Product at $2f_1-f_2 = f_0$
overpowers desired signal.



Solutions

Use higher power LNA.
Decrease LNA gain.
Filter out f_1, f_2





NOTE

Could occur in later stages
also (especially mixer.)

Non-linear Distortion & Compression

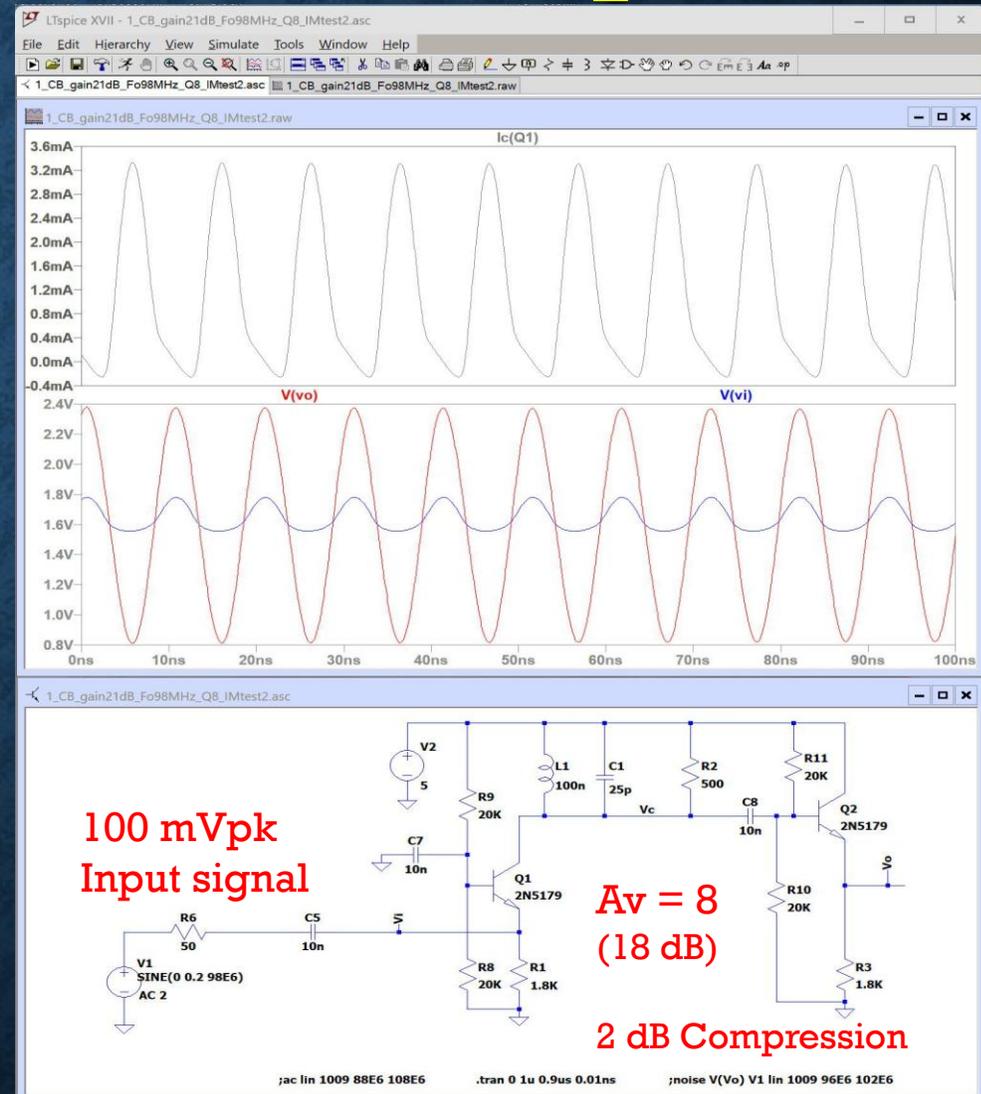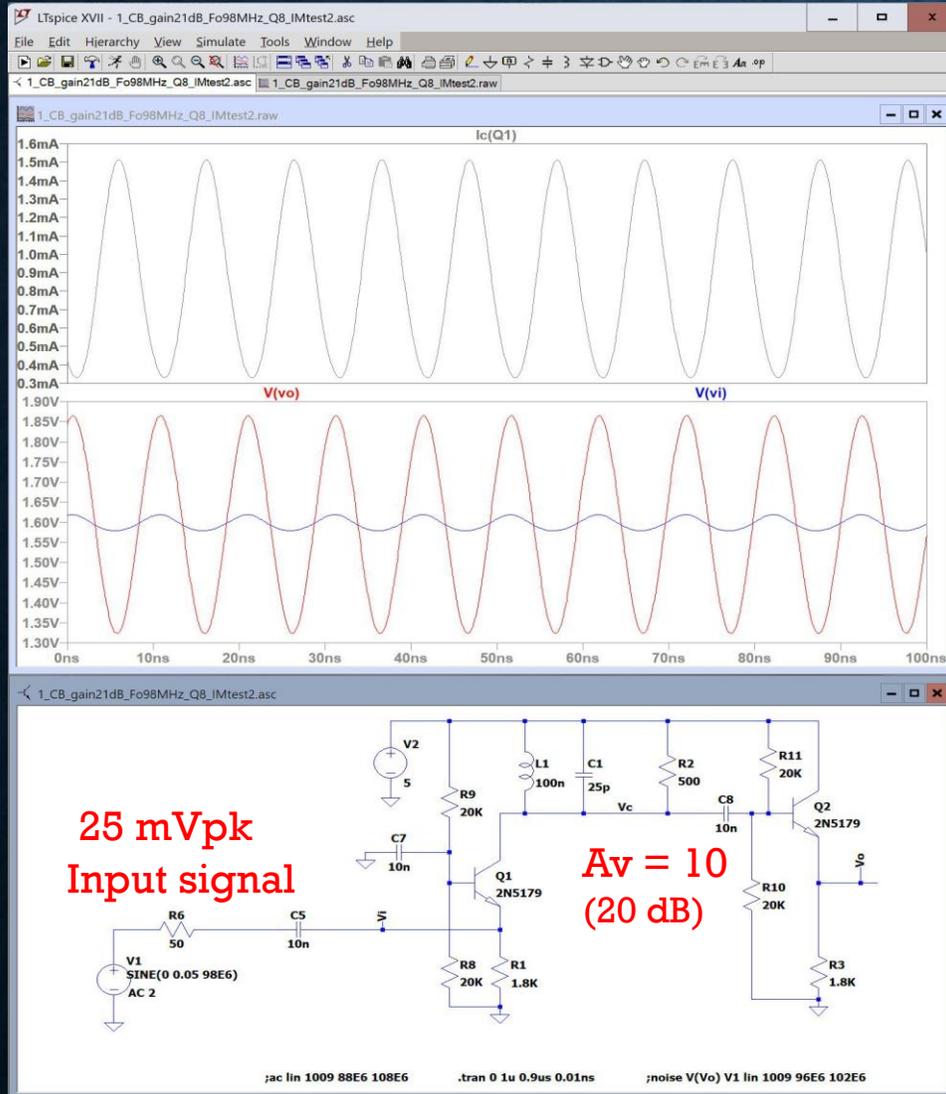


Intermod Simulation

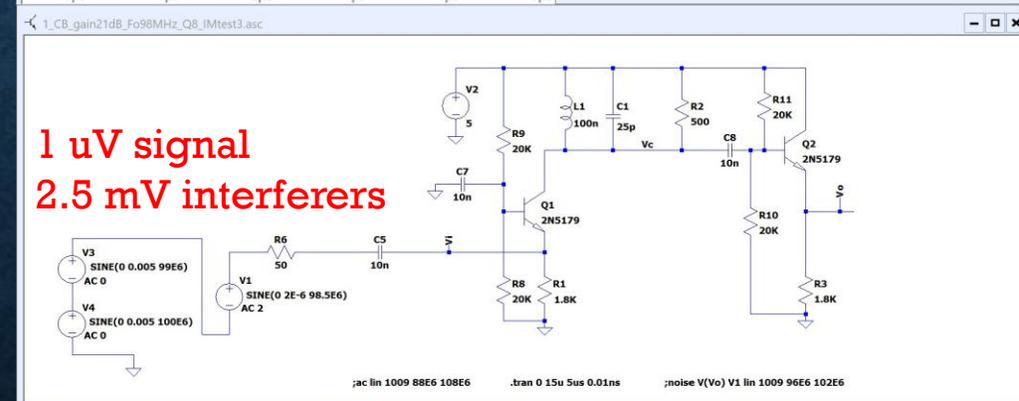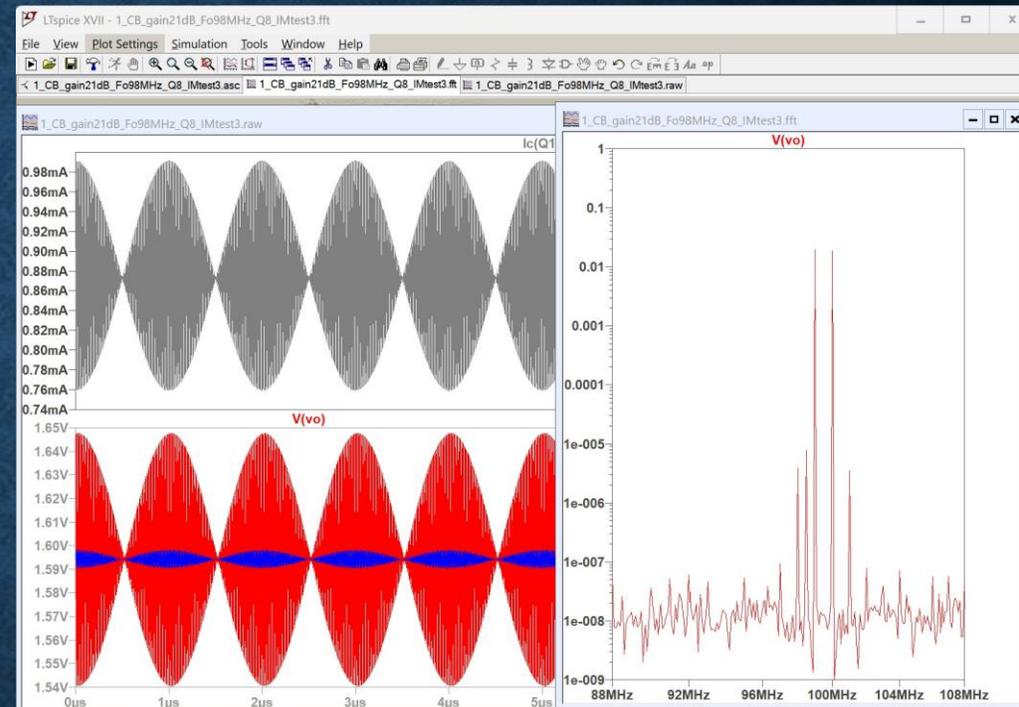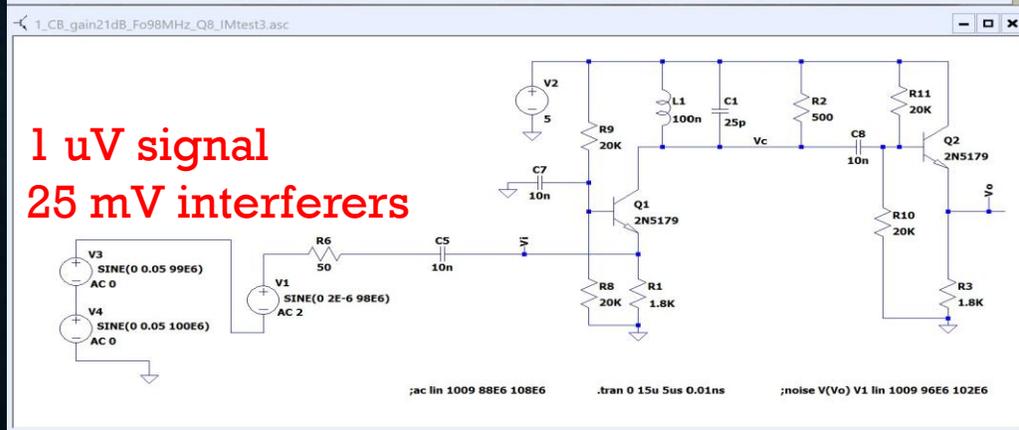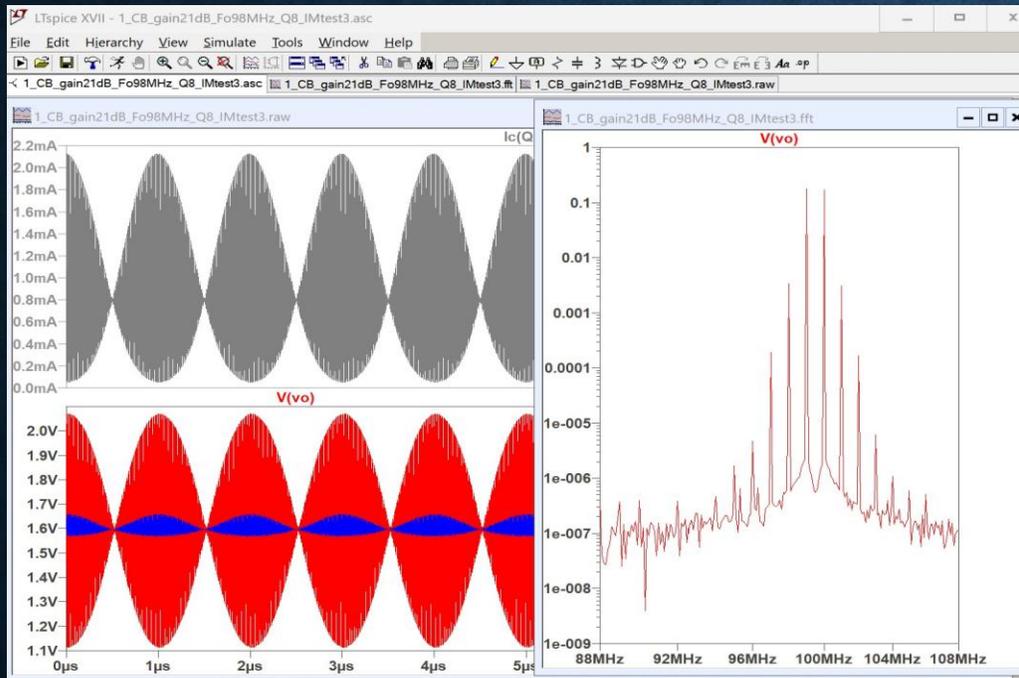

Proposed Solution

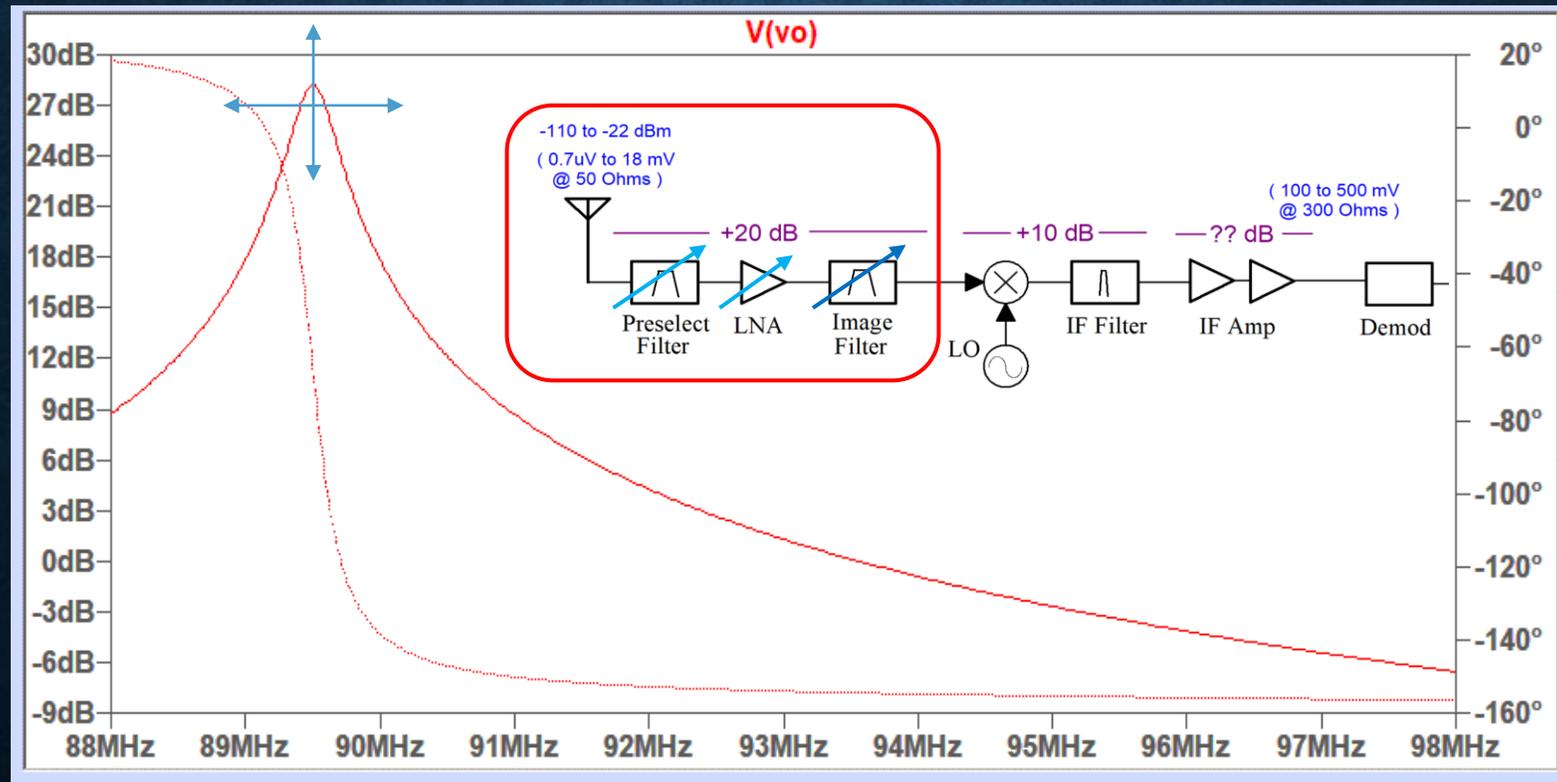
*Reduce front end bandwidth to signal bandwidth,
not just width of service-band*



Q-enhanced Filter 1st Prototype





(From Radio Design 101 Epilogue 3)

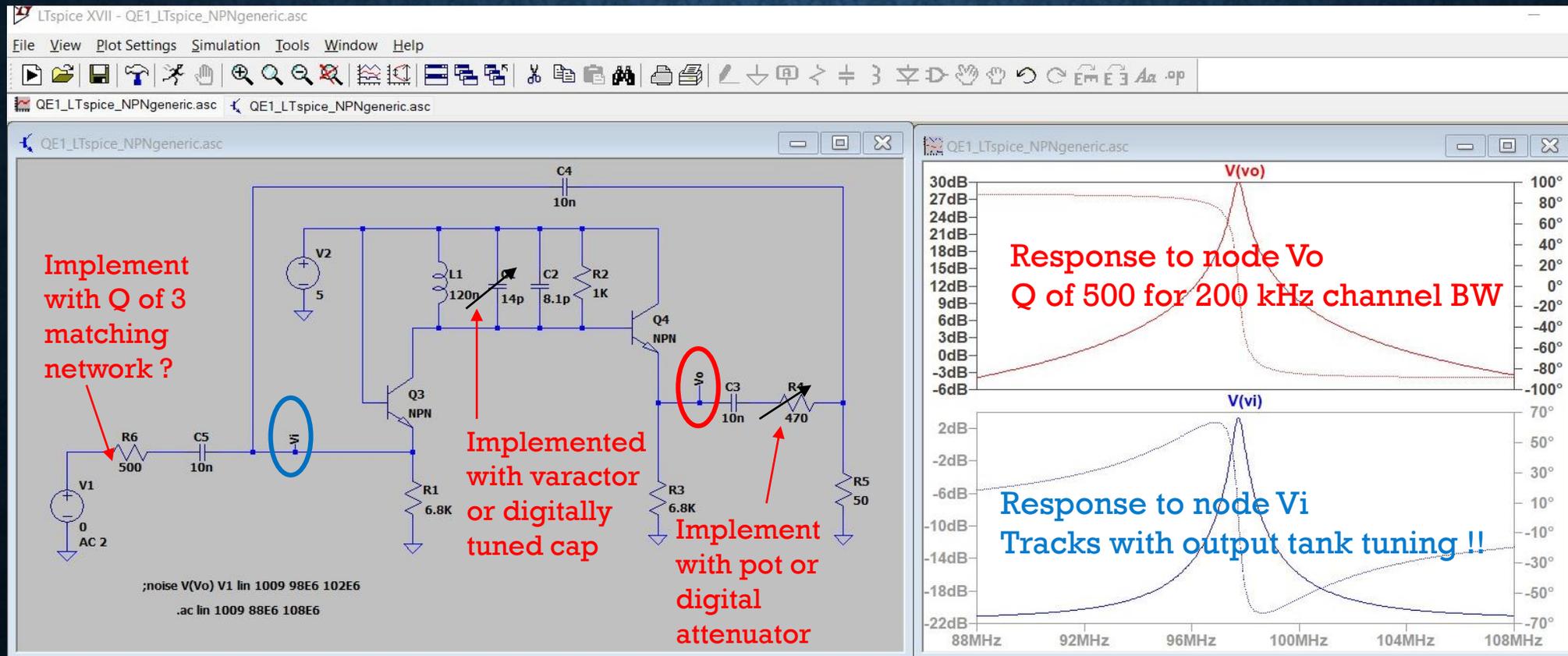Important: Provides filtering before Q3 !





1.2 mA at 5 V (6 mW)

25+ dB Improvement in SIR

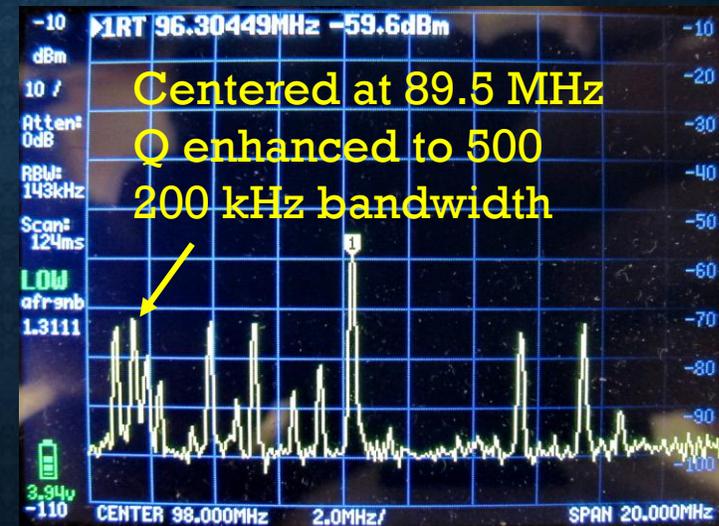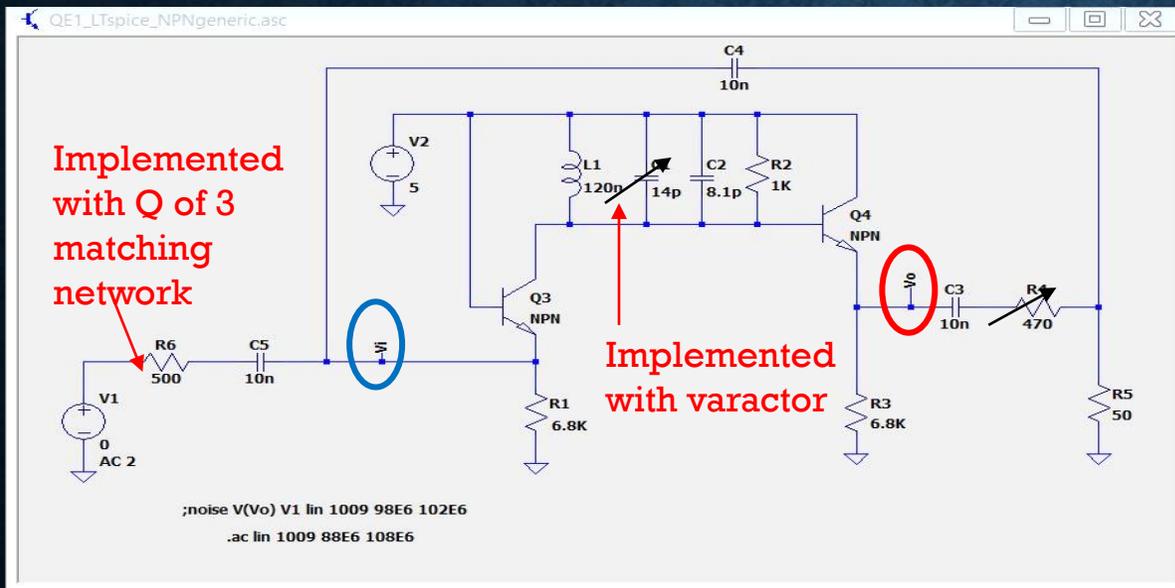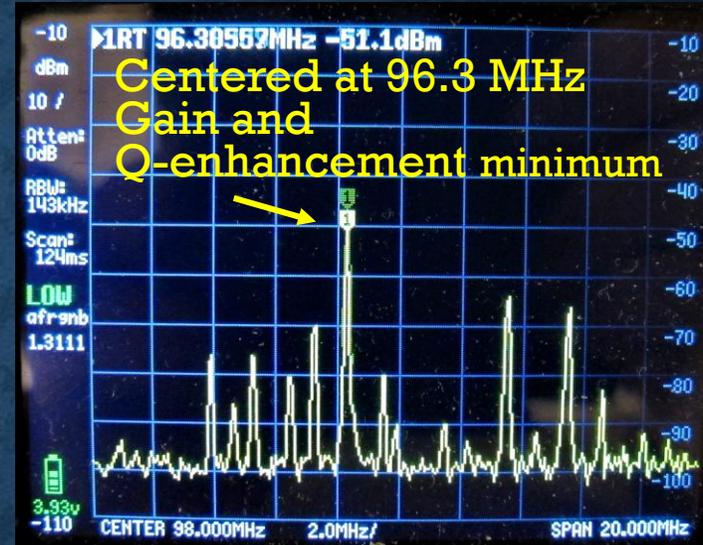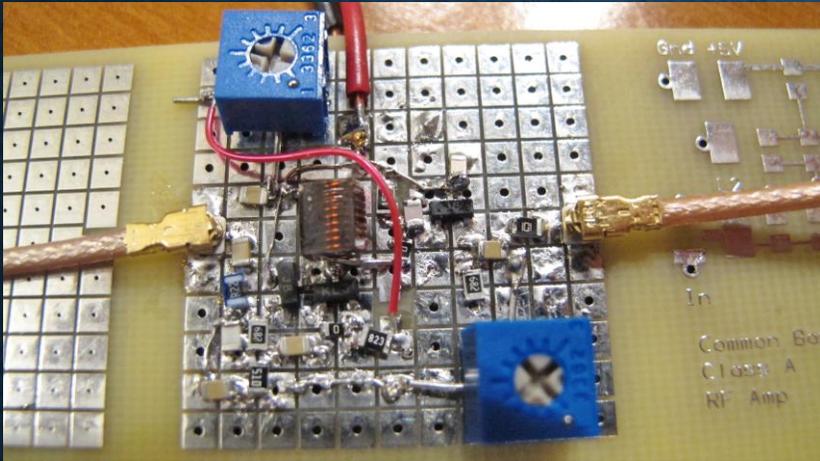


Pulling out Really Weak Signals !

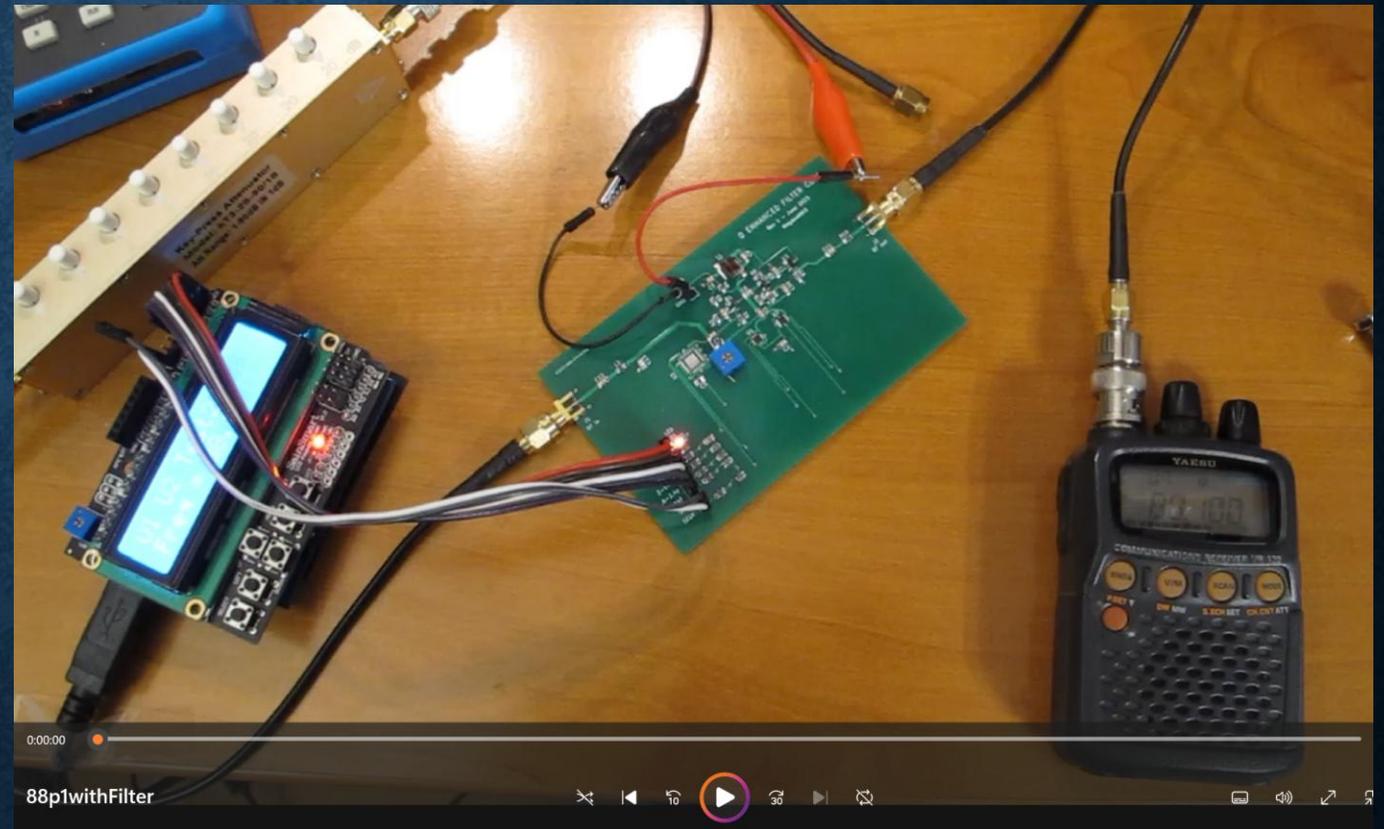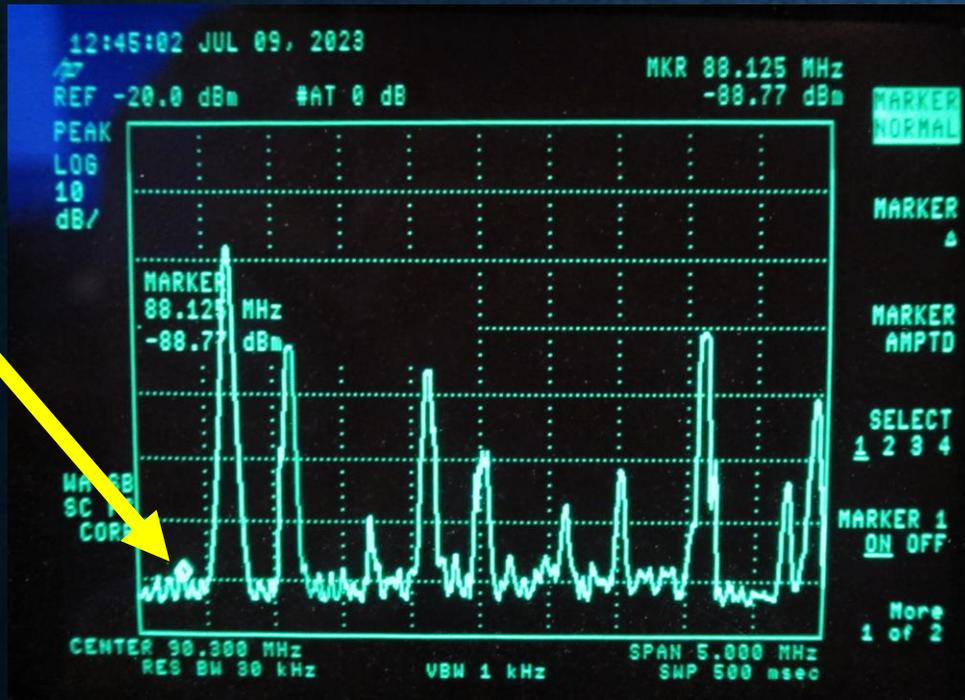

Additional Solutions

Directional and/or High Q Antennas

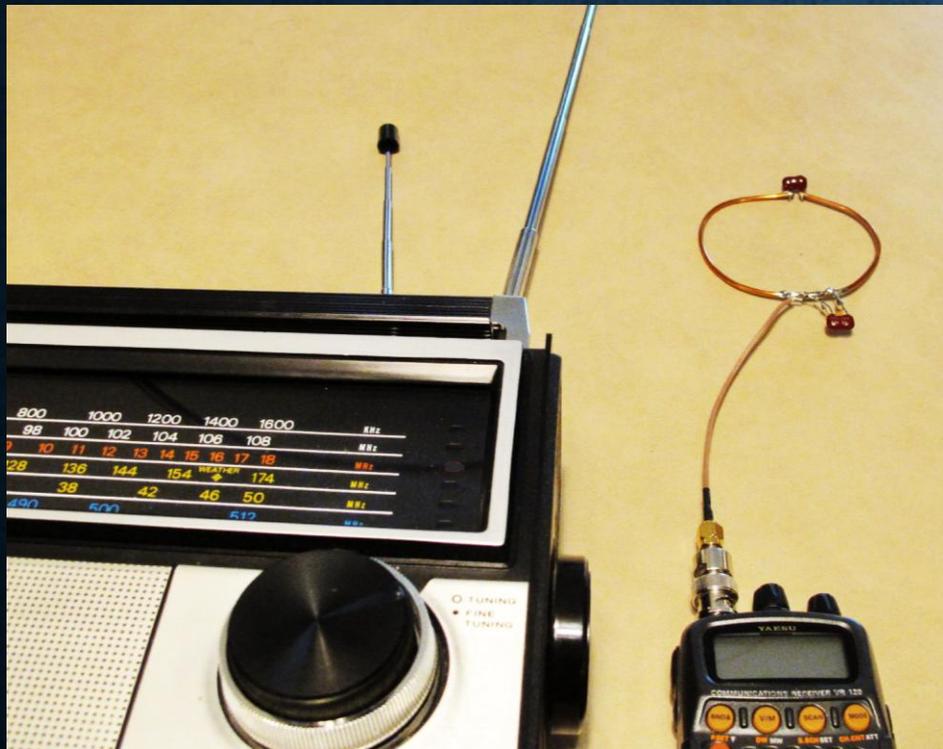

Q-Enhancement and Digitally Tuned Caps

Antenna integrated with Q-enhanced LNA

Product Specification
PE64102
UltraCMOS® Digitally Tunable Capacitor (DTC) 100-3000 MHz

General Description
The PE64102 is a DUNE™-enhanced digitally tunable capacitor (DTC) based on global UltraCMOS® technology. DTC products provide a monolithically integrated impedance tuning solution for demanding RF applications. They also offer a linear capacitance change versus tuning data and excellent harmonic performance compared to varactor-based tunable solutions.

Features

- 3-wire (SPI compatible) 5-bit serial interface with built-in base voltage generation and standby mode for reduced power consumption
- DUNE™-enhanced UltraCMOS® device

Figure 1. Functional Block Diagram

Small Loop Antennas for FM / VHF / UHF Radio Receivers - Antenna Briefs #9

MegawattKS
9.88K subscribers

Analytics Edit video

237

Share

Today's Outline



- ✓ • *Introduction*
- • *Basic Research in Low Power Receivers*
- *Circuit-level Solution Examples*
- *Future Episodes in This Series*

← Please cite as <https://www.youtube.com/user/MegawattKS>

Some Radios Through the Years

(See Part 1 & Radio Design 101, Epilogue 3)

1970s and 1980's HF radios

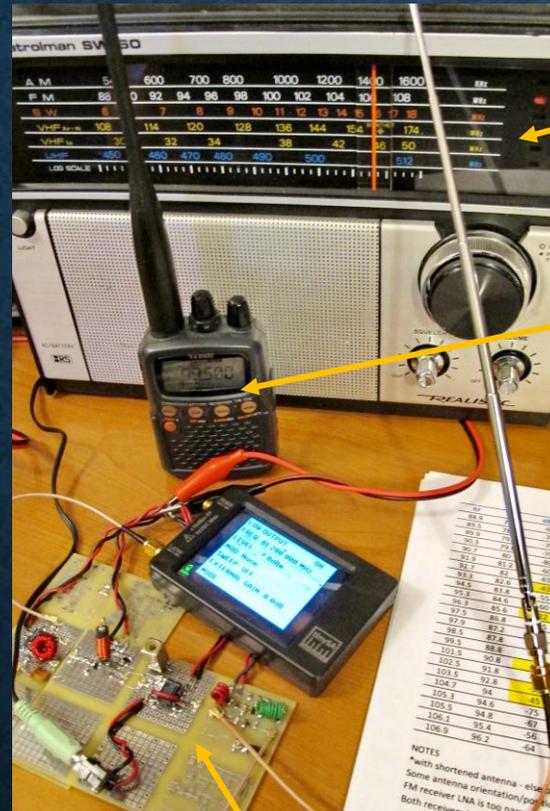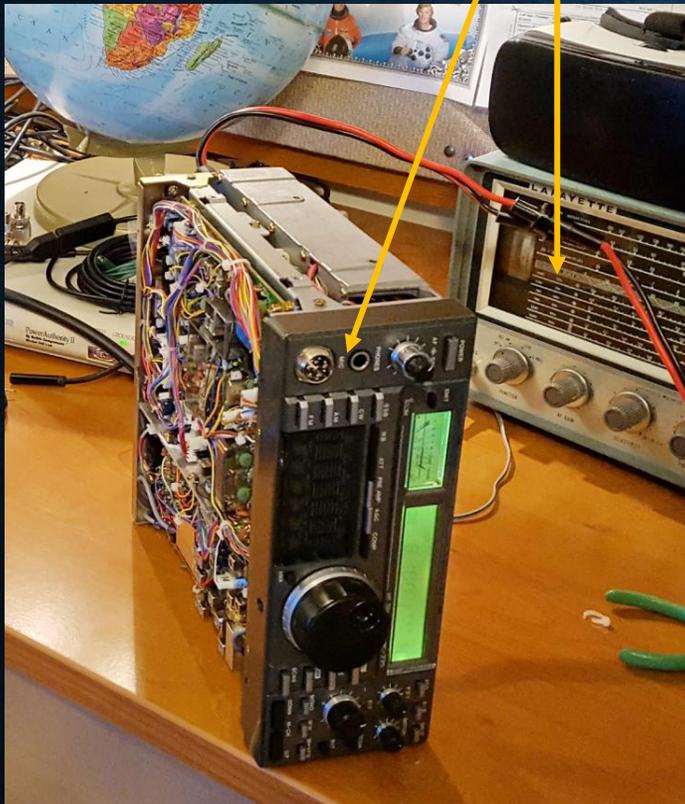

1990 Portable multi-band receiver (Patrolman SW-60)

2003 Yaesu wideband handheld receiver (VR-120)

2024 Software-Defined Radio (ATS-25)



2022 Homebrew FM superhet (From Radio Design 101 series)

Origins of This Research

4	Alternative Receiver Architectures	93
4.1	Early Receiver Architectures	94
4.1.1	Tuned RF Receivers	94
4.1.2	Regenerative Receivers	96
4.1.3	Super-Regenerative Receivers	98
4.2	Superheterodyne Receivers	100
4.2.1	Modern Single Conversion Implementations	101
4.2.2	Multiple Conversion Implementations	102
4.2.3	Up Conversion Implementations	104
4.2.4	Designs with Ultra-Low IFs	106
4.2.5	Designs with Image Rejection Mixers	108
4.2.6	Designs with Selective Demodulators	109
4.3	Direct Conversion Receivers	110
4.4	Digital Receivers	113
4.5	Ideal Low-Power Receivers	115

From: “Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies”,
William B. Kuhn, PhD dissertation, Virginia Tech, 1995 .

Some Related Research Papers

ieeexplore.ieee.org/abstract/document/1237356

IEEE.org | IEEE Xplore | IEEE SA | IEEE Spectrum | More Sites

IEEE Xplore® Browse My Settings Help Institutional Sign In

All

Journals & Magazines > IEEE Transactions on Circuits... > Volume: 50 Issue: 10

Dynamic range performance of on-chip RF bandpass filters

Publisher: IEEE

Cite This PDF

W.B. Kuhn; D. Nobbe; D. Kelly; A.W. Orsborn All Authors

61 Cites in Papers 1424 Full Text Views

Abstract

Document Sections

I. Introduction

II. Filter Technologies

III. DR Requirements

Active

Abstract: Despite decades of research in developing "single-chip" radio transceivers, most commercial designs continue to rely on off-chip components for RF bandpass filtering. Implementing these filters on-chip remains nearly as challenging today as it was ten years ago due to problems in meeting system requirements. Recent advances in silicon-on-insulator IC processes targeted at RF designs, however, offer the possibility of producing commercially-viable on-chip filters in the coming years using Q-enhancement techniques. This paper reviews filter implementation alternatives and dynamic range (DR) requirements, illustrating the fundamental advantages of Q-

Total citations Cited by 114

https://scholar.google.com/scholar?oi=bibs&hl=en&cites=2076378922797813086&as_sdt=5&as_ylo=2024&as_yhi=2024

Year	Total Citations
09	10
2010	12
2011	15
2012	10
2013	12
2014	8
2015	5
2016	18
2017	12
2018	15
2019	8
2020	5
2021	12
2022	10
2023	8
2024	15

Scholar 6 results (0.02 sec)

Dynamic range performance of on-chip RF bandpass filters

Search within citing articles

2024 - 2024

Nanofabricated high turn-density spiral coils for on-chip electromagneto-optical conversion [PDF] nature.com

I.Bok, A.Ashtiani, Y Gokhale, J Phillips, T.Zhu... - Microsystems & ..., 2024 - nature.com

Circuit-integrated electromagnets are fundamental building blocks for on-chip signal transduction, modulation, and tunability, with specific applications in environmental and ...

Save Cite Cited by 2 Related articles All 8 versions

Interferer-Tolerant RX Front-End Architectures [PDF] ieee.org

D.Manstretta - 2024 IEEE Custom Integrated Circuits ..., 2024 - ieeexplore.ieee.org

The proliferation of multiple bands dedicated to mobile communications in the frequency range 1 (FR 1), below 7.1 GHz, has multiplied the sources of interference in wireless ...

Save Cite Related articles All 2 versions

A 0.1-1 GHz N-path Bandpass Filter with High In-band Linearity [PDF] ieee.org

X Luo, S Xu, S Qi, H Xia, G Wu... - 2024 3rd International ..., 2024 - ieeexplore.ieee.org

A design methodology of high-order N-path active filter with high in-band linearity is introduced. Based on 130 nm CMOS SOI process, a tunable 6th-order differential N-path ...

Save Cite Related articles

5G SAW-less FDD architecture design [PDF] unipv.it

S Lecchi - 2024 - iris.unipv.it

This thesis introduces a new Full-Duplex (FD) architecture for mobile communication standards, eliminating the need for external Surface Acoustic Wave (SAW) filters. It starts ...

Save Cite Related articles All 3 versions

Why Does this Research Matter ?

- Receive more stations !
- Also ...
 - Spectrums have become more crowded
 - Need more efficient use of spectrum resources
 - Regulatory agencies are focusing increasingly on receiver performance
 - ITU Internationally
 - NTIA and FCC in United States
 - Low-power consumption is good for IOT and energy harvesting radios
 - Power reductions of 10x to 100x or more may be possible

Regulatory Focus on Receivers

2023

FCC FACT SHEET*

Principles for Promoting Efficient Use of Spectrum and Opportunities for New Services Policy Statement, ET Docket No. 23-122

Background: The demand for spectrum continues to grow dramatically. As the Commission continuously evaluates opportunities to identify new sources of licensed, unlicensed, and shared spectrum to satisfy this growing demand, it must find ways to promote more intensive use of spectrum while ensuring coexistence among both new and existing services.



This Policy Statement takes a fresh look at the Commission's spectrum management principles and provides guidance on how the Commission intends to manage spectrum efficiently and effectively going forward. In particular, it seeks to promote a balanced and comprehensive approach to spectrum management that holistically considers both the transmitter and receiver components of wireless systems, consistent with the goals of the FCC's April 2022 *Notice of Inquiry on Promoting Efficient Use of Spectrum through Improved Receiver Interference Immunity Performance* (ET Docket No. 22-173). The

<https://docs.fcc.gov/public/attachments/DOC-392197A1.pdf>

See also: <https://its.ntia.gov/publications/download/TR-03-404.pdf>





Radio Design 401

Episode 1 *Part 3 of 3*

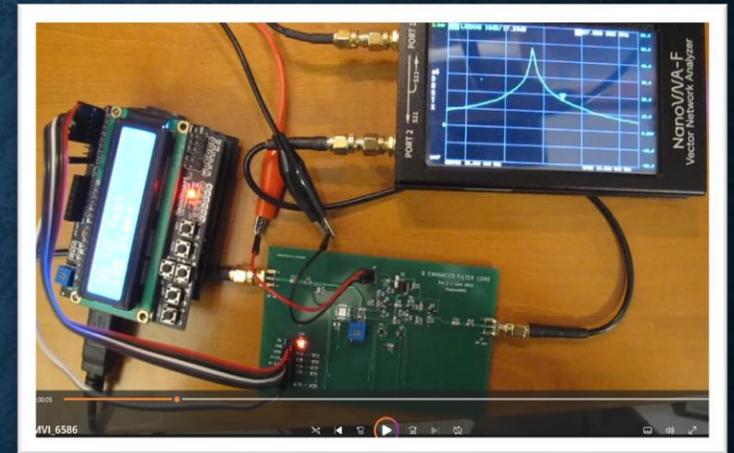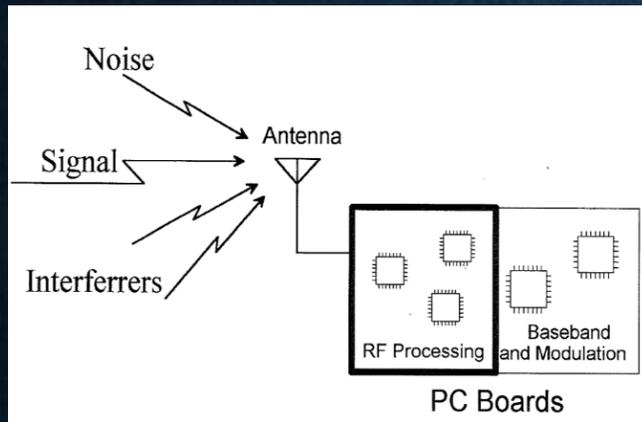


Low-power Receivers in Crowded Spectrum Environments

Receiver Signal Environment

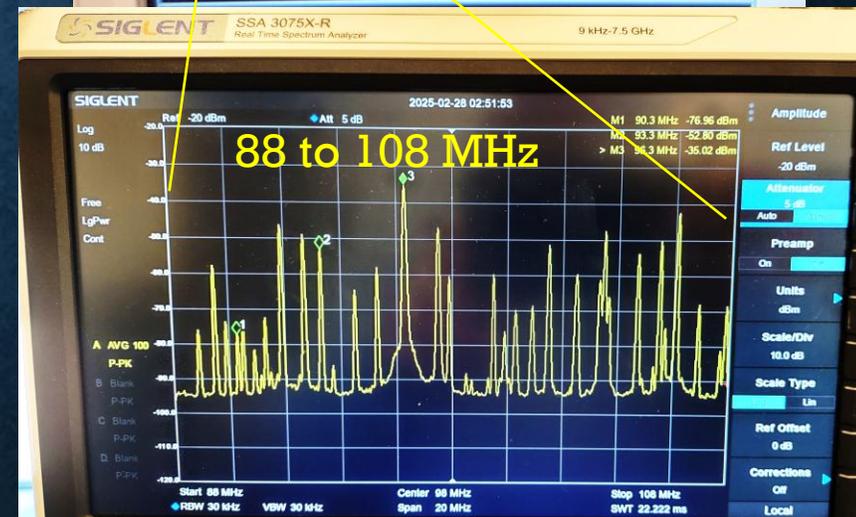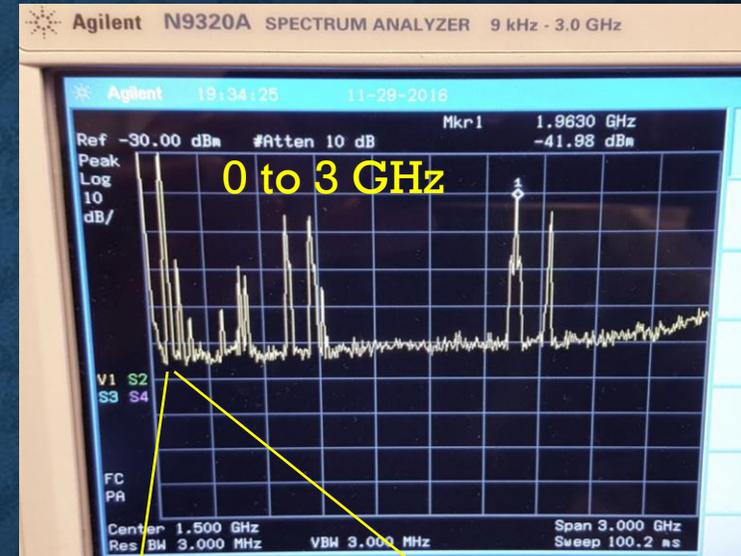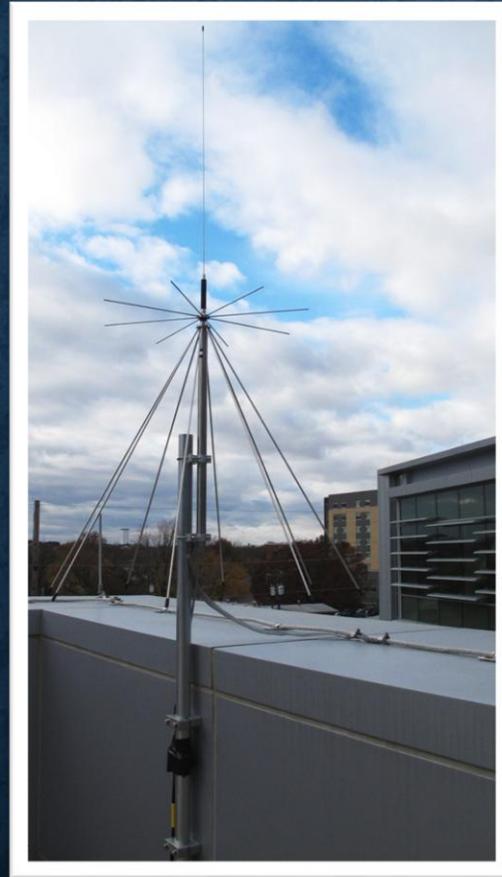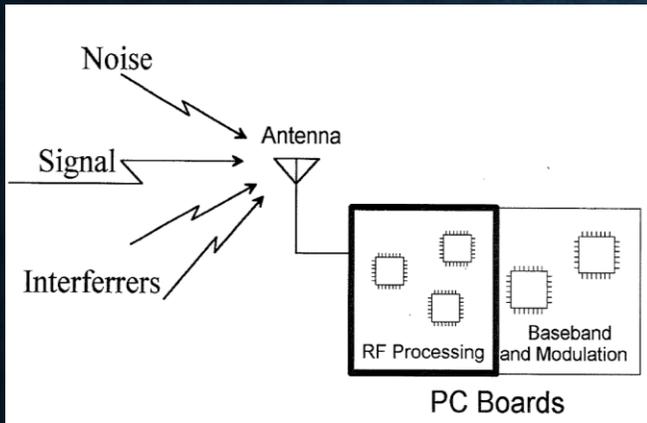

Classic Superhet Receiver

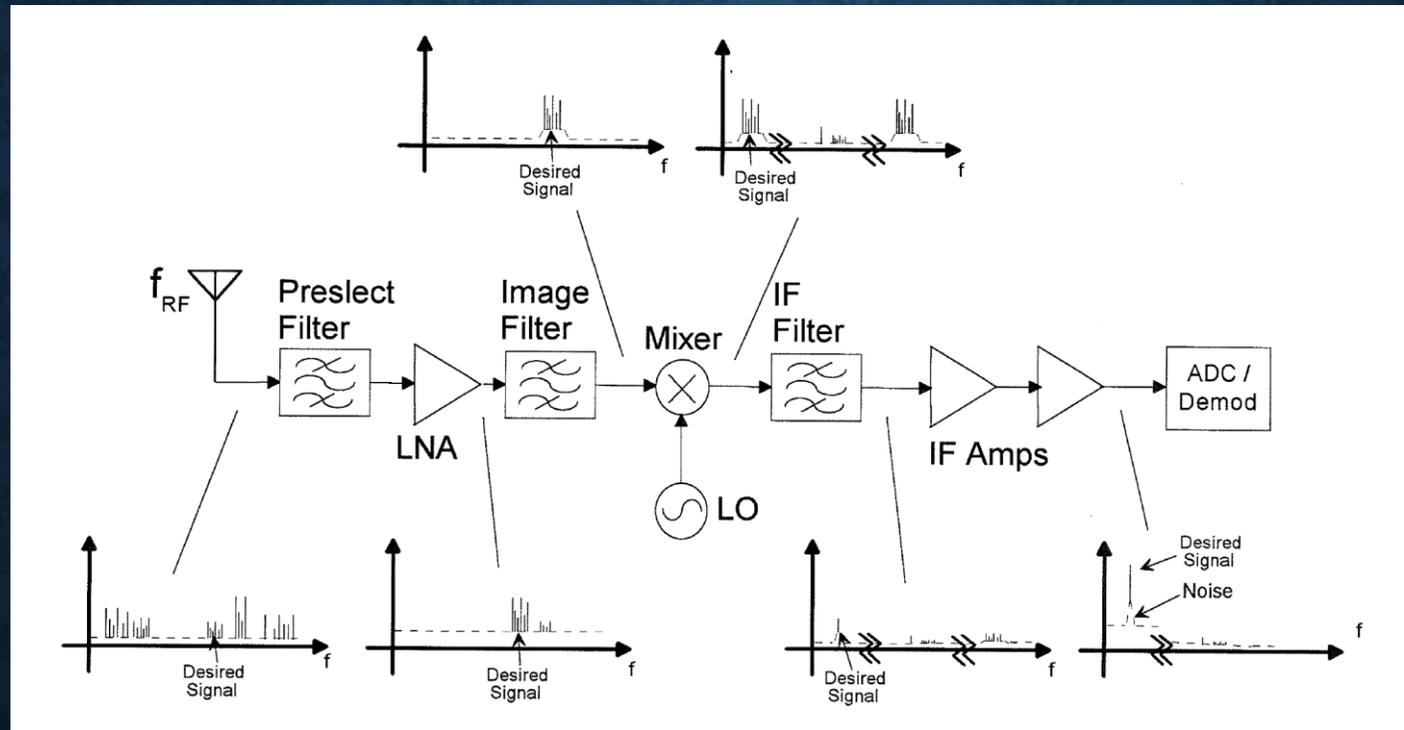


Passes entire “service band” to LNA and mixer




Blocking and Intermod Issues

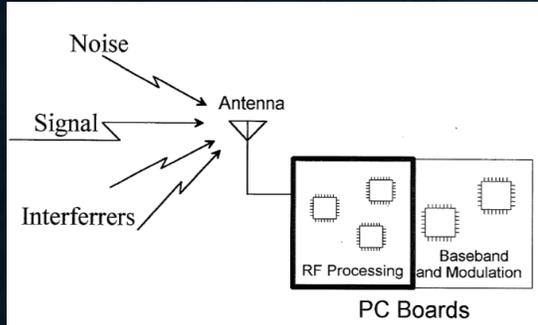Strong interferers can overwhelm weak signals !



Blocking Problem

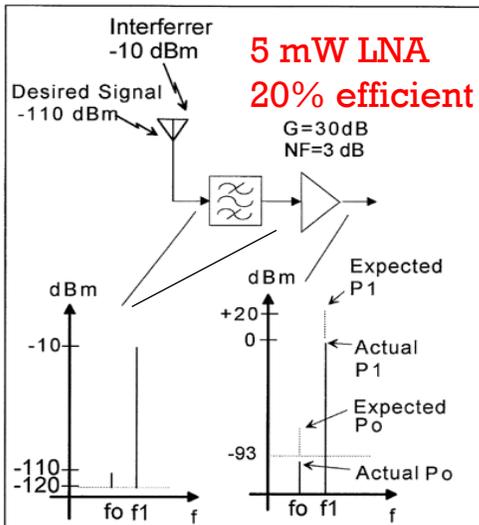

Effects

Gain compression
Desired signal below noise floor at output


Solutions

Use higher power LNA
Decrease LNA gain
Filter out f_1

NOTE

Could occur in later stages
also **Like Mixer !!**

Intermod Problem

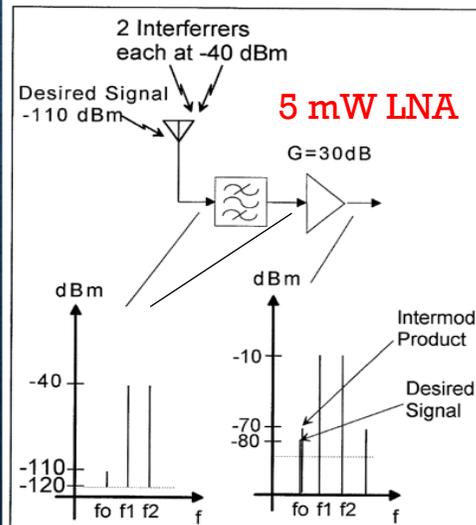

Effects

LNA generates “intermod products” at $2f_2-f_1$ & $2f_1-f_2$.
Product at $2f_1-f_2 = f_0$
overpowers desired signal.


Solutions

Use higher power LNA.
Decrease LNA gain.
Filter out f_1, f_2

NOTE


Could occur in later stages
also (especially mixer.)

Receiver Sensitivity Limitations

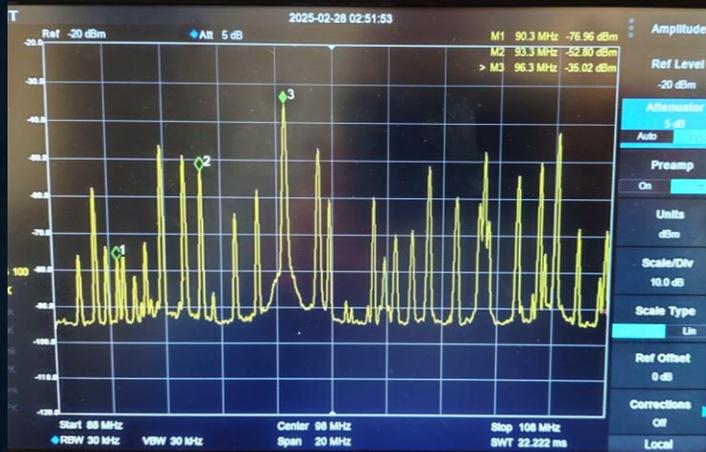




Typical receiver may miss half the available signals or more (Car radios are better, depending on where they're parked)

Spectrum analyzer Noise Figure = 30 dB !

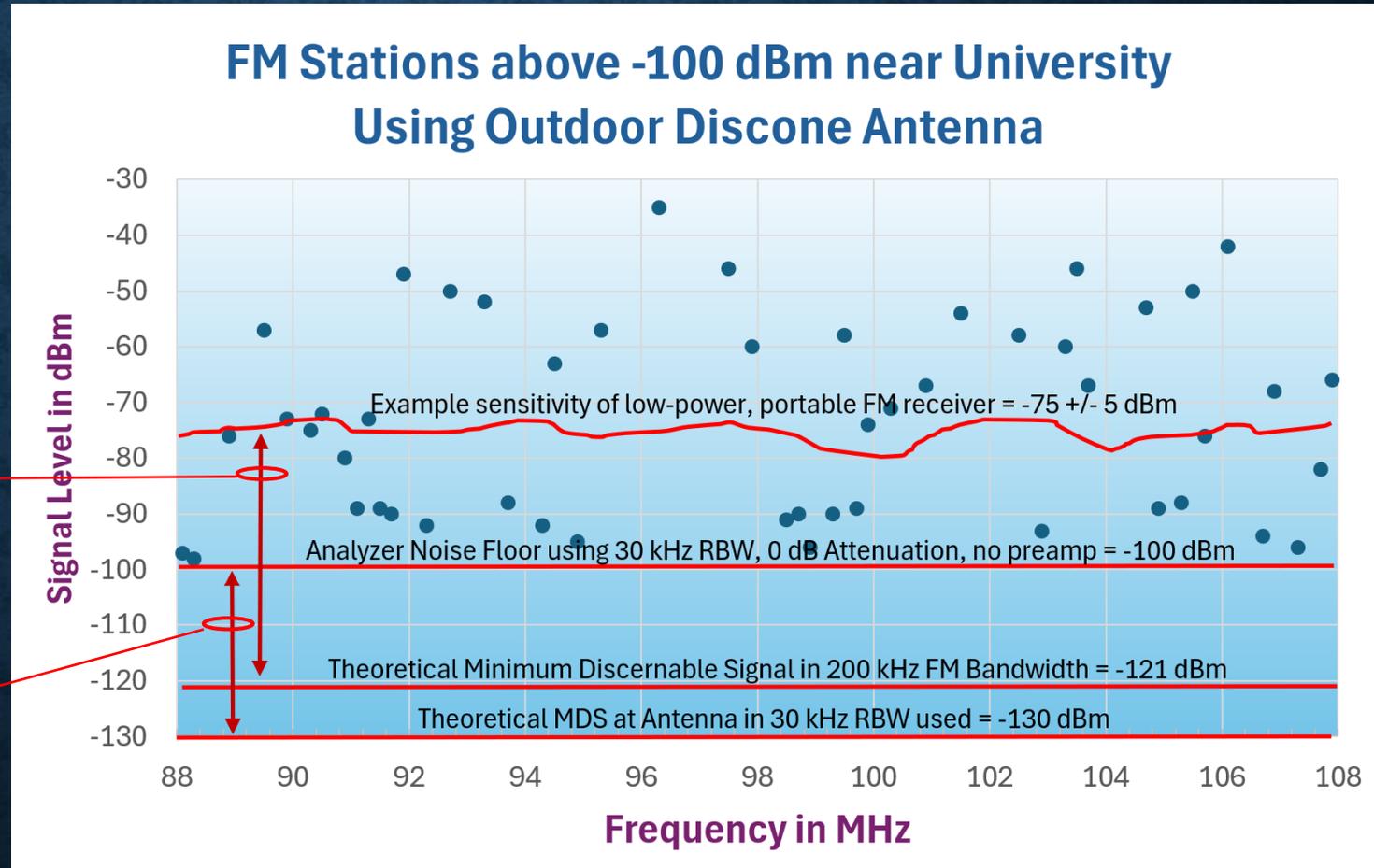

Additional Receiver Architectures

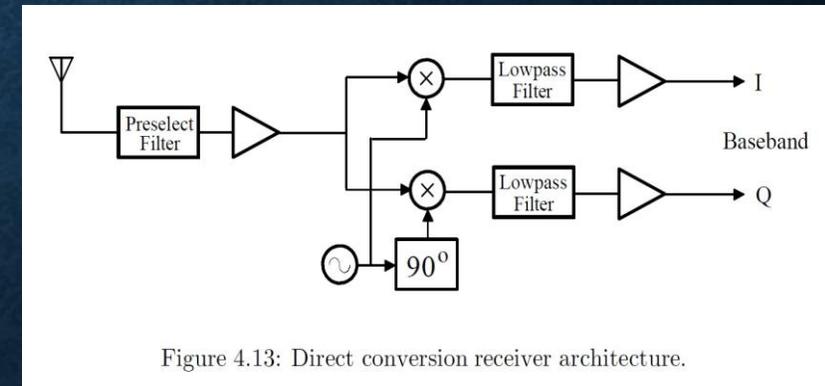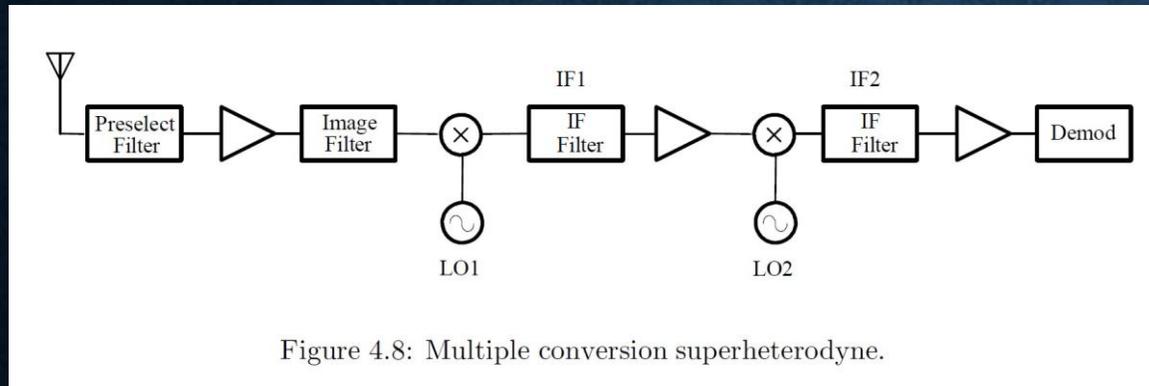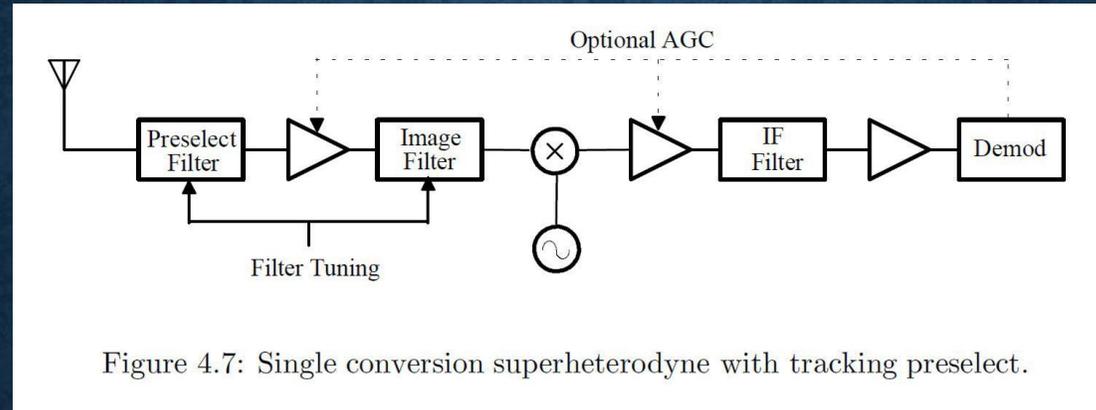Motivated mostly by “image” problems in down-conversion.
Still passes all (or most) of service band to LNA and mixer ☹️



See Radio Design 101 video series, Epilogue 3

Ideal Low Power Receiver

Reduce Preselect Filter bandwidth to signal bandwidth !

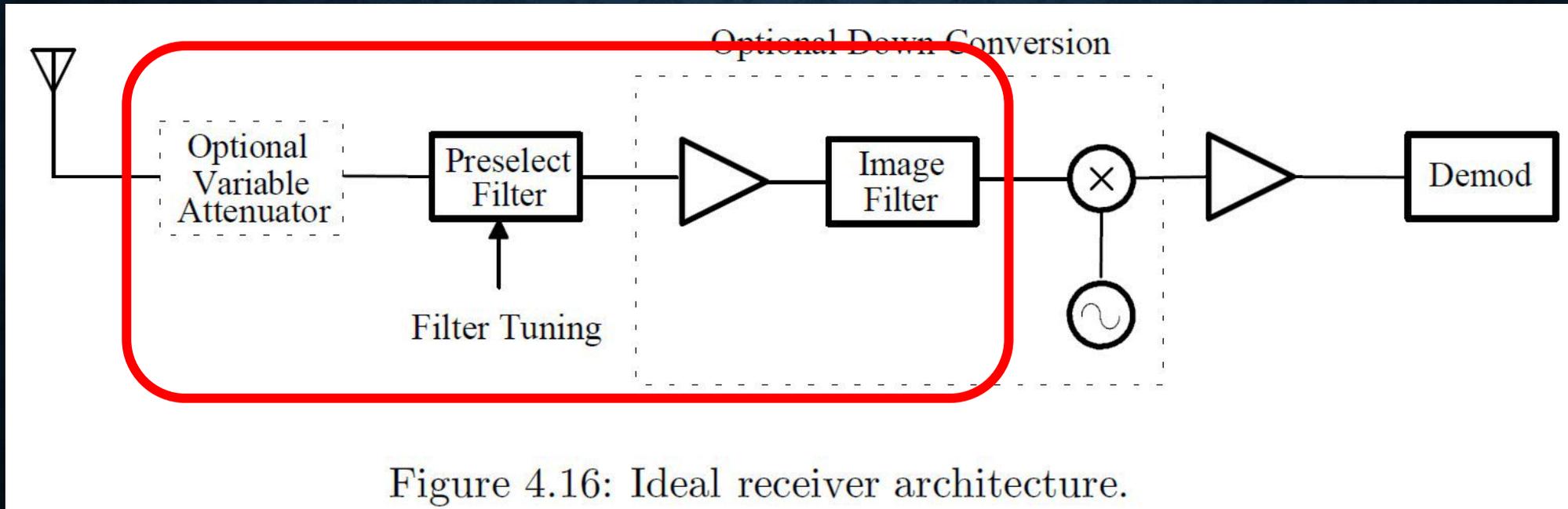


Figure 4.16: Ideal receiver architecture.


From: “Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies”,
PhD dissertation, Virginia Tech, 1995

Today's Outline

- ✓ • *Introduction*
- ✓ • *Basic Research in Low Power Receivers*
- • *Circuit-level Solution Examples*
- *Key Takeaways*
- *Future Episodes in This Series*

Proposed Solution

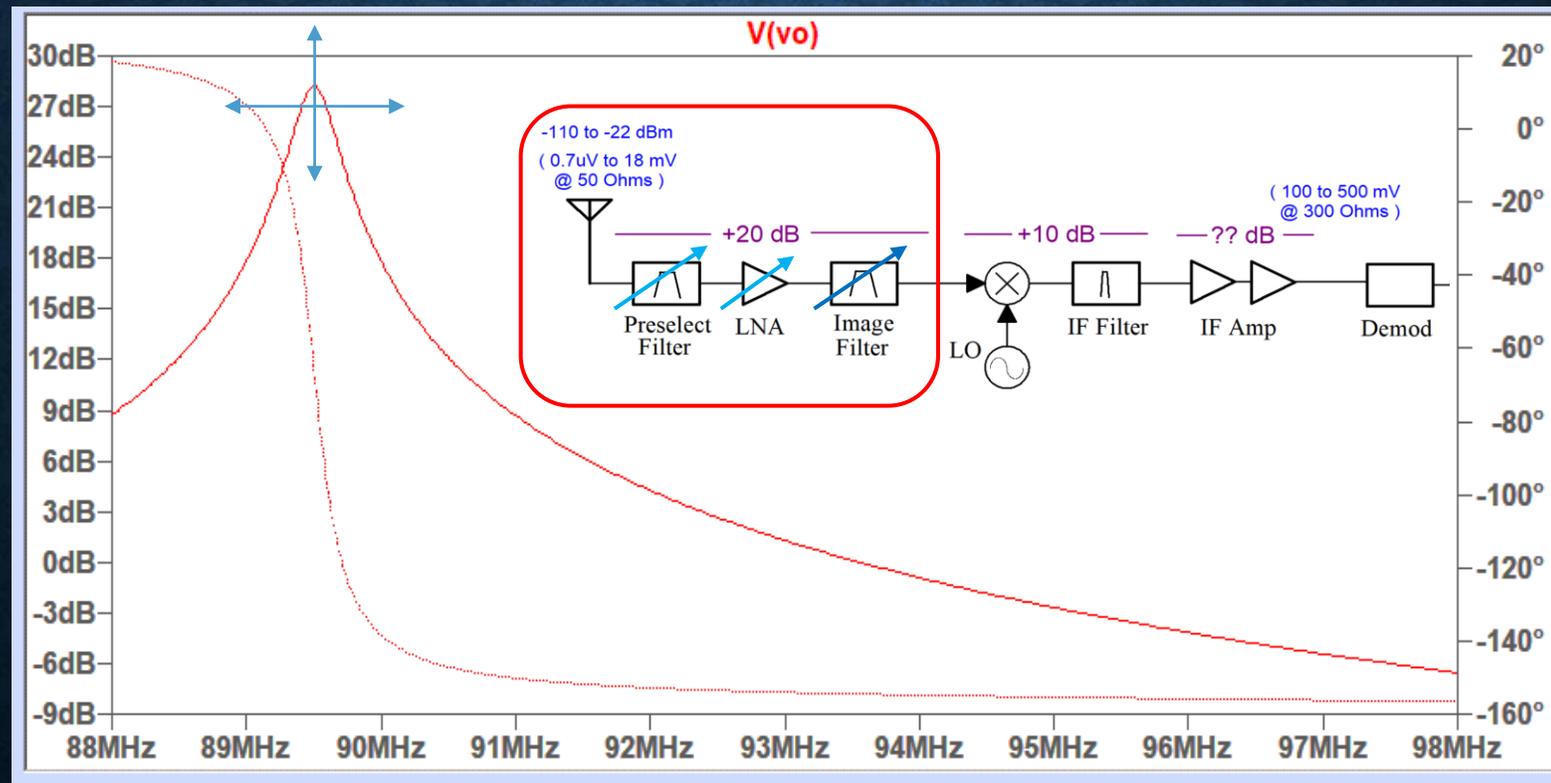*Reduce front end bandwidth to signal bandwidth,
not just width of service-band*



Early Common-source Design 1

No Preselect Filtering ☹️

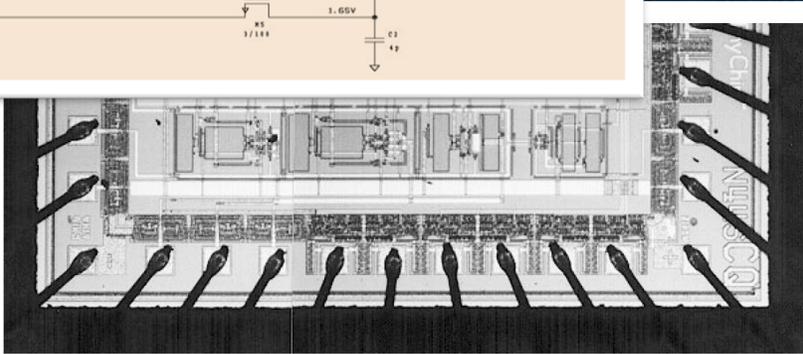
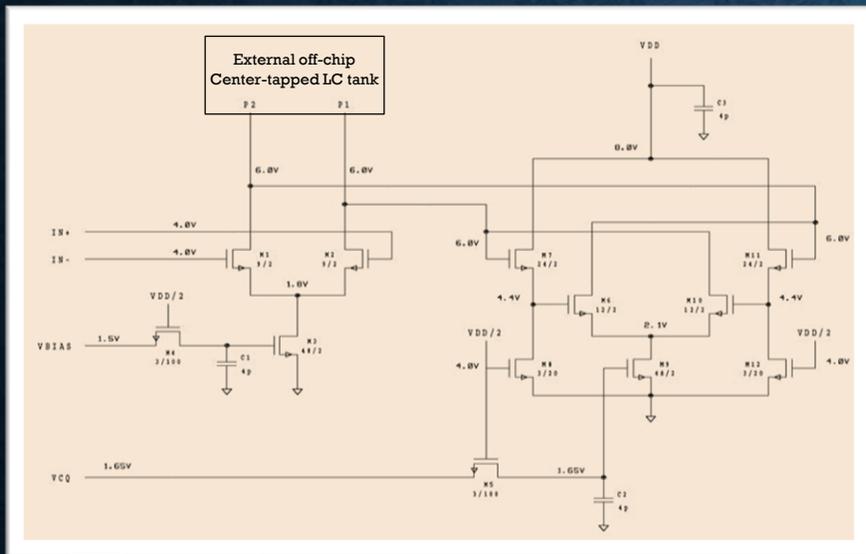


Figure 9.5: VHF front-end IC photograph.

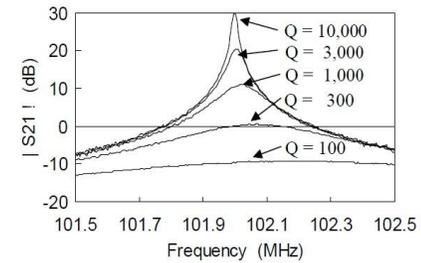


Figure 9.8: Measured transfer functions of Q-enhanced filter.

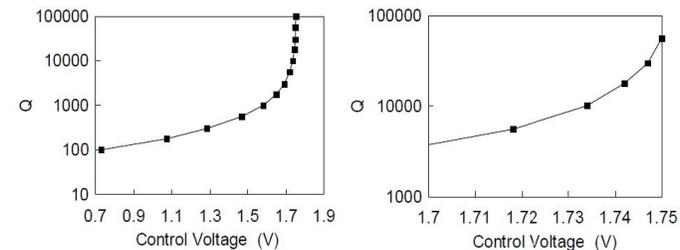


Figure 9.9: Measured Q factor versus control voltage.

Short-term stability of both frequency and Q were found to be excellent as shown in Table 9.1, indicating that the filter is suitable for use with either the self-tuning or orthogonal reference tuning techniques and their simplifications discussed in Chapter 7.

From: “Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies”,
William B. Kuhn, PhD dissertation, Virginia Tech, 1995

Early 2-pole Design

For 200 MHz IF - No Preselect Filtering ☹

A photograph of the fabricated circuitry is shown in Figure 9.14. To provide minimum possible inductor coupling between the two identical second-order sections implemented on the die, the inductors were oriented diagonally opposite to each other. Chip area not used by the circuits discussed above was used to provide on-chip decoupling and supply bypass capacitors and to implement test structures. Total chip area for both second-order sections, excluding pads, is 3.3 mm².

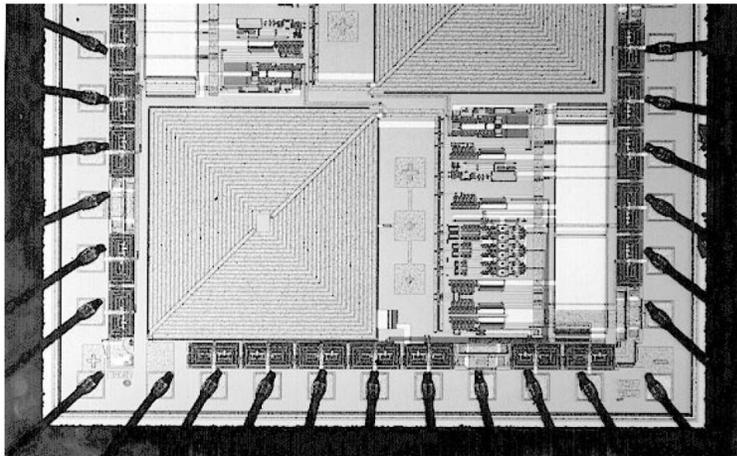


Figure 9.14: Photograph of chip layout.

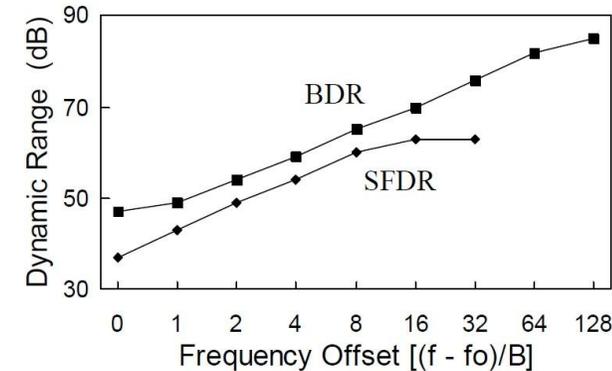


Figure 9.18: Measured blocking and spurious-free dynamic range.


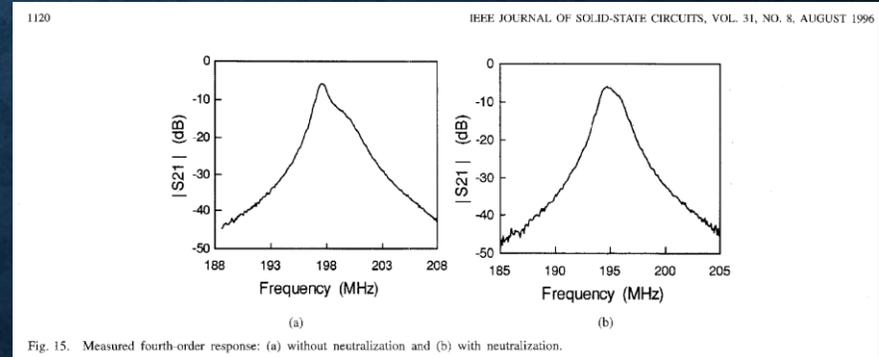
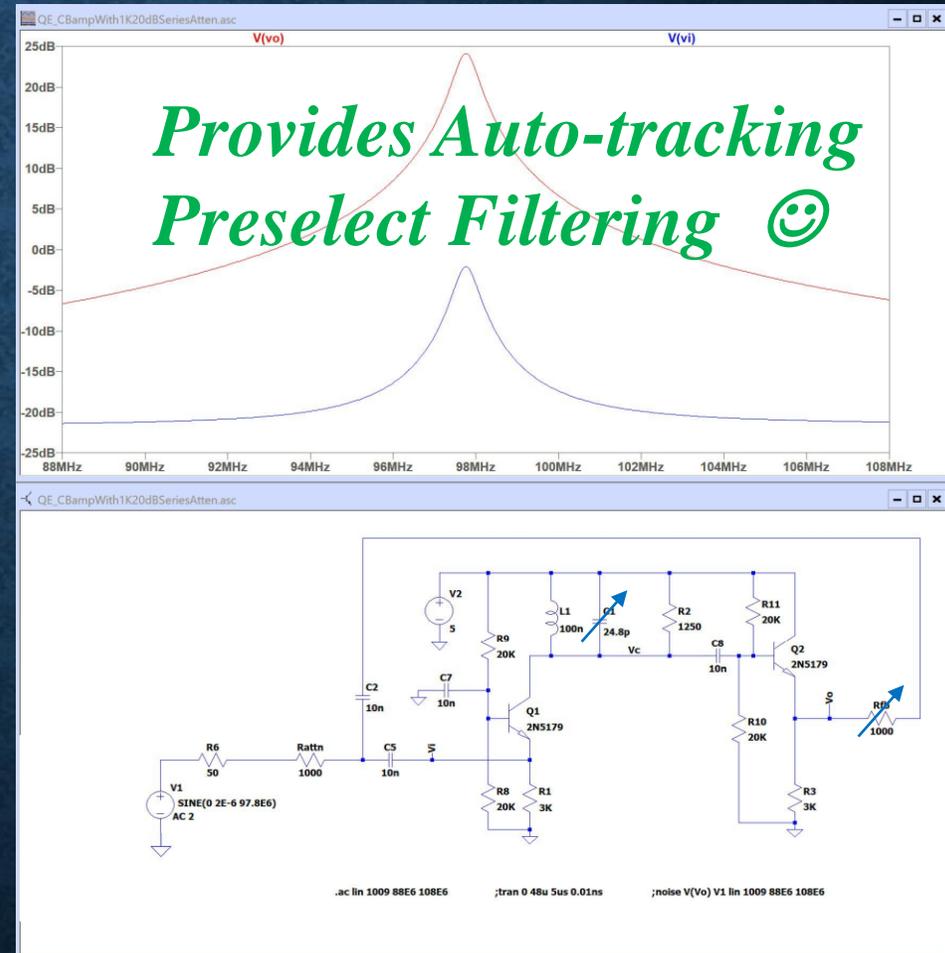


Fig. 15. Measured fourth order response: (a) without neutralization and (b) with neutralization.





From: "A 200 MHz CMOS Q-enhanced LC Bandpass Filter"

W B Kuhn, F W Stephenson, A Elshabini-Riad - IEEE Journal of Solid-State Circuits, 1996


Basic LNA vs New CB QE LNA

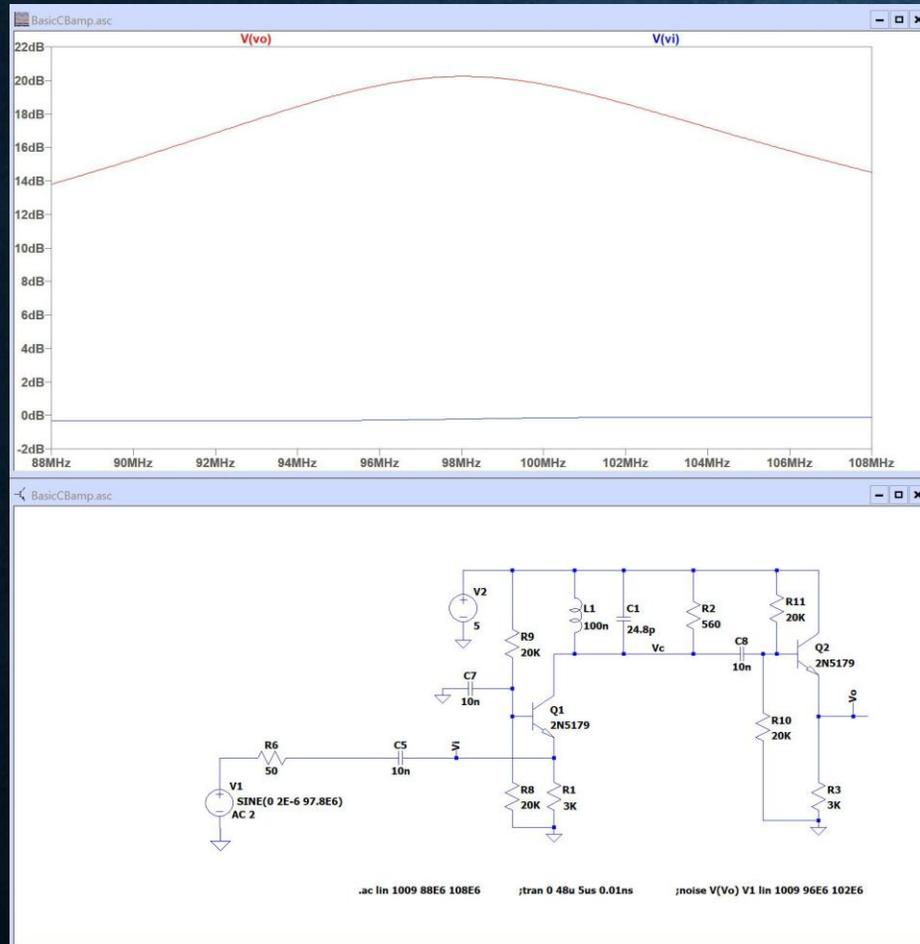

Basic LNA vs QE LNA Intermod Sims

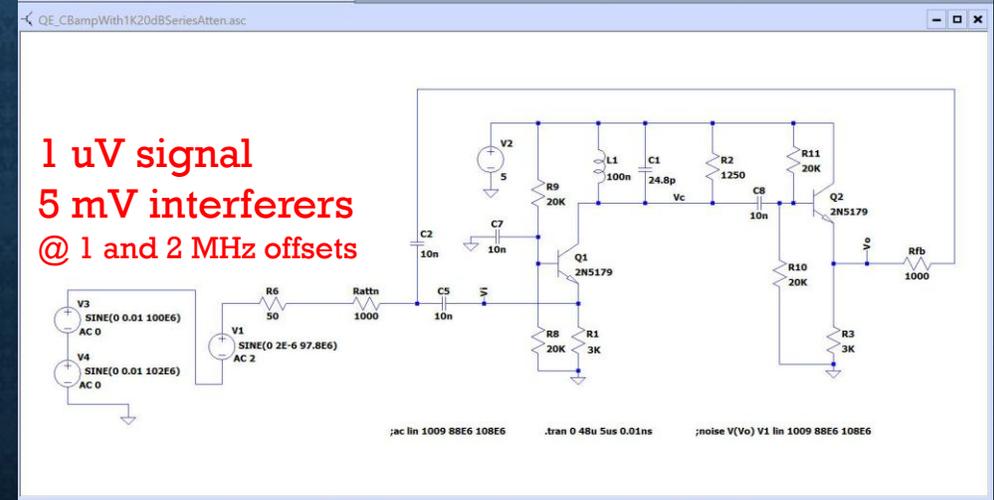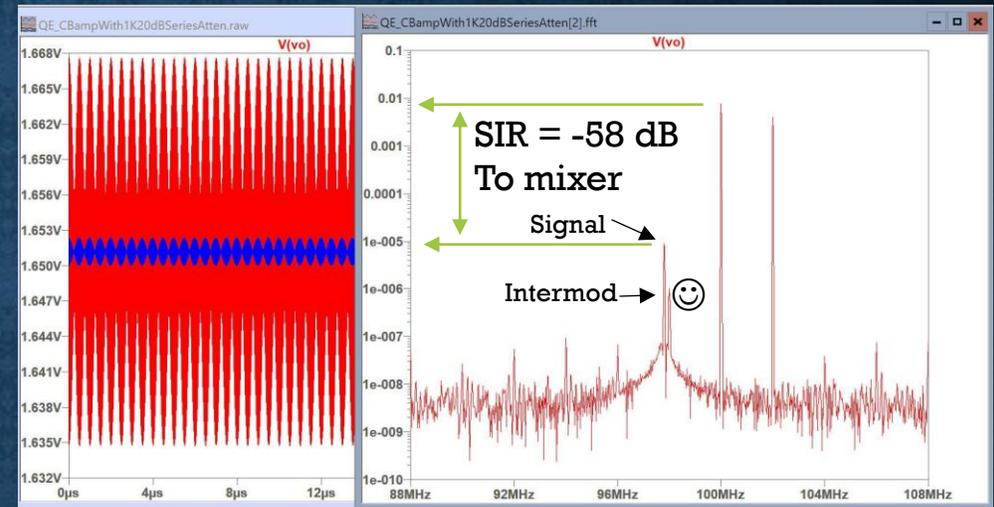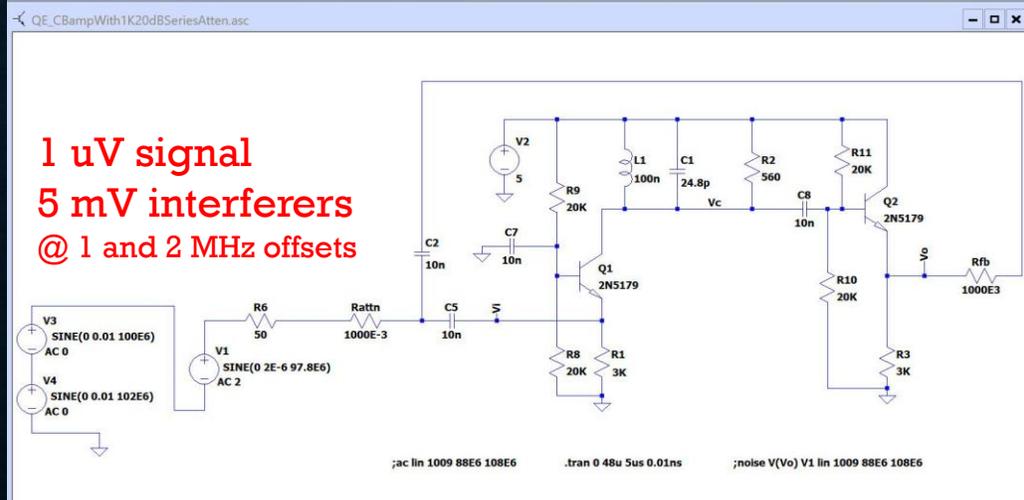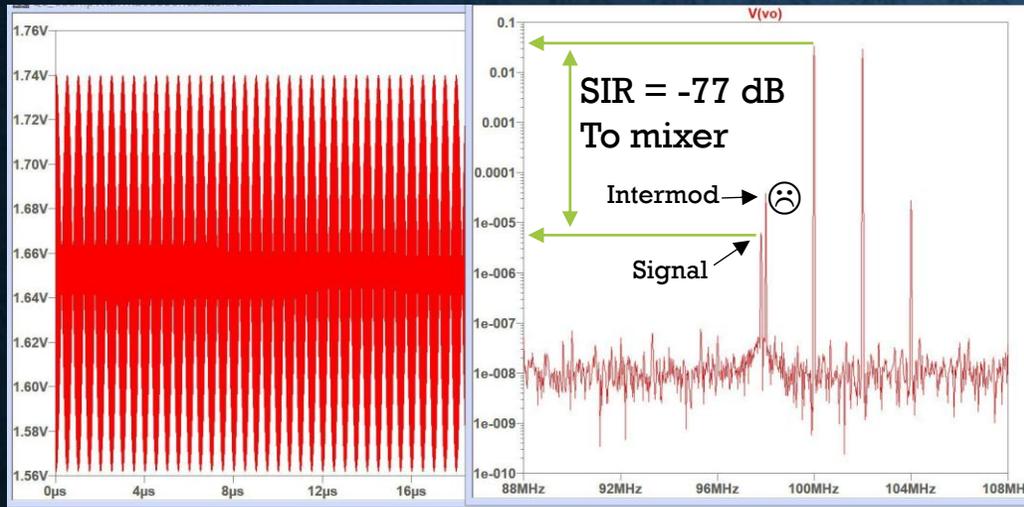


CB Q-enhanced Filter Prototype 2 (2023)

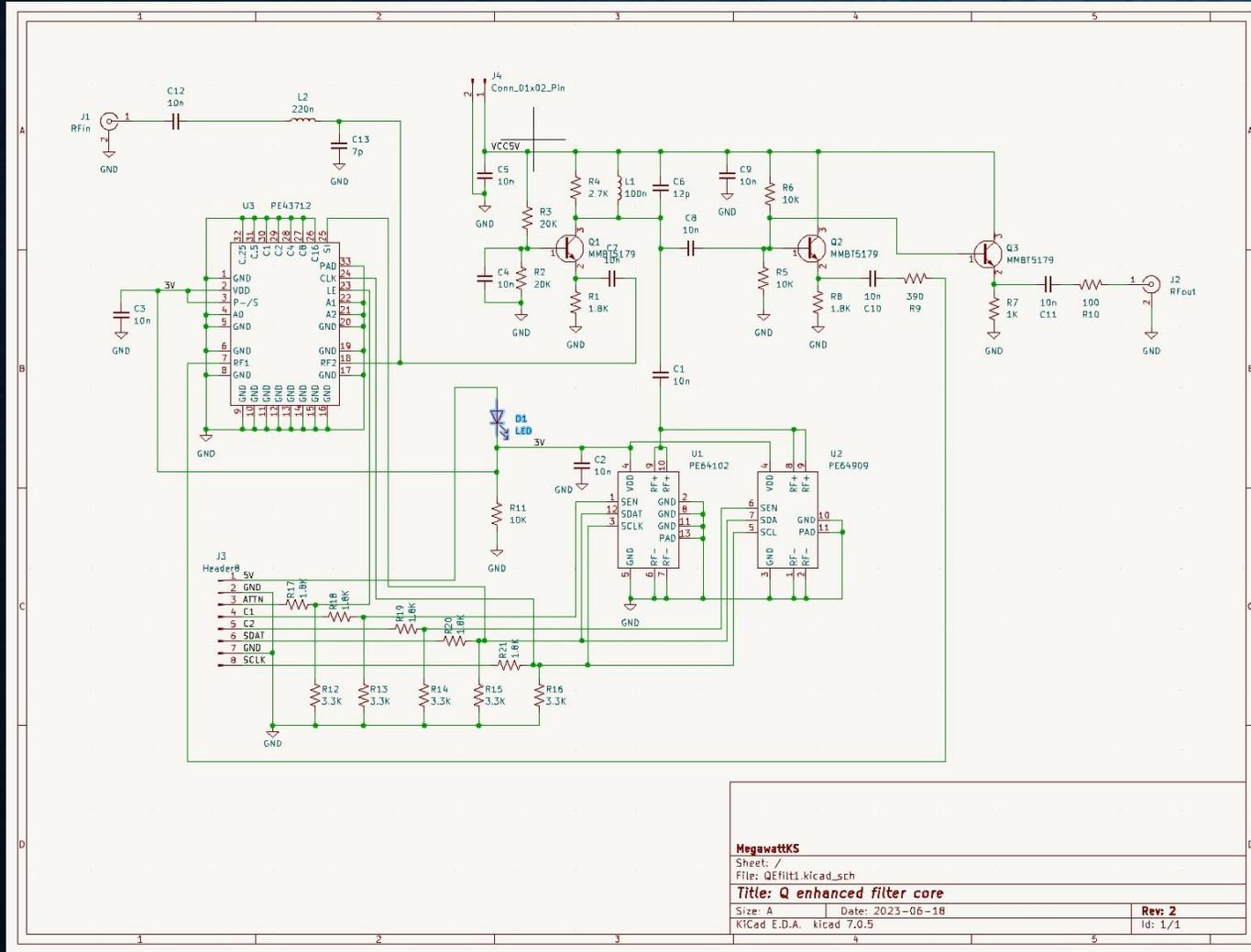

pSemi's DuNE™ technology enhancements deliver high linearity and exceptional harmonics performance. It is an innovative feature of the UltraCMOS® process, providing performance superior to GaAs with the economy and integration of conventional CMOS.


Figure 1. Functional Block Diagram

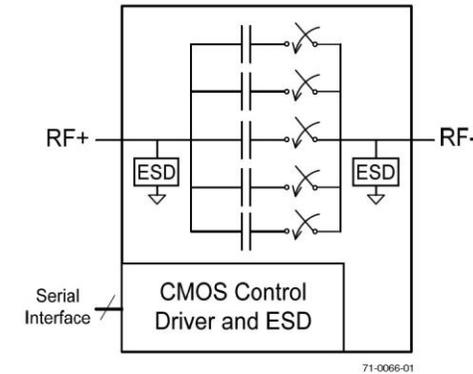


low current consumption
 (typ. $I_{DD} = 30 \mu A @ 2.8V$)

- Optimized for shunt configuration, but can also be used in series configuration
- Excellent 2 kV HBM ESD tolerance on all pins
- Applications include:
 - Antenna tuning
 - Tunable filters
 - Phase shifters


Figure 2. Package Type
 12-lead 2 x 2 x 0.55 mm QFN

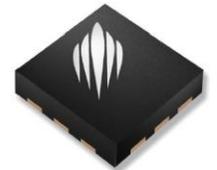
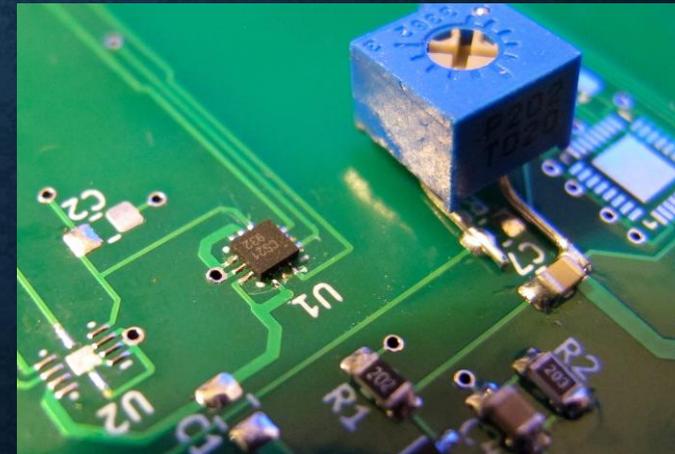
<https://www.psemi.com/pdf/datasheets/pe64102ds.pdf>



Digitally Controlled Tuning

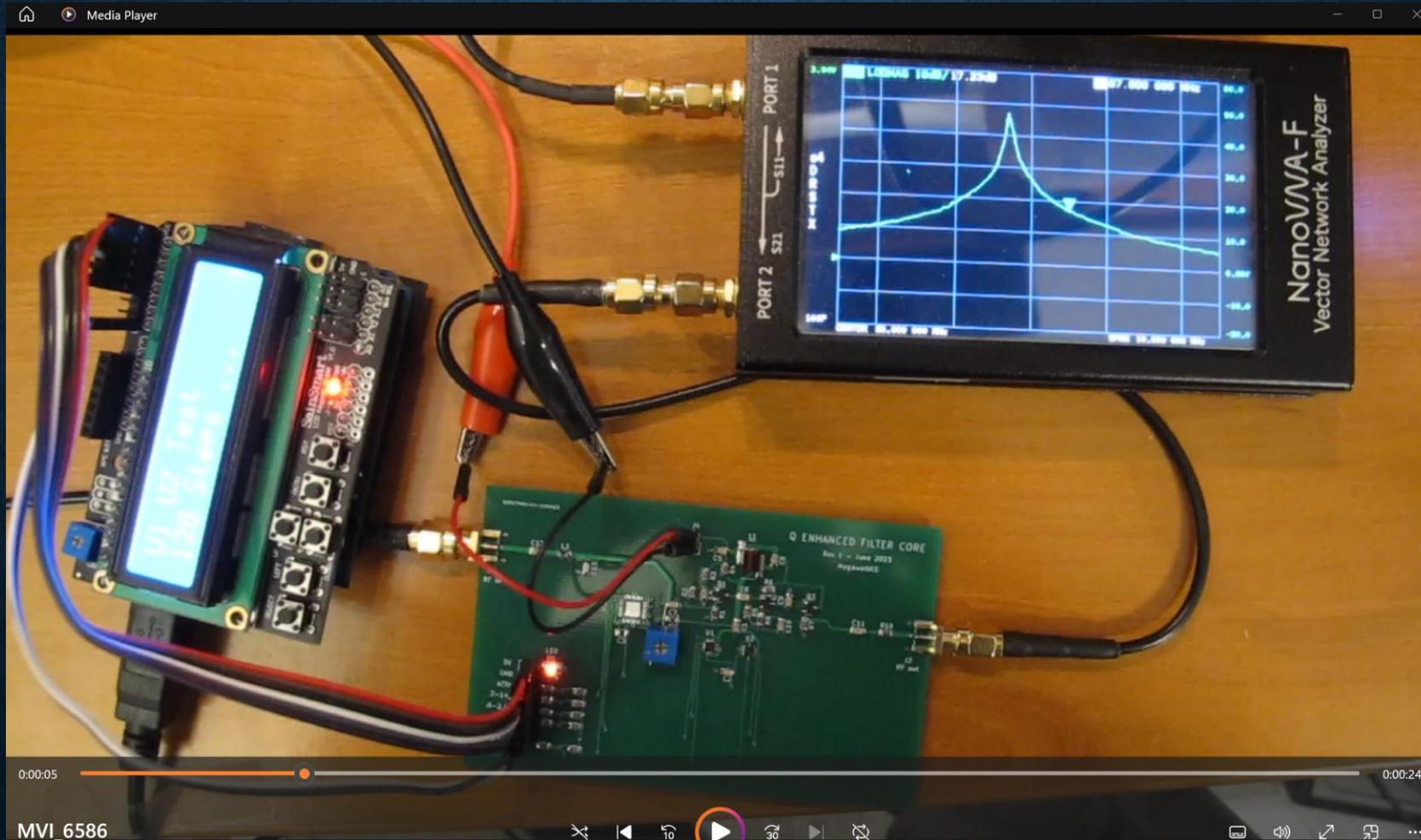

KIS Self-Tuning


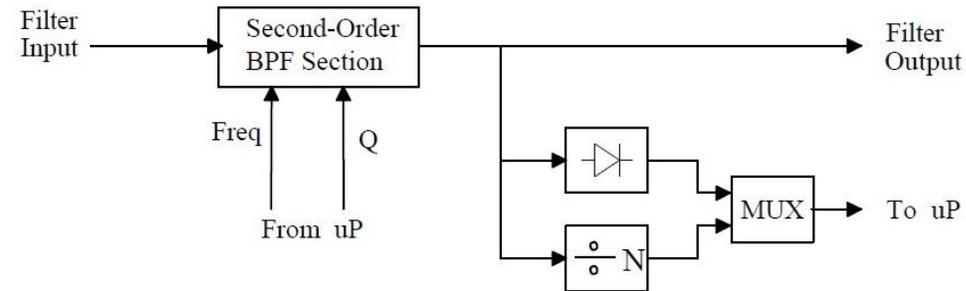
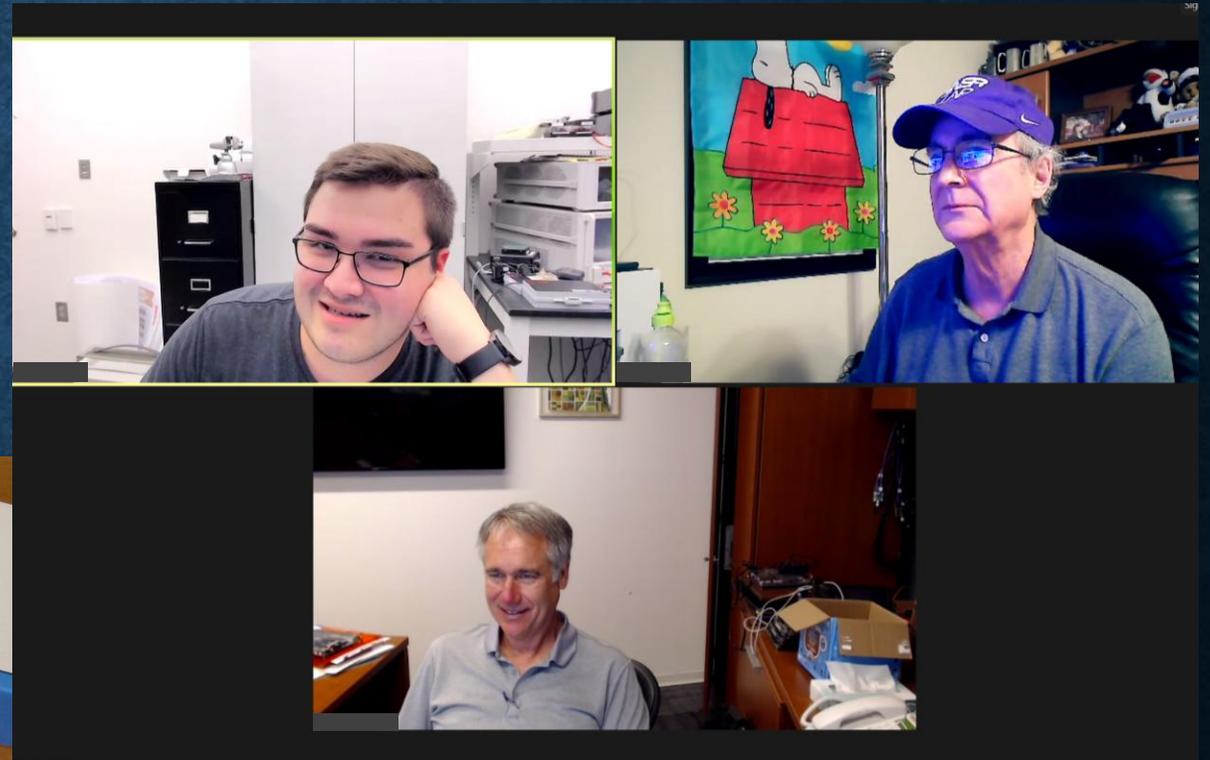


Figure 7.18: Self-tuning simplifications in superheterodyne receivers.

As before, filter frequency and Q control inputs are derived from the host receiver's microprocessor. However, measurement of frequency and Q is now performed using an amplitude detector and frequency prescaler incorporated into the filter die. Periodically, the filter is taken off-line and the Q is increased until the amplitude detector indicates that oscillation is present. The frequency of oscillation is then measured by the microprocessor's built-in

From: “[Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies](#)”,
William B. Kuhn, PhD dissertation, Virginia Tech, 1995.

Recent Prototyping

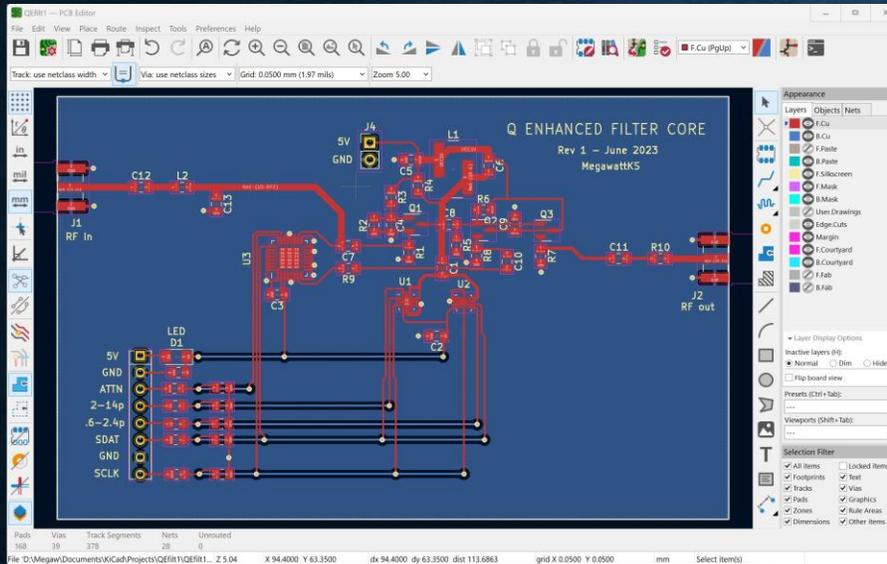


Today's Outline

- ✓ • *Introduction*
- ✓ • *Basic Research in Low Power Receivers*
- ✓ • *Circuit-level Solution Examples*
- • *Key Takeaways*
- *Future Episodes in This Series*

Key Takeaways from Episode 1

- Strong-signals can create blocking and intermod problems in existing receivers (from in-band interferers)
- Traditional solutions
 - Preselect (and image) filtering – Fixed bandwidth or (low-Q) tracking preselect architecture
 - Use RF (and IF) gain control and/or attenuators/AGC (trades noise figure for intermod mitigation)
 - Selective antennas (Directional and/or high-Q resonant)
 - Burn more power in LNA and mixer !


High-Power HF Receiver Circuits

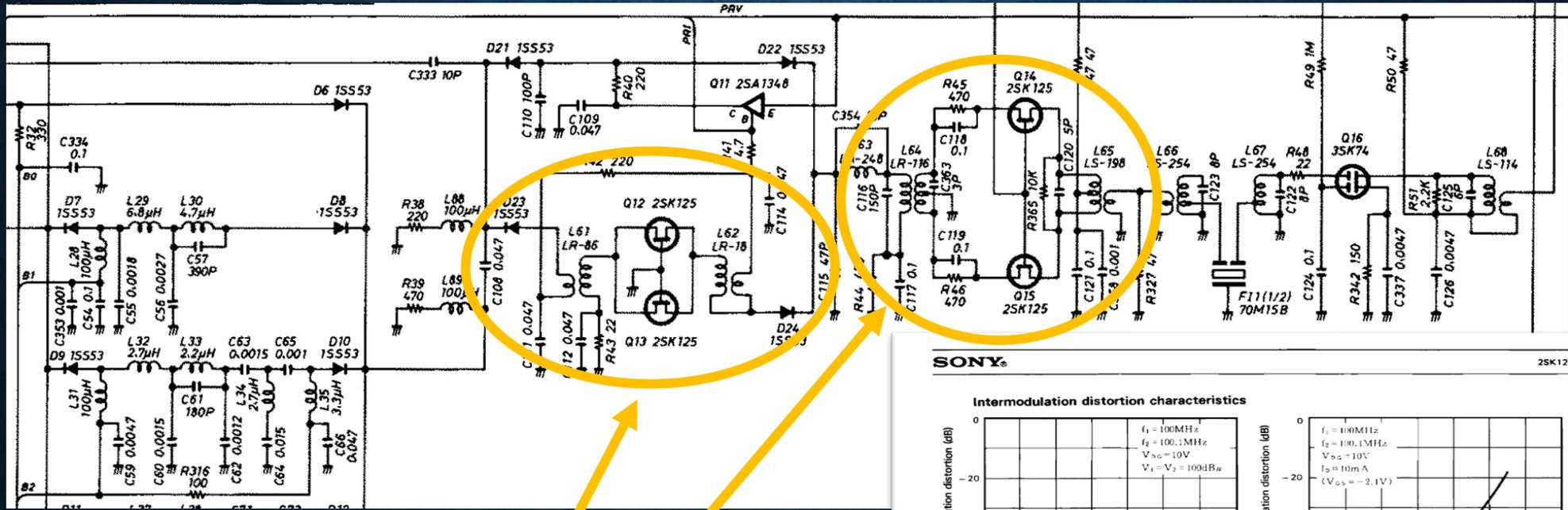

High Power (1/2 Watt) LNA

High Power (1/2 Watt) Mixer
(upconversion to 70 MHz)

2SK125 FET Intermod Characteristics

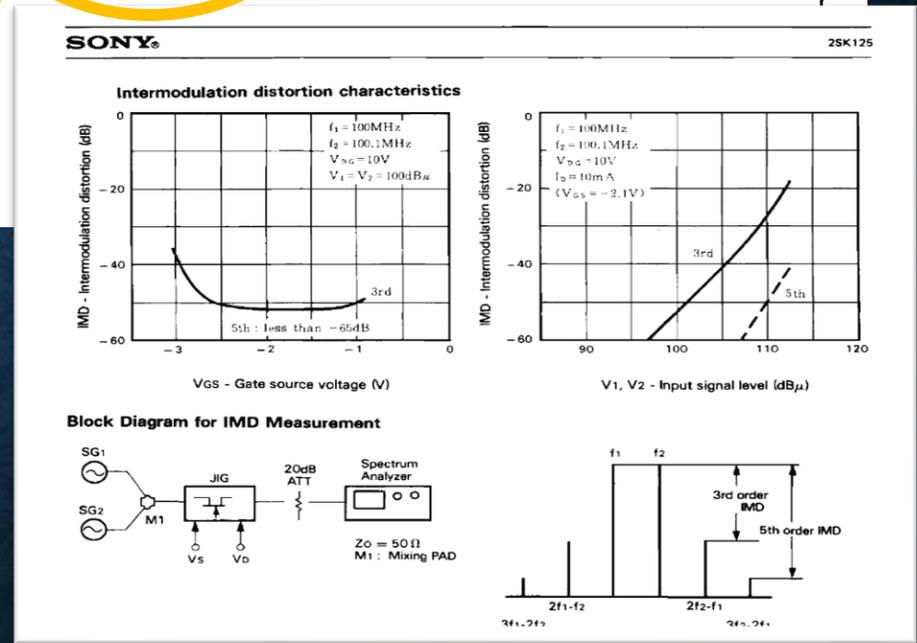


Key Takeaways (continued)

- Leveraging vintage technique of regeneration (positive feedback) in common-base form, using modern uP control (Q-enhanced filtering) is an easy way to make a significantly improved (low power) LNA
- CB QE-filter LNA architecture provides channel-width pre-select filtering that automatically tracks LC tank image-reject filter tuning 😊
- Can reduce power consumption required in receiver significantly (e.g. 10x to 100x reduction for front-end) !
- Not a panacea (yet... 😊)

Proposed Low Power Solution

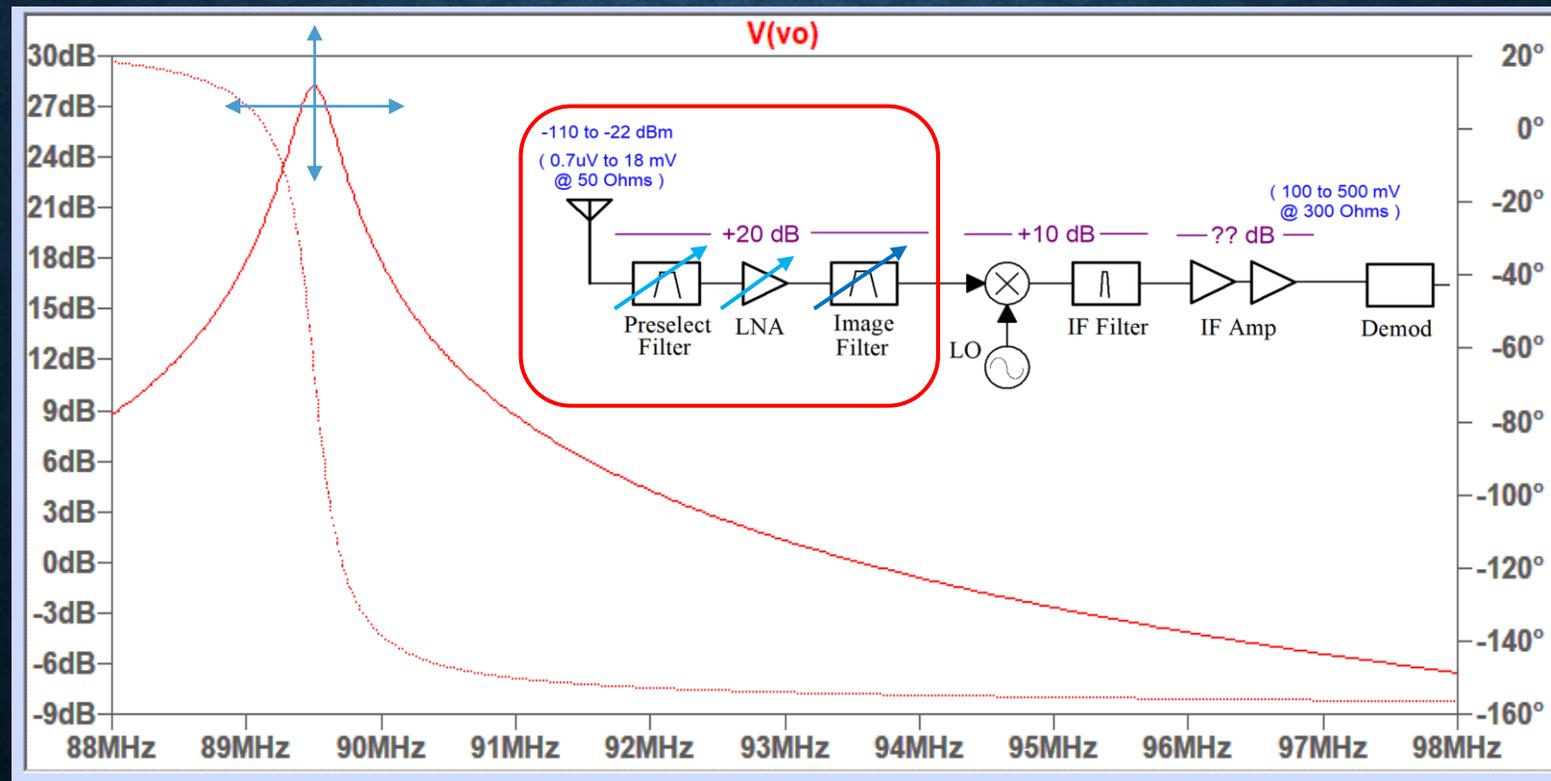*Reduce front end bandwidth to signal bandwidth,
not just width of service-band*



Limitations and Alternatives

- Filter response of current design is only “one-pole”
- It’s still partly an active filter - but superior to earlier types, and traditional LNA designs
- Requires real-time tuning
- A (tunable, very-high-Q) electro-mechanical/acoustic design might be superior, if possible and sufficiently small (MEMs anyone?), and low cost
- **Always remember :** Antenna is also a very important part of the receiver system, and using attenuators can also work wonders !

Today's Outline

- ✓ • *Introduction*
- ✓ • *Basic Research in Low Power Receivers*
- ✓ • *Circuit-level Solution Examples*
- ✓ • *Key Takeaways*
- • *Future Episodes in This Series*

Possible Future Videos

- *Receiver Performance Measures (the math)*
 - *Compression, Intermodulation and 3rd Order Intercept Point*
 - *Noise Figure and Tradeoffs with Intermod Performance*
- *Design and simulation of common-base Q-enhanced Filters*
- *Self-tuning hardware and software*
- *Effects of LED lighting, switch-mode power-supplies, and general EMC on actual system noise floor and receiver sensitivity*

Thanks For Watching !

For research publications, please cite:
<https://www.youtube.com/user/MegawattKS>
<https://ecefiles.org>
or specific sub-pages/publication/video

Thanks !