



Semester Project – LNA Design and System Test - Radio Design 401, Episode 8

Slides downloaded from: <https://ecefiles.org/>

Companion videos at: <https://www.youtube.com/playlist?list=PL9Ox3wpmB0krNexW2k5JMCaewXN7LoRXd>




This material is provided by ecefiles.org for educational use .

This is Episode 8 - the final episode in the Radio Design 401 series. In it, we validate that the Q-enhanced LNA technology introduced in Episode 1 together with the improved overall receiver architecture from Episode 5, outperforms some of the best commercial receivers, while operating at 10 times lower power consumption. The full system is tested in various spectral environments and compared to a modern automobile radio receiver. The goal is to receive weak signals in the presence of strong interferers as discussed throughout this series.

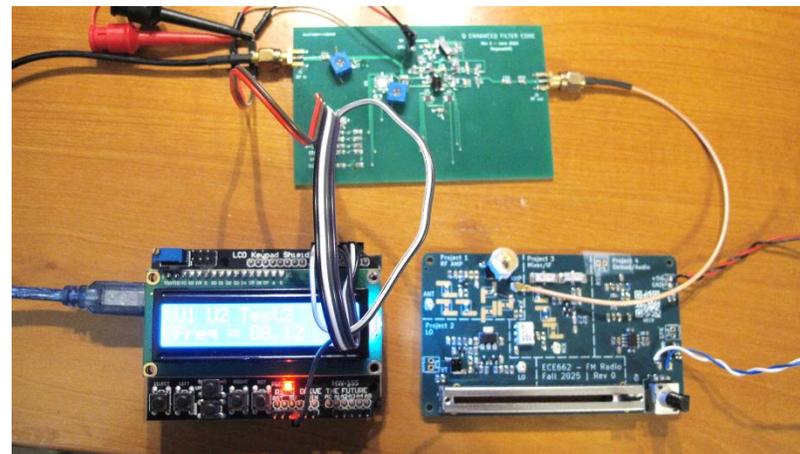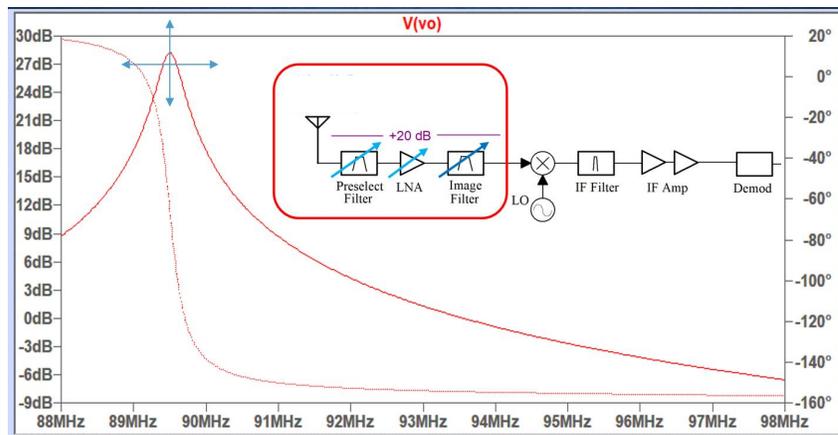

Radio Design 401 – Episode 8

LNA Design and System Testing

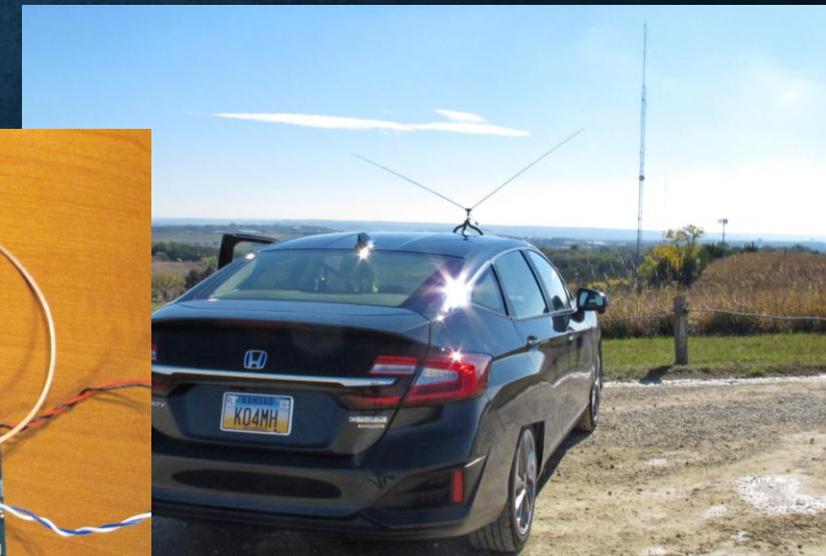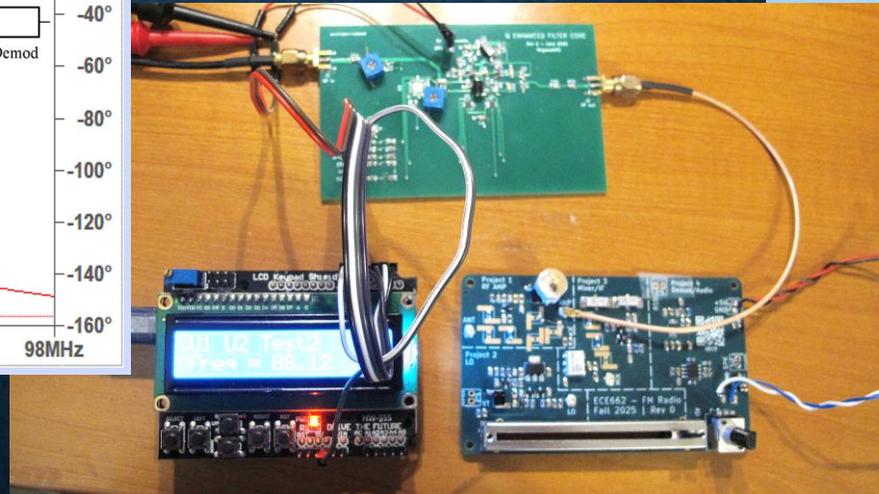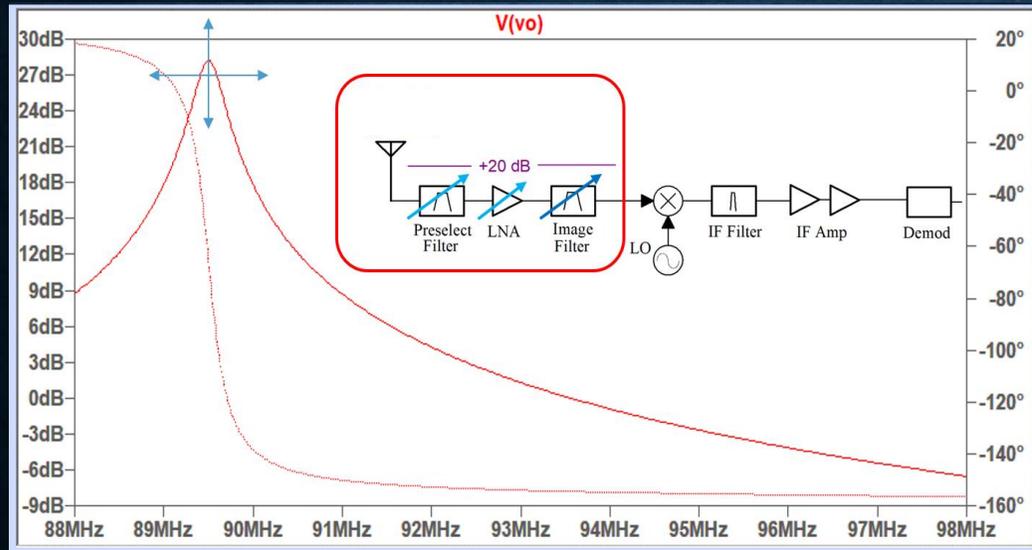

Overview





In a design and system testing

◆ AI Overview

LNA design involves a systematic process of selecting components and topologies to amplify very weak RF signals while adding minimal noise, ^{and achieving} ~~to achieve~~ specific performance goals (gain, noise figure, stability, linearity, etc.). System testing then verifies that the fabricated LNA meets these specifications and functions correctly within the overall receiver system, often using sophisticated RF test equipment. [🔗](#)



RD401 LNA in Receiver Context

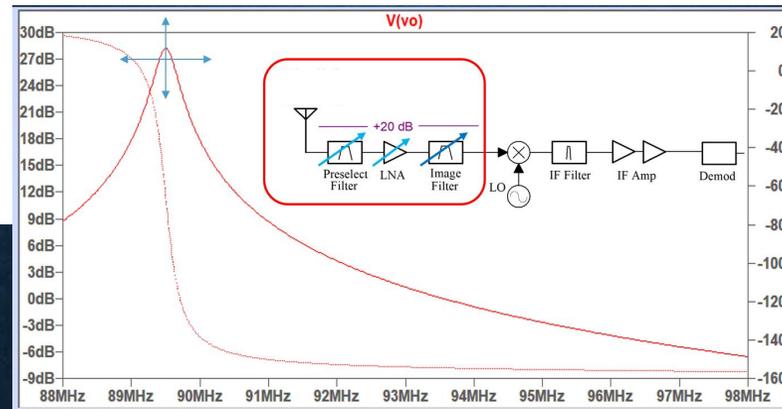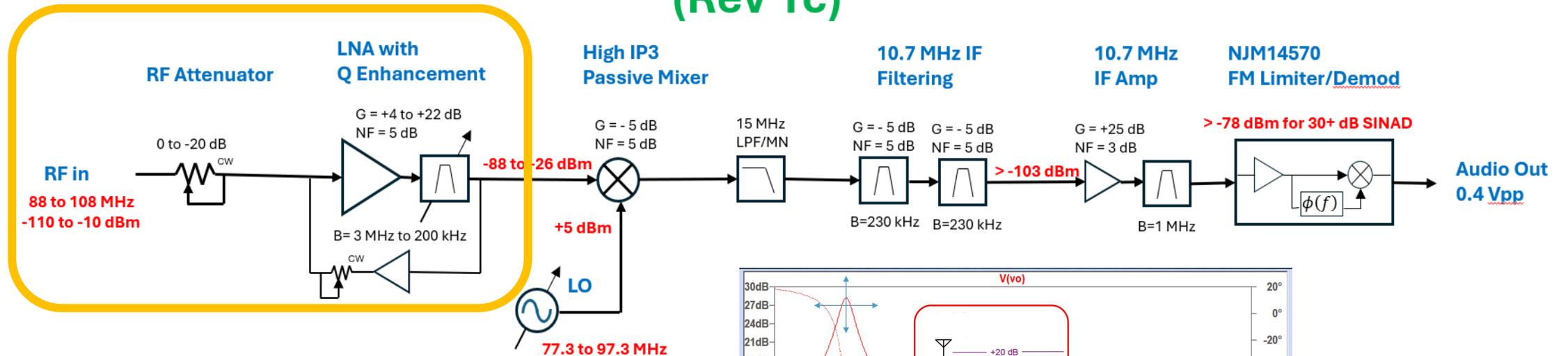Radio Design 401 Project Block Diagram (Rev 1c)




Q-enhanced LNA Design

See also Episode 1

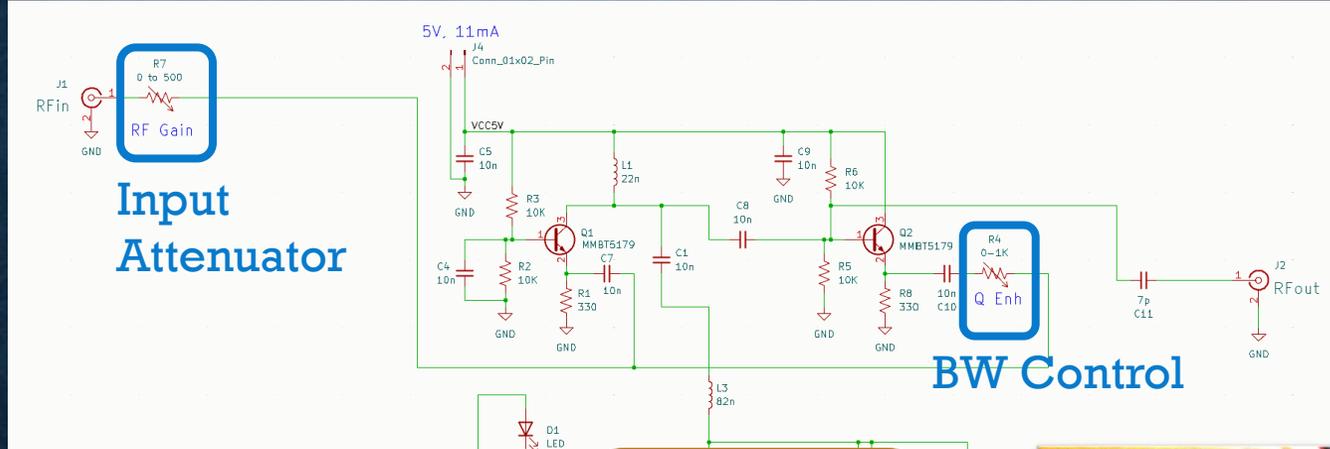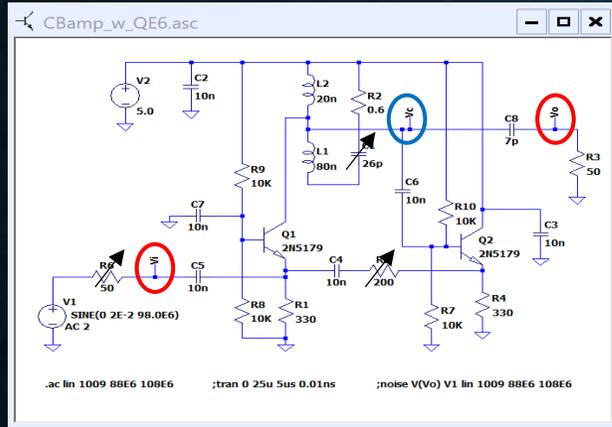



Input Attenuator

BW Control

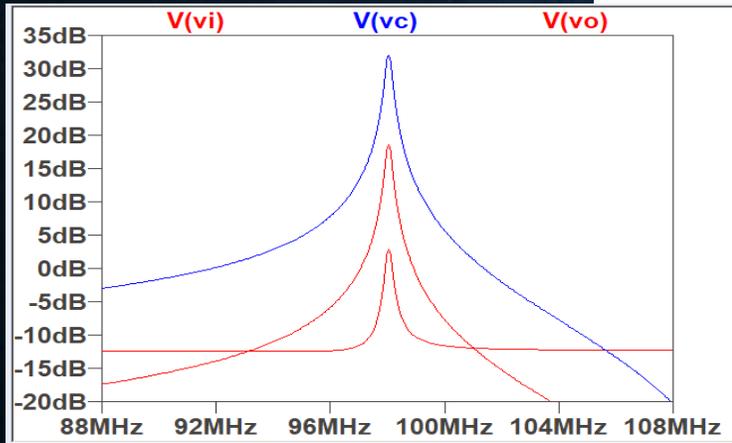

Frequency Control





Digitally Tuned Capacitors

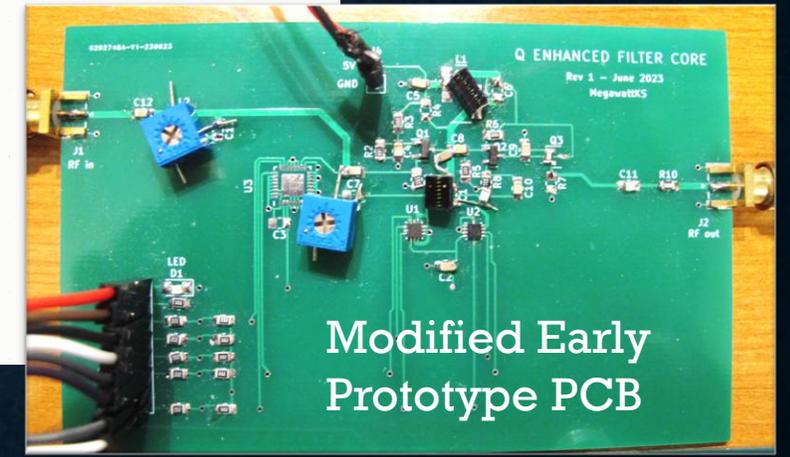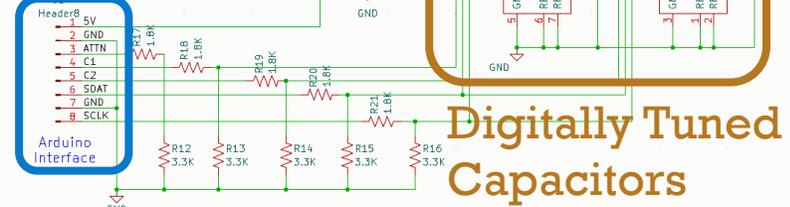

Modified Early Prototype PCB

LO, Mixer, IF, Demod

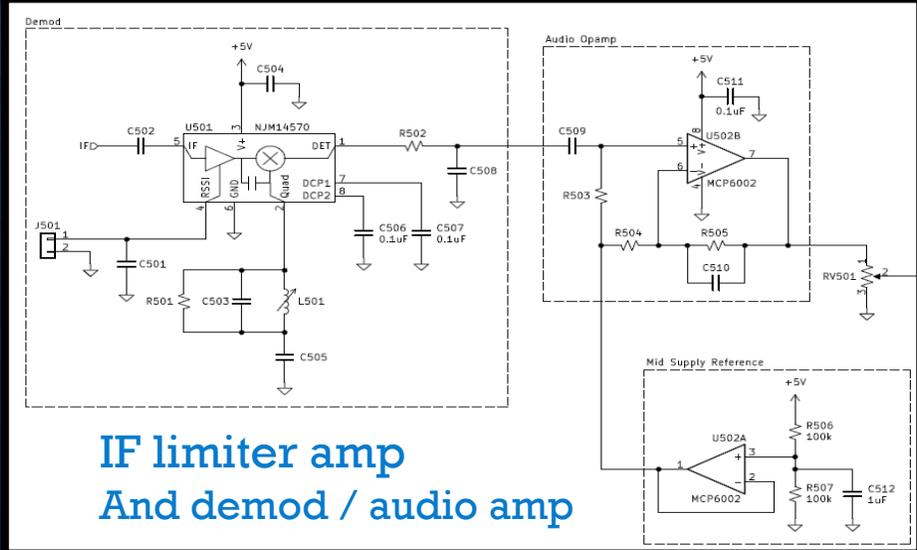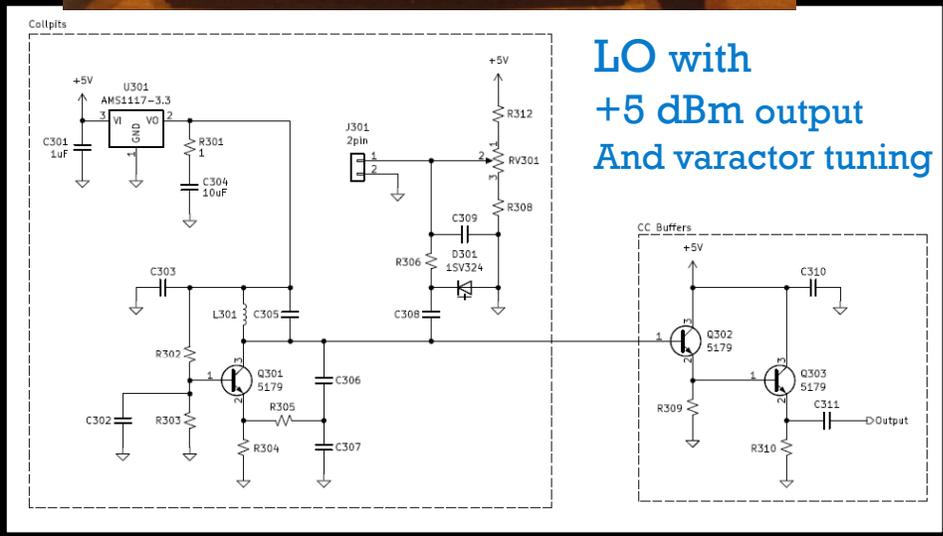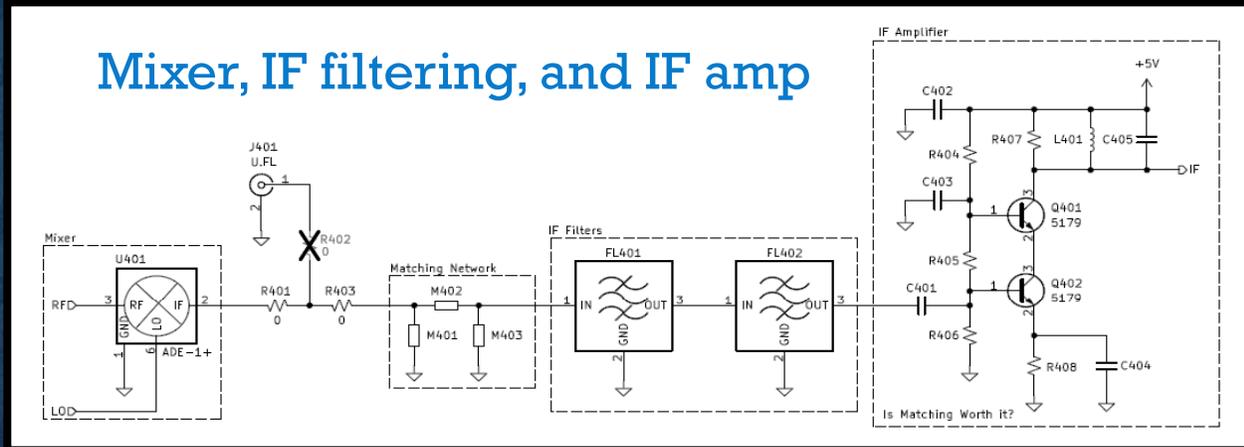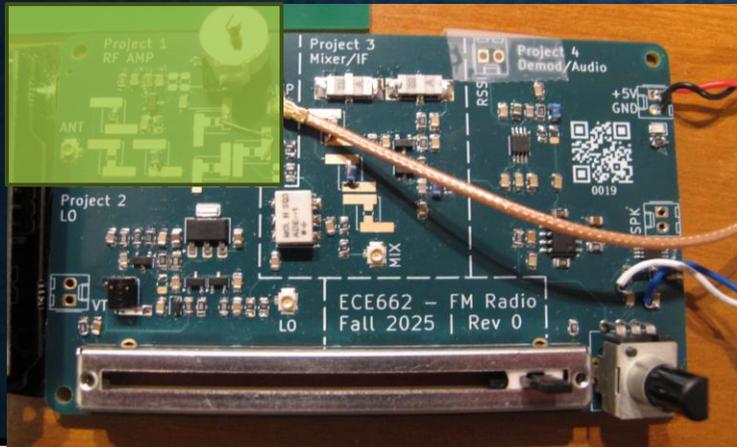
(KiCad Drawings and PCB Courtesy of Garrett Peterson)



Testing (vs Car Radio)



0:00:14
MVI_8838

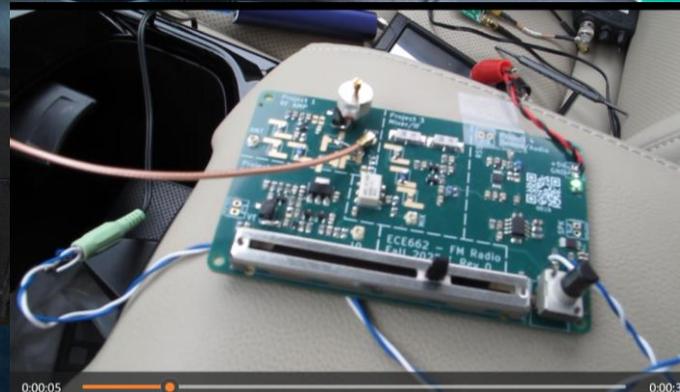

0:00:05
VideoDemo

Testing (at the Top of the World)



Presentation Outline



Signal Environments

Background and Prior Episodes

LNA Design



Classic Lab Testing (Gain, NF, P1dB, Pdc)

Real-World Test Results

Conclusions and Future Directions

Noise in Indoor Environments


Noise Floor is RFI-Limited

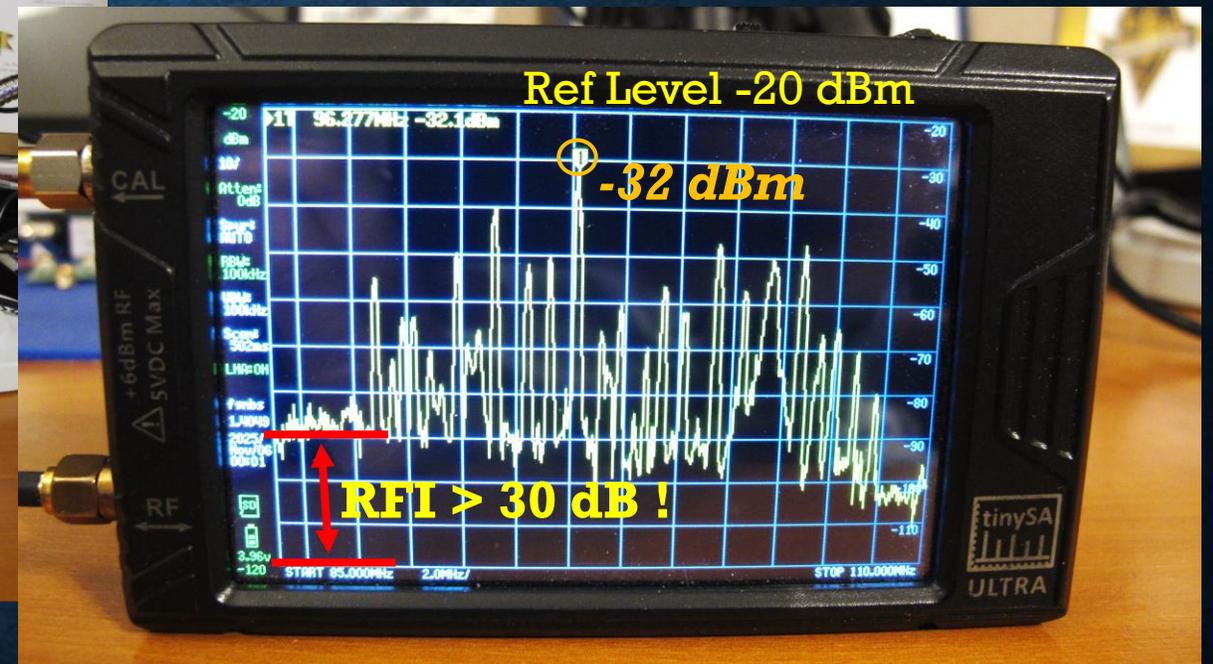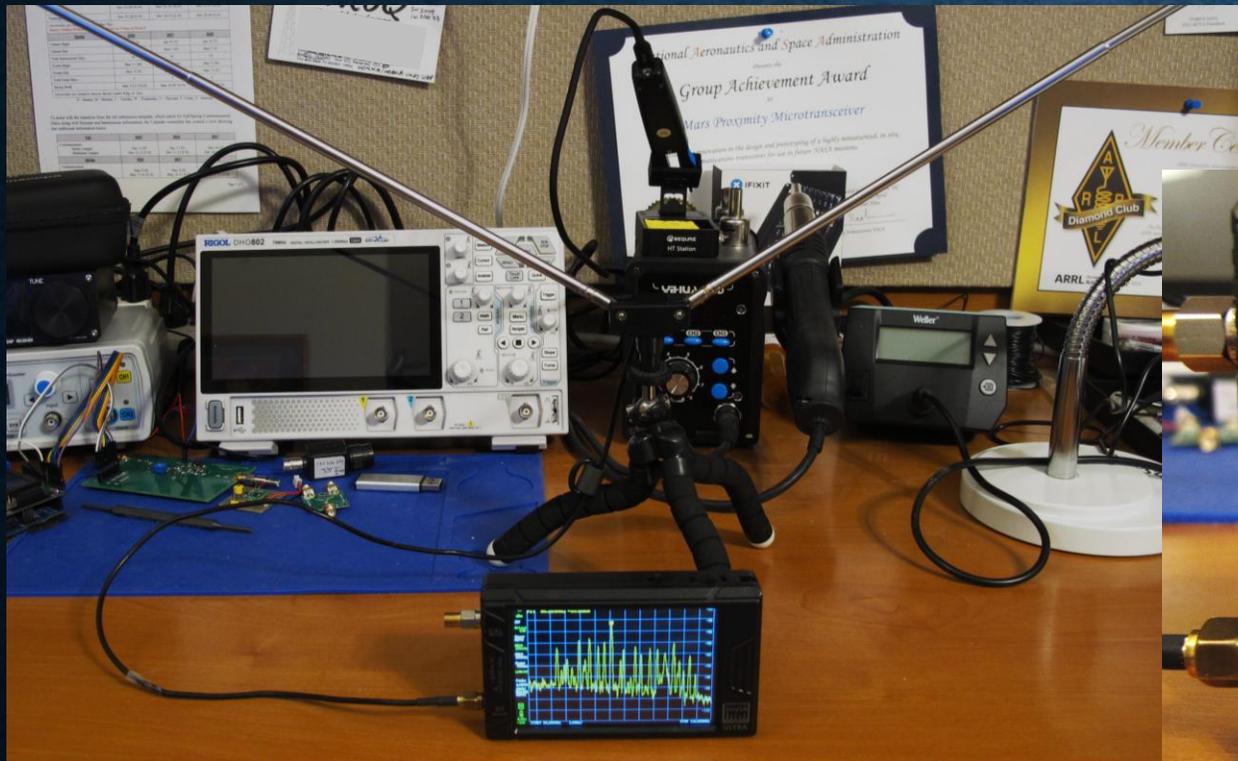


TinySA LNA is ON

Crowded Outdoor Environments

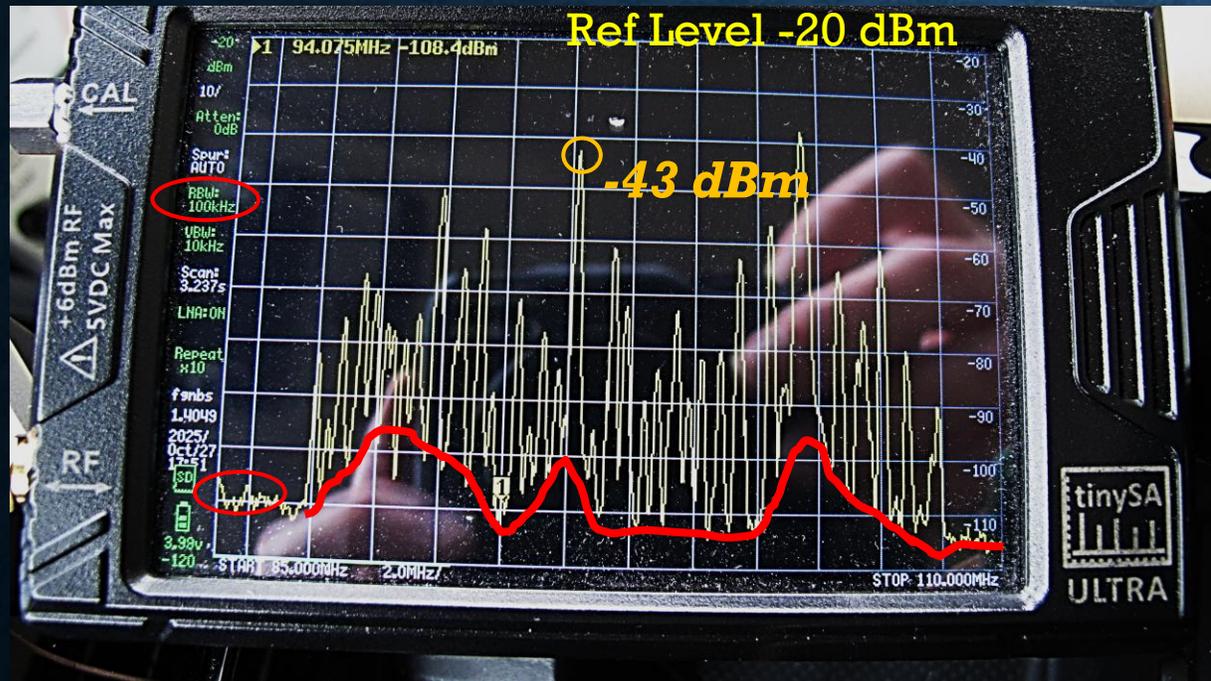Noise Floor is Intermodod / IF Filter Limited



TinySA LNA is ON

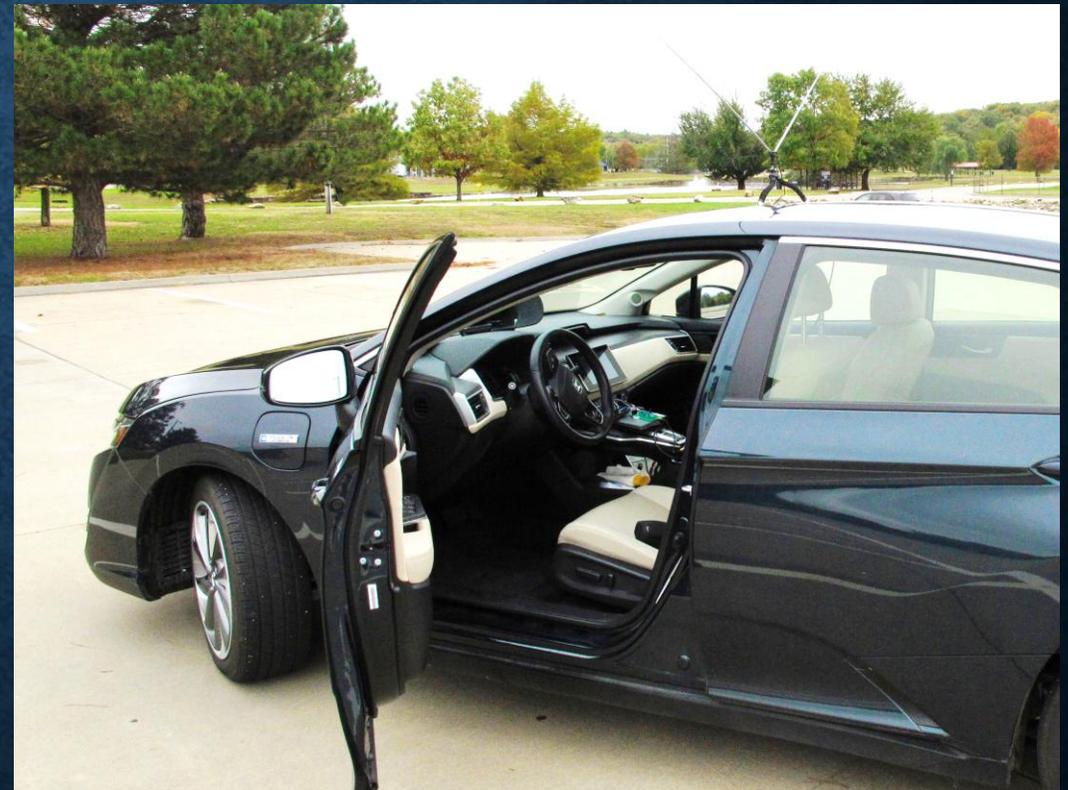


Testing at the “Top of the World” !

Noise Floor is Dynamic-Range and Spurious-Emission Limited



6-element
Vertical
Array

Pt = 7.5 kW
EIRP=21 kW

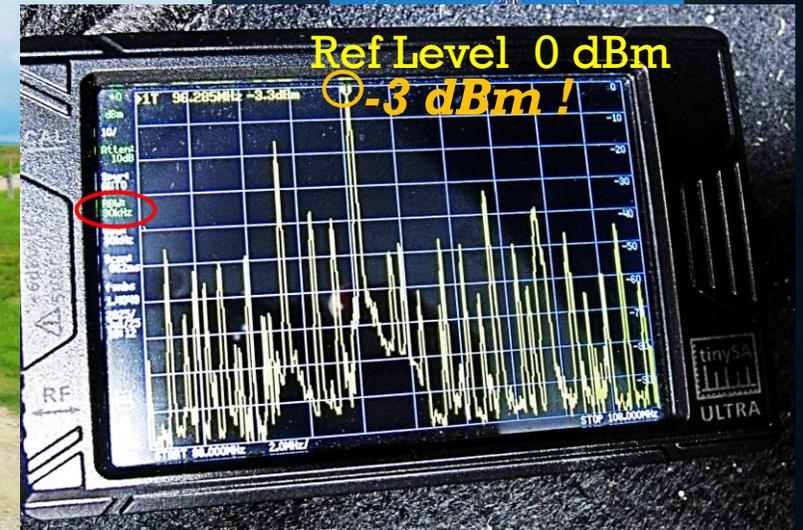

LNA is OFF

Presentation Outline

Signal Environments



Background and Prior Episodes

LNA Design

Classic Lab Testing (Gain, NF, P_{1dB}, P_{dc})




Real-World Test Results

Conclusions and Future Directions

Background

University Class and Radio Design 101 YouTube Course

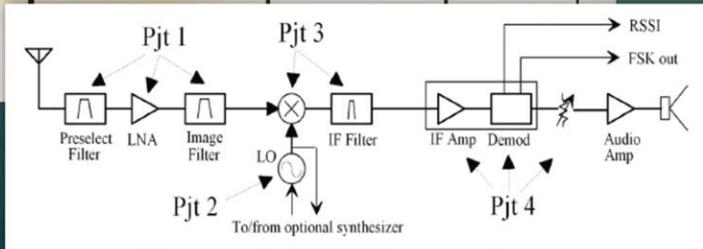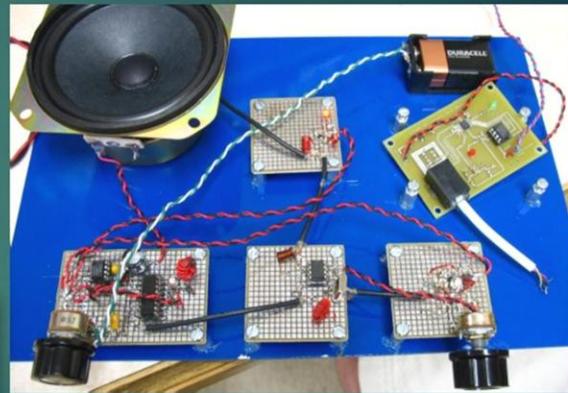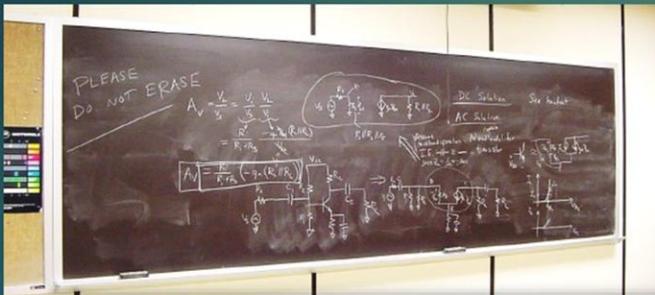New Radio Design 101 series
Abstracted from a senior-design University class



RF Circuits Course Notes - ecefiles.org

ECEFILES.ORG
ecefiles.org

RF Circuits Course Notes

Designing and Building Transmitters and Receivers in a Single Semester

This page was created to document a [senior design course](#) taught by the author for 20 years at Kansas State University. It is related to the "Radio Design 101" series of videos on YouTube, but goes into more depth (at the expense of being less polished in presentation)

End of Semester Checkoffs

ECE 662 Final Exam – Fall 2015

Your "Final Exam" will consist of demonstrating and explaining (during the question/answer session of the final) your FM broadcast-band / Purpletooth receiver built from projects 1 through 4. Due date is:

Complete on or before the end of exam week (Friday, Dec 18, 5pm).

There will be a sign-up sheet in the lab with 60 minute timeslots (20 minutes demo, 30 minutes quiz).

Demonstration

Demonstrating your receiver will include actual "off-the-air" tests showing that you can receive strong and weak FM stations alike. In the demonstration, you must also show that you meet the following specifications using suitable laboratory-generated signals (**with you doing the tests and your instructor observing**). You must also show proficiency in operating the test equipment to verify these specifications.

- Tuning range 88 MHz to 108 MHz
- Threshold sensitivity Better than -110 dBm (12 dB SINAD at 98 MHz)
- 30 dB quieting sensitivity Better than -100 dBm (98 MHz)
- Audio frequency response 100 Hz to 10 kHz or better (+3 dB) after accounting for 75us equalization rolloff
- Audio output power > 2.5 Watts with 75 kHz peak deviation
- Distortion (at 1 Watt) < 2% THD for 1 kHz sinewave with 75 kHz peak deviation
- Purple-tooth support FSK and RSSI outputs functional
- Power consumption < 70 mA at 9V (zero volume)



Quiz

The quiz is designed to check your knowledge of all aspects of radio theory and circuits we have discussed in class. You should bring your project schematics and circuits with you. I will start by asking some basic questions and then increase the difficulty to try to see the depth of your knowledge. The questions may cover material from any of the projects as well as other material presented in class.

DC power	Tuning Range	Thresh Sens	Audio Freq Response	Audio Pout	Distortion	FSK demod	RSSI	Notes
52 mA	88-108	-90 dBm -114 dBm	2.2 kHz corner	2.44 W	0.4%	Working	?	17 stations, Great Sound
63 mA	✓	-102 dBm -118 dBm	2.3 kHz	✓	< 1%	✓		21 stations, Great Sound, Synt
72 mA	88-108	-95 -112	65-3.1K	1/2 W	0.7%			17 of 20 stations Synt K2086 5 unique, Lots of Refers
72 mA	88-108	-100 -112	370-4.4K	OK	1.7%	AC coupled?		20+ stations, Very clear But several small issues
56 mA	88-108	-82 -108	14-12K	Low	✓	✓		12:36 (distorted along station) K2 Demand package
61 mA			Not yet working					5 Very low sound, looks at pot
69 mA	✓	-50 -88	10 kHz - 30 kHz	Low	✓			
68 mA	88-108	-96 -108	1K - 16K	✓	1.6%	X		15 stations
53 mA	88-108	-90 -112	500-5.9K	✓	1.2%	✓		21 stations
57 mA			Not yet working					
	92/108	-70	10-3.5K		~10%			No 6V regulator No sound, Osc not legit
52 mA	✓	-100 -112	30-2.5K	✓	✓	✓		No hiss, D. started audio, Very weak audio Osc is on
	88-108	-95 -116	30-2.9	✓	✓	✓		20 Stations good audio
74 mA	90-108	-90 -106	25-2.9	✓	✓	✓		20 Sound good!
								16 Sounds good

Radio Design 101 Testing

See Epilogues 1 - 3

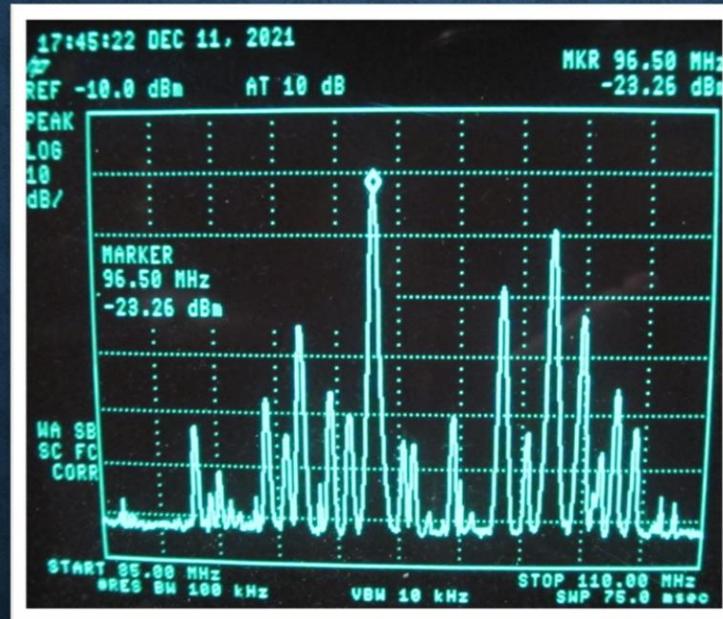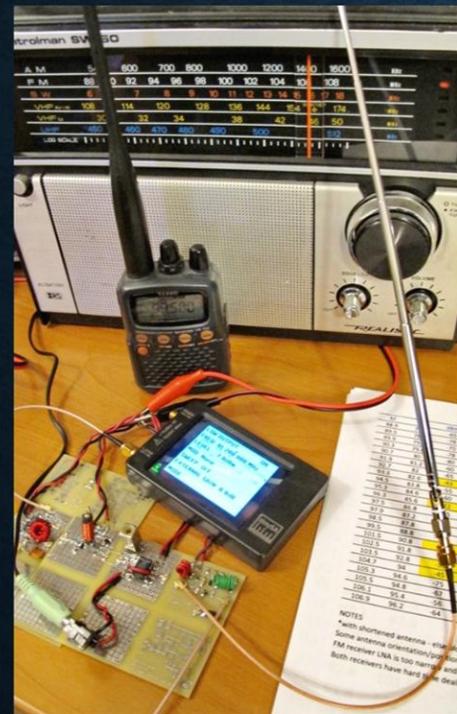


RF	LO	dBm	FMrx	FMrxFixed	VR120	VR120atten	Old Radio
88.9	78.2	-65				yes	yes
89.5	78.8	-78			yes		yes
89.9	79.2	-70	quiet	quiet	yes	yes	yes
90.3	79.6	-78		quiet		yes	yes
90.7	80	-80					yes
91.9	81.2	-60	quiet	good	yes	yes	yes
92.7	82	-65		good		yes	yes
93.3	82.6	-43	excellent	excellent	yes	yes	yes
94.5	83.8	-55	quiet	good	yes	yes	yes
95.3	84.6	-60	quiet	good	yes	yes	yes
96.3	85.6	-22	excellent	excellent	yes	yes	yes
97.5	86.8	-65		good		yes	yes
97.9	87.2	-67	quiet	quiet	yes	yes	yes
98.5	87.8	-80					?
99.5	88.8	-61	?	excellent*		yes	yes
101.5	90.8	-40	excellent	excellent	yes	yes	yes
102.5	91.8	-62					yes
103.5	92.8	-30	excellent	excellent	yes	yes	yes
104.7	94	-45	good	excellent	yes	yes	yes
105.3	94.6	-75					yes
105.5	94.8	-67			yes	yes	yes
106.1	95.4	-56		very quiet	yes	yes	yes
106.9	96.2	-64			yes	yes	yes

NOTES

*with shortened antenna - else blocked by 96.3

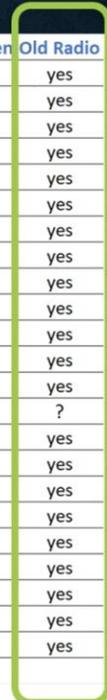Some antenna optimization done to get best signal for all cases



Radio Design 401 - Prior Episodes

Radio Design 401

Episode 1

Low-power Receivers in Crowded Spectrum Environments

(An Advanced "Course" & "White Paper")

MegawattKS - YouTube

ecefiles.org

Radio Design 401
Episode 2
SNR, Noise Figure, and Receiver Sensitivity



MegawattKS - YouTube ecefiles.org

Radio Design 401
Episode 3
RFI Noise in Buildings



MegawattKS - YouTube ecefiles.org

Radio Design 401
Episode 4
Intermodulation in Real-World Circuits and Systems



MegawattKS - YouTube ecefiles.org

Radio Design 401 - Episode 5
"Semester Project"
High Performance Receiver Design



MegawattKS - YouTube ecefiles.org

Radio Design 401 - Episode 6
Advanced Receiver Design
LNAs and Noise Analysis
Part 1 of 2



MegawattKS - YouTube ecefiles.org

Radio Design 401 - Episode 7 Semester Project Building a Better Receiver



MegawattKS - YouTube

ecefiles.org

Presentation Outline

Signal Environments

Background and Prior Episodes



LNA Design

Classic Lab Testing (Gain, NF, P1dB, Pdc)




Real-World Test Results

Conclusions and Future Directions


Amplifier Design Basics

See Radio Design 101 (esp. Episode 3)

BJT Amplifier Configurations

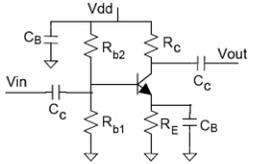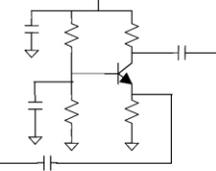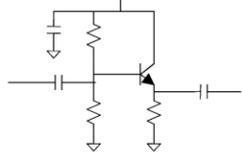Configuration	Representative Circuit	Approx. Formulas	$A_{V_{no-load}}$	R_i	R_o
Common Emitter		$A_{V_{no-load}} = -g_m (R_c r_o)$ $R_i = r_{\pi} R_{b1} R_{b2}$ where $r_{\pi} = h_{fe}/g_m$ $R_o = R_c r_o$	High	Med	Med
Common Base		$A_{V_{no-load}} = +g_m (R_c r_o)$ $R_i = 1/g_m R_E r_{\pi}$ $R_o = R_c r_o$	High	Low	Med
Common Collector (Emitter follower)		$A_{V_{no-load}} \approx 1$ $R_i = R_{b1} R_{b2} r_{\pi}(1 + g_m R_E)^*$ $R_o = 1/g_m^{**}$	Unity	High	Low

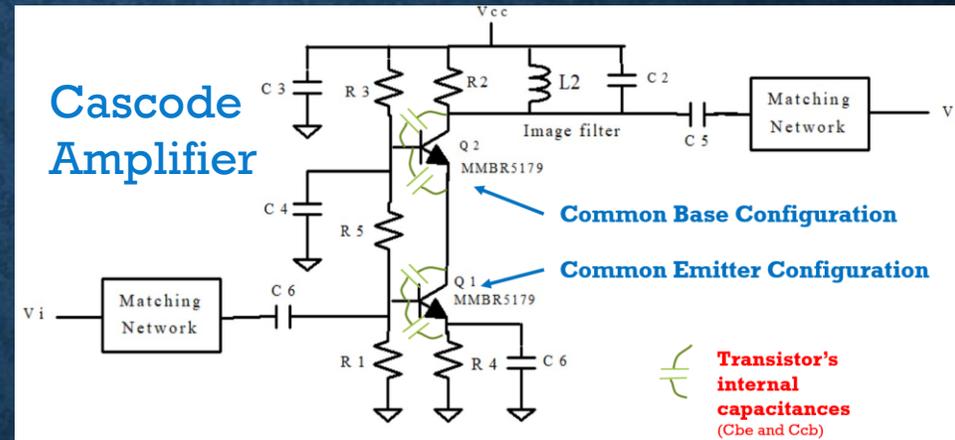* Assumes unloaded output
 ** Assumes low source R



UHF Fully Integrated LNA

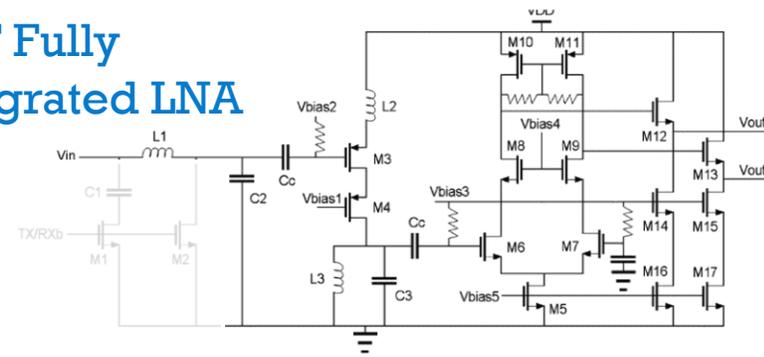


Fig. 23. Schematic diagram of LNA with integrated T/R switch circuits.

2034 PROCEEDINGS OF THE IEEE | Vol. 95, No. 10, October 2007

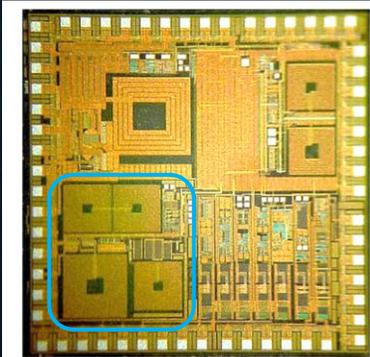



Fig. 39. Die photo of fully integrated single-chip 100-mW transceiver.

Vol. 95, No. 10, October 2007 | PROCEEDINGS OF THE IEEE 2041

Common-Base LNA Examples

See Radio Design 401, Episode 6

How Do We Find the NF of an LNA ?

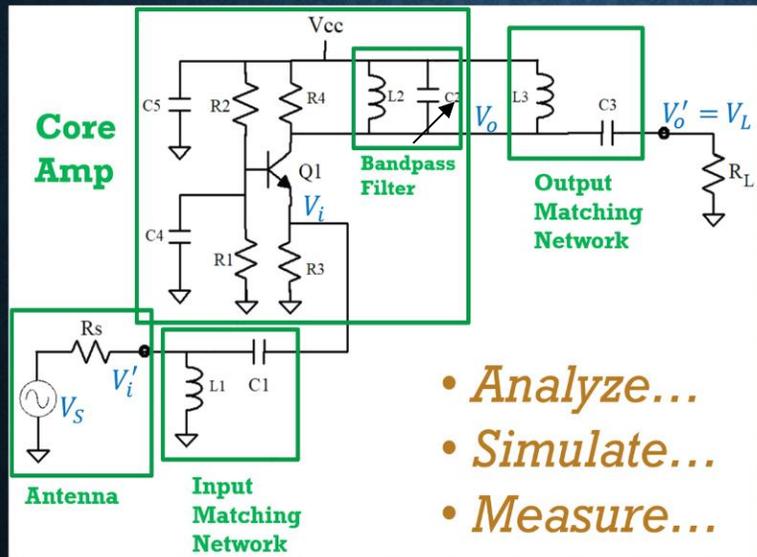


- Analyze...
- Simulate...
- Measure...

Example:

Common-base LNA
from Radio Design 101 series

Need “noise models”
for components ...

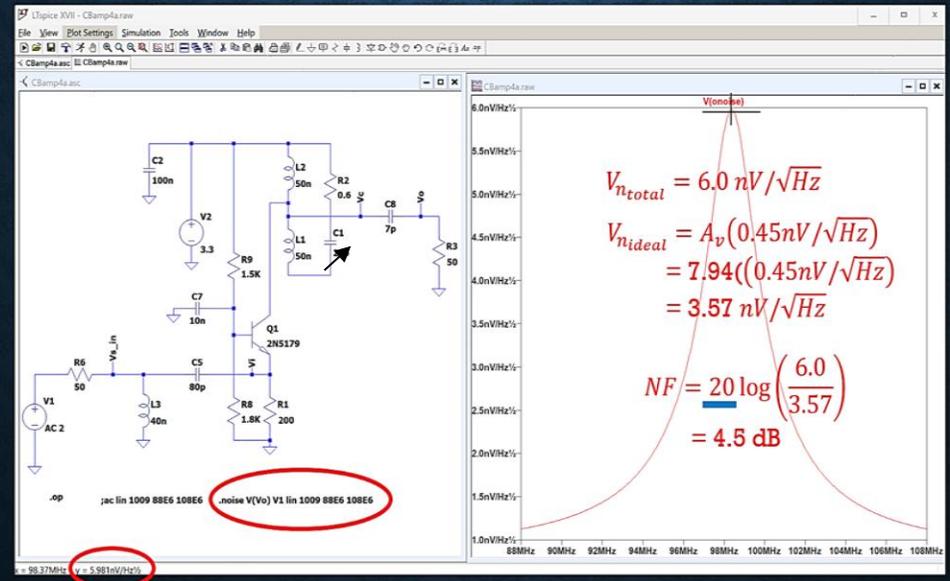LT-Spice Noise Analysis (Matched input case)



Commercial LNA Examples

See RD401, Episodes 4 and 6

Real-World Amplifier Specs

LNA used in TinySA-Ultra Spectrum Analyzer



<http://www.kerrywong.com/2023/06/16/tinysa-ultra-teardown-pictures/>

BGA2817
MMIC wideband amplifier
Rev. 7 — 30 March 2017


Product data sheet

1. Product profile

1.1 General description
Silicon Monolithic Microwave Integrated Circuit (MMIC) wideband amplifier with internal matching circuit in a 6-pin SOT363 plastic SMD package.

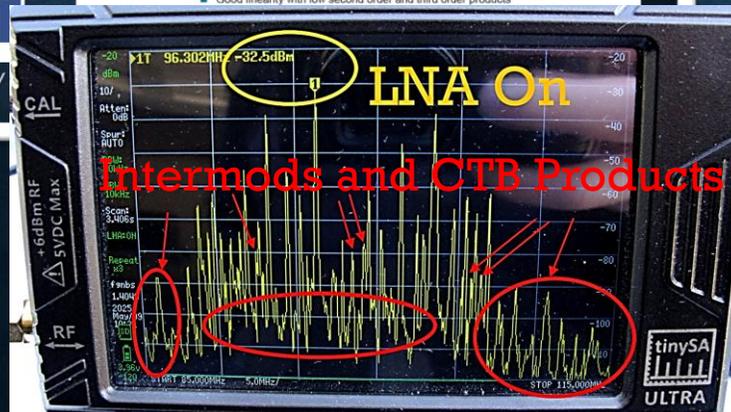1.2 Features and benefits


- Internally matched to 50 Ω
- A gain of 24.4 dB at 2150 MHz
- Output power at 1 dB gain compression = 5 dBm at 2150 MHz
- Supply current = 20.0 mA at a supply voltage of 3.3 V
- Reverse isolation > 35 dB up to 2150 MHz
- Good linearity with low second order and third order products



Marine GPS Antenna



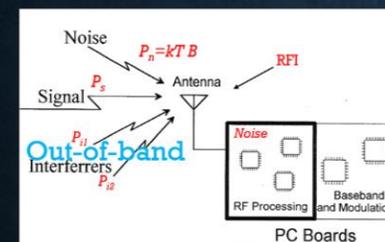Dielectrically Loaded Patch Antenna In Radome



Ideal Low Power Receiver

Reduce Preselect Filter bandwidth to signal bandwidth !
See Episode 1


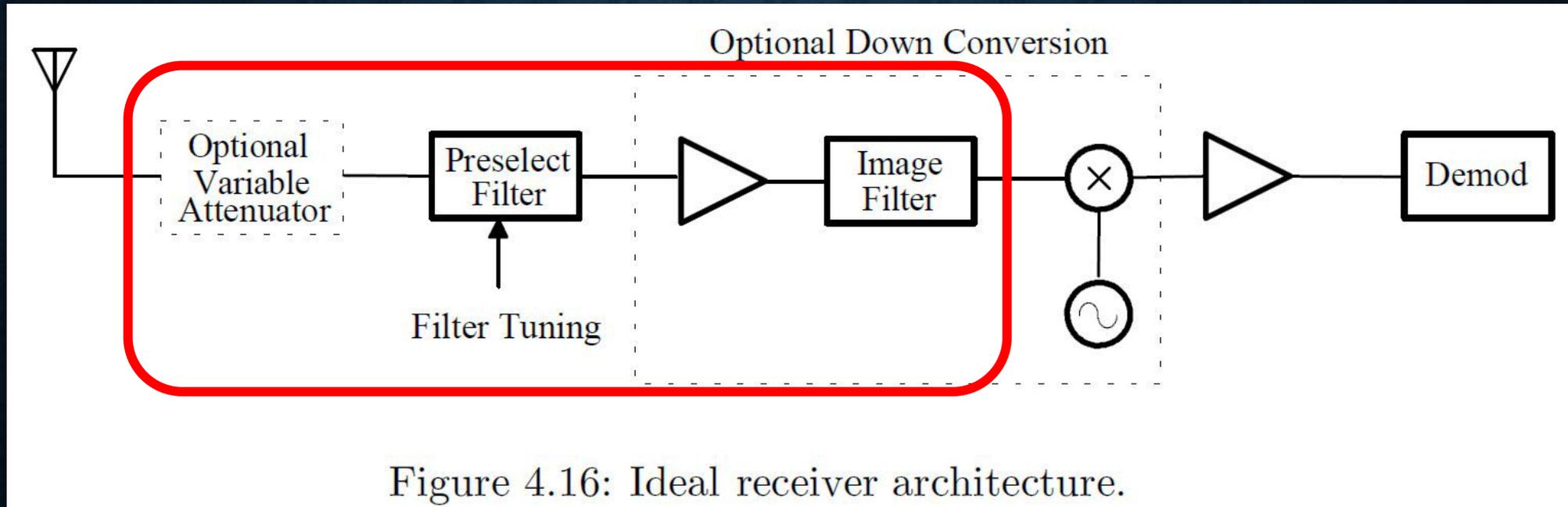


Figure 4.16: Ideal receiver architecture.

From: “Design of Integrated, Low Power, Radio Receivers in BiCMOS Technologies”,
PhD dissertation, Virginia Tech, 1995

Q-enhanced LNA 1st Prototype

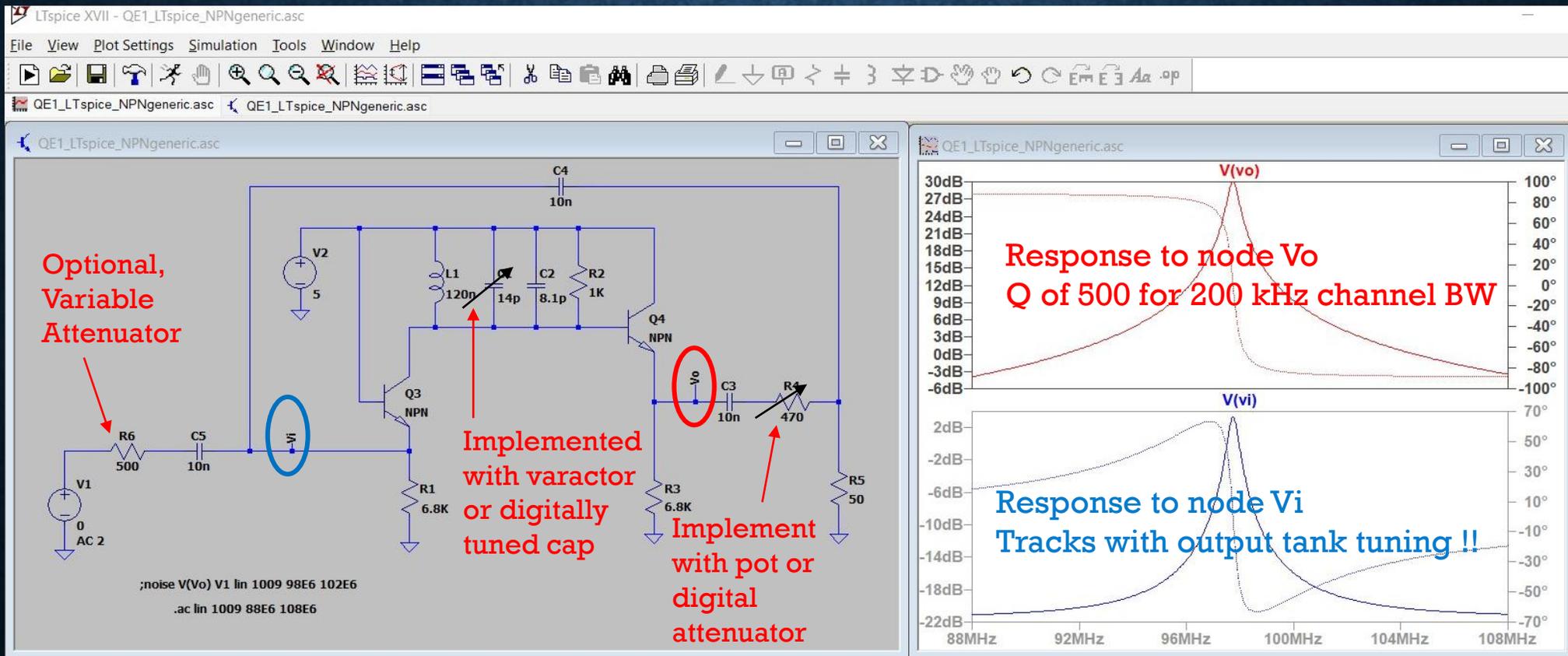Provides narrow BW and tracking-preselect filtering
See Episode 1






1.2 mA at 5 V (6 mW)

Latest Q-enhanced LNA

Uses original Rev 1 board and firmware, but...

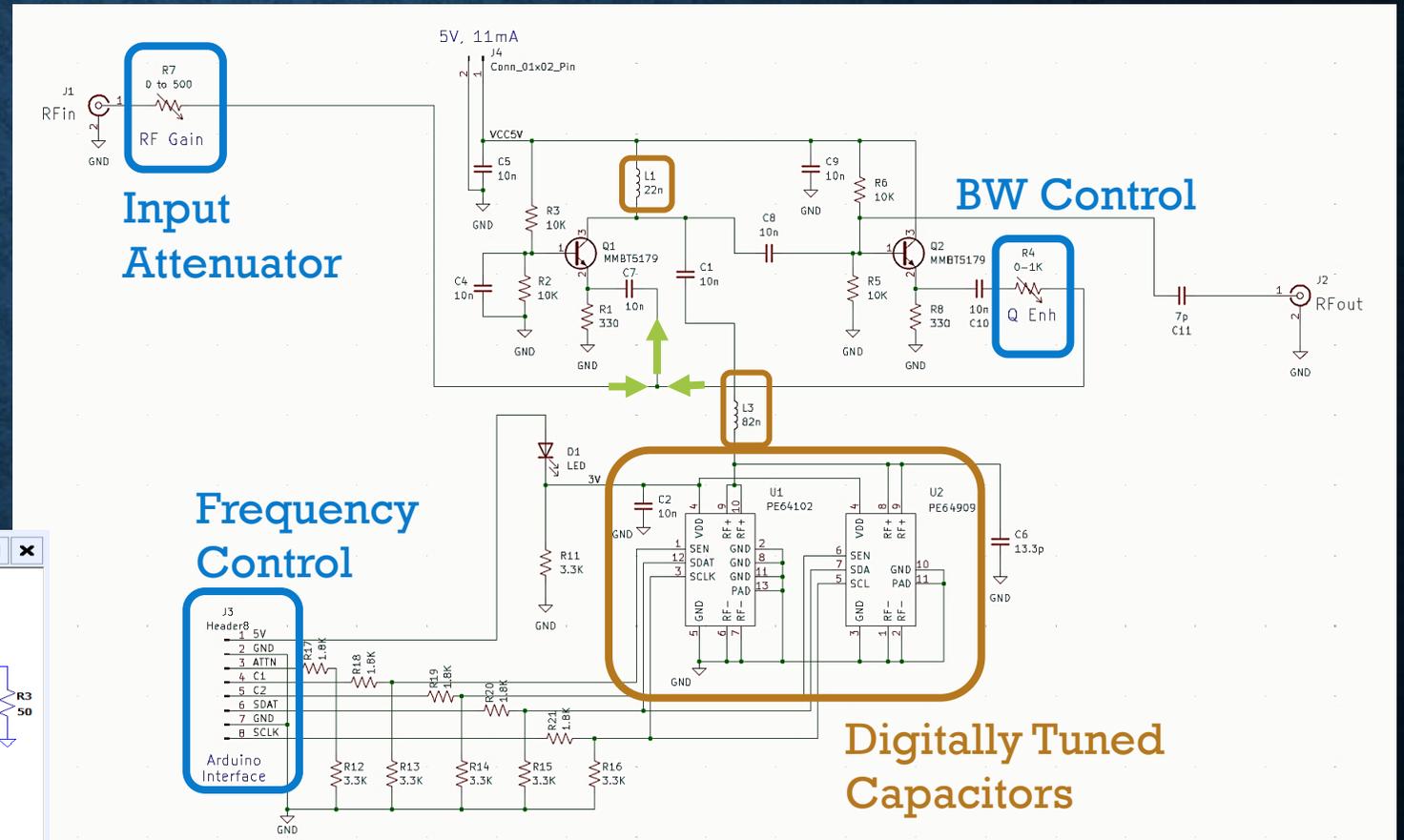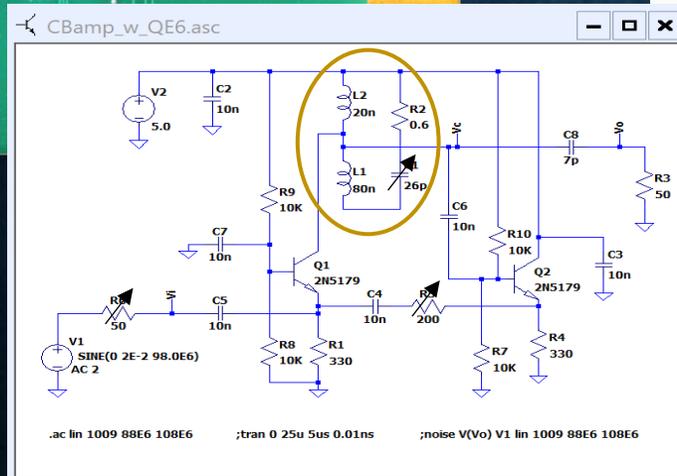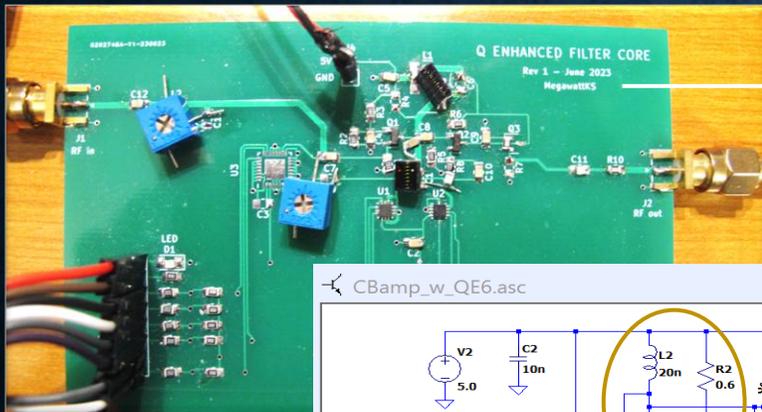Modified for lower gain using split-L tank circuit, and higher Pdc




11 mA at 5 V (55 mW)

Presentation Outline

Signal Environments

Background and Prior Episodes

LNA Design

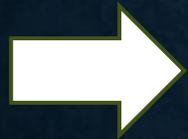

Classic Lab Testing (Gain, NF, P1dB, Pdc)

Real-World Test Results


Conclusions and Future Directions

Lab Testing Setup

Kinda Messy ...

Step Attenuator

DUT

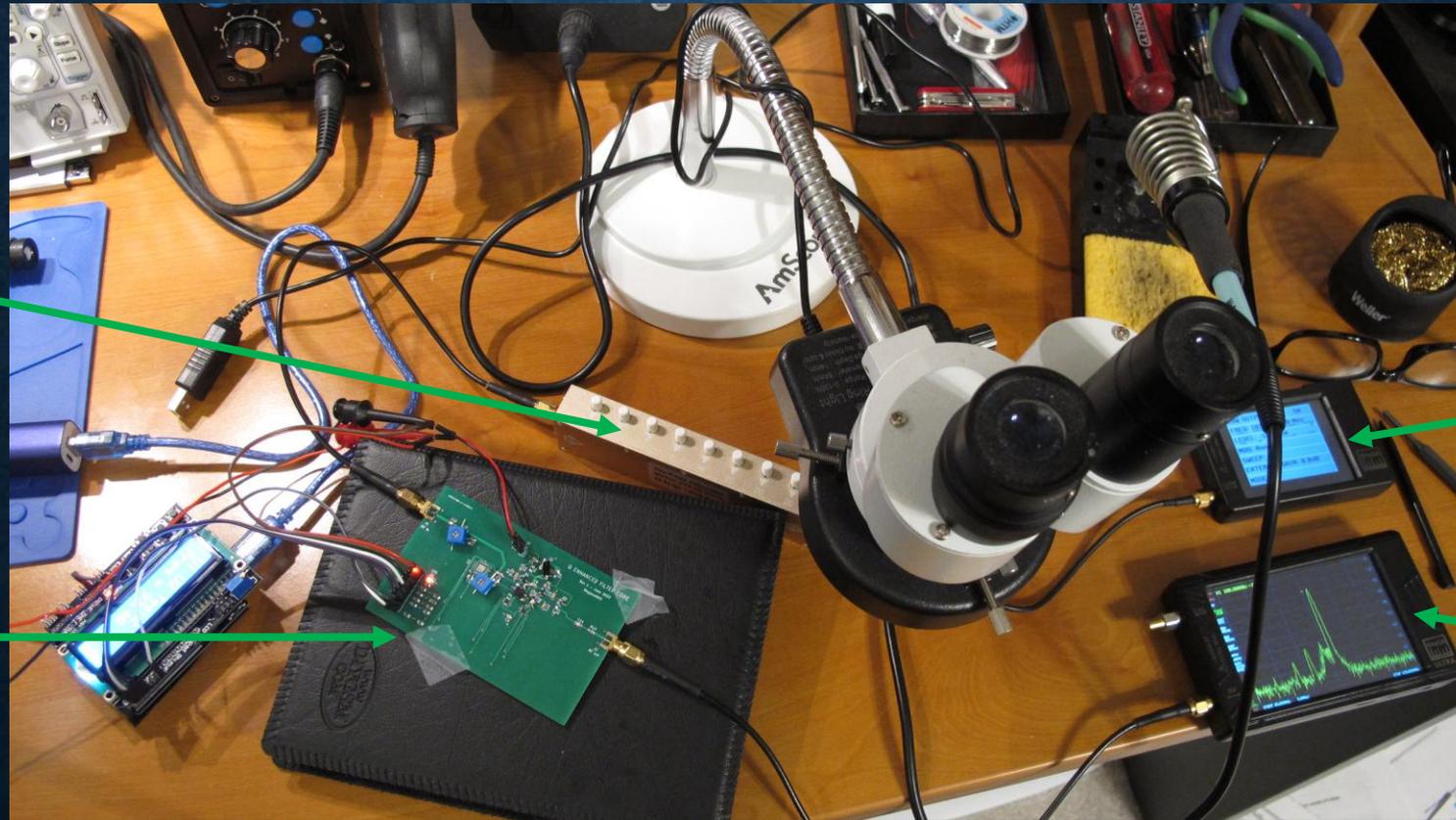

Signal Generator

Spectrum Analyzer

Lab Test Results

(with filter BW adjusted to 200 kHz)

$P_{dc} = 11 \text{ mA @ } 5\text{V} \text{ (55mW)}$



$G = 18 \text{ to } 22 \text{ dB} \text{ (22 dB during NF checks at 109 MHz)}$

$NF = \text{approximately } 5 \text{ dB}$

$P_{i1dB} = -30 \text{ dBm on-channel}$

$P_{i1dB} = -10 \text{ dBm at } 2 \text{ MHz above}$


Insertion Gain Testing

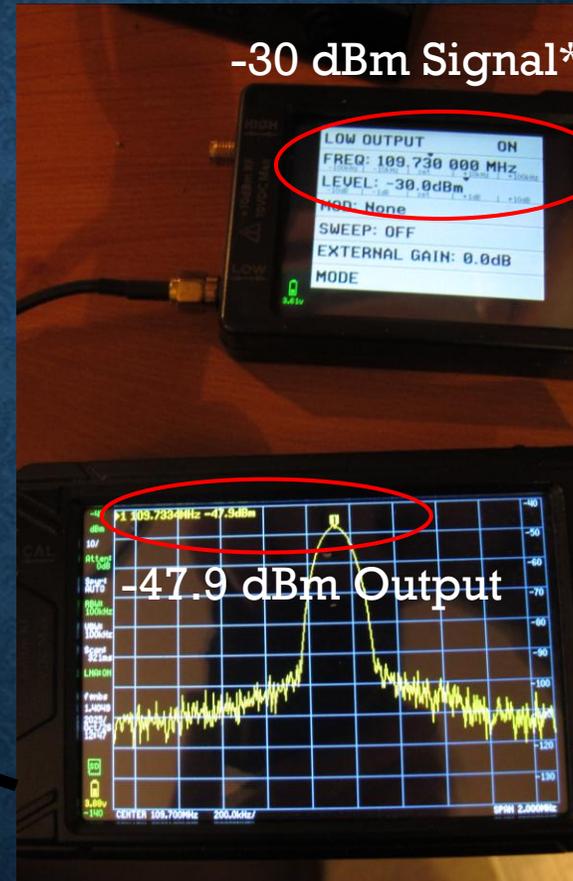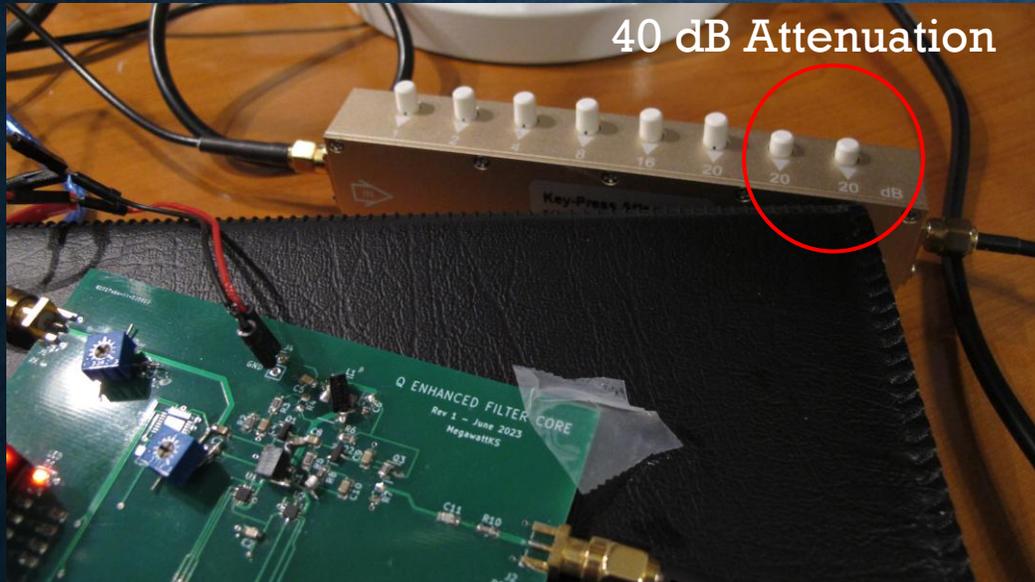

$$\begin{aligned} \text{Gain} &= -47.9 \text{ dBm} - (-30 \text{ dBm} - 40 \text{ dB}) \\ &= 22.1 \text{ dB @ } 109.73 \text{ MHz} \\ &\text{(with filter BW adjusted to about } 200 \text{ kHz)} \end{aligned}$$

Output Noise and NF

(with input terminated in 50 Ohms)

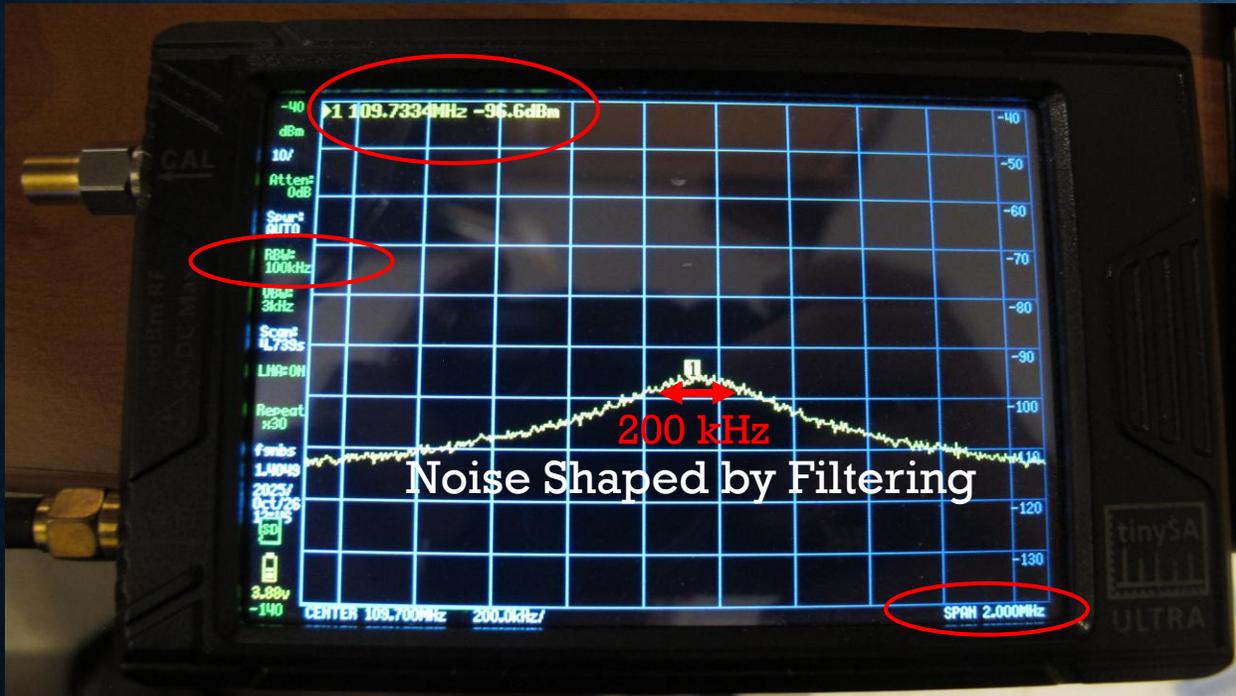

Theoretical Output Noise
in 100 kHz RBW


$$\begin{aligned} &= -174 \text{ dBm} + 10 \log(100\text{k}) + \text{Gain} \\ &= -174 + 50 + 22.1 \\ &= -101.9 \text{ dBm} \end{aligned}$$

Measured Output Noise
= -96.6 dBm

$$\begin{aligned} \text{NF} &= -96.6 \text{ dBm} - (-101.9 \text{ dBm}) \\ &= 5.3 \text{ dB} \\ & \text{ (+/- a dB or two ;-)} \end{aligned}$$

P_{1dB} Input Compression Point(s)

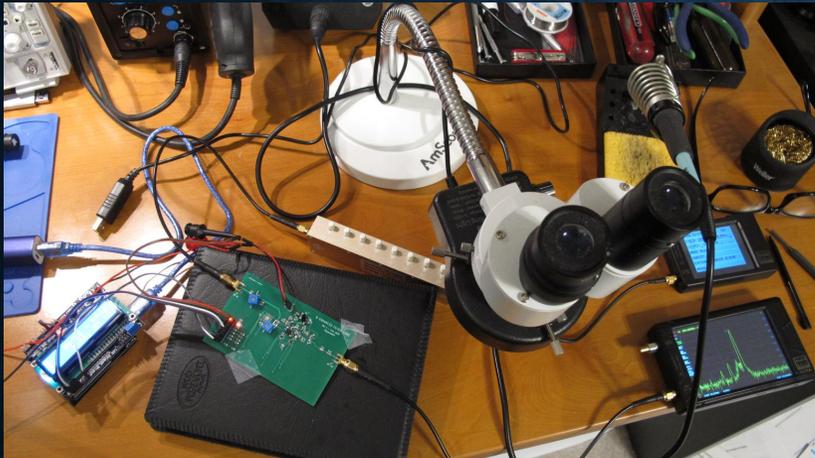
(with filter centered at 99.2 MHz and BW adjusted to 200 kHz)



Step attenuator used to find P_{1dB}
(if 4dB attenuation removed and output increases by only 3dB, we're there)



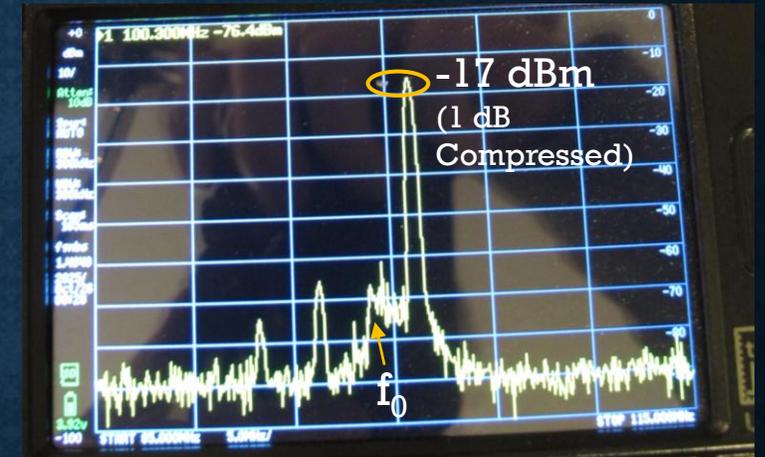Tests run at 99.2 MHz and at
101.2 MHz (2 MHz above f_0)



-17 dBm output with -10 dBm
signal at 2 MHz above f_0 .
Expect -26 dB gain from filter rolloff
(-10 dBm + 20 dB - 26 dB = -16 dBm ☺)

$$P_{i1dB} = -30 \text{ dBm on-channel}$$

$$P_{i1dB} = -10 \text{ dBm at 2 MHz offset}$$

Presentation Outline

Signal Environments

Background and Prior Episodes

LNA Design

Classic Lab Testing (Gain, NF, P1dB, Pdc)




Real-World Test Results










Conclusions and Future Directions

Off the Air (Indoor) Test

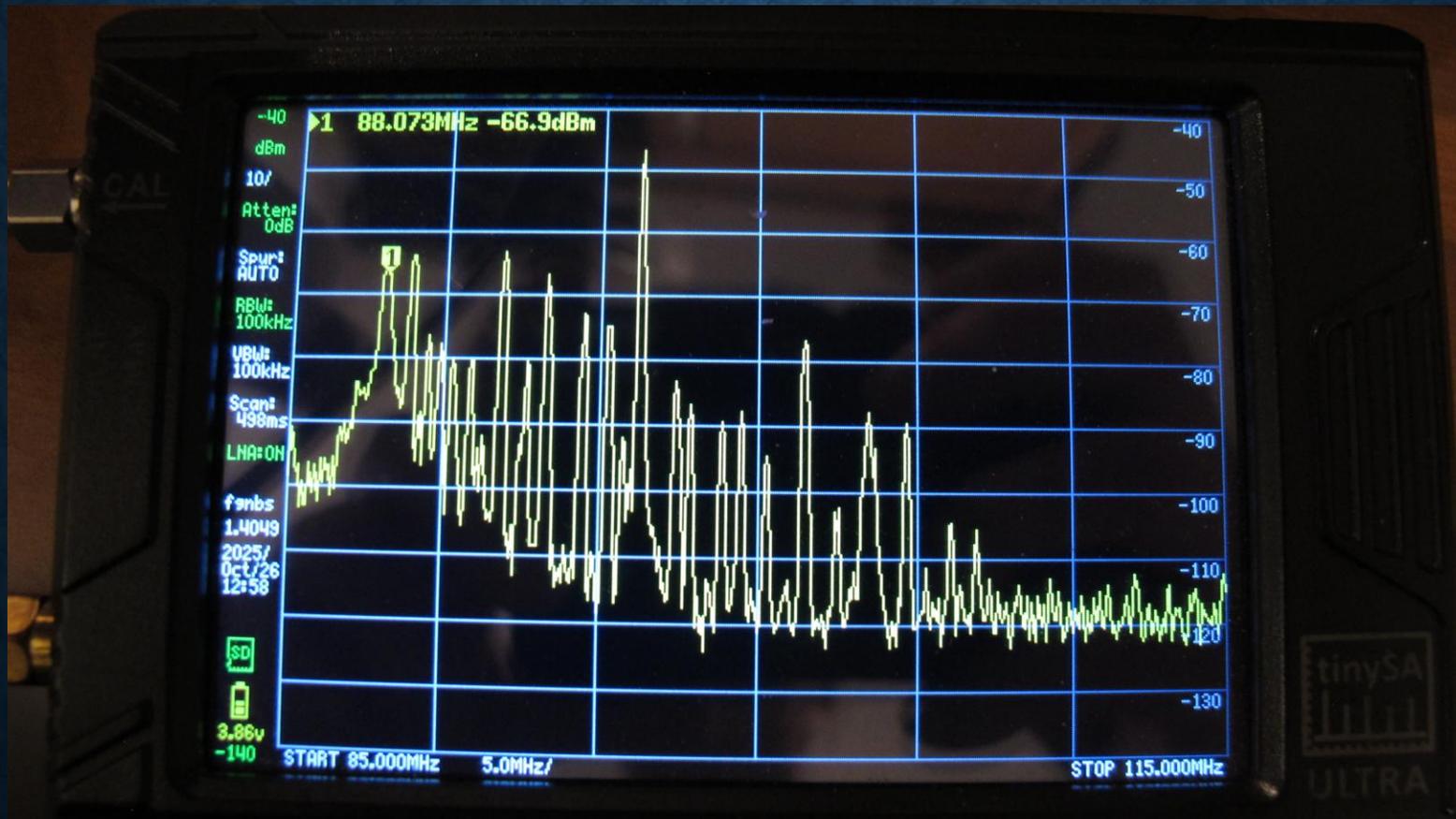(with filter centered at 88.1 MHz and BW adjusted to 200 kHz)



Tuning Through the Band

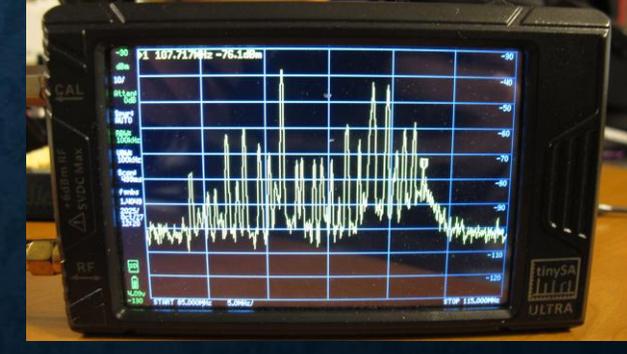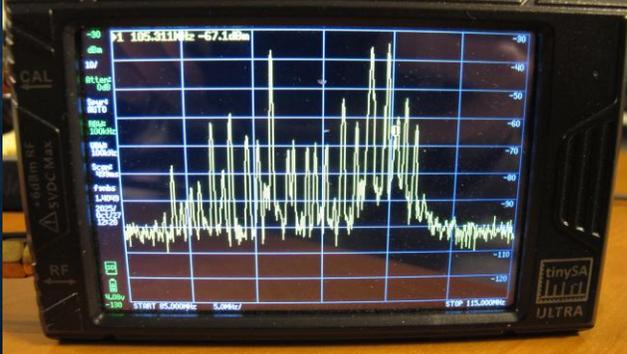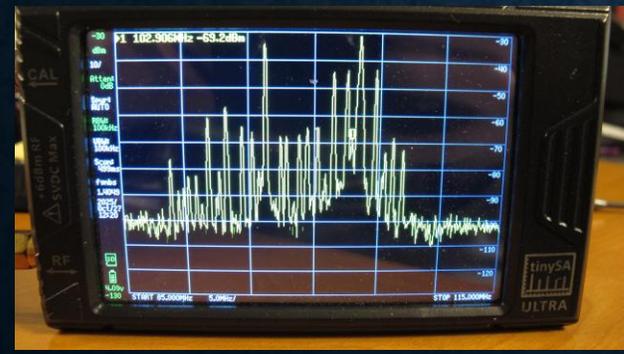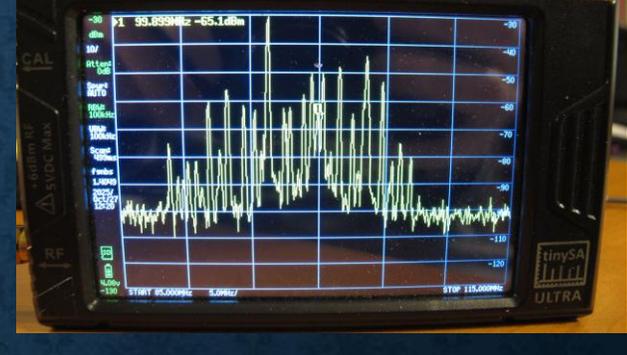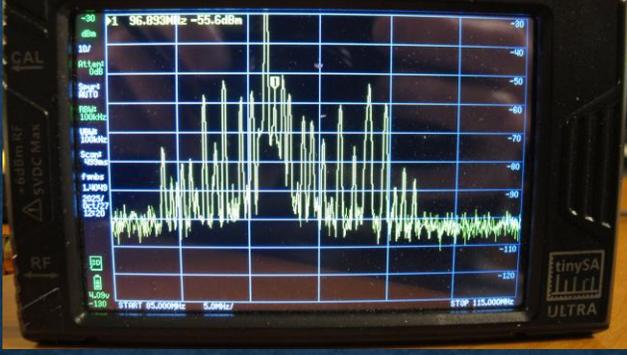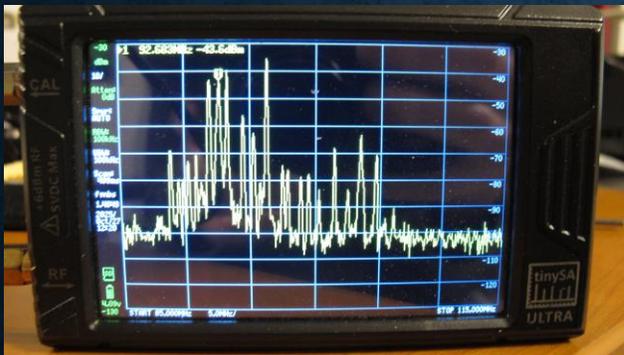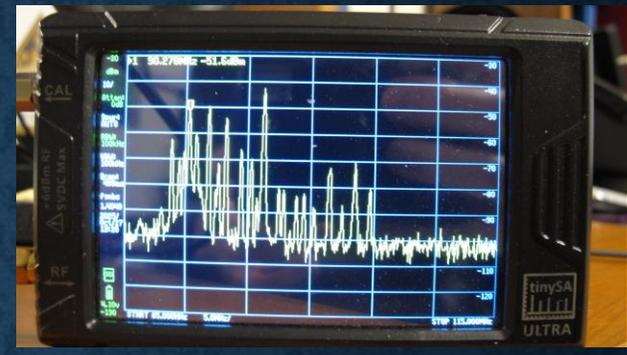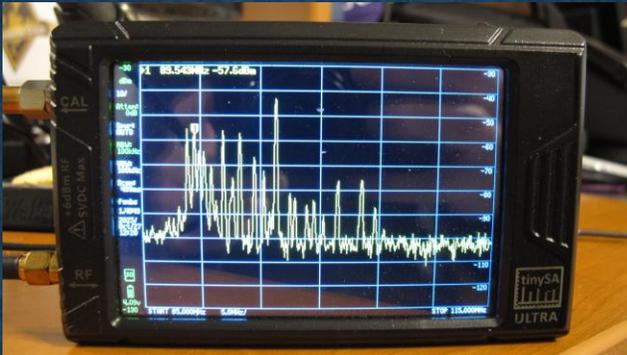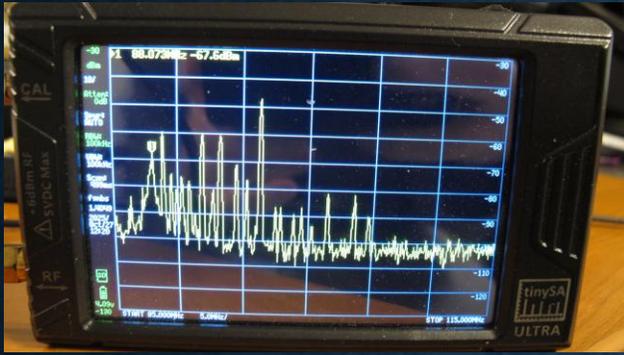

Testing (in Local Park)



Testing (at the Top of the World)



Presentation Outline

Signal Environments

Background and Prior Episodes

LNA Design

Classic Lab Testing (Gain, NF, P_{1dB}, P_{dc})

Real-World Test Results






Conclusions and Future Directions

Conclusions

Radio Design 401 receiver with QE LNA meets or exceeds performance of the best commercial receivers in automobiles

Narrowband preselect filtering allows operation in harsh, crowded spectrum environment at 1/10th the power

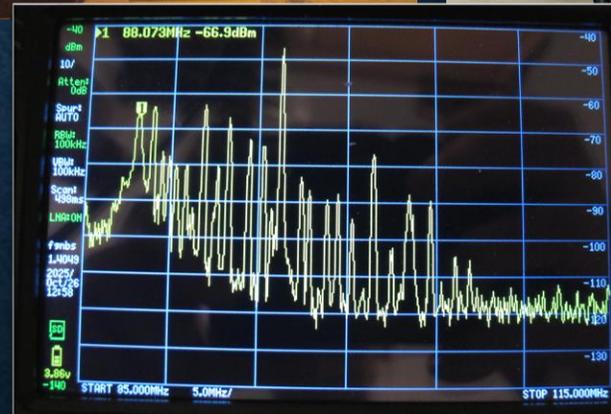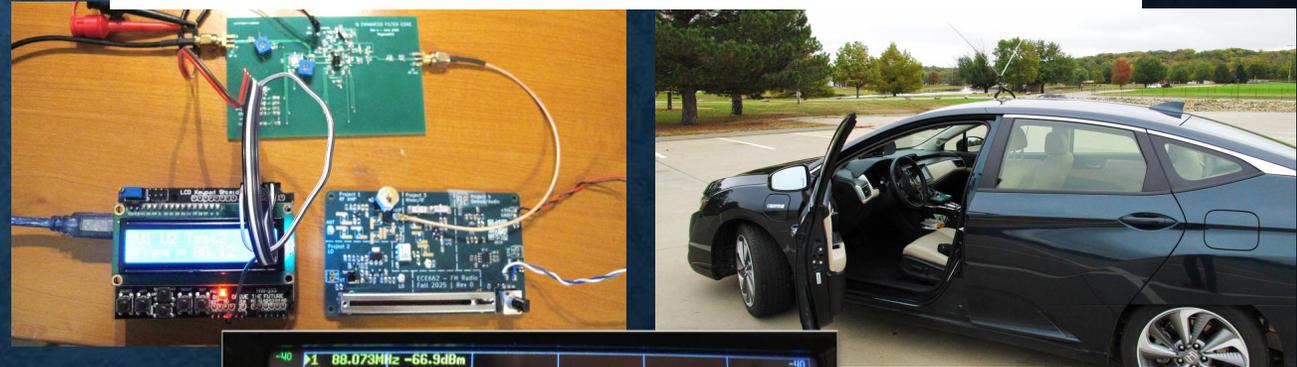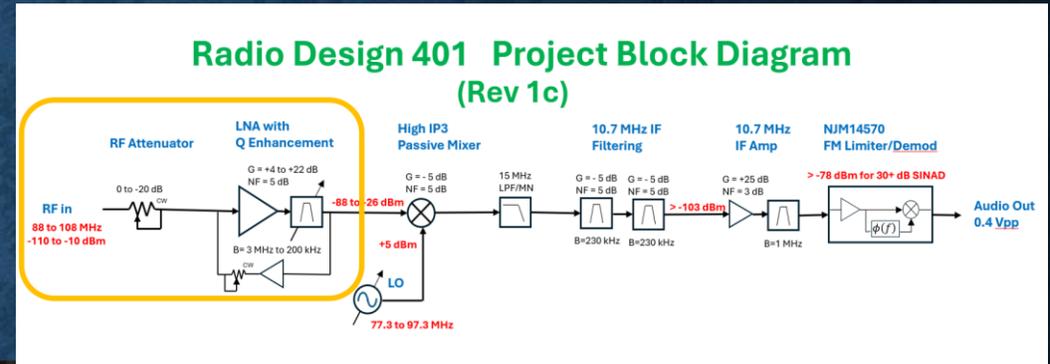Field tests in real-world environments validate the “white paper” theory from episode 1 😊



Future Directions

Radio Design 401 receiver with QE LNA approaches the realization of an Ideal Receiver 😊


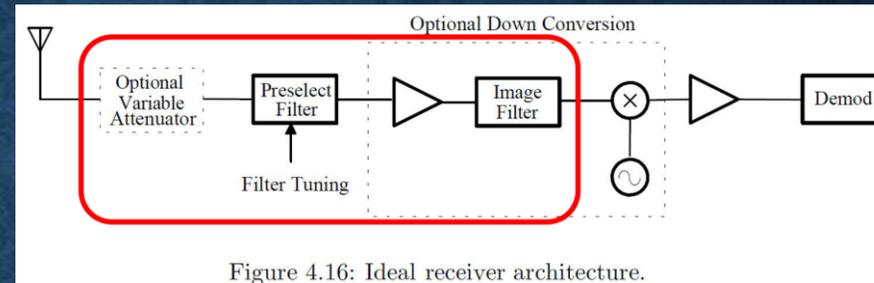
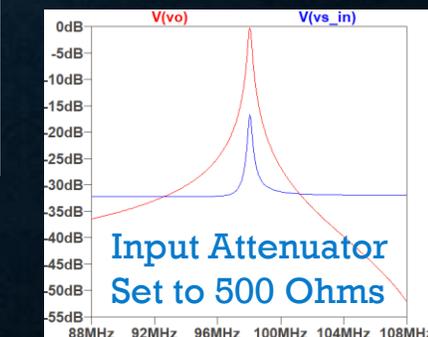
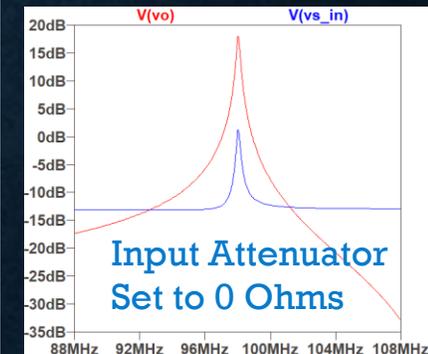


Figure 4.16: Ideal receiver architecture.

Still requires attenuator for very strong signals due to single-pole bandpass response and limited preselect-filter off-channel attenuation

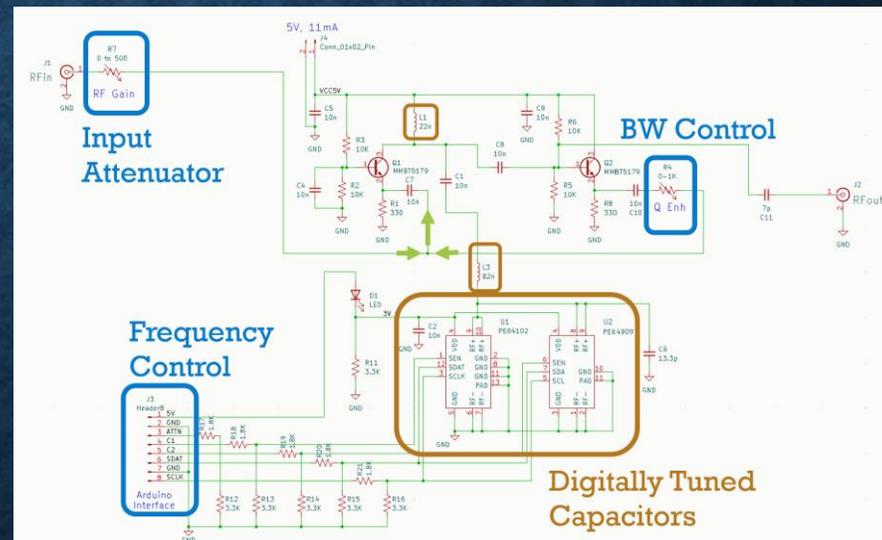Future work on additional filtering before amplifier could improve results further



The End ...

Thanks For Watching !